

EC 160: Experiment 10Basic Properties of Operational Amplifier

- Objective :- (i) to study inverting Op-Amp
(ii) to study non-inverting Op-Amp.
(iii) to study gain.

Theory :- Operational Amplifier, commonly known as Op-Amp, is a linear electronic device having three terminals, two high impedance input and one output terminal. Op-Amp can perform multiple function when attached to different feedback combinations like resistive, capacitive or both. Generally it is used as voltage amplifier and the output voltage of Op-Amp is the difference between the voltages at its two input terminals.

Ideal and Practical characteristics of Op-Amp.

An ideal op-amp is an amplifier with infinite input impedance, infinite open-loop gain, zero output impedance, infinite bandwidth and offset voltage is zero. It has positive and negative inputs which allow circuits that use feedback to achieve a wide range of functions.

In practical Op-Amp, the input impedance is maximum and finite (in the order of 100 k or more), open-loop gain is of the order of thousands,


output impedance is low (of the order of hundred ohms) which can be reduced further with the help of negative feedback. The bandwidth of practical op-amp is very small. Practical Op-Amp has non-zero offset voltage. That is, the zero output is obtained for the non-zero differential input voltage only.

For ideal Op-Amp, no current flows into the input. The practical Op-Amps do have some input currents (of the order of 10^{-6} A to 10^{-14} A).

Inverting Op-Amp :- An inverting amplifier is a type of Op-Amp circuit which produces an output which is out of phase with respect to its input by 180° .

The open loop gain (A_o) of Op-Amp is very high which makes it unstable. To make it stable, a feedback is applied through some external resistor (R_f) from its output to input terminal resulting in reduced gain. So, the voltage at inverting terminal is now the sum of actual input and feedback voltages, and to separate both a input resistor (R_i) is introduced in the circuit. The non-inverting terminal of Op-Amp is grounded, and the inverting terminal behaves like a virtual ground as the junction of input and feedback signal are at same potential.

The circuit of an Op-Amp is given below.

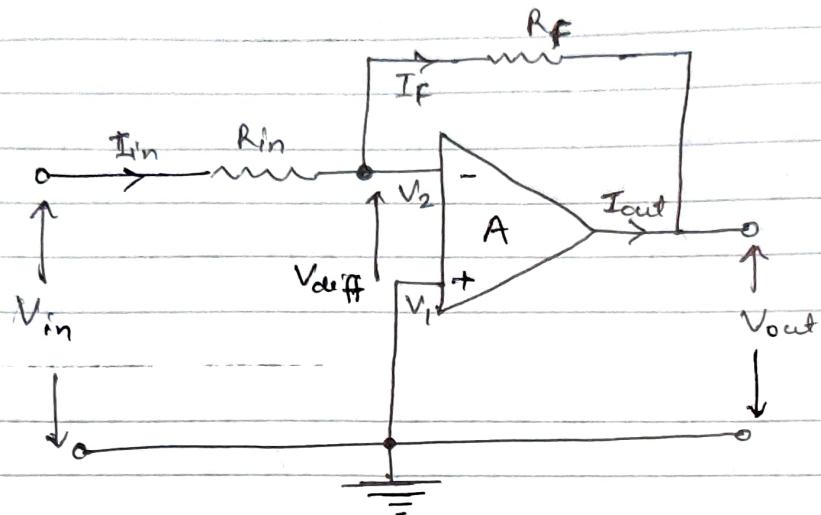

current can be given as,

$$I = \frac{V_{in} - V_{out}}{(R_{in} + R_f)} = \frac{V_{in} - V_2}{R_{in}} = \frac{V_2 - V_{out}}{R_f}$$

$$\therefore \frac{V_{in}}{R_{in}} - \frac{V_2}{R_{in}} = \frac{V_2}{R_f} - \frac{V_{out}}{R_f}$$

$$\frac{V_{in}}{R_{in}} = V_2 \left(\frac{1}{R_{in}} + \frac{1}{R_f} \right) - \frac{V_{out}}{R_f}$$

and as $V_2 = 0$

$$I = \frac{V_{in} - 0}{R_{in}} = \frac{0 - V_{out}}{R_f}$$

$$\therefore \frac{R_f}{R_{in}} = - \frac{V_{out}}{V_{in}}$$

$$\therefore \text{the close loop gain } (A_{cl}) = \frac{V_{out}}{V_{in}} = - \frac{R_f}{R_{in}}$$

$$\text{and output voltage } V_{out} = - \frac{R_f}{R_{in}} \times V_{in}$$

The input resistance with feedback (R_{if}) = $\frac{V_{in}}{I_{in}}$

$$\boxed{R_{if} = R_{in} + \frac{R_f R_{in}}{R_f + R_{in} + A_{ol} R_{in}}}$$


The output resistance with feedback (R_{of}) = $\frac{V_o}{I_o}$

$$\boxed{R_{of} = \frac{R_o}{1 + A_{ol}\beta} = \frac{R_o}{\frac{R_o}{R_{in} + R_f} + A_{ol} R_{in}} = \frac{R_o (R_{in} + R_f)}{R_{in} + R_f + A_{ol} R_{in}}}$$

β is gain of feedback circuit and $\beta = \frac{R_{in}}{R_{in} + R_f}$

Non-Inverting Op-Amp : In this configuration, the input signal is directly fed to non-inverting terminal resulting in a positive gain and output voltage in phase with input. To stabilise the circuit a negative feedback is applied through a resistor (R_f) and the inverting terminal is grounded with a input resistor R_2 . This inverting Op-Amp like layout at the inverting terminal creates a virtual ground at the summing point and make the R_f and R_2 a potential divider across inverting terminal, hence determines the gain of the circuit.

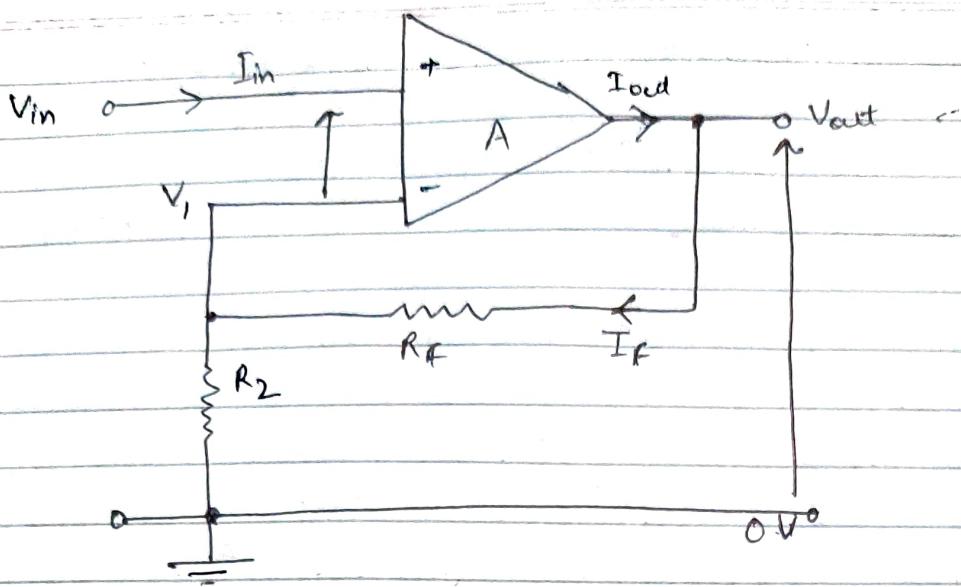The circuit for a Non-inverting Op-Amp is given below,



Potential difference V_i can be written as

$$V_i = \frac{R_2 V_{out}}{R_2 + R_f}$$

in ideal condition $V_i = V_{in}$, so,

$$V_{in} = \frac{R_2 V_{out}}{R_2 + R_f}$$

since, close loop gain (A_{cl}) = $\frac{V_{out}}{V_{in}}$

$$\therefore A_{cl} = \frac{R_2 + R_f}{R_2} = 1 + \frac{R_f}{R_2}$$

$$\text{and, output voltage } (V_{out}) = A_{cl} \times V_{in} \\ = \left(1 + \frac{R_f}{R_2}\right) \times V_{in}$$

Input resistance with feedback (R_{if}),

$$R_{if} = 1 + \frac{A_v R_2}{R_2 + R_f} = R_2 (1 + A_v \beta)$$

Output resistance with feedback (R_{of})

$$R_{of} = \frac{R_o}{1 + A_v \beta}$$

Procedure for the Experiment

1. Connect the circuit and check if it is a right connection.
2. Set the resistance value (R_i) { $1\text{ k}\Omega - 50\text{ k}\Omega$ }
3. Set the feedback resistance (R_f) value { $2\text{ k}\Omega - 100\text{ k}\Omega$ }
4. Set input voltage V_{in} (-15 to 50V)
5. Note the output voltage and click on 'Add to Table'.
6. Increase the input voltage by a factor of 2.
7. Click on 'Plot' button to plot the output voltage versus input voltage.

Simulation Results



An MoE Govt of India Initiative



INSTRUCTION


Inverting Opamp

CONTROLS

Input volt : Volt
 Resistance (R_1) : Kohms
 Resistance (R_f) : Kohms

Add to Table Plot Clear
 -34.0 0.0167 -2.428571
 Check connection Delete all connection


EXPERIMENTAL TABLE			
Serial No.	Input Voltage V	Output Voltage V	Current mA
1	-15	36.4	-0.0179
2	-12	29.1	-0.0143
3	-6	14.6	-0.00717
4	-2	4.86	-0.00239
5	2	4.86	0.00239

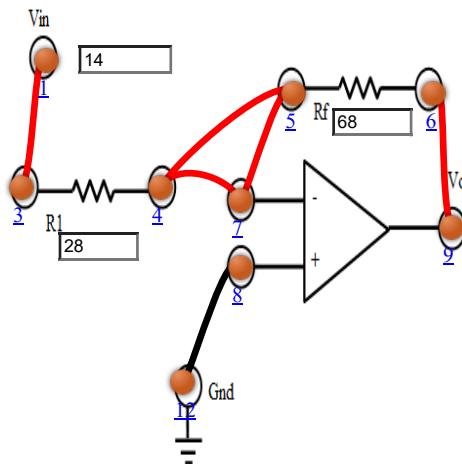

GRAPH PLOT

Vo-Vi Plot

Print

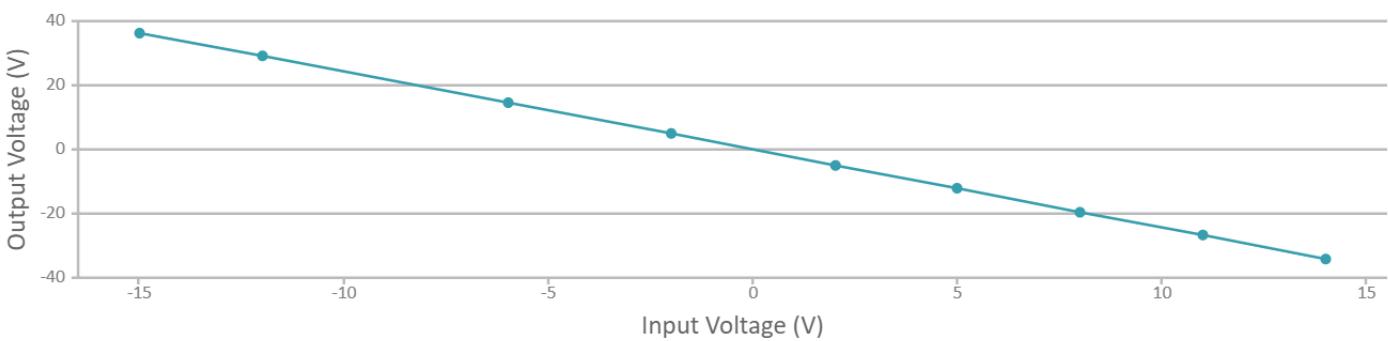



An MoE Govt of India Initiative



INSTRUCTION

Inverting Opamp

CONTROLS


Input volt : Volt
 Resistance (R_1) : Kohms
 Resistance (R_f) : Kohms

Add to Table Plot Clear
 -37.8
 0.0168
 -2.7

EXPERIMENTAL TABLE


Resistance: 30 K Ω

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	-15	40.5	-0.0180
2	-11	29.7	-0.0132
3	-9	24.3	-0.0108
4	-7	18.9	-0.00841
5	-4	10.8	-0.00480

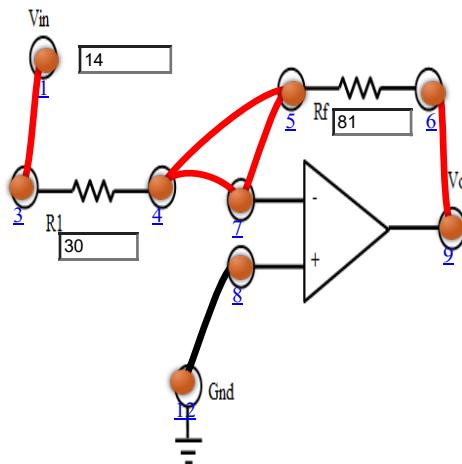

GRAPH PLOT

Vo-Vi Plot

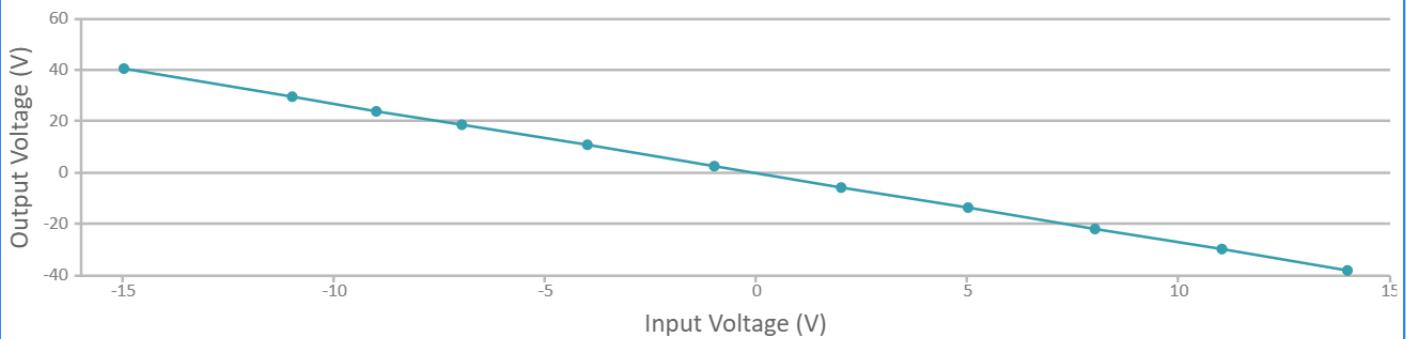 Print




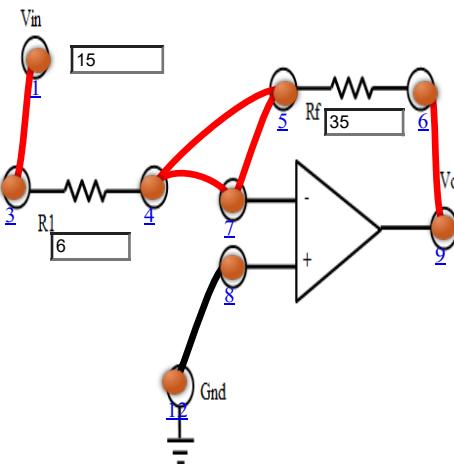

INSTRUCTION

Inverting Opamp

CONTROLS

Input volt : Volt
 Resistance (R_1) : Kohms
 Resistance (R_f) : Kohms

Add to Table Plot Clear
 -87.5 0.161
 Check connection Delete all connection
 -5.833333




EXPERIMENTAL TABLE

Resistance: K Ω

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	-15	87.5	-0.161
2	-12	70.0	-0.129
3	-9	52.5	-0.0969
4	-6	35.0	-0.0646
5	-1	5.83	-0.0108

GRAPH PLOT

Vo-Vi Plot

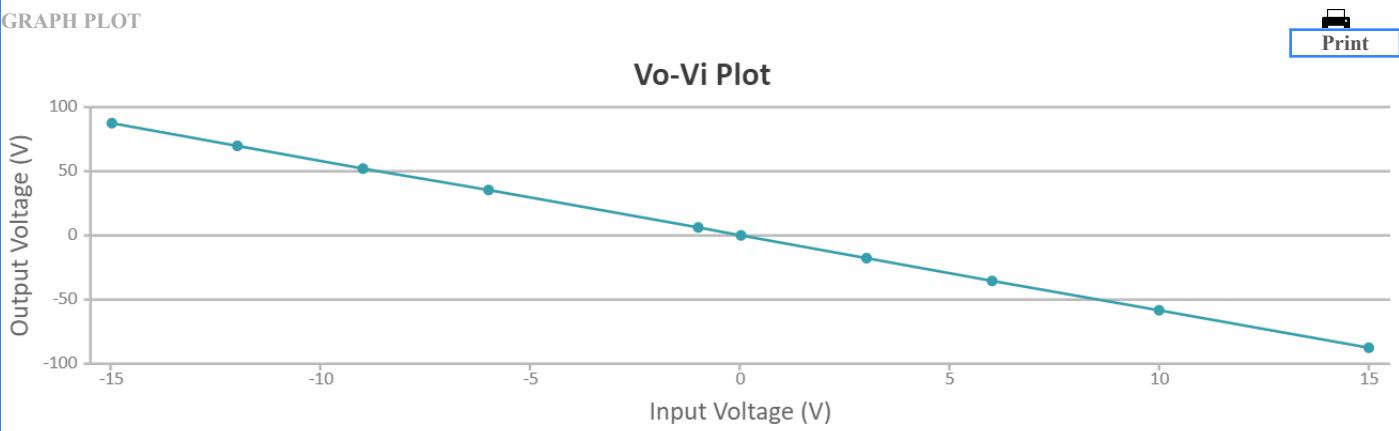



An MoE Govt of India Initiative

INSTRUCTION


Non Inverting Opamp

CONTROLS


Input volt : Volt
 Resistance (R_1) : Kohms
 Resistance (R_f) : Kohms

Take another sets of readings for different R_1 and R_f

EXPERIMENTAL TABLE			
Serial No.	Input Voltage V	Output Voltage V	Current mA
1	-15	-76.9	-0.109
2	-13	-66.6	-0.0948
3	-10	-51.3	-0.0732
4	-8	-41.0	-0.0588
5	-5	-25.6	-0.0360

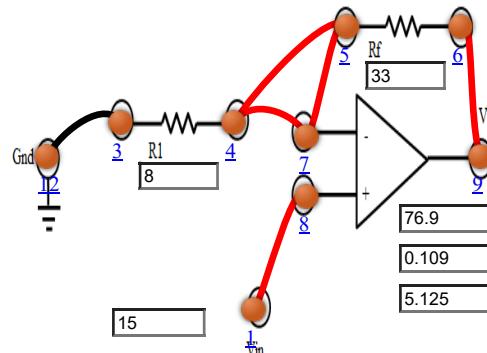

GRAPH PLOT

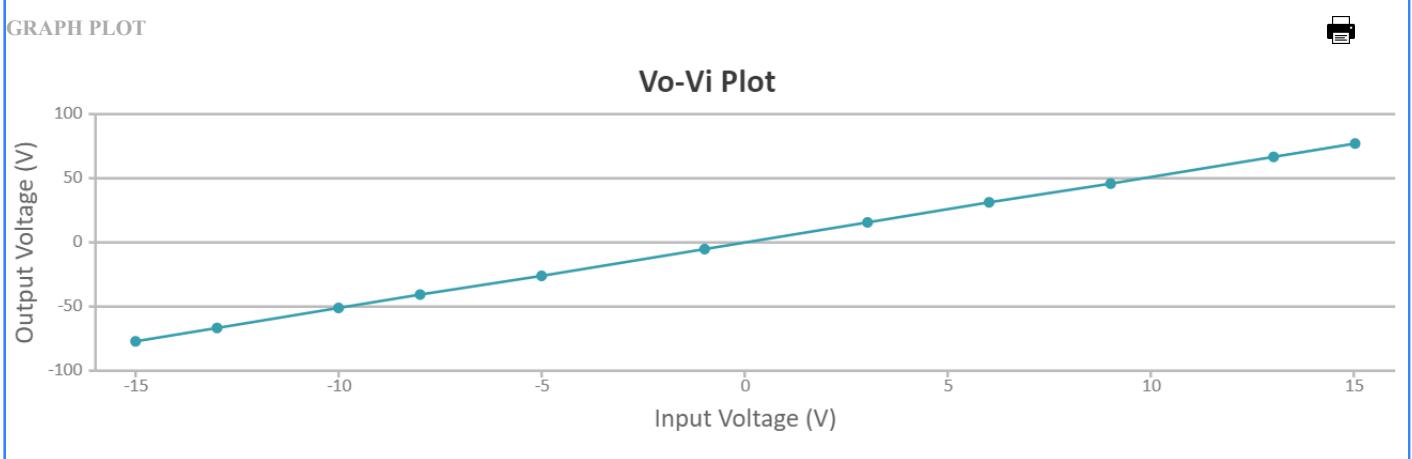



An MoE Govt of India Initiative

INSTRUCTION

Non Inverting Opamp



CONTROLS

Input volt : Volt
 Resistance (R_1) : Kohms
 Resistance (R_f) : Kohms

[Print It](#)

Take another sets of readings for different R_1 and R_f

EXPERIMENTAL TABLE			
Serial No.	Input Voltage V	Output Voltage V	Current mA
1	-15	-80.0	-0.0607
2	-13	-69.3	-0.0524
3	-10	-53.3	-0.0403
4	-8	-42.7	-0.0319
5	-4	-21.3	-0.0160

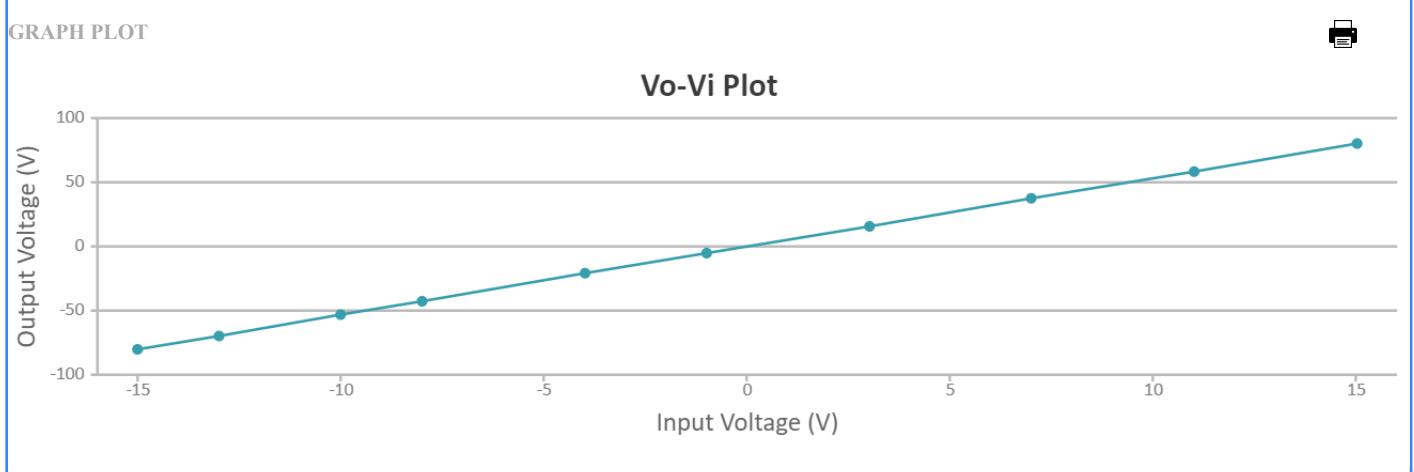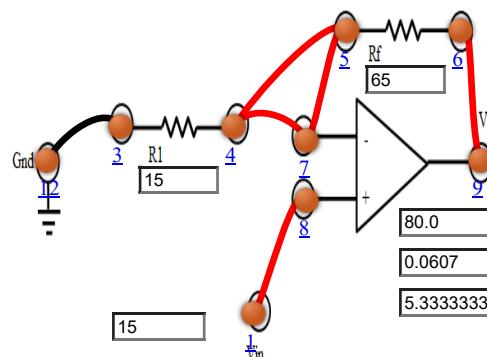



INSTRUCTION

Non Inverting Opamp

CONTROLS

Input volt : Volt
 Resistance (R_1) : Kohms
 Resistance (R_f) : Kohms

Add to Table Plot Clear

Check connection Delete all connection



Print It

Take another sets of readings for different
 R_1 and R_f

EXPERIMENTAL TABLE

Resistance: KΩ

Serial No.	Input Voltage V	Output Voltage V	Current mA
1	-15	-63.5	-0.0252
2	-12	-50.8	-0.0200
3	-8	-33.9	-0.0132
4	-5	-21.2	-0.00840
5	-2	-8.47	-0.00323

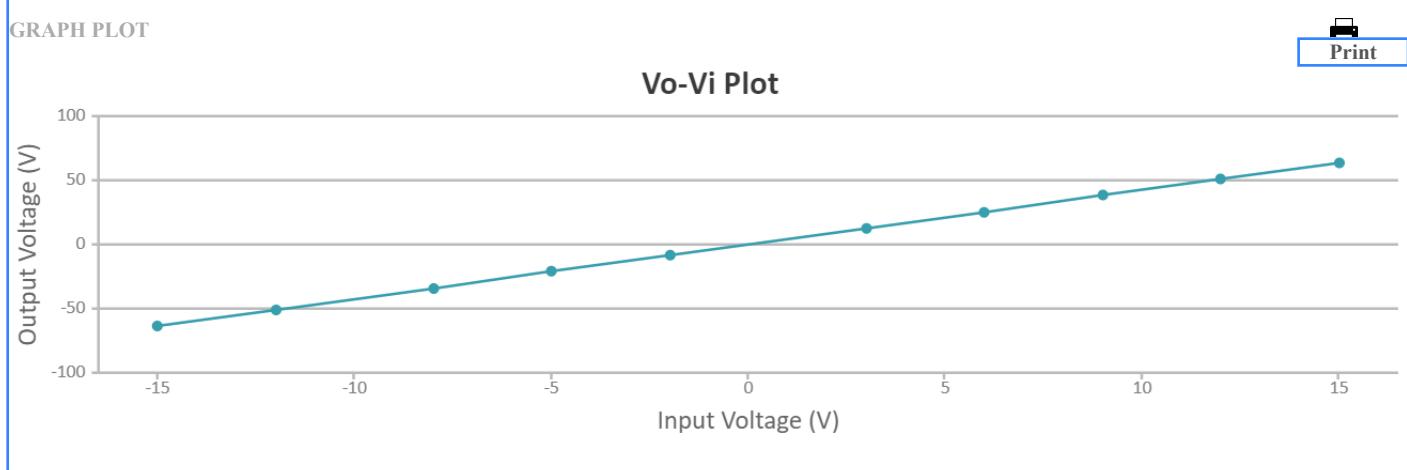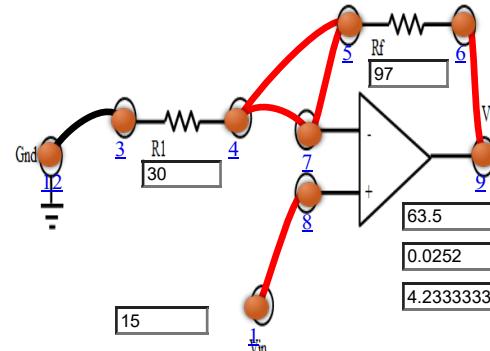

Conclusion:- Performing the experiment we have studied the following.

- i) the characteristics of ideal and practical Op-Amp.
- ii) the working of Inverting and Non-Inverting Op-Amp.
- (iii) the output voltage, feedback factor, input resistance and output resistance with feedback, close loop gain, voltage gain etc. for Inverting and Non-Inverting Op-Amp's.