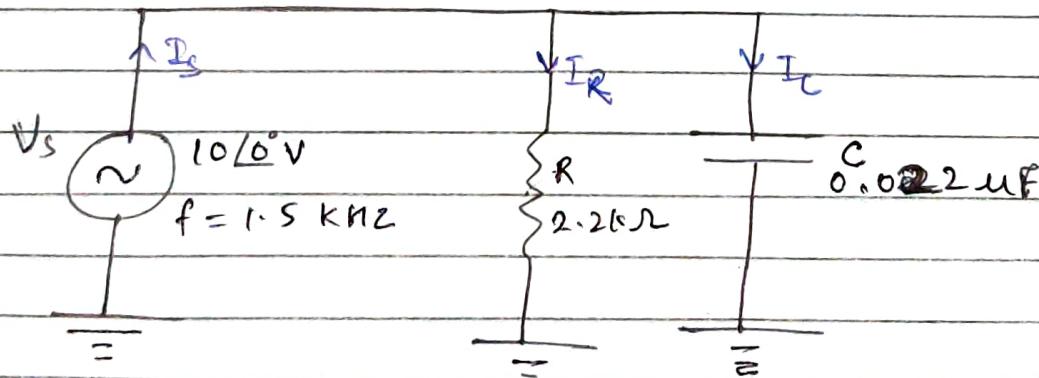


## EE160: Experiment 2


Objective :- Design and simulate any three (of given 5) circuits in SPICE. Plot the voltages (across each element), currents (through each element), and total current. Find the phase difference between the source voltage ( $V_s$ ) and all other voltages and currents from your simulations. Calculate these voltages and currents theoretically. Draw the phasor diagram from your theoretical calculations. Compare the theoretical results with the simulation results. Also, plot total power ( $V_s \times T_{total}$ ) of the circuit.

### Mathematical Expressions and Theoretical Calculations
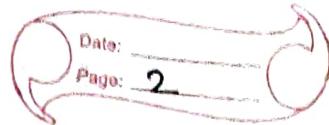
#### CIRCUIT 1 :-



Name: Archit Agrawal  
Student ID: 202052307



$$Z_c = -j X_c$$

$$X_c = \frac{1}{\omega C} = \frac{1}{2\pi \times (1.8\text{K}) \times (0.022\mu)} \text{ } \Omega$$

$$X_c = 4.825 \text{ k} \Omega$$

$$\therefore Z_c = -j(4.825 \text{ k}) \Omega$$

$$\bar{Z}_c = 4.825 \text{ k} [ -90^\circ ] \Omega$$

$$\bar{Z}_R = 2.2 \text{ k} [ 0^\circ ] \Omega$$

Since, R and C are in parallel with voltage source

$$\boxed{\bar{V}_s = \bar{V}_R = \bar{V}_C = 10 [ 0^\circ ] \text{ V}}$$

$$\therefore \bar{I}_R = \frac{\bar{V}_R}{\bar{Z}_R} = \frac{10 [ 0^\circ ]}{2.2 \text{ k} [ 0^\circ ]}$$

$$\boxed{I_R = 4.545 [ 0^\circ ] \text{ mA}}$$

$$\text{and, } \bar{I}_C = \frac{\bar{V}_C}{\bar{Z}_C} = \frac{10 [ 0^\circ ]}{4.825 \text{ k} [ -90^\circ ]}$$

$$\boxed{\bar{I}_C = 2.073 [ 90^\circ ] \text{ mA}}$$

Using KCL,

$$I_{\text{tot}} = I_C + I_R$$


$$I_{\text{tot}} = \left\{ j(2.073) + 4.545 \right\} \text{ mA}$$

Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 3

$$I_{\text{tot}} = 11.995 \angle 24.518^\circ \text{ mA}$$

### Phasor Diagram

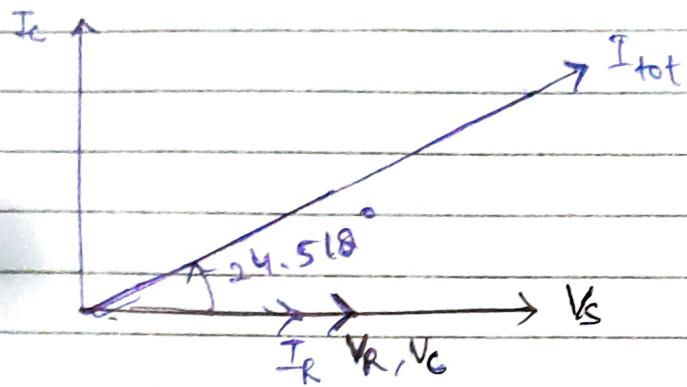

### Time Domain

Given  $V_s = 10 \angle 0^\circ \text{ V}$

$$\therefore V_{\text{rms}} = 10 \text{ V}$$

$$\therefore V_m = 10\sqrt{2} \text{ V}$$

In time domain, we write peak value;

$$\therefore V_R = V_C = V_s = 10\sqrt{2} \sin(9420t + 0^\circ) \text{ V}$$


$$I_{\text{tot}} = 4.995\sqrt{2} \sin(9420t + 24.518^\circ) \text{ mA}$$

$$I_R = 4.545\sqrt{2} \sin(9420t + 0^\circ) \text{ mA}$$

$$I_c = 2.073\sqrt{2} \sin(9420t + 90^\circ) \text{ mA}$$

The time domain graph just gives an idea of phase of  $V_s$  and  $I_{\text{tot}}$  and the magnitude of  $I_{\text{tot}}$  and  $V_{\text{tot}}$  is not implied by it.

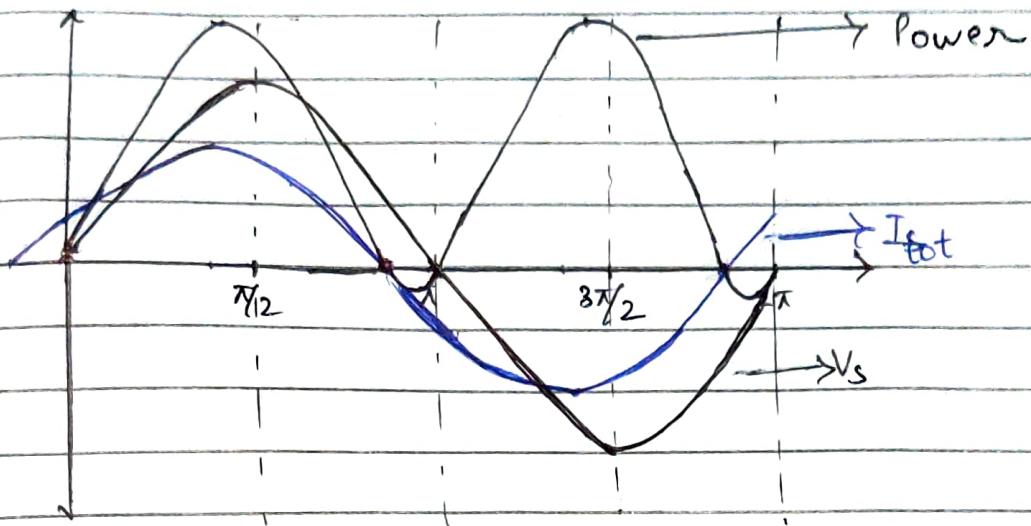
Name : Archit Agrawal  
Student ID : 202052307




Comparison between Spice Simulations and Theory Calculations

We can see that the time domain graph of  $I_{tot}$  and total power is inverted. The reason behind this is explained below -

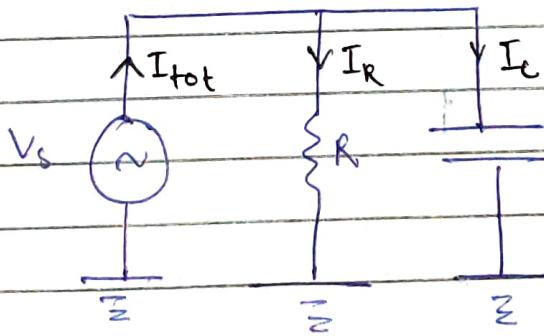The directions of current ~~are~~ chosen for theory calculation are given below,



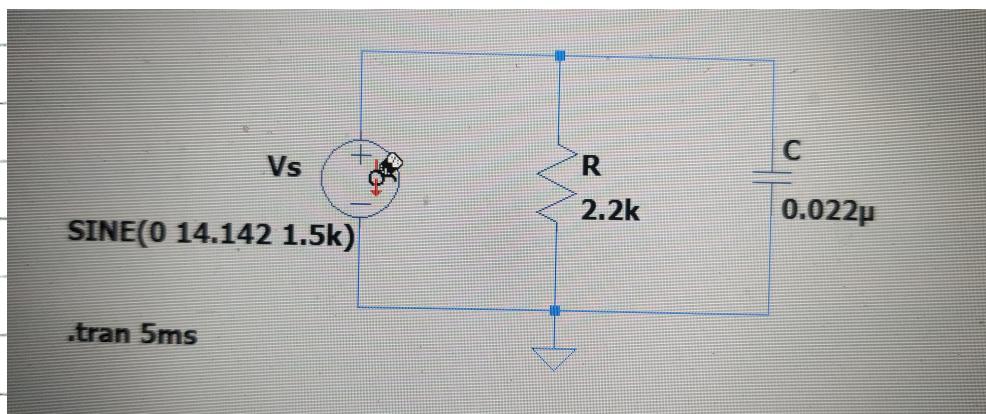On SPICE, direction of  $I_R$  and  $I_c$  is same but the direction of  $I_s$  is inverted.



As you can see the arrow is pointing downwards. That is why, the total current and total power time domain graphs are inverted on SPICE.

Now, the phase angle


<del>Component</del>	Angle
$V_s$	$0^\circ$
$I_C$	$90^\circ$
$I_R$	$0^\circ$
$I_{tot}$	$24.518^\circ$

On SPICE, phase angle of  $I_{tot}$  is given to be  $-155.479^\circ$ . This is because of the same reason mentioned above.



Because of the reverse direction the phase changes by  $180^\circ$ . Clearly,  $24.518^\circ - 180^\circ$  equals  $-155.482^\circ$ .

# EE160 : Experiment 2

## Circuit

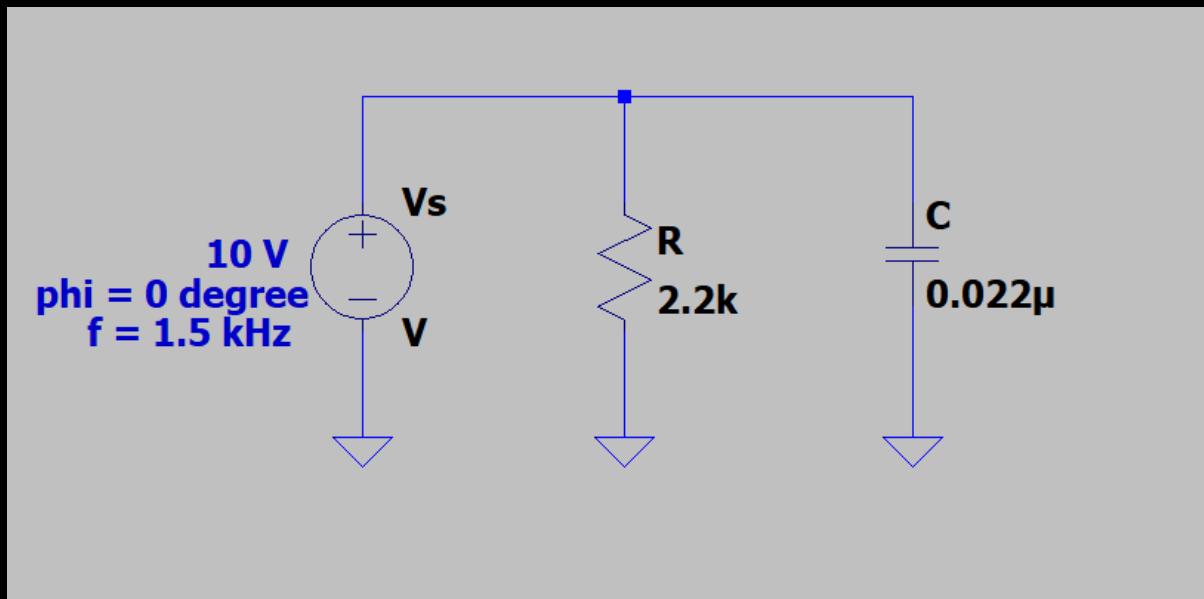

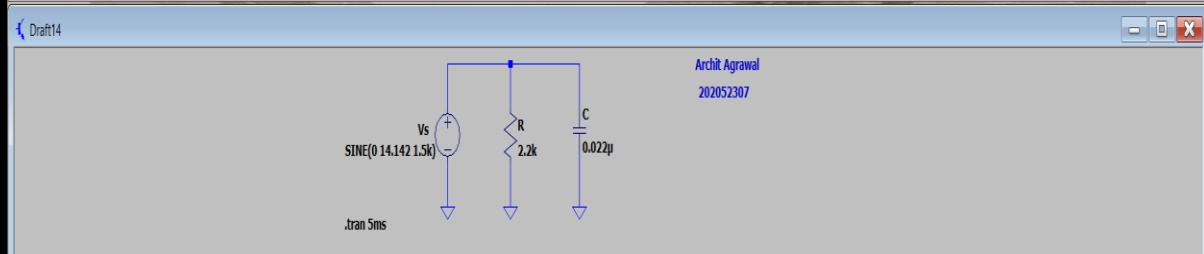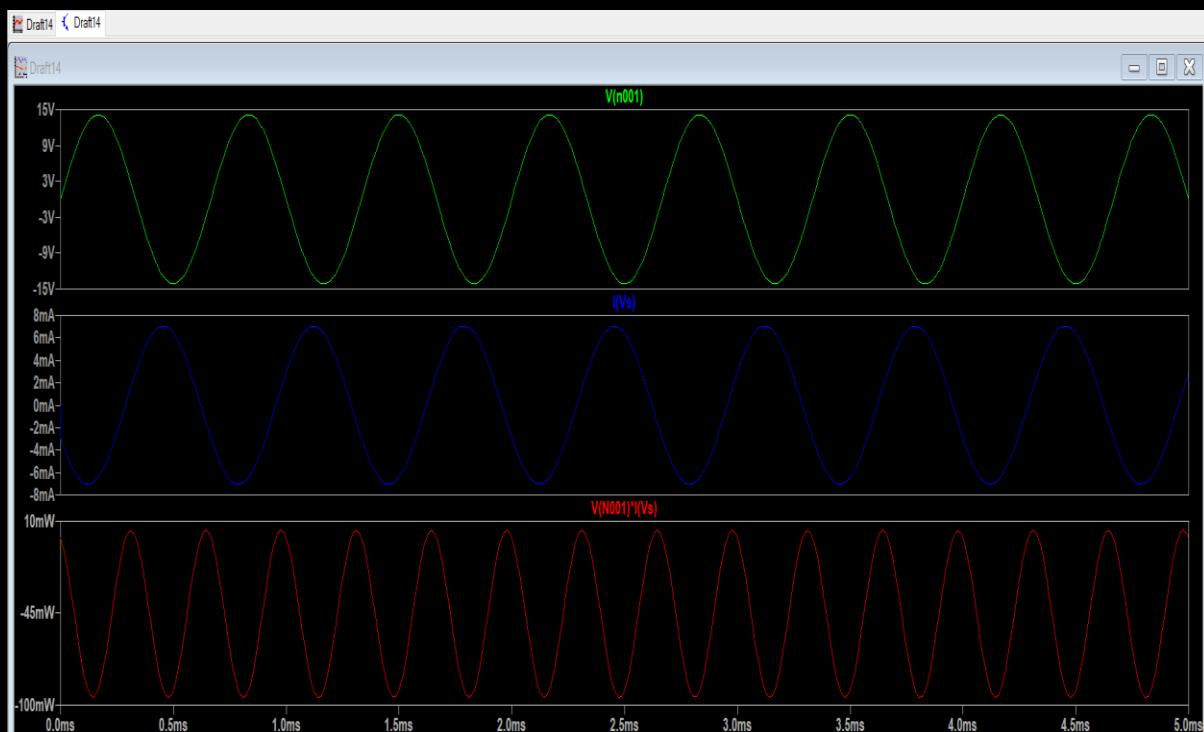
## Source Voltage, Total Current and Total Power




# EE160 : Experiment 2
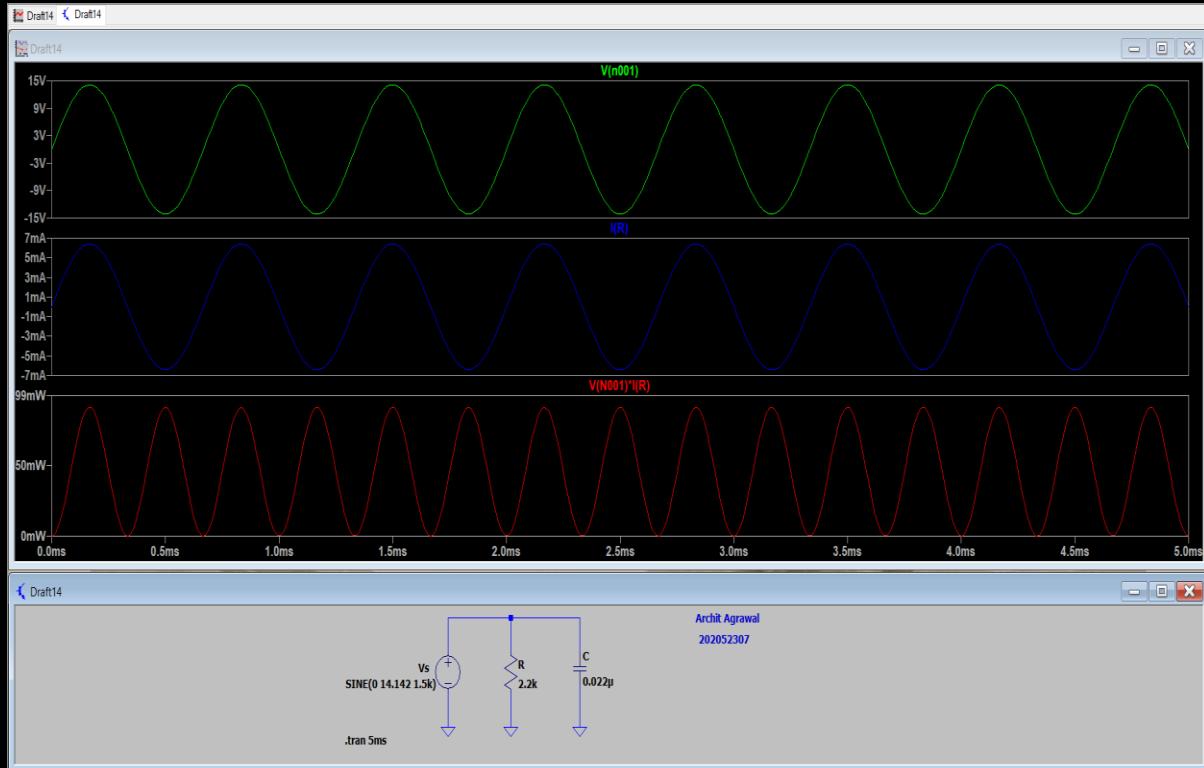
## Voltage, current and Power across Resistor


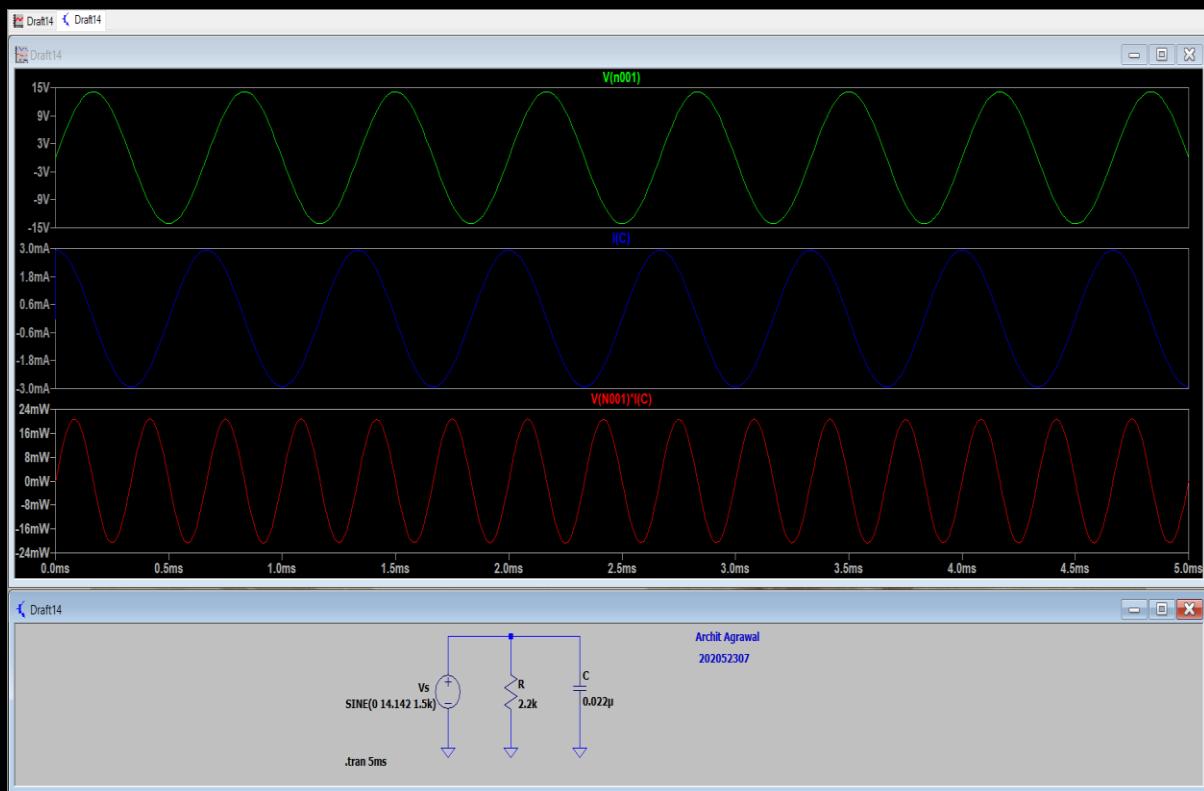
## Voltage, current and Power across Capacitor




# EE160 : Experiment 2

## AC Analysis


```
* C:\Users\Archit\Documents\LTspiceXVII\Draft14.asc
--- AC Analysis ---

frequency:      1500          Hz
V(n001) :       mag:        10 phase:      0°           voltage
I(C) :          mag: 0.00207345 phase:    90°           device_current
I(R) :          mag: 0.00454545 phase:     0°           device_current
I(Vs) :         mag: 0.00499603 phase: -155.479°       device_current
```

## CIRCUIT 2

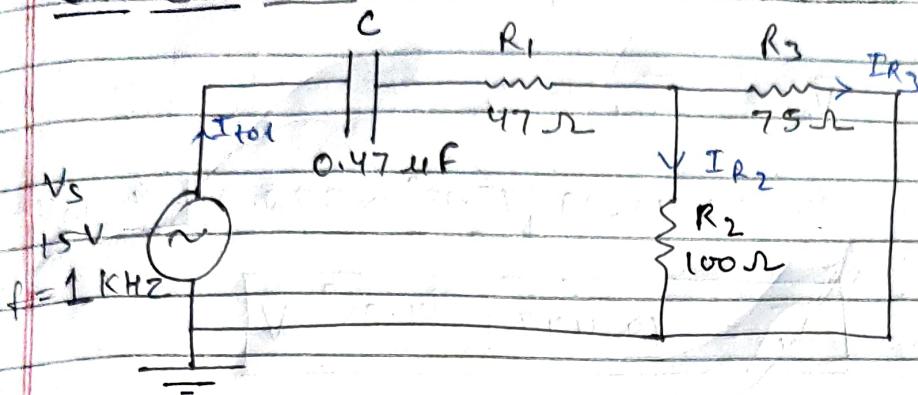

The circuit can be redrawn as

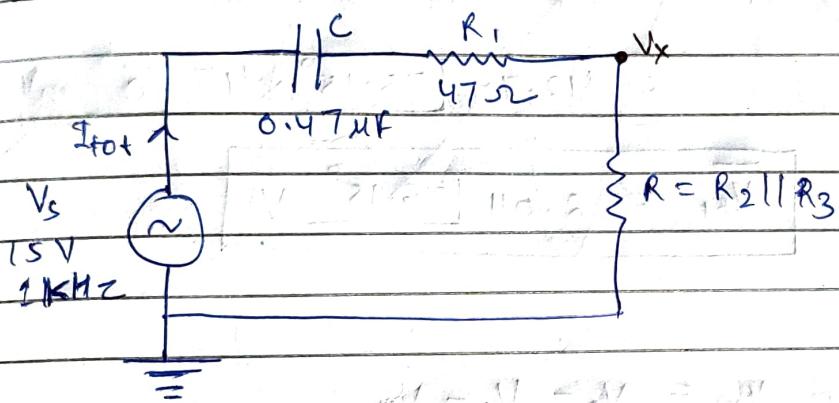

$$\therefore R = \frac{100 \times 75}{100 + 75} = 42.857 \Omega$$

$$V_x = 15 \sin(2\pi \times 1000t) - 175 \sin(2\pi \times 1000t) = -160 \sin(2\pi \times 1000t)$$

$$X_C = \frac{1}{j \omega C} = \frac{1}{j \times 2\pi \times 1000 \times 0.47 \times 10^{-6}} = 338.8 \Omega$$

$$Z = (47 + j42.857) + j(338.8) \Omega$$

$$Z = 350.50 \angle 75.15^\circ \Omega$$

$$\therefore I_{tot} = \frac{V_s}{Z} = \frac{15 \angle 0^\circ}{350.50 \angle 75.15^\circ}$$

$$I_{tot} = 42.79 \angle 75.15^\circ \text{ mA}$$

$$I_{tot} = 10.967 + j(41.36) \text{ mA}$$

Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 7

$$\therefore \bar{I}_c = \bar{I}_{R_1} = \bar{I}_{tot}$$

$$\therefore \bar{V}_c = \bar{I}_{tot} \times Z_c$$

$$\bar{V}_c = 42.79 | 75.15^\circ \times 338.8 | -90^\circ \text{ mV}$$

$$\boxed{\bar{V}_c = 44.497 | -14.85^\circ \text{ V}}$$

and  $\bar{V}_{R_1} = \bar{I}_{tot} \times \bar{Z}_{R_1}$

$$= 42.79 | 75.15^\circ \times 47 | 0^\circ \text{ mV}$$

$$\boxed{\bar{V}_{R_1} = 2.011 | 75.15^\circ \text{ V}}$$

$$\therefore \text{Now, } V_x = V_s - V_c - V_{R_1}$$

$$\text{and, } V_c = 14.013 - j(3.715) \text{ V}$$

$$\text{and, } V_{R_1} = 0.515 + j(1.944) \text{ V}$$

$$\therefore V_x = 15 - (14.013 - j(3.715)) - (0.515 + j(1.944))$$

$$V_x = 0.472 + j(1.771) \text{ V}$$

$$\bar{V}_x = 1.834 | 75.15^\circ \text{ V}$$

Since,  $\bar{V}_{R_2} = \bar{V}_{R_3} = \bar{V}_x = 1.834 | 75.15^\circ \text{ V}$

$$\therefore \bar{I}_{R_2} = \frac{\bar{V}_{R_2}}{\bar{Z}_{R_2}} = \frac{1.834 | 75.15^\circ}{100 | 0^\circ} \text{ A}$$

$$\boxed{\bar{I}_{R_2} = 18.34 | 75.15^\circ \text{ mA}}$$


Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 8

$$\bar{I}_{R_3} = \frac{\bar{V}_{R_3}}{Z_{R_3}} = \frac{1.834}{75} \angle 75.15^\circ \text{ A}$$

$$\bar{I}_{R_2} = 24.453 \angle 75.15^\circ \text{ mA}$$

### Phasor Diagram

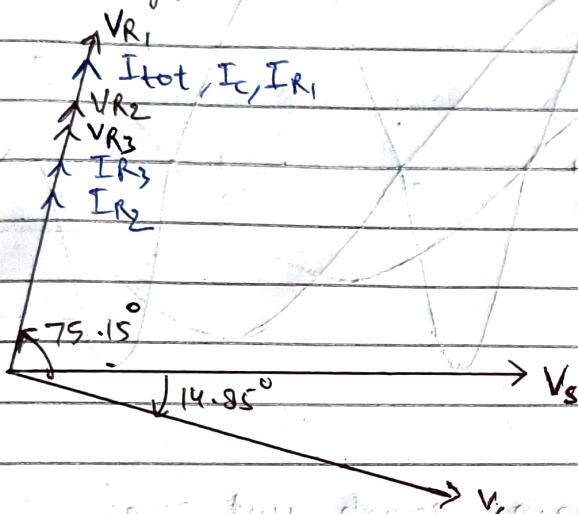

### Time Domain

Given  $\bar{V}_s = 15 \angle 0^\circ \text{ V}$

$V_{rms} = 15 \text{ V}$

$$V_m = 15\sqrt{2} \text{ V}$$

In time domain, we write peak value

$$V_s = 15\sqrt{2} \sin(6280t + 0^\circ)$$

$$V_c = 14.447\sqrt{2} \sin(6280t + 75.15^\circ - 90^\circ) \text{ V}$$

$$V_c = 14.447\sqrt{2} \sin(6280t - 14.85^\circ) \text{ V}$$

$$V_{R_1} = 2.011\sqrt{2} \sin(6280t + 75.15^\circ) \text{ V}$$

$$V_{R_2} = V_{R_3} = 1.834\sqrt{2} \sin(6280t + 75.15^\circ) \text{ V}$$


Name: Archit Agrawal  
 Student ID: 202052307

Date: \_\_\_\_\_  
 Page: 9

$$I_{\text{tot}} = I_c = I_{R_1} = 42.79\sqrt{2} \sin(6280t + 75.15^\circ) \text{ mA}$$

$$I_{R_2} = 18.34\sqrt{2} \sin(6280t + 75.15^\circ) \text{ mA}$$
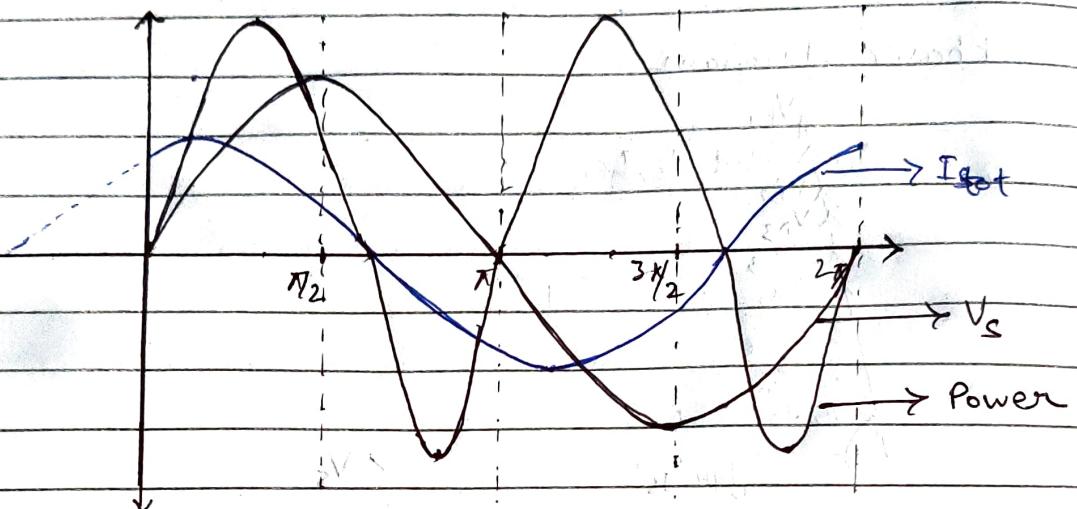
$$I_{R_3} = 24.453\sqrt{2} \sin(6280t + 75.15^\circ) \text{ mA}$$




an idea

The time domain graph just gives us of phase of  $V_s$  and  $I_{\text{tot}}$  and the magnitude of  $I_{\text{tot}}$ ,  $V_s$  and power are not implied by it.

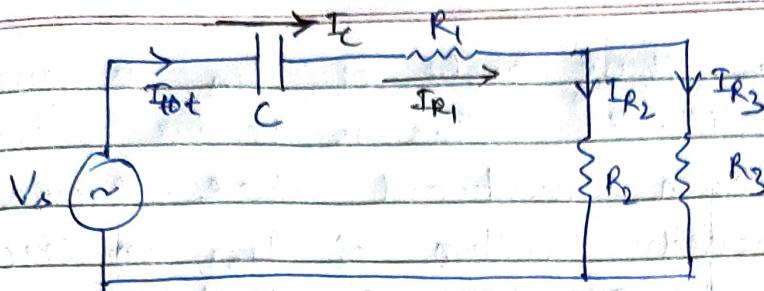
### Comparison between Spice Simulations and Theory Calculations

We can see the time domain graph of  $I_{\text{tot}}$  and total power is inverted. The reason behind this is explained below.

The direction of currents chosen for theory calculations are drawn in the circuit



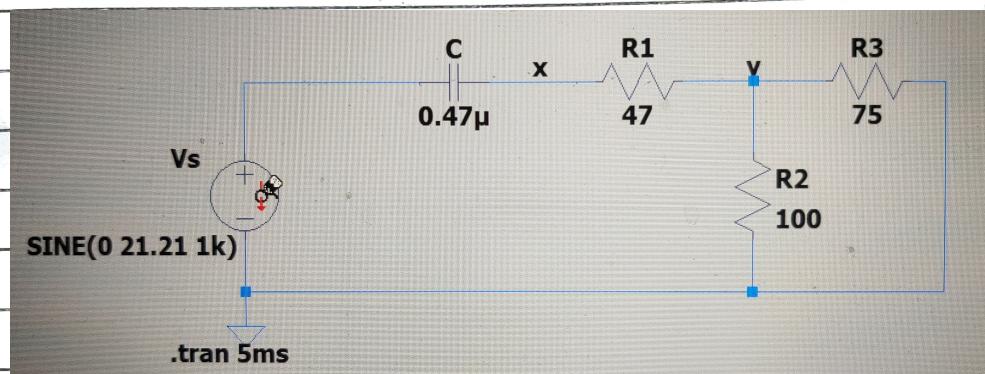On SPICE, the direction of currents is same as this except for the direction of  ~~$I_{tot}$~~   $I_{tot}$ .



As you can see the arrow is pointing downwards. That is why, the total current and total power time domain graphs are inverted on SPICE.

Now, the phase angles

Component	Angle
$V_s$	$0^\circ$
$V_c$	$-14.85^\circ$
$V_{R_1}, V_{R_2}, V_{R_3}$	$75.15^\circ$
$I_{tot}, I_c, I_{R_1}$	$75.15^\circ$
$I_{R_2}, I_{R_3}$	$75.15^\circ$

Name: Archit Agrawal  
Student ID: 202052307


Date:

Page: 11



On SPICE, phase angle of  $I_{tot}$  is given to be  $-104.86^\circ$ . This is because of the same reason mentioned above. Because of the reversed direction of  $I_{tot}$  on SPICE, the phase decreases by  $180^\circ$ . Clearly,  $75.15^\circ - 180^\circ \approx -104.86^\circ$ .

# EE160 : Experiment 2

## Circuit

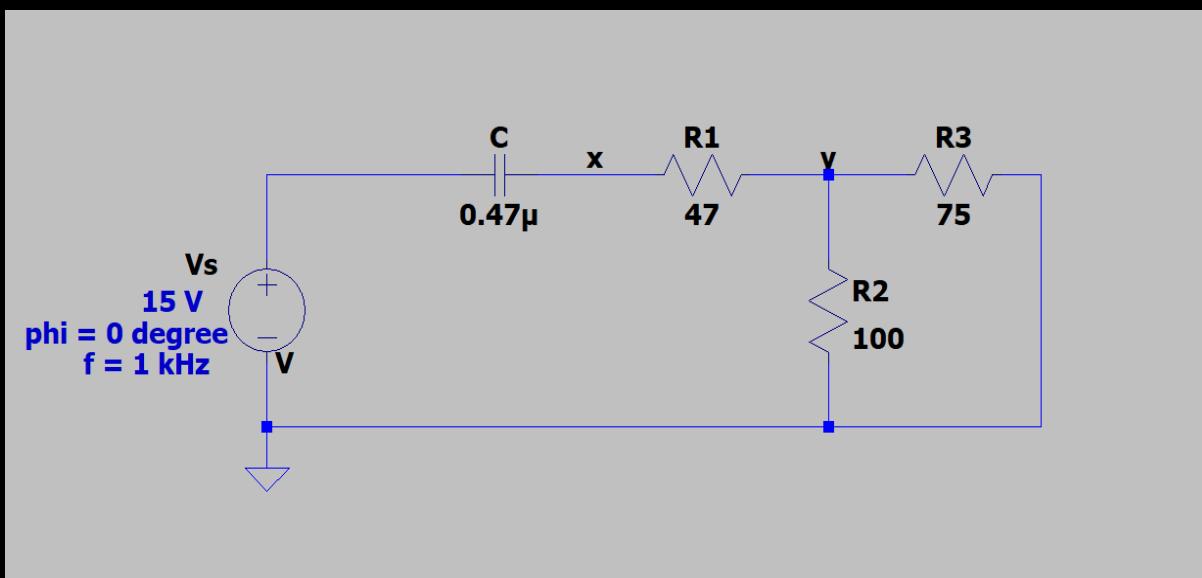

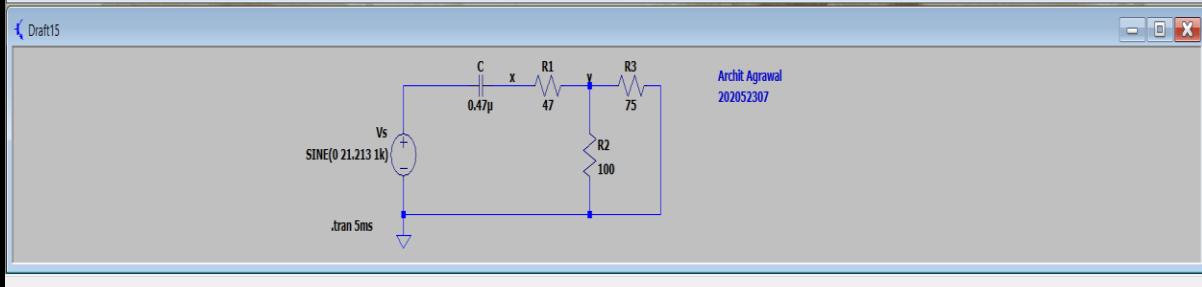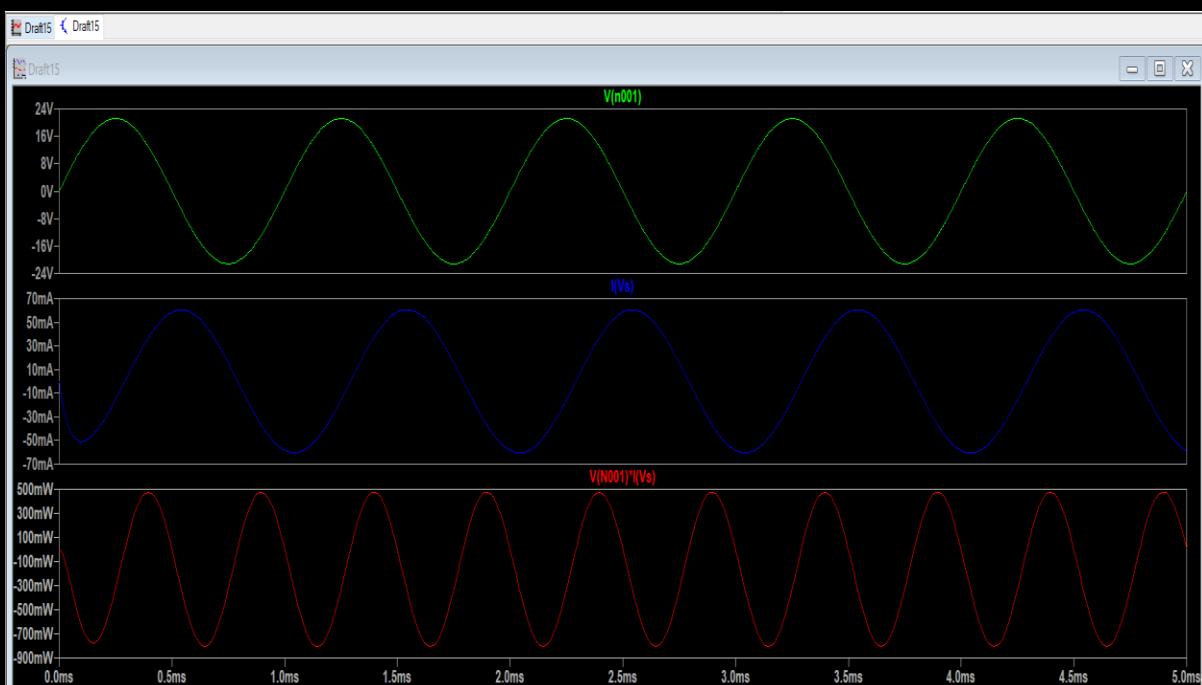
## Source Voltage, Total Current and Total Power




# EE160 : Experiment 2
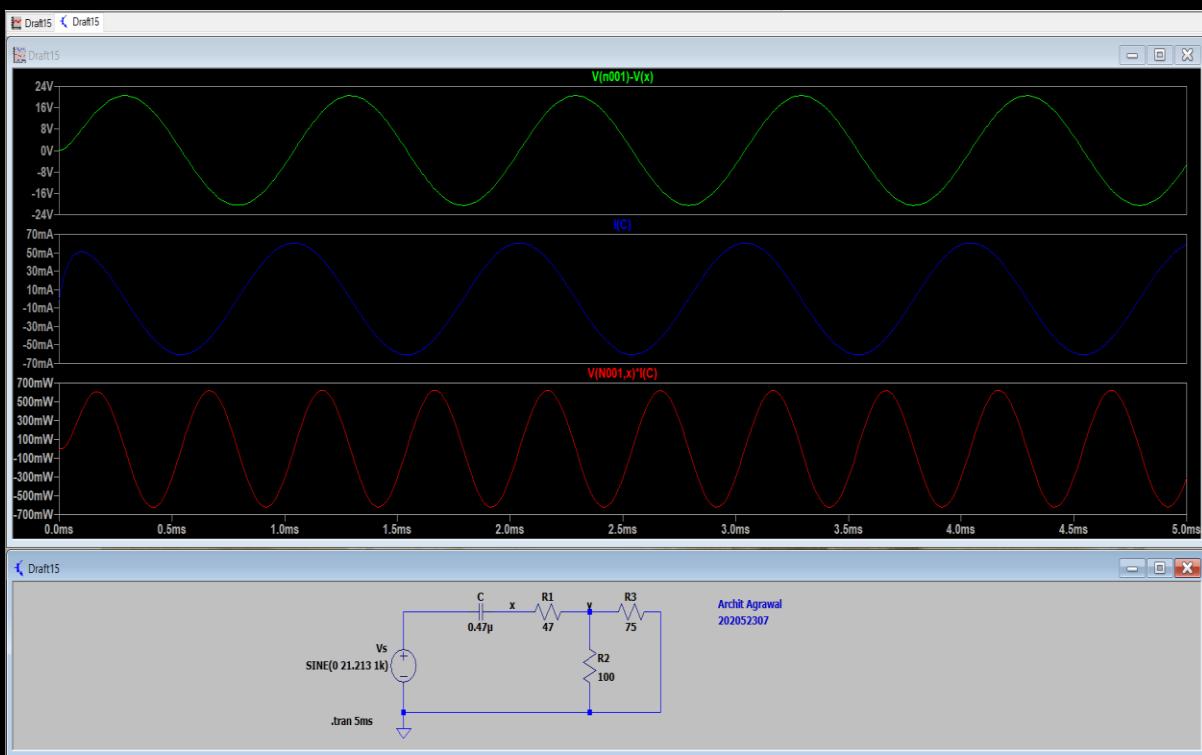
## Voltage, current and Power across Capacitor



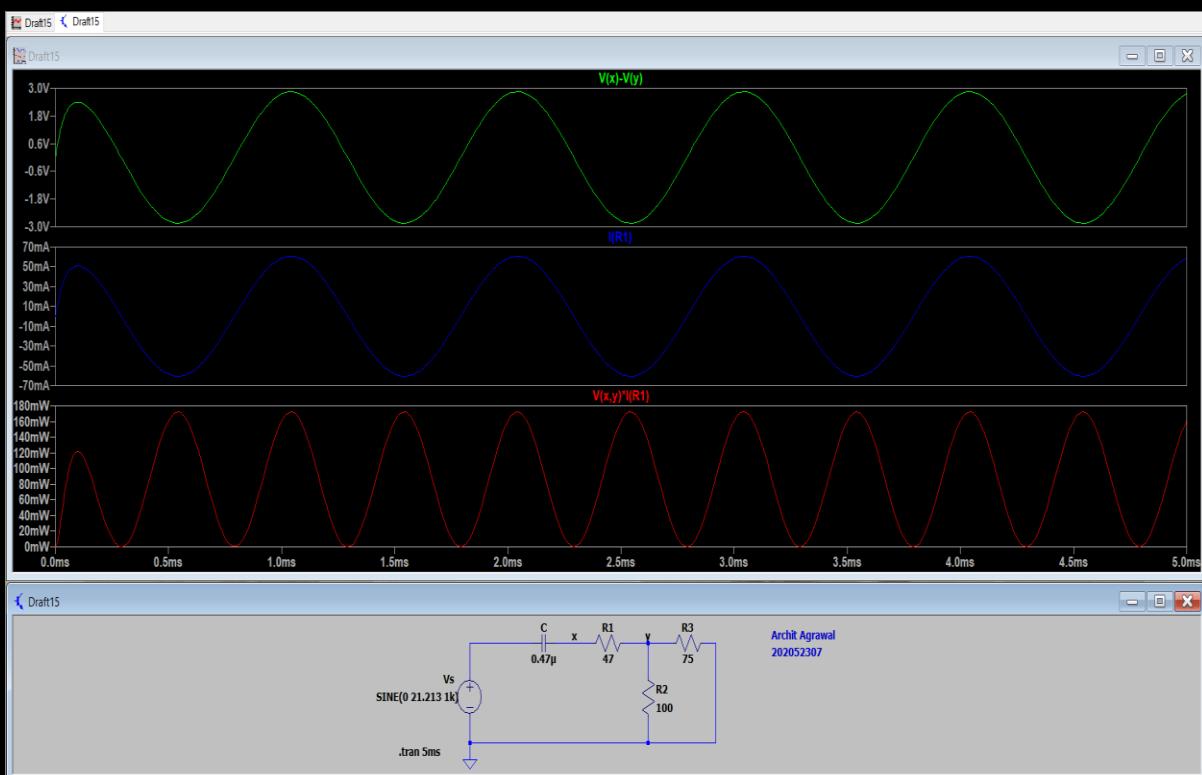
## Voltage, current and Power across Resistor $R_1$




# EE160 : Experiment 2
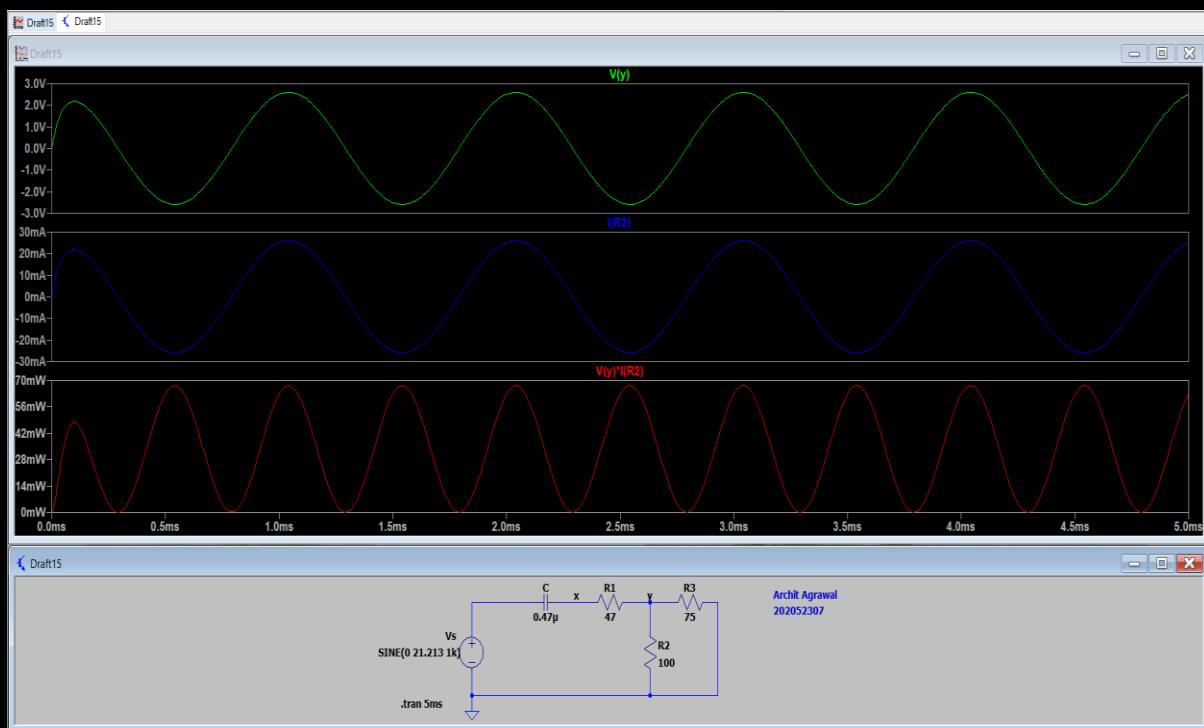
## Voltage, current and Power across Resistor $R_2$


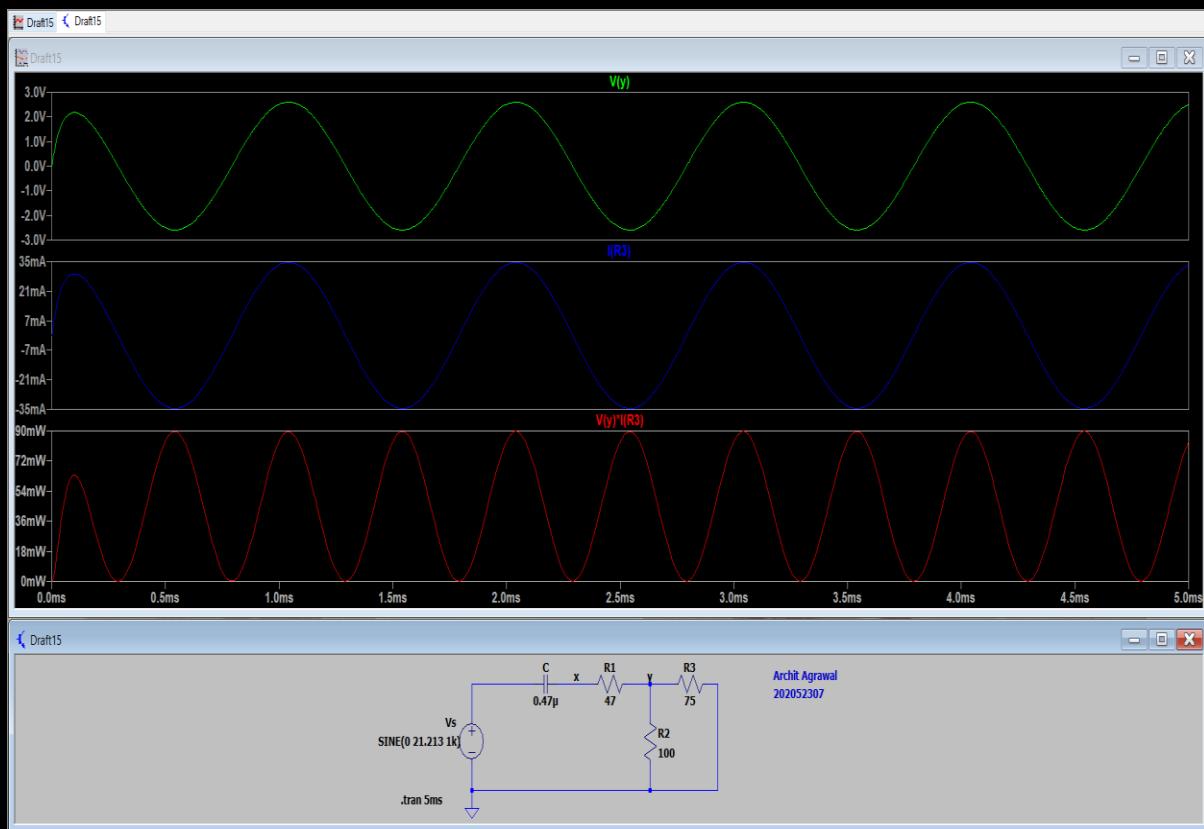
## Voltage, current and Power across Resistor $R_3$




# EE160 : Experiment 2

## AC Analysis


```
* C:\Users\Archit\Documents\LTspiceXVII\Draft15.asc
--- AC Analysis ---

frequency:      1000          Hz
V(n001):        mag:    15 phase: 1.6963e-015°      voltage
V(x):           mag:  3.84721 phase: 75.1387°      voltage
V(y):           mag: 1.83492 phase: 75.1387°      voltage
I(C):           mag: 0.0428147 phase: 75.1387°      device_current
I(R3):          mag: 0.0244656 phase: 75.1387°      device_current
I(R1):          mag: 0.0428147 phase: 75.1387°      device_current
I(R2):          mag: 0.0183492 phase: 75.1387°      device_current
I(Vs):          mag: 0.0428147 phase: -104.861°      device_current
```

### CIRCUIT 3 :-

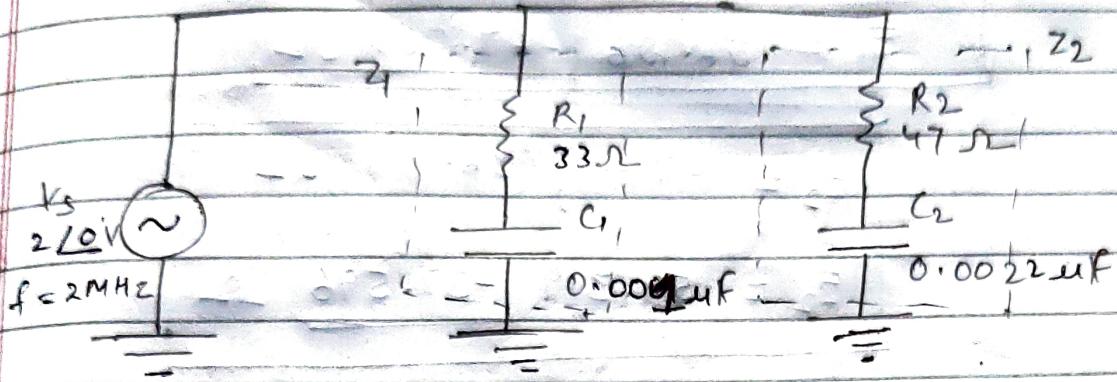

the circuit can be redrawn as

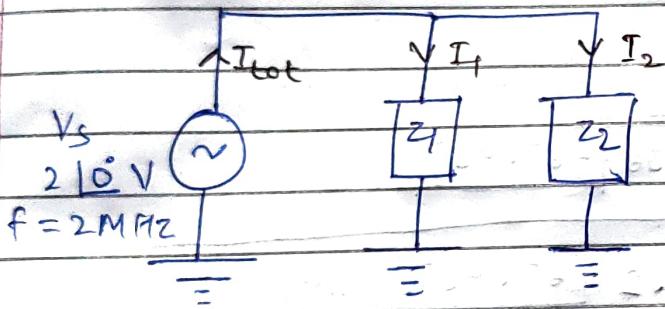

where  $Z_1$  and  $Z_2$  are net impedances of  $R_1, C_1$  and  $R_2, C_2$  respectively.

$$X_{C_1} = \frac{1}{2\pi f(C_1)} = \frac{1}{2 \times 3.14 \times 2M \times 0.001 \mu}$$

$$X_{C_1} = 79.61 \Omega$$

$$\text{and } X_{C_2} = \frac{1}{2\pi f(C_2)} = \frac{1}{2 \times 3.14 \times 2M \times 0.0022 \mu}$$

$$X_{C_2} = 36.19 \Omega$$

Name : Archit Agrawal  
Student ID : 202052307

Date:

Page:

13

$$\therefore Z_1 = 33 + j(79.618) \Omega$$

$$\bar{Z}_1 = 86.186 \angle -67.487^\circ \Omega$$

and  $Z_2 = 47 - j(36.19) \Omega$

$$\bar{Z}_2 = 59.319 \angle -37.596^\circ \Omega$$

$$\therefore \bar{I}_1 = \frac{\bar{V}_S}{\bar{Z}_1}$$

$$= 2 \angle 0^\circ \text{ A}$$

$$86.186 \angle -67.487^\circ$$

$$\bar{I}_1 = 23.2 \angle 67.487^\circ \text{ mA}$$

$$I_1 = 8.083 + j(21.432) \text{ mA}$$

and  $\bar{I}_2 = \frac{\bar{V}_S}{\bar{Z}_2}$

$$= 2 \angle 0^\circ \text{ A}$$

$$59.319 \angle -37.596^\circ$$

$$\bar{I}_2 = 33.72 \angle 37.596^\circ \text{ mA}$$

$$I_2 = 26.72 + j(20.57) \text{ mA}$$

from KCL,

$$I_{\text{tot}} = I_1 + I_2$$

$$I_{\text{tot}} = (8.083 + 26.72) + j(21.432 + 20.57) \text{ mA}$$

Name: Archit B Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 14

$$I_{\text{tot}} = 35.603 + j(42.002) \text{ mA}$$

$$\boxed{\overline{I}_{\text{tot}} = 55.061 [49.713^\circ] \text{ mA}}$$

$$\therefore \overline{I}_{R_1} = \overline{I}_{C_1} = \overline{I}_i = 23.2 [67.487^\circ] \text{ mA}$$

$$\therefore \overline{V}_{R_1} = \overline{I}_{R_1} \times \overline{Z}_{R_1}$$

$$= 23.2 [67.487 \times 33] 0^\circ \text{ mV}$$

$$\boxed{\overline{V}_{R_1} = 0.766 [67.487^\circ] \text{ V}}$$

$$\text{and, } \overline{V}_{C_1} = \overline{I}_{C_1} \times \overline{Z}_{C_1}$$

$$= 23.2 [67.487 \times 79.618] -90^\circ \text{ mV}$$

$$\boxed{\overline{V}_{C_1} = 1.847 [-22.513^\circ] \text{ V}}$$

$$\therefore \overline{I}_{R_2} = \overline{I}_{C_2} = \overline{I}_o = 33.72 [37.596^\circ] \text{ mA}$$

$$\therefore \overline{V}_{R_2} = \overline{I}_{R_2} \times \overline{Z}_{R_2}$$

$$= 33.72 [37.596^\circ \times 47] 0^\circ \text{ mV}$$


$$\boxed{\overline{V}_{R_2} = 1.585 [37.596^\circ] \text{ V}}$$

$$\text{and, } \overline{V}_{C_2} = \overline{I}_{C_2} \times \overline{Z}_{C_2}$$

$$= 33.72 [37.596 \times 36.19] -90^\circ \text{ mV}$$

$$\boxed{\overline{V}_{C_2} = 1.22 [-52.404^\circ] \text{ V}}$$

### Phasor Diagram

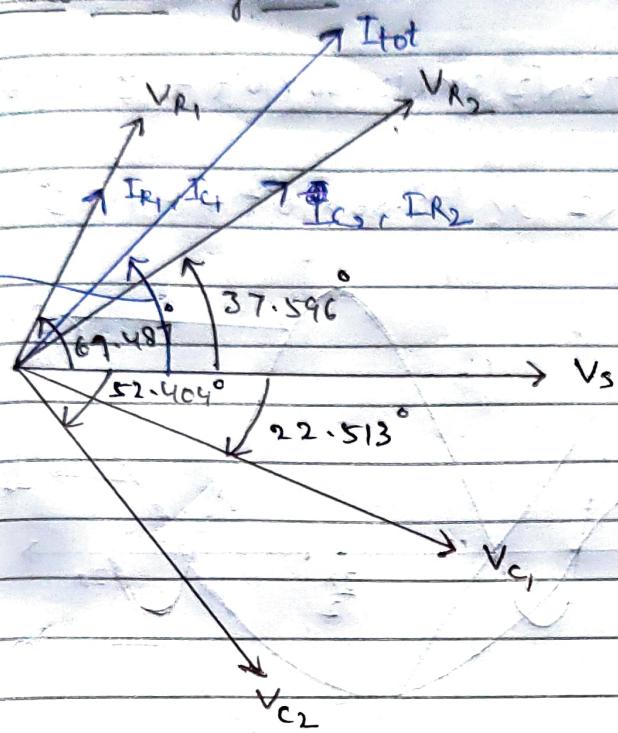

### Time Domain

Given  $V_s = 210^\circ \text{ V}$

$$\therefore V_{rms} = 2 \text{ V}$$

$$\therefore V_m = 2\sqrt{2} \text{ V}$$

In time domain, we write peak values,

$$\therefore V_s = 2\sqrt{2} \sin(12.56 \times 10^6 t + 0^\circ) \text{ V}$$

$$V_{R1} = 0.766 \sqrt{2} \sin(12.56 \times 10^6 t + 67.487^\circ) \text{ V}$$

$$V_{C1} = 1.847 \sqrt{2} \sin(12.56 \times 10^6 t - 22.513^\circ) \text{ V}$$

$$V_{R2} = 1.585 \sqrt{2} \sin(12.56 \times 10^6 t + 37.596^\circ) \text{ V}$$

$$V_{C2} = 1.22 \sqrt{2} \sin(12.56 \times 10^6 t - 52.404^\circ) \text{ V}$$


Name: Archit Agrawal  
Student ID: 201052307

Date: \_\_\_\_\_  
Page: 16

$$I_{R_1} = I_C = 23.2\sqrt{2} \sin(12.56 \times 10^6 t + 67.487^\circ) \text{ mA}$$

$$I_{R_2} = I_C = 33.72\sqrt{2} \sin(12.56 \times 10^6 t + 37.596^\circ) \text{ mA}$$
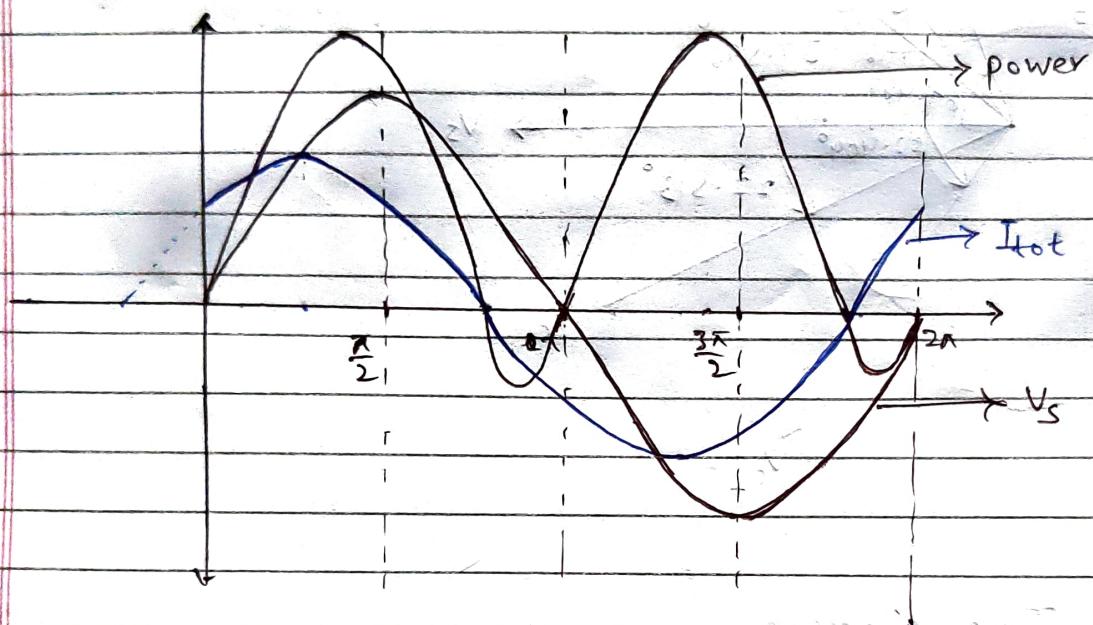
$$I_{\text{tot}} = 55.061\sqrt{2} \sin(12.56 \times 10^6 t + 49.713^\circ) \text{ mA}$$




The time domain graph just gives an idea of phase of  $V_s$  and  $I_{\text{tot}}$  and the magnitude of  $I_{\text{tot}}$ ,  $V_s$  and power is not implied by it.

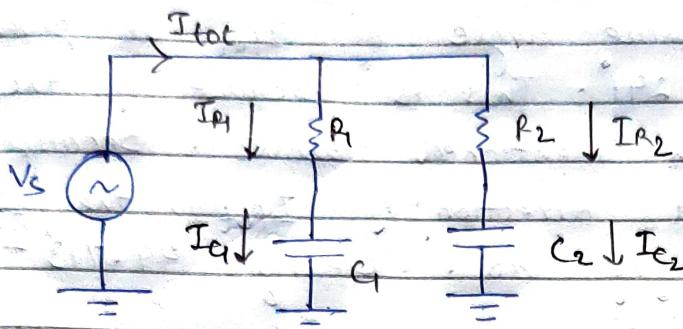
### Comparison between SPICE Simulations and Theory Calculations

We can see the time domain graph of  $I_{\text{tot}}$  and total power are inverted on SPICE. The reason behind this is explained below -

The direction chosen for theory calculations are given in the circuit



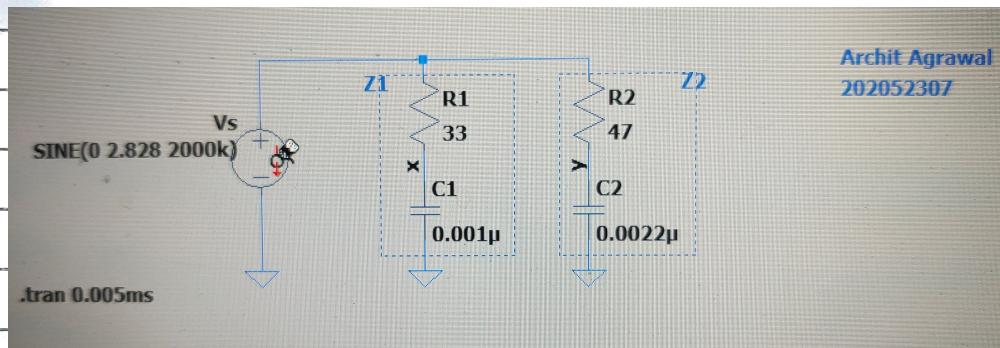On SPICE, the direction of currents are similar to this except for  $I_{tot}$ .



As you can see the arrow is pointing downwards. That is why, the total power and total current time domain graphs are inverted on SPICE.

Now, the phase angles

Component	Angle
$V_s$	$0^\circ$
$V_{R_1}$	$67.487^\circ$
$V_{R_2}$	$37.596^\circ$
$V_{C_1}$	$-22.513^\circ$
$V_{C_2}$	$-52.404^\circ$
$I_{tot}$	$49.713^\circ$
$I_{R_1}, I_{C_1}$	$67.487^\circ$
$I_{R_2}, I_{C_2}$	$37.596^\circ$


Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 18


In SPICE, phase angle of  $I_{tot}$  is given to be  $-130.29^\circ$ . This is because of the same reason mentioned above. Because of the reversed direction of  $I_{tot}$ , the phase decreases by  $180^\circ$ . Clearly  $49.713^\circ - 180^\circ \approx 130.29^\circ$ .

# EE160 : Experiment 2

## Circuit

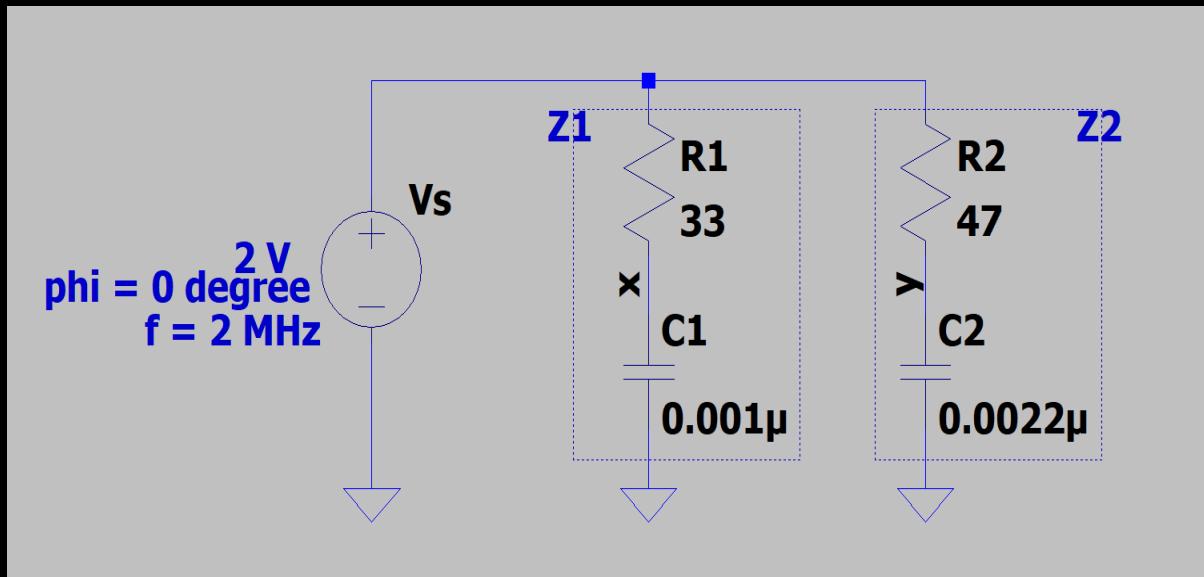

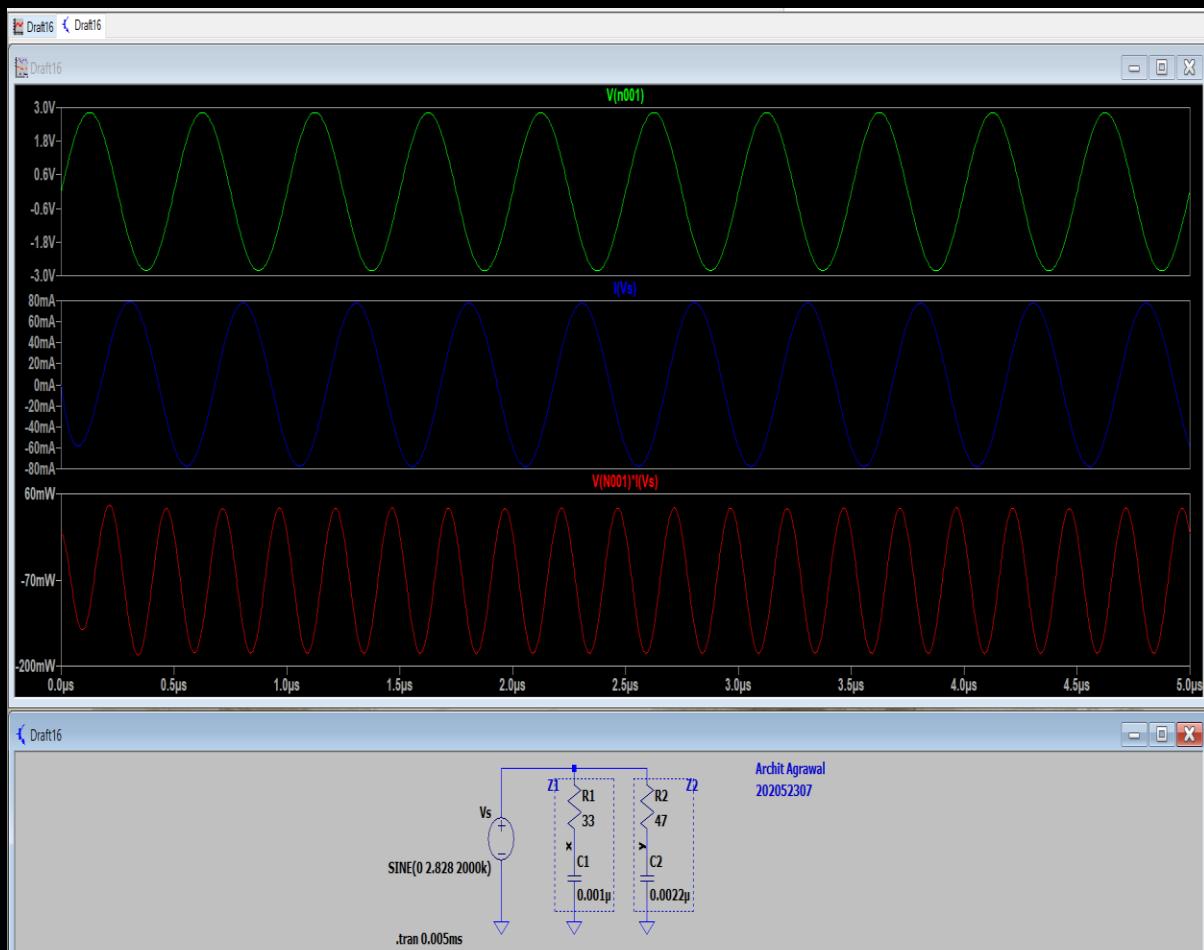
## Source Voltage, Total Current and Total Power




# EE160 : Experiment 2
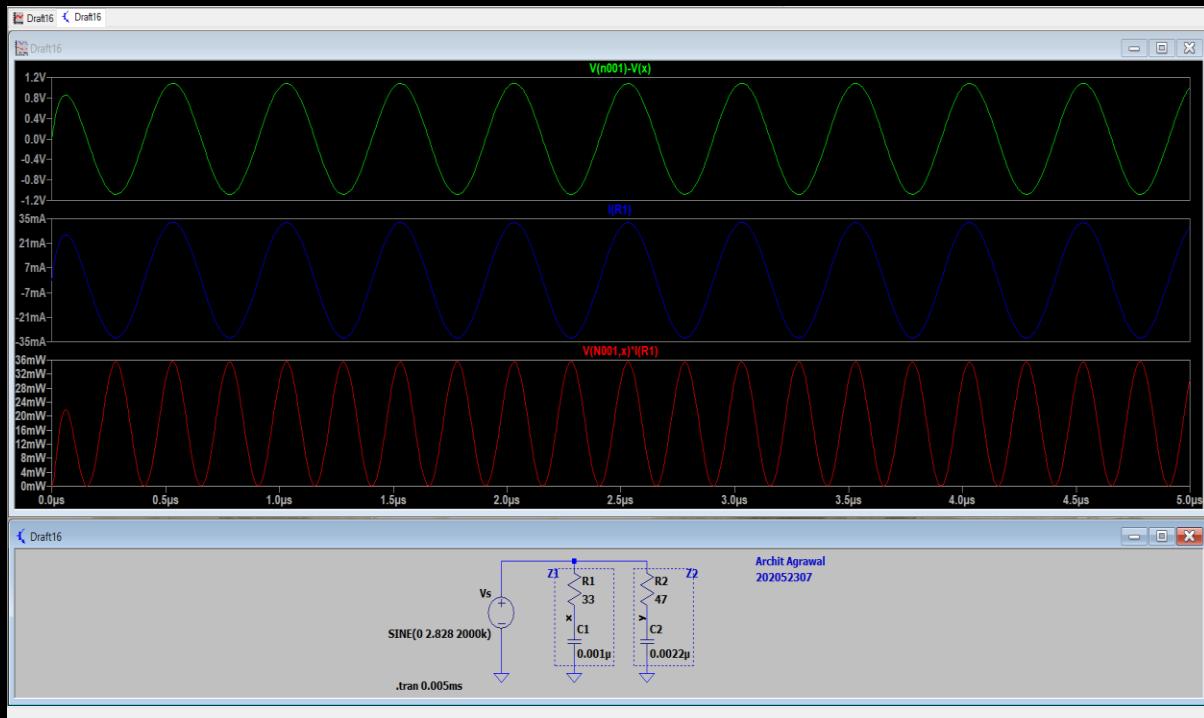
## Voltage, current and Power across Resistor $R_1$



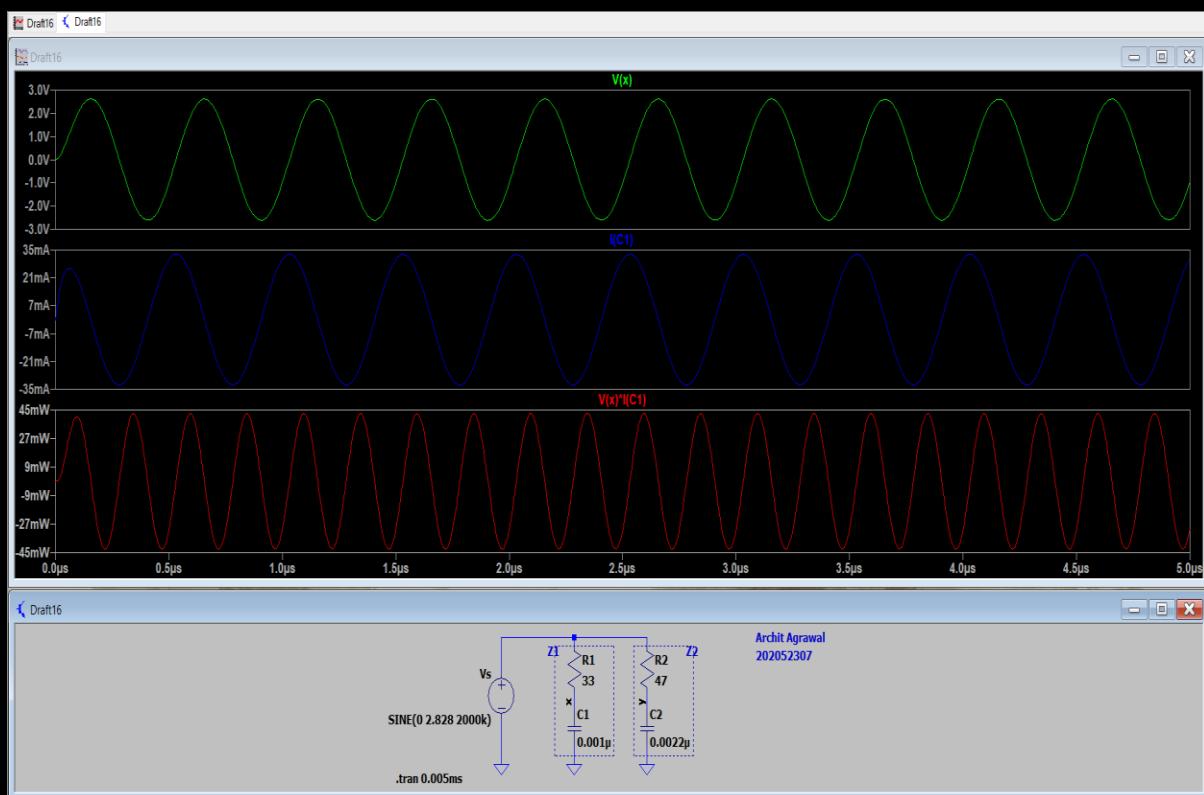
## Voltage, current and Power across Capacitor $C_1$




# EE160 : Experiment 2
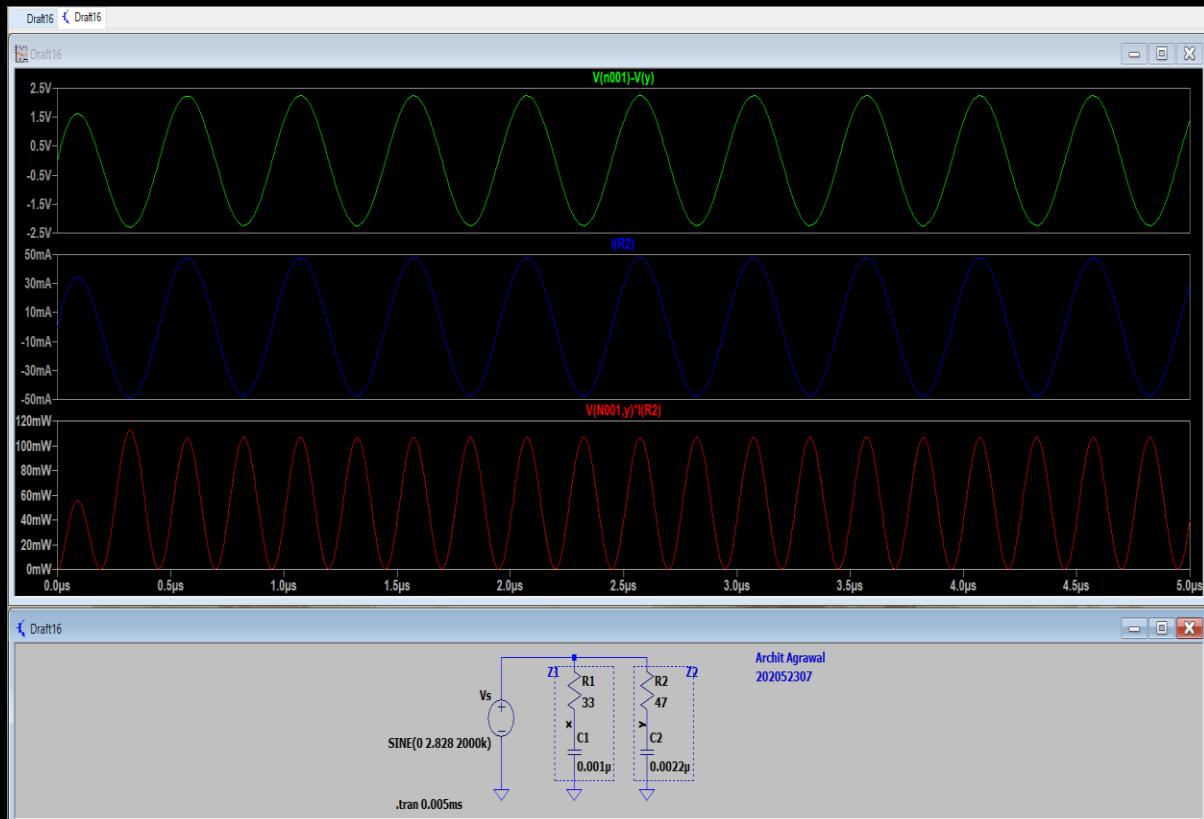
## Voltage, current and Power across Resistor $R_2$


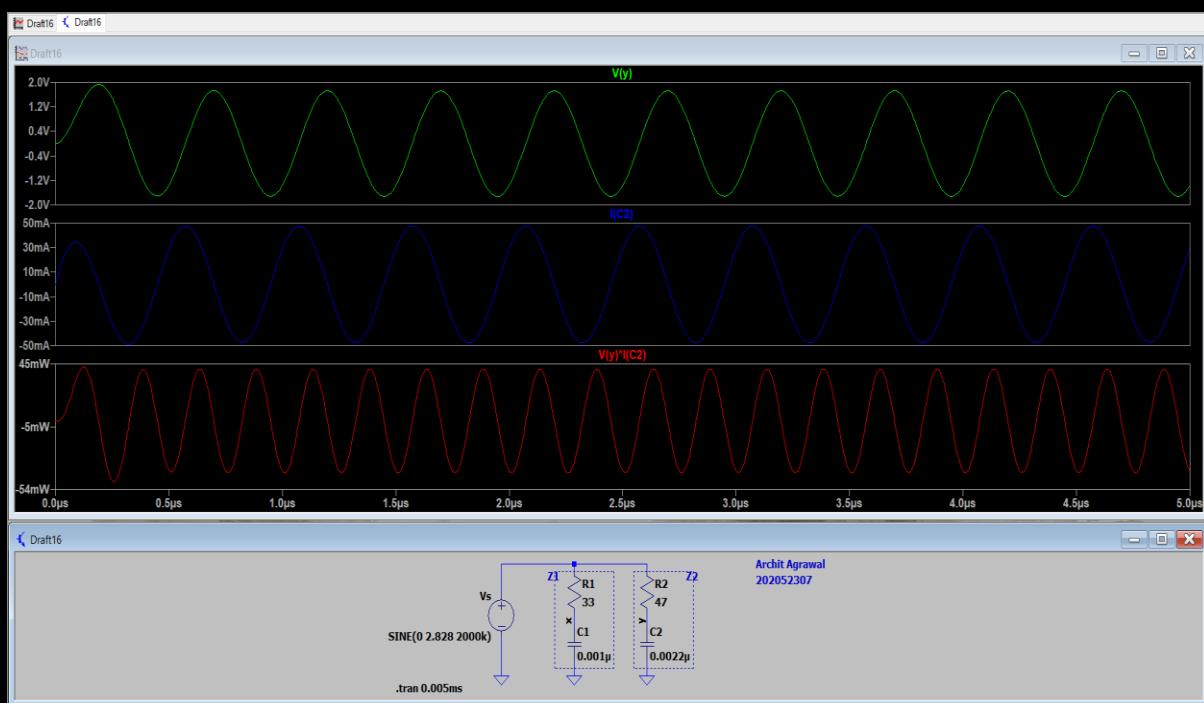
## Voltage, current and Power across Capacitor $C_2$



# EE160 : Experiment 2

## AC Analysis

```
* C:\Users\Archit\Documents\LTspiceXVII\Draft16.asc
--- AC Analysis ---

frequency: 2e+006 Hz
V(x): mag: 1.84745 phase: -22.5233° voltage
V(y): mag: 1.2198 phase: -52.4178° voltage
V(n001): mag: 2 phase: 0° voltage
I(C2): mag: 0.0337225 phase: 37.5822° device_current
I(C1): mag: 0.0232157 phase: 67.4767° device_current
I(R2): mag: 0.0337225 phase: 37.5822° device_current
I(R1): mag: 0.0232157 phase: 67.4767° device_current
I(Vs): mag: 0.0550784 phase: -130.291° device_current
```

### Observations and Conclusions :-

Performing the experiment, following conclusions can be drawn

- (i) the current through a resistor is in phase with the voltage across it.
- (ii) the current through a capacitor leads the voltage across it by  $90^\circ$ .
- (iii) A resistor is a power-dissipating device while a capacitor only stores and releases energy in an AC circuit.