

## EE160: Experiment 3


Objectives:- (i) Design and simulate given circuits in SPICE. Plot the voltage (across each element), currents (through each element) and total current. Find the phase difference between source voltage and all other currents and voltages.

(ii) Calculate the above required voltages and currents theoretically. Compare theoretical results with SPICE results. Draw a phasor diagram.

(iii) Perform "RLC Circuit Analysis" experiment.

Mathematical Expressions and Theoretical Calculations

### CIRCUIT 1:-

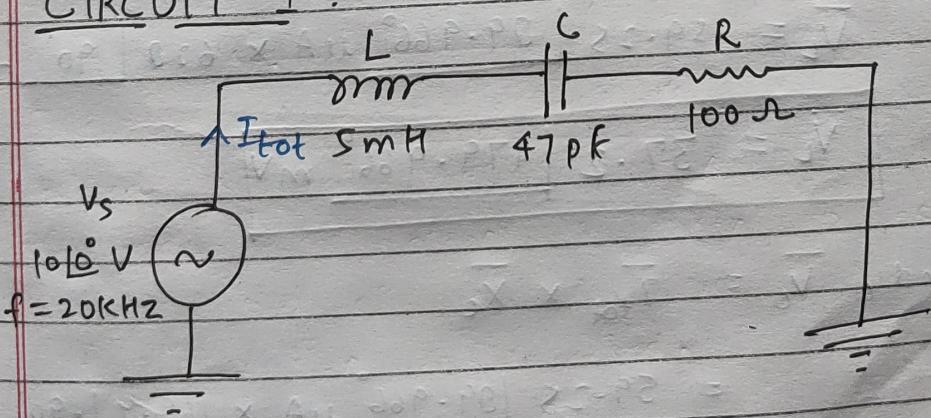

$$X_L = 2\pi f L = 628 \Omega$$

$$X_C = \frac{1}{2\pi f C} = 169399.647 \Omega = 169.4 \text{k}\Omega$$

Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 2

$$\therefore Z = R + j(X_L - X_C)$$

$$Z = 100 + j(628 - 169399.647) \Omega$$

$$Z = 100 - j168771.647 \Omega$$

$$\bar{Z} = 168771.67 \angle -89.966^\circ \Omega$$

$$\therefore \bar{I}_{tot} = \frac{\bar{V}_S}{\bar{Z}}$$

$$= \frac{10 \angle 0^\circ}{168.77 \angle -89.966^\circ} = 59.25 \angle 89.966^\circ \mu A$$

$$\boxed{\bar{I}_{tot} = 59.25 \mu A \quad \phi_{I_{tot}} = 89.966^\circ}$$

$$I_L = I_R = I_C = I_{tot} = 59.25 \angle 89.966^\circ \mu A$$

$$\therefore \bar{V}_L = \bar{I}_{tot} \times \bar{X}_L$$

$$\bar{V}_L = 59.25 \angle 89.966^\circ \mu A \times 628 \angle 90^\circ \Omega$$

$$\boxed{\bar{V}_L = 37.2 \angle 179.966^\circ mV}$$

$$\text{and, } \bar{V}_C = \bar{I}_{tot} \times \bar{X}_C$$

$$= 59.25 \angle 89.966^\circ \mu A \times 169.4 \angle -90^\circ K\Omega$$

$$\boxed{\bar{V}_C = 10.037 \angle -0.034^\circ V}$$

and  $\bar{V}_R = \bar{I}_{tot} \times \bar{R}$

$$= 59.25 [89.966^\circ] \mu A \times 100 \Omega [0^\circ]$$

$$\boxed{\bar{V}_R = 5.925 [89.966^\circ] mV}$$


Phase Difference between source voltage and total current  $\phi$ .

$$\phi = \phi_v - \phi_{I_{tot}}$$

$$= 0^\circ - 89.966^\circ$$

$$\boxed{\phi = -89.966^\circ}$$


### Phasor Diagram

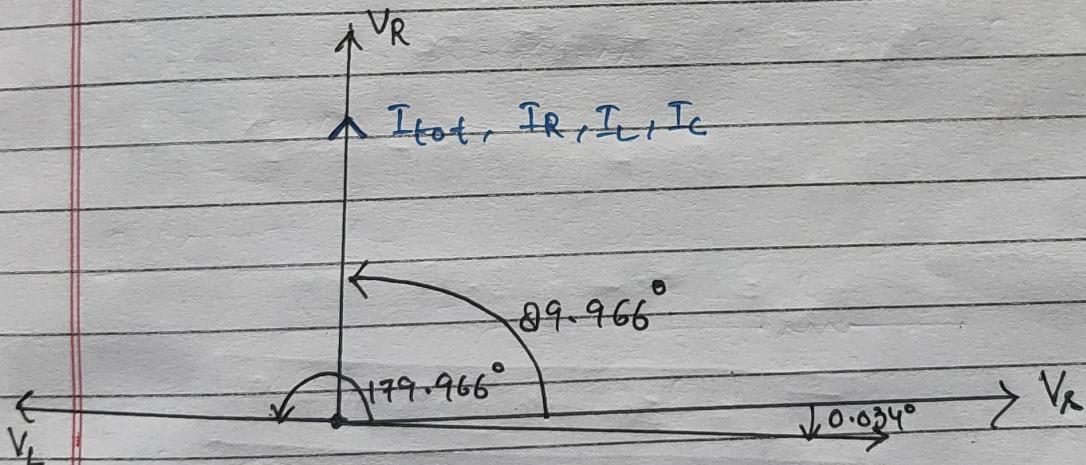
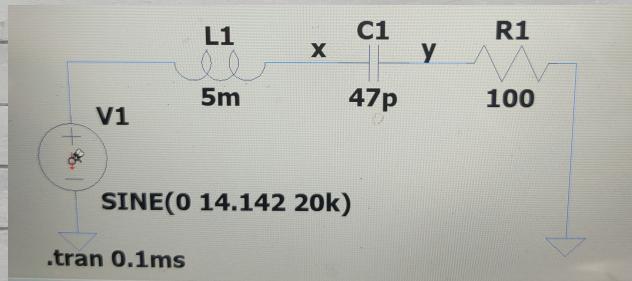
### Comparison between Spice Results and Theory Calculations

The theoretical results match well with the SPICE AC-Analysis results. The only error in SPICE results is that it shows the phase angle of  $I_{tot}$  to be  $-90.034^\circ$ .


This is not an error actually, the reason behind this is that the direction of current ( $I_{tot}$ ) for theory calculation is taken to be coming out from voltage source's positive terminal, but in SPICE this direction is reversed.




Hence, the phase of  $I_{tot}$  reduces by  $180^\circ$  in SPICE. Clearly,  $89.966^\circ - 180^\circ = -90.034^\circ$ .

# EE160 : Experiment 3

## Circuit

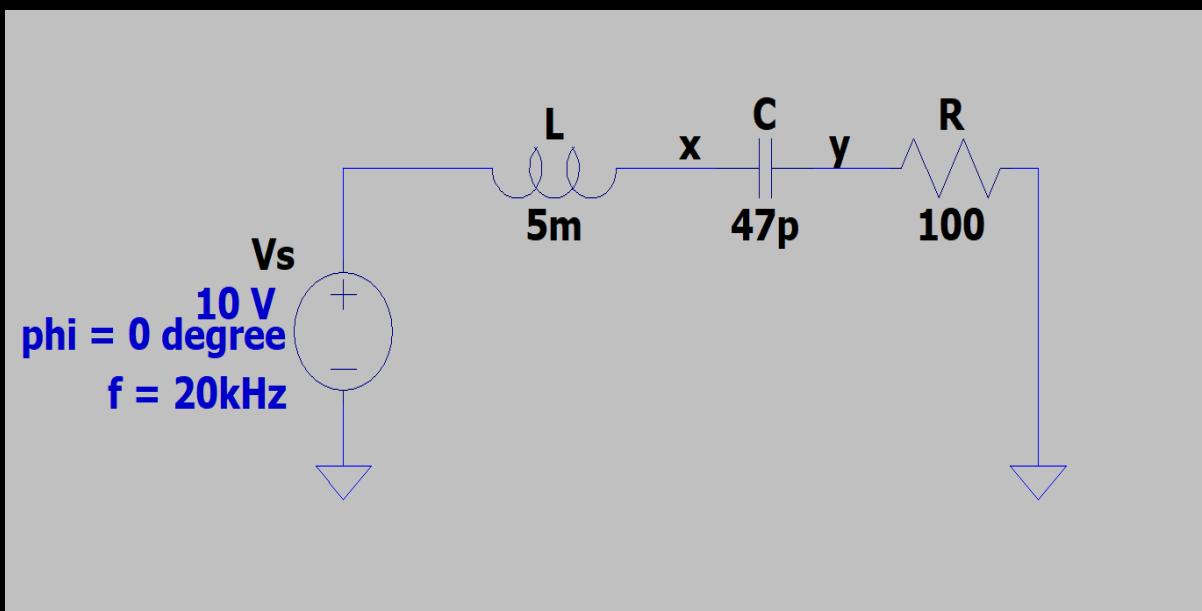

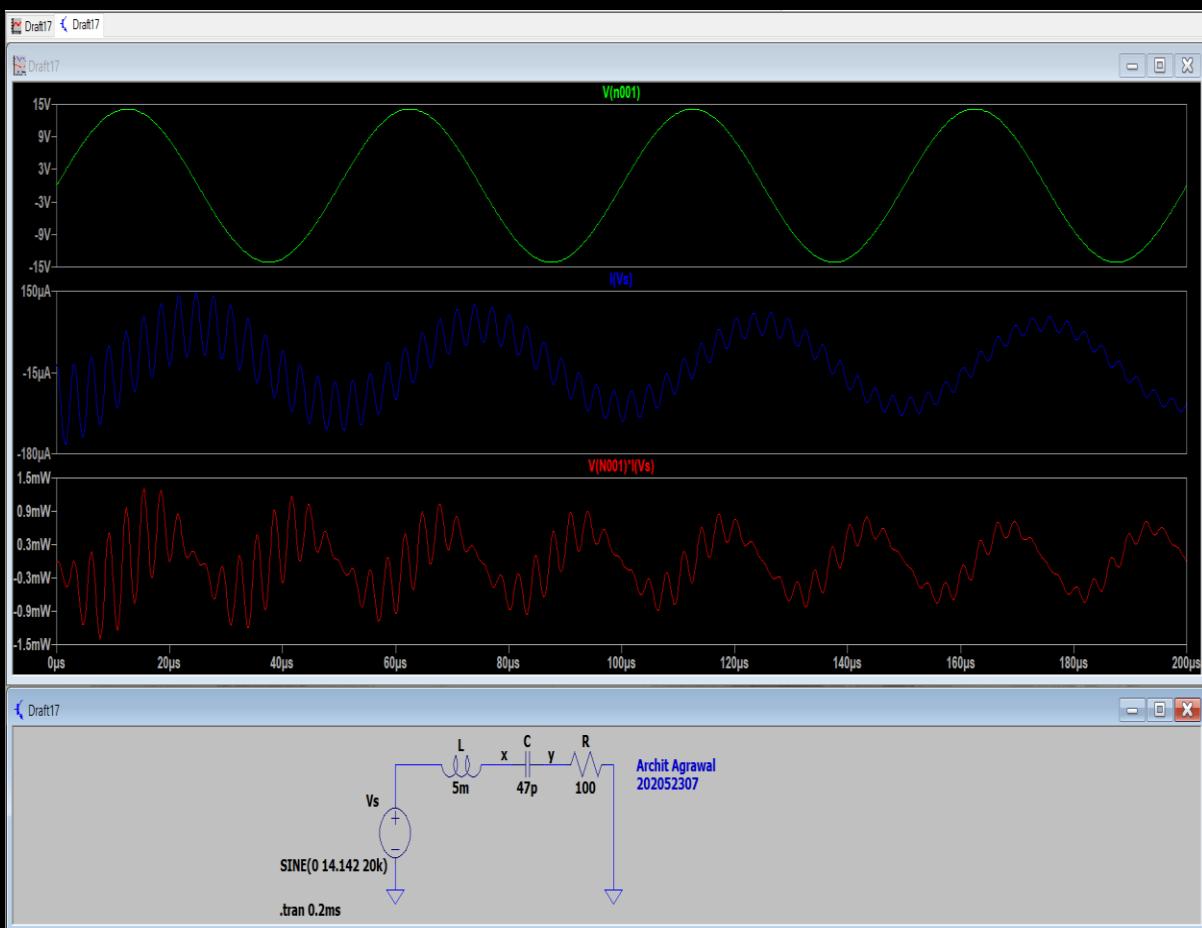
## Source Voltage, Total Current and Total Power




# EE160 : Experiment 3
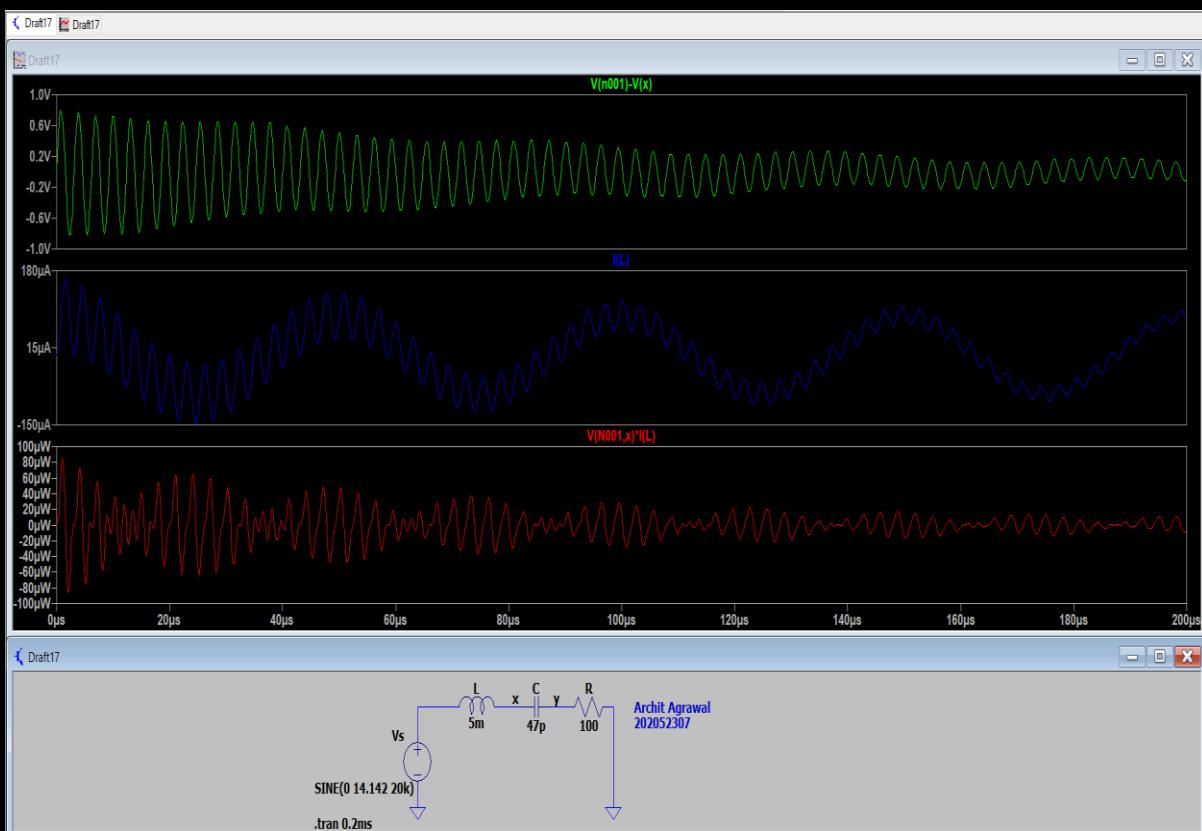
## Voltage, current and Power across Inductor



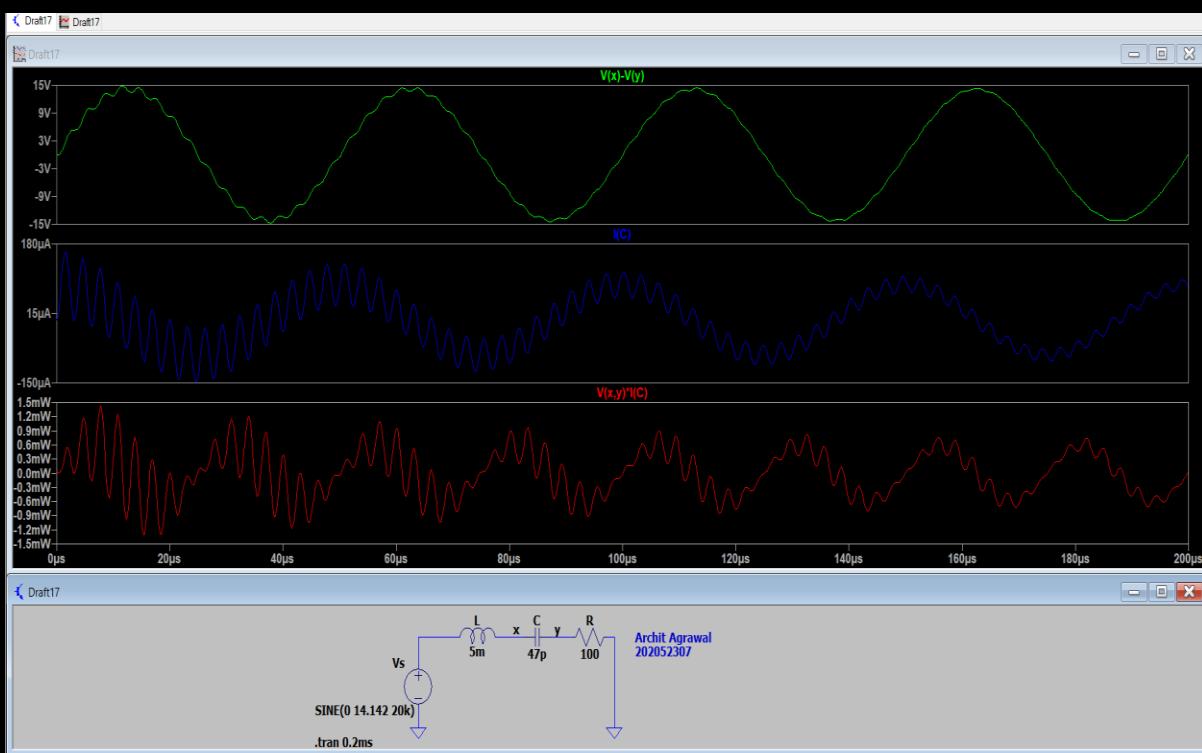
## Voltage, current and Power across Capacitor



# EE160 : Experiment 3
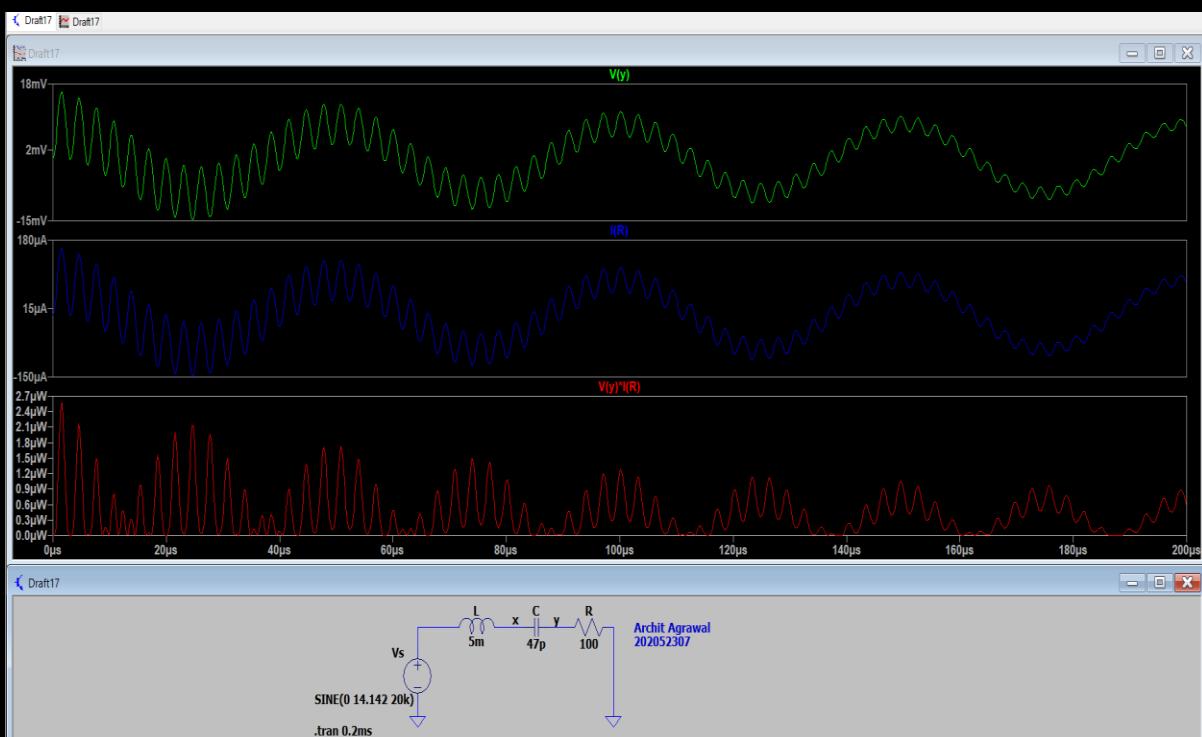
## Voltage, current and Power across Resistor




## AC Analysis

```
---- AC Analysis ----

frequency:      20000      Hz
V(n001):       mag: 10 phase: 0°      voltage
V(x):          mag: 10.0372 phase: -0.000126387°  voltage
V(y):          mag: 0.00592819 phase: 89.966°      voltage
I(C):          mag: 5.92819e-005 phase: 89.966°    device_current
I(L):          mag: 5.92819e-005 phase: 89.966°    device_current
I(R):          mag: 5.92819e-005 phase: 89.966°    device_current
I(Vs):         mag: 5.92819e-005 phase: -90.034°   device_current
```

### CIRCUIT 2:

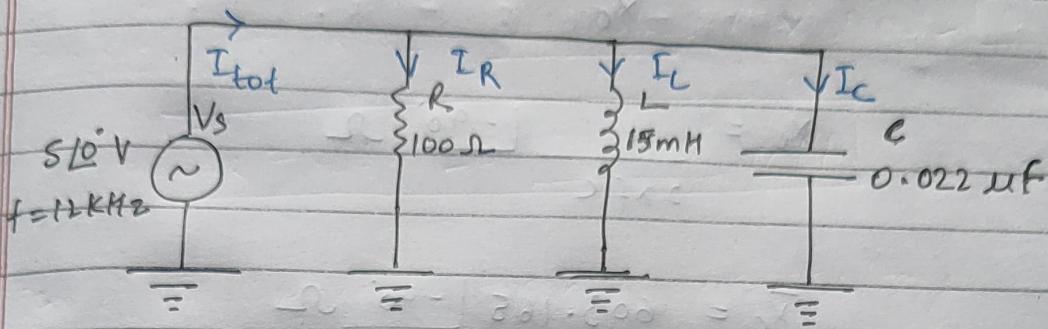

$$\text{Since, } \bar{V}_R = \bar{V}_L = \bar{V}_C = \bar{V}_s = 5\angle 0^\circ V$$

$$\therefore \bar{I}_R = \frac{\bar{V}_s}{Z_R} = \frac{5\angle 0^\circ}{100\angle 0^\circ} A$$

$$\begin{aligned} \bar{I}_R &= 50\angle 0^\circ \text{ mA} \\ I_R &= 50 + j0 \text{ mA} \end{aligned}$$

$$\text{and } \bar{I}_L = \frac{\bar{V}_s}{X_L}$$

$$\begin{aligned} \bar{X}_L &= 2\pi f L \angle 90^\circ \Omega \\ &= 1130.4 \angle 90^\circ \Omega \end{aligned}$$

$$\therefore \bar{I}_L = \frac{5\angle 0^\circ}{1130.4 \angle 90^\circ} A$$

$$\bar{I}_L = 4.42 \angle -90^\circ \text{ mA}$$

$$I_L = 0 - j(4.42) \text{ mA}$$

Name: Archit Agrawal  
Student ID: 202052307

Date:

Page:

6

$$\text{and } \bar{I}_c = \frac{\bar{V}_s}{\bar{X}_c}$$

$$\bar{X}_c = \frac{1}{2\pi f C} \angle -90^\circ \Omega$$

$$\bar{X}_c = 603.165 \angle -90^\circ \Omega$$

$$\therefore \bar{I}_c = \frac{5 \angle 0^\circ}{603.165 \angle -90^\circ} A$$

$$\bar{I}_c = 8.29 \angle 90^\circ \text{ mA}$$

$$I_c = 0 + j(8.29) \text{ mA}$$

$$\text{Now, } I_{\text{tot}} = I_R + I_L + I_c$$

$$\therefore I_{\text{tot}} = 50 + j(8.29 - 4.42) \text{ mA}$$

$$I_{\text{tot}} = 50 + j 3.87 \text{ mA}$$

$$\bar{I}_{\text{tot}} = 50.149 \angle 4.426^\circ \text{ mA}$$


Phase Difference between source voltage and total current  $\phi$

$$\phi = \phi_v - \phi_{I_{\text{tot}}}$$

$$\phi = 0^\circ - 4.426^\circ$$

$$\phi = -4.426^\circ$$


## Phasor Diagram

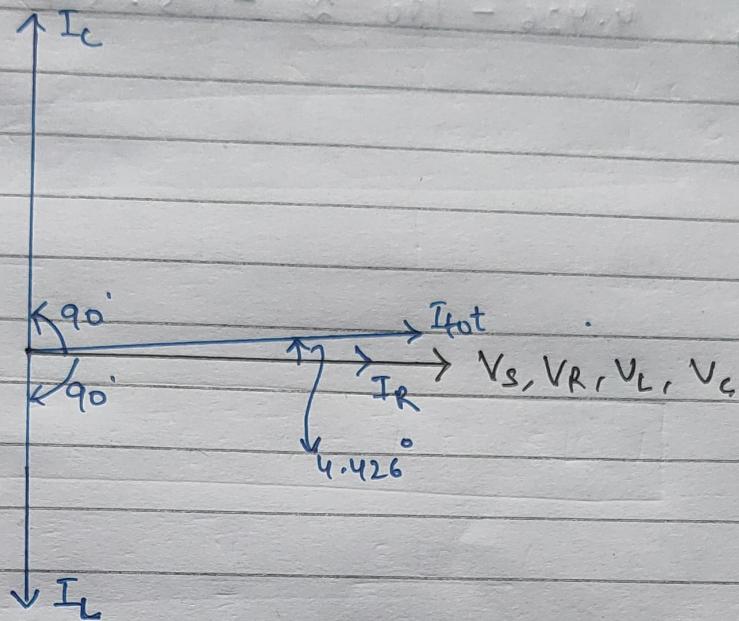
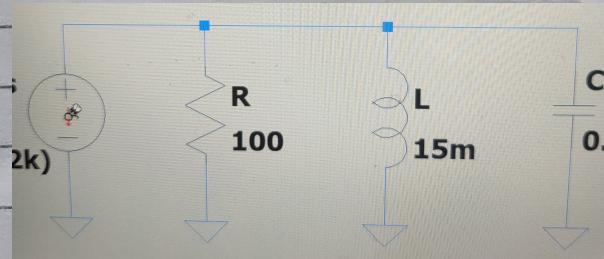
## Comparison Between SPICE results and Theory Calculations

The theoretical results match well with the SPICE AC-analysis results. The only error in SPICE results is that it shows the phase angle of  $I_{tot}$  to be  $-175.571$ .

The reason behind this is that the direction of current ( $I_{tot}$ ) for theory calculation is taken to be coming out of voltage source's positive terminal, but in SPICE this direction is reversed.



Name: Archit Agrawal  
Student ID: 202052307


Date: \_\_\_\_\_

Page: 0


Hence, phase of  $I_{tot}$  is reduced by  $180^\circ$ .  
Clearly,  $4.426^\circ - 180^\circ \approx -175.571^\circ$ .

# EE160 : Experiment 3

## Circuit

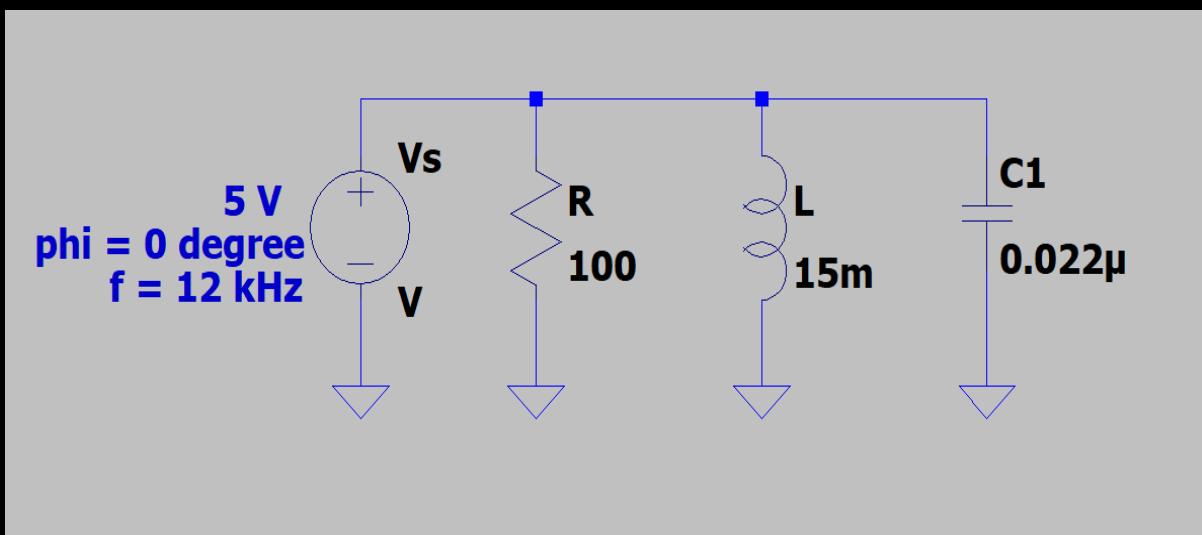

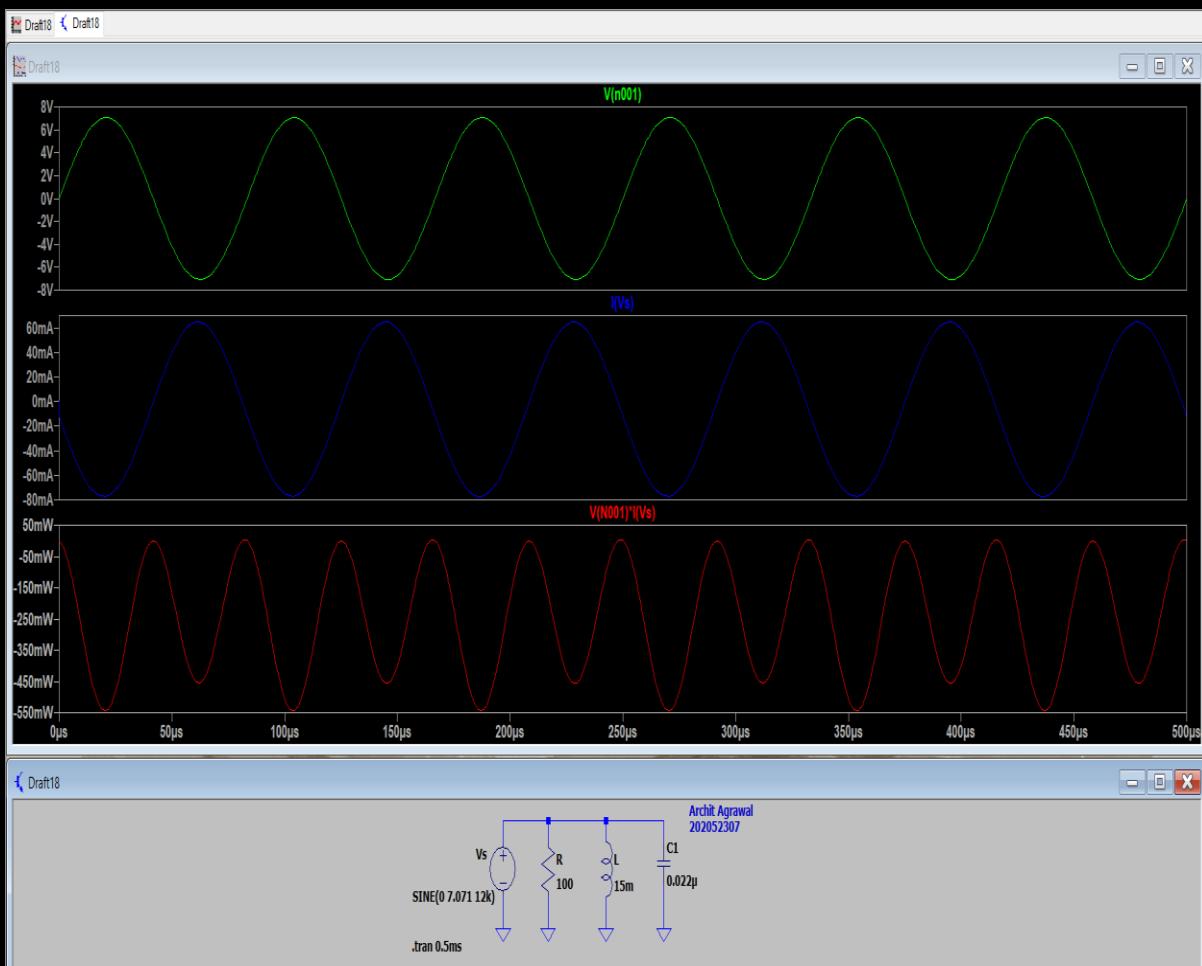
## Source Voltage, Total Current and Total Power




# EE160 : Experiment 3
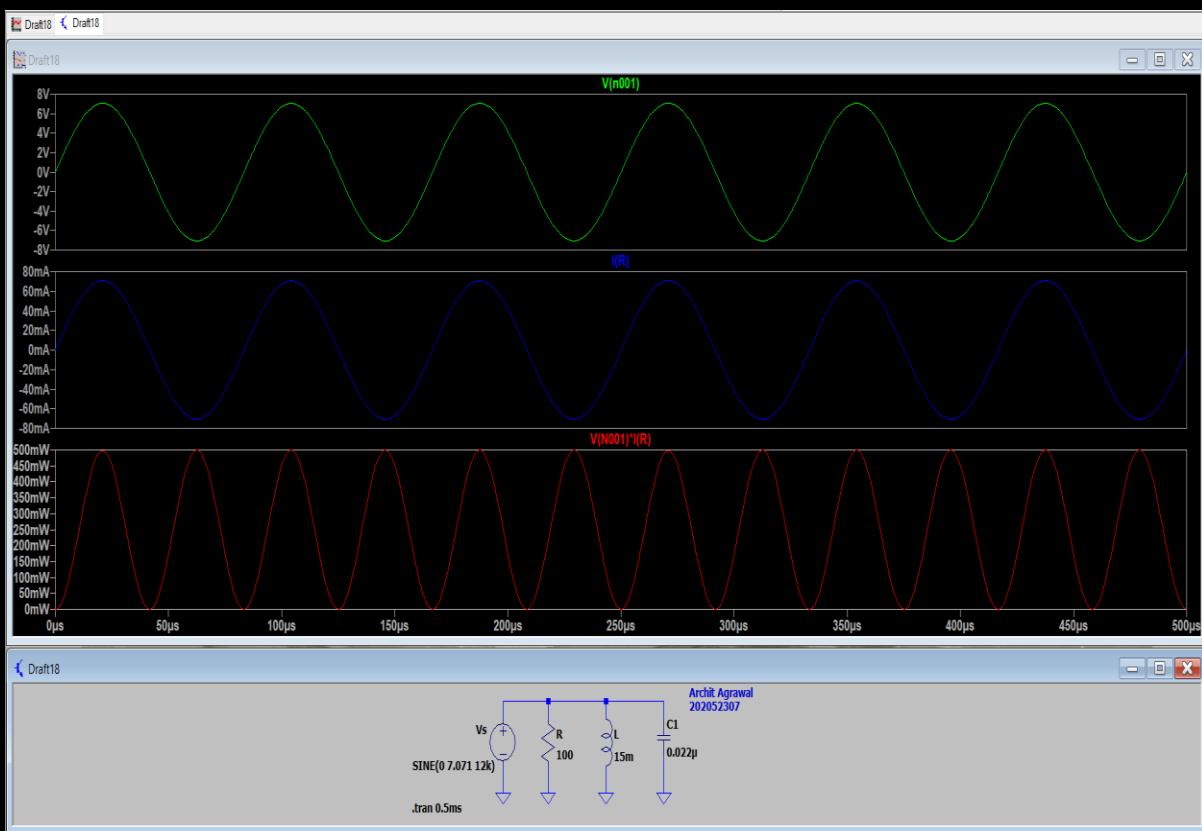
## Voltage, current and Power across Resistor



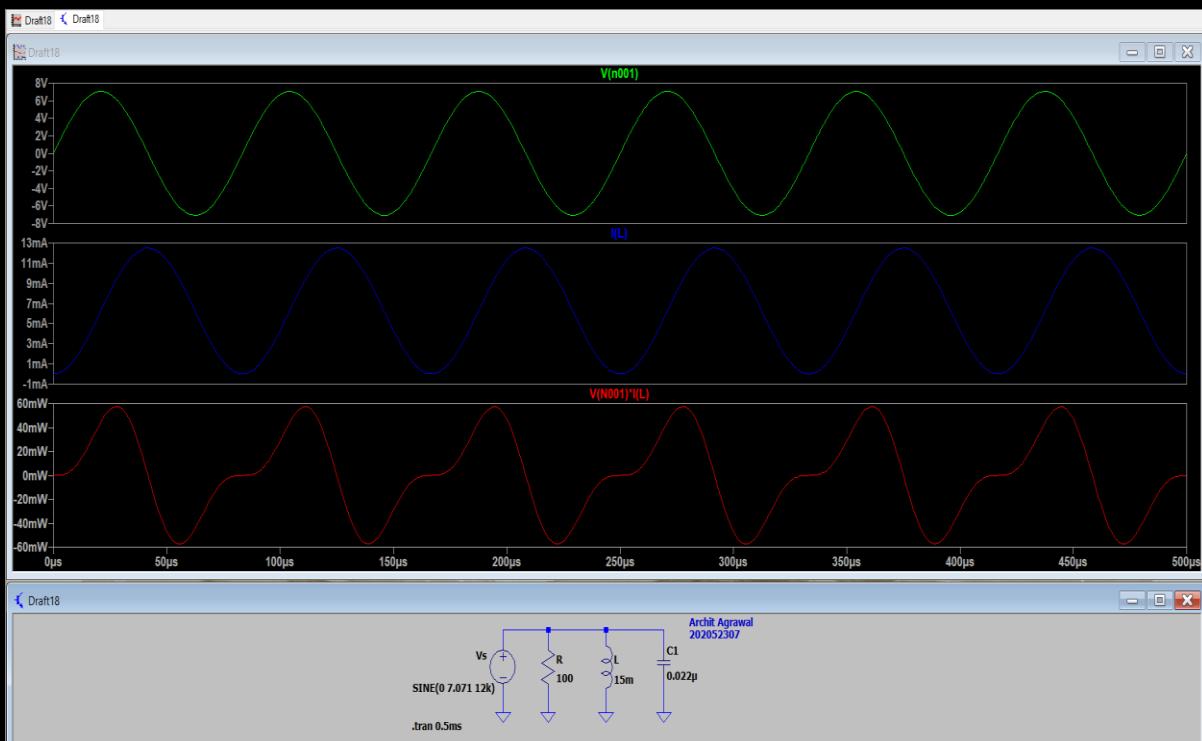
## Voltage, current and Power across Inductor



# EE160 : Experiment 3

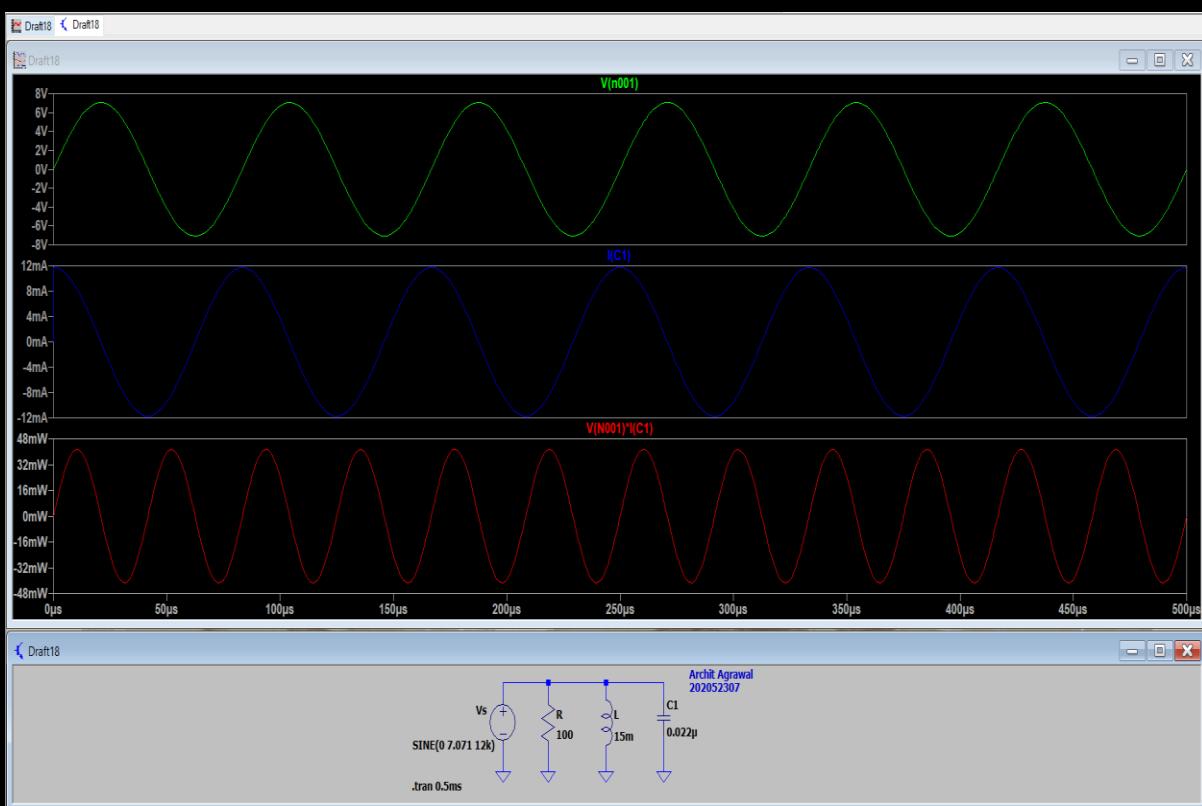
## Voltage, current and Power across Capacitor




## AC Analysis

```
--- AC Analysis ---  
frequency: 12000 Hz  
V(n001): mag: 5 phase: -6.36111e-016° voltage  
I(C1): mag: 0.0082938 phase: 90° device_current  
I(L): mag: 0.00442097 phase: -89.9999° device_current  
I(R): mag: 0.05 phase: -6.36111e-016° device_current  
I(Vs): mag: 0.0501498 phase: -175.571° device_current
```

### CIRCUIT 3

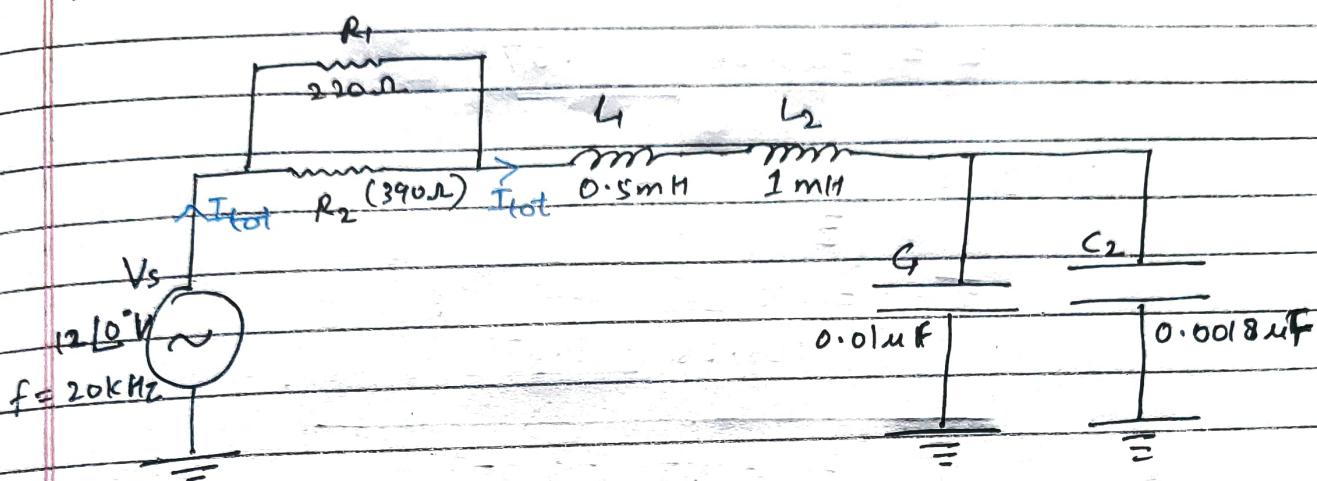

The circuit can be redrawn as

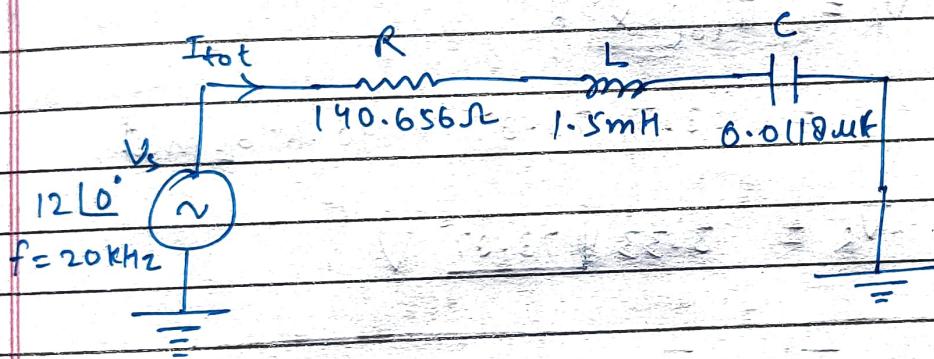

where  $R = R_1 \parallel R_2$

$$R = \frac{220 \times 390}{220 + 390} \Omega = 140.656 \Omega$$

Now,  $X_L = 2\pi f L = 2\pi(20k)(1.5m) = 188.4 \Omega$

and,  $X_C = \frac{1}{2\pi f C} = 674.727 \Omega$

$$\therefore Z = R + j(X_L - X_C)$$

$$Z = 140.656 + j(188.4 - 674.727) \Omega$$

Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 10

$$Z = 140.656 - j 486.327 \Omega$$

$$\bar{Z} = 506.26 \angle -73.87^\circ$$

$$\therefore \bar{I}_{\text{tot}} = \frac{\bar{V}_S}{\bar{Z}}$$

$$\bar{I}_{\text{tot}} = \frac{12 \angle 0^\circ}{506.26 \angle -73.87^\circ} \text{ A}$$

$$\boxed{\bar{I}_{\text{tot}} = 23.7 \angle 73.87^\circ \text{ mA}}$$

$$\therefore \bar{V}_R = \bar{I}_{\text{tot}} \times R$$

$$= 23.7 \angle 73.87^\circ \times 140.656 \text{ mV}$$

$$\bar{V}_R = 3.33 \angle 73.87^\circ \text{ V}$$

$$\therefore \bar{V}_{R_1} = \bar{V}_{R_2} = \bar{V}_R = 3.33 \angle 73.87^\circ \text{ V}$$

$$\therefore \bar{I}_{R_1} = \frac{\bar{V}_{R_1}}{R_1}$$

$$\bar{I}_{R_1} = \frac{3.33 \angle 73.87^\circ}{220 \angle 0^\circ} \text{ A}$$

$$\boxed{\bar{I}_{R_1} = 15.136 \angle 73.87^\circ \text{ mA}}$$

$$\bar{I}_{R_2} = \frac{3.33 \angle 73.87^\circ}{390 \angle 0^\circ} \text{ mA}$$

$$\boxed{\bar{I}_{R_2} = 8.54 \angle 73.87^\circ \text{ mA}}$$

Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 11

From the circuit, it is clear that  $\bar{I}_{L_1} = \bar{I}_{L_2} = \bar{I}_{\text{tot}}$

$$\therefore \bar{I}_L = \bar{I}_{L_2} = 23.7 |73.87^\circ \text{ mA}|$$

$$\therefore \bar{V}_{L_1} = \bar{I}_{L_1} \times \bar{X}_{L_1}$$

$$\begin{aligned}\bar{X}_{L_1} &= 2\pi f L_1 |90^\circ \Omega| \\ &= 62.8 |90^\circ \Omega|\end{aligned}$$

$$\therefore \bar{V}_{L_1} = 23.7 |73.87^\circ \times 62.8 |90^\circ \text{ mV}|$$

$$\bar{V}_{L_1} = 1.488 |163.87^\circ \text{ V}|$$

and,  $\bar{V}_{L_2} = \bar{I}_{L_2} \times \bar{X}_{L_2}$

$$\begin{aligned}\bar{X}_{L_2} &= 2\pi f L_2 |90^\circ| \\ &= 125.6 |90^\circ \Omega|\end{aligned}$$

$$\therefore \bar{V}_{L_2} = 23.7 |73.87^\circ \times 125.6 |90^\circ \text{ mV}|$$

$$\bar{V}_{L_2} = 2.976 |163.87^\circ \text{ V}|$$

Now,  $\bar{V}_C = \bar{I}_{\text{tot}} \times \bar{X}_C$

$$\bar{V}_C = 23.7 |73.87^\circ \times 674.727 |-90^\circ \text{ mV}$$

$$\bar{V}_C = 15.99 |-16.13^\circ \text{ V}|$$

Clearly  $\bar{V}_{C_1} = \bar{V}_{C_2} = \bar{V}_C = 15.99 |-16.13^\circ \text{ V}|$

$$\therefore \overline{I}_{C_1} = \overline{V}_{C_1} \times \overline{X}_{C_1}$$

$$\overline{X}_{C_1} = \frac{1}{2\pi f C_1} \angle -90^\circ \Omega$$

$$\overline{X}_{C_1} = 796.178 \angle -90^\circ \Omega$$

$$\therefore \overline{I}_{C_1} = \frac{15.99 \angle -16.13^\circ}{796.178 \angle -90^\circ} A$$

$$\boxed{\overline{I}_{C_1} = 20.08 \angle 73.87^\circ mA}$$

and,  $\overline{I}_{C_2} = \frac{\overline{V}_{C_2}}{\overline{X}_{C_2}}$

$$\overline{X}_{C_2} = \frac{1}{2\pi f C_2} \angle -90^\circ \Omega$$

$$\overline{X}_{C_2} = 4423.21 \angle -90^\circ \Omega$$

$$\therefore \overline{I}_{C_2} = \frac{15.99 \angle -16.13^\circ}{4423.21 \angle -90^\circ} A$$


$$\boxed{\overline{I}_{C_2} = 3.615 \angle 73.87^\circ mA}$$

Phase Difference between source voltage and total current  $\phi$

$$\phi = \phi_{Vs} - \phi_{I_{tot}} = 0^\circ - 73.87^\circ$$

$$\boxed{\phi = -73.87^\circ}$$

## Phasor Diagram

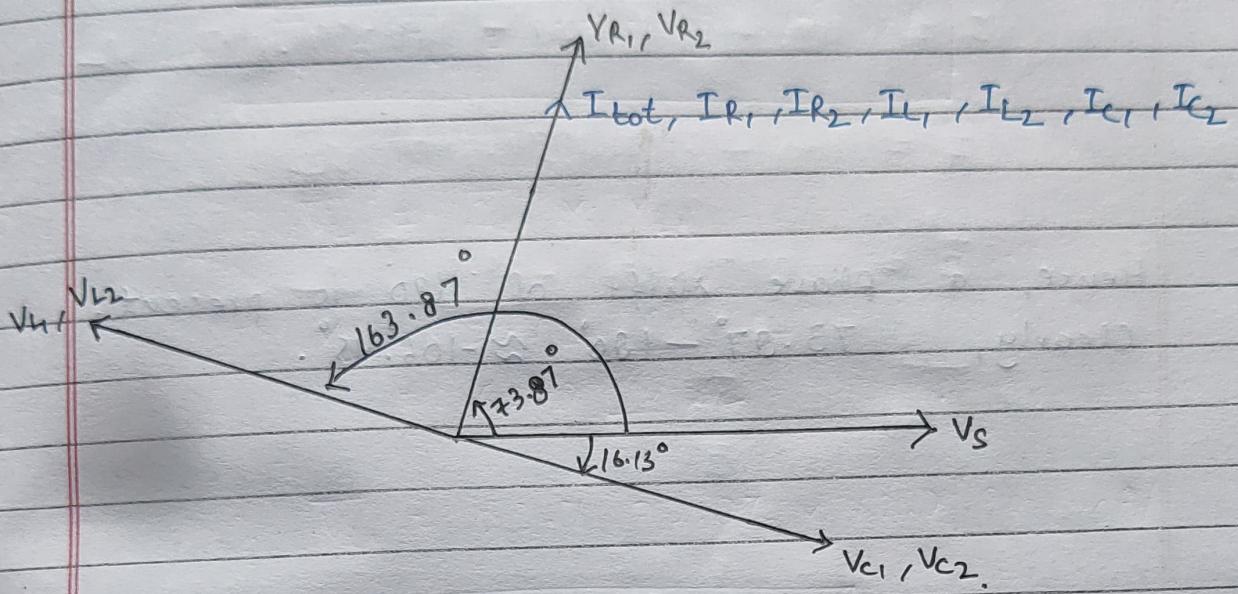


### Comparison between SPICE Results and theory calculations

The theoretical results match well with the SPICE AC-Analysis results. The only difference error in the SPICE results is that it shows the phase angle of  $I_{tot}$  to be  $-106.45^\circ$ .

This is not an error actually, the reason behind this is that the direction of current ( $I_{tot}$ ) for theory calculation is taken to be coming out of voltage source but in SPICE the direction is reversed.

Name: Archit Agrawal  
Student ID: 202052307


Date: \_\_\_\_\_  
Page: 14

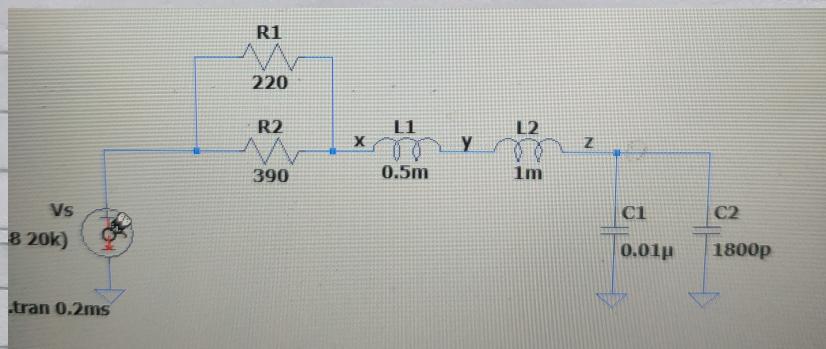



Hence, a phase shift of  $180^\circ$  is present.  
Clearly,  $73.87^\circ - 180^\circ \approx -106.45^\circ$ .

# EE160 : Experiment 3

## Circuit

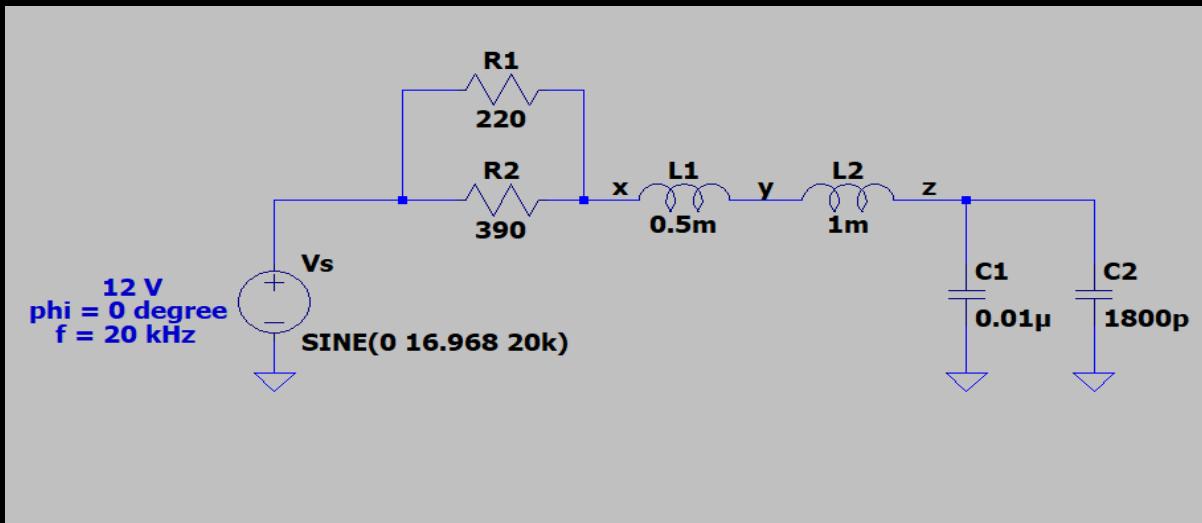

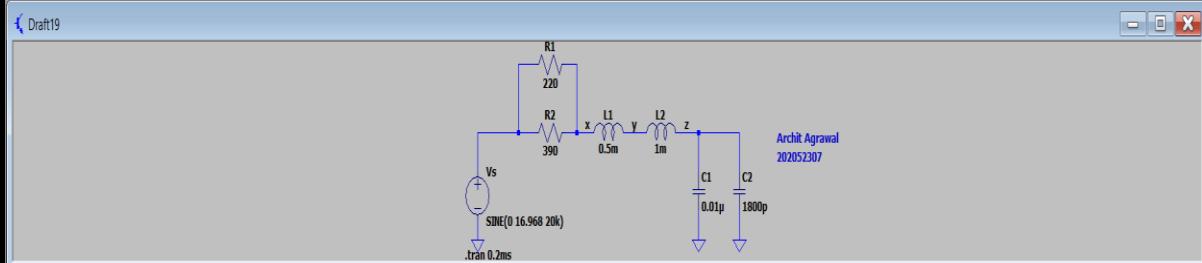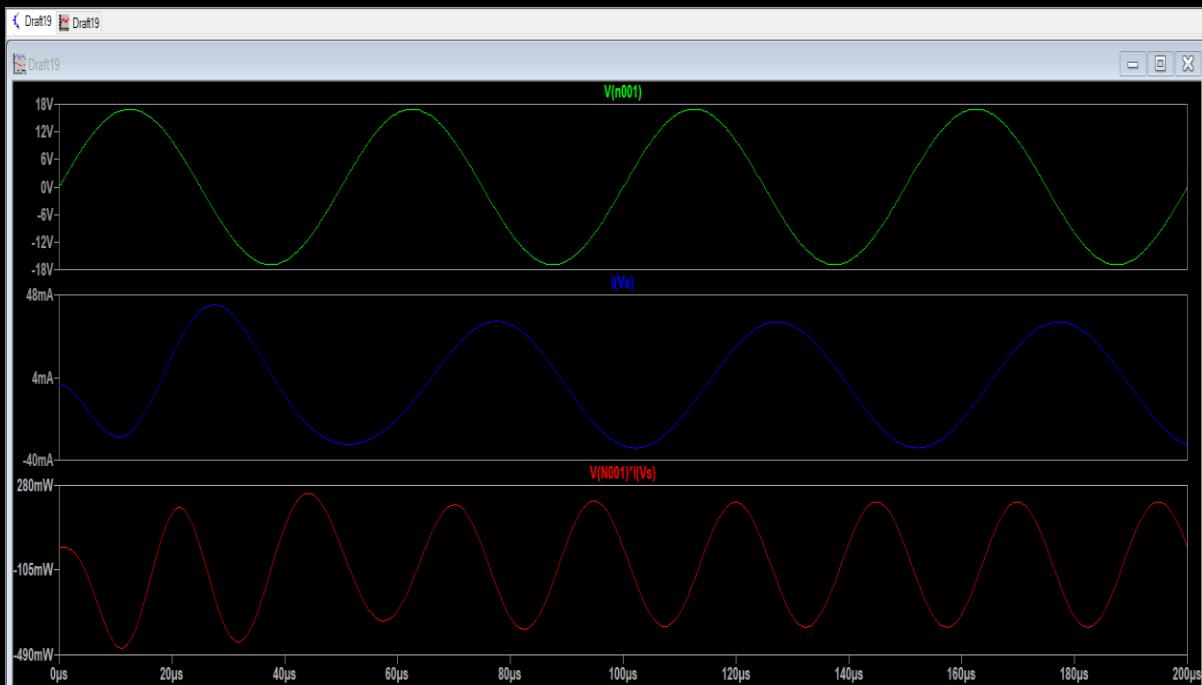
## Source Voltage, Total Current and Total Power




# EE160 : Experiment 3
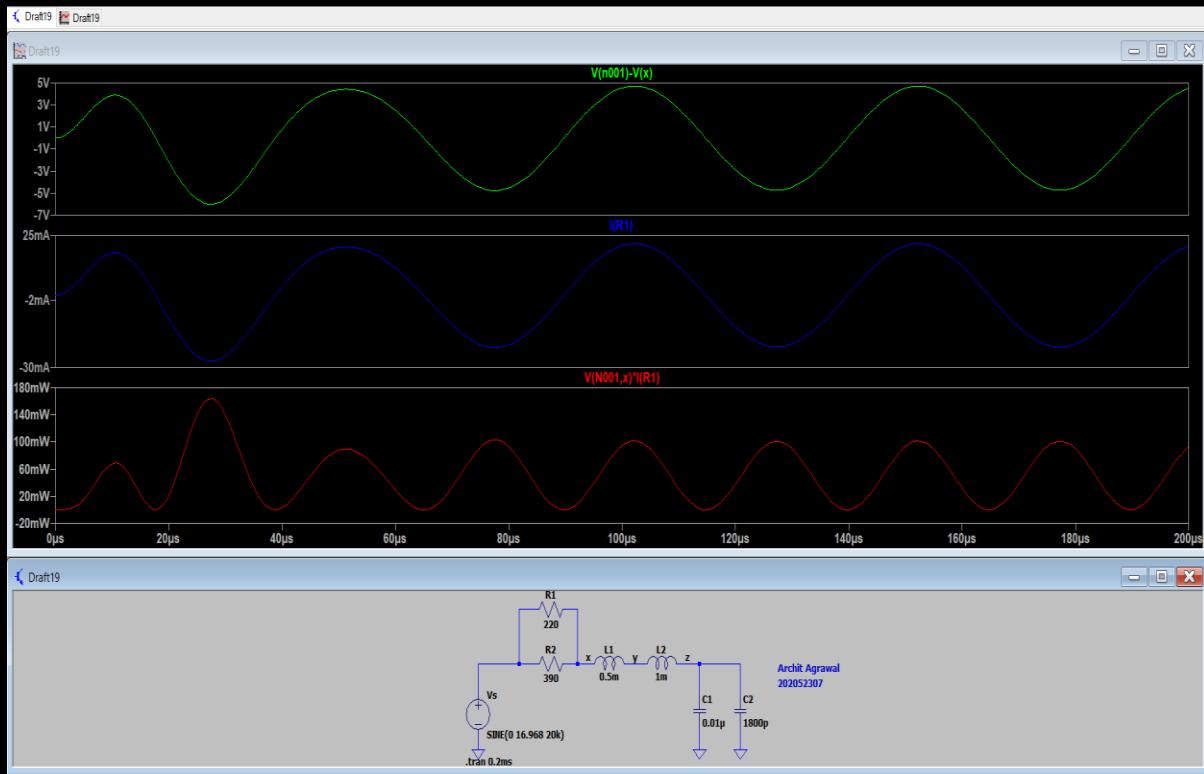
## Voltage, current and Power across Resistor $R_1$



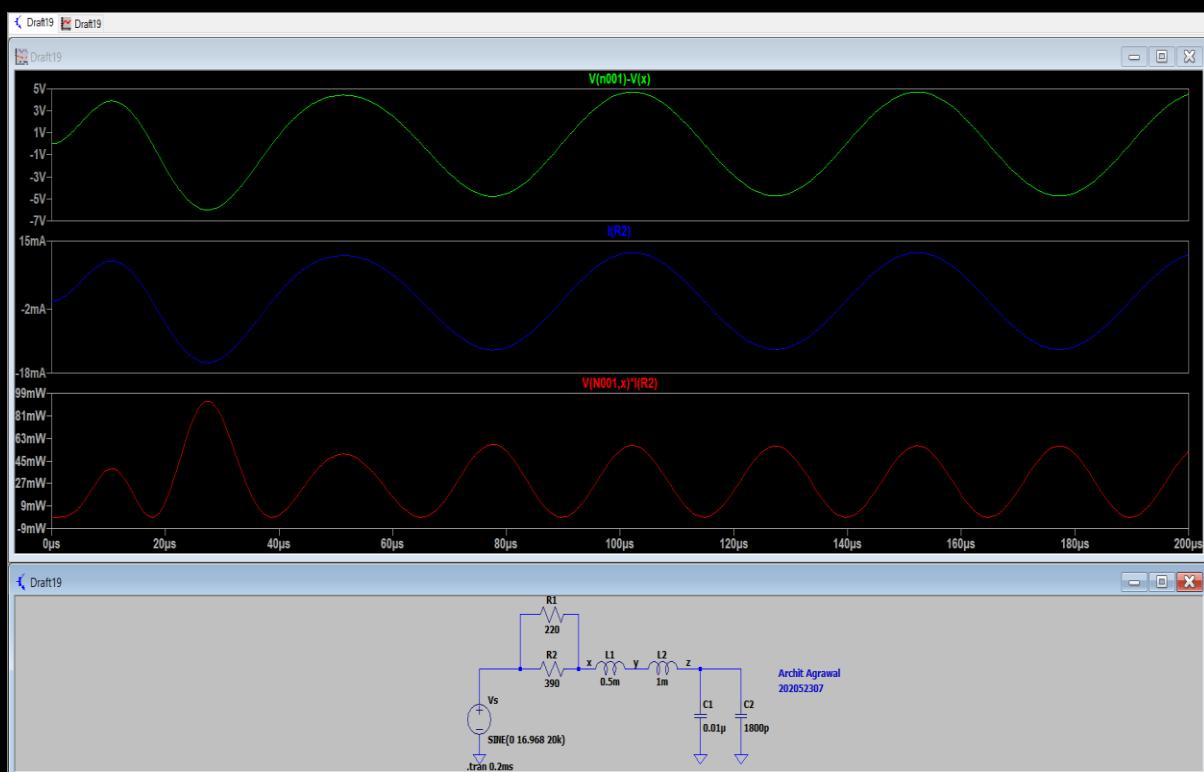
## Voltage, current and Power across Resistor $R_2$




# EE160 : Experiment 3
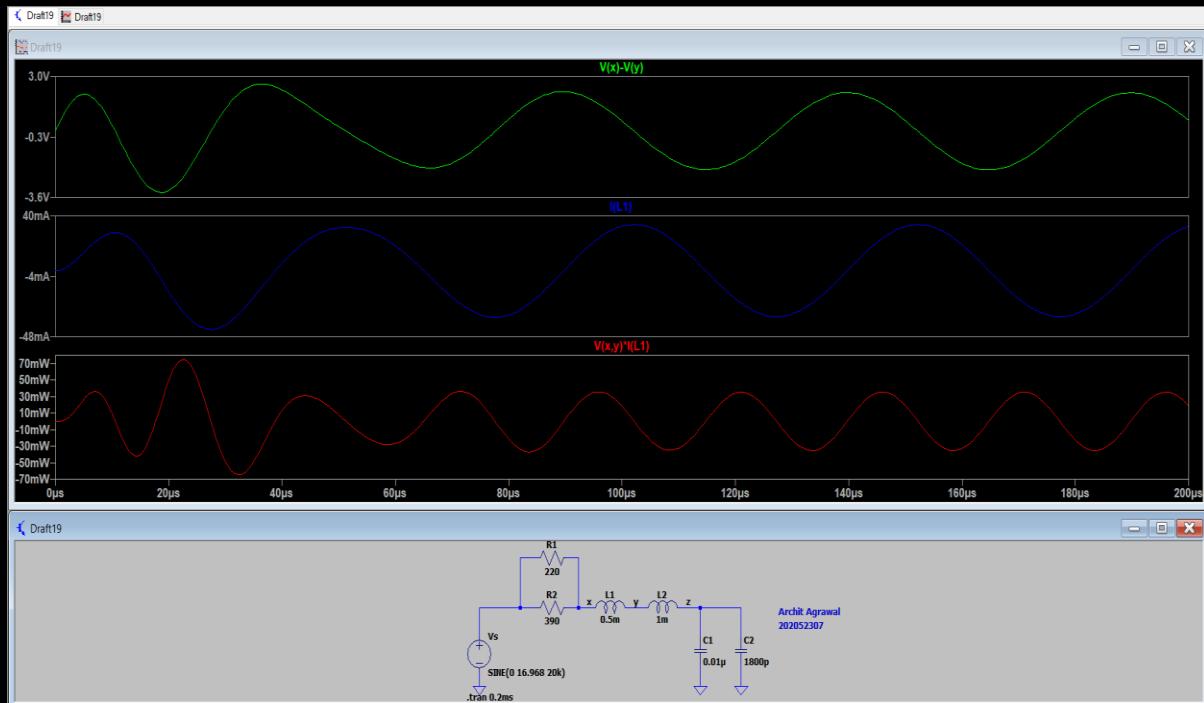
## Voltage, current and Power across Inductor $L_1$



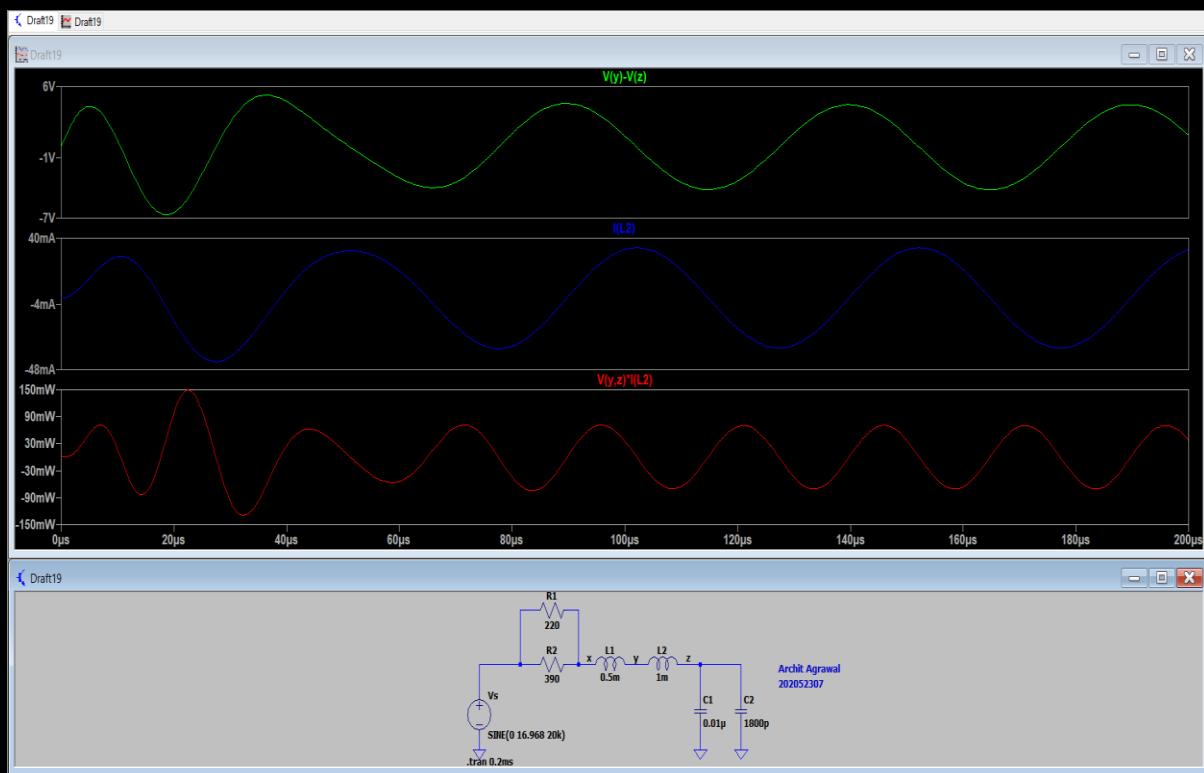
## Voltage, current and Power across Inductor $L_2$




# EE160 : Experiment 3
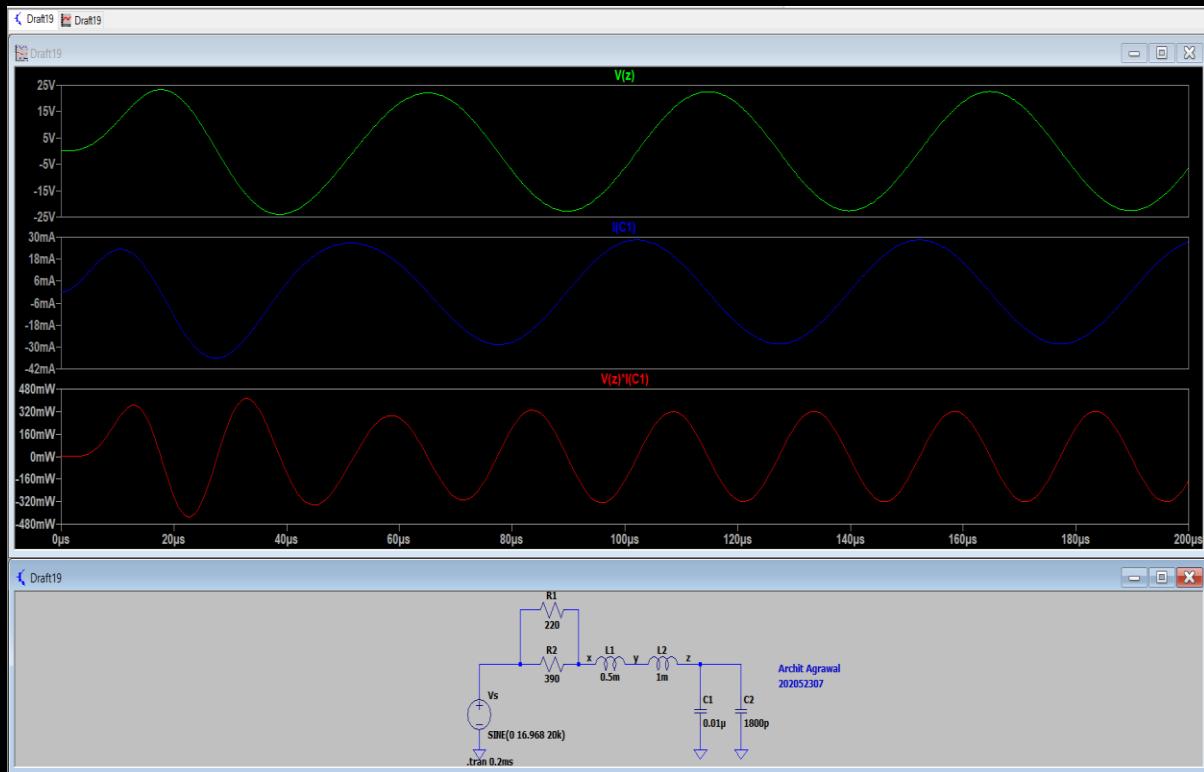
## Voltage, current and Power across Capacitor $C_1$


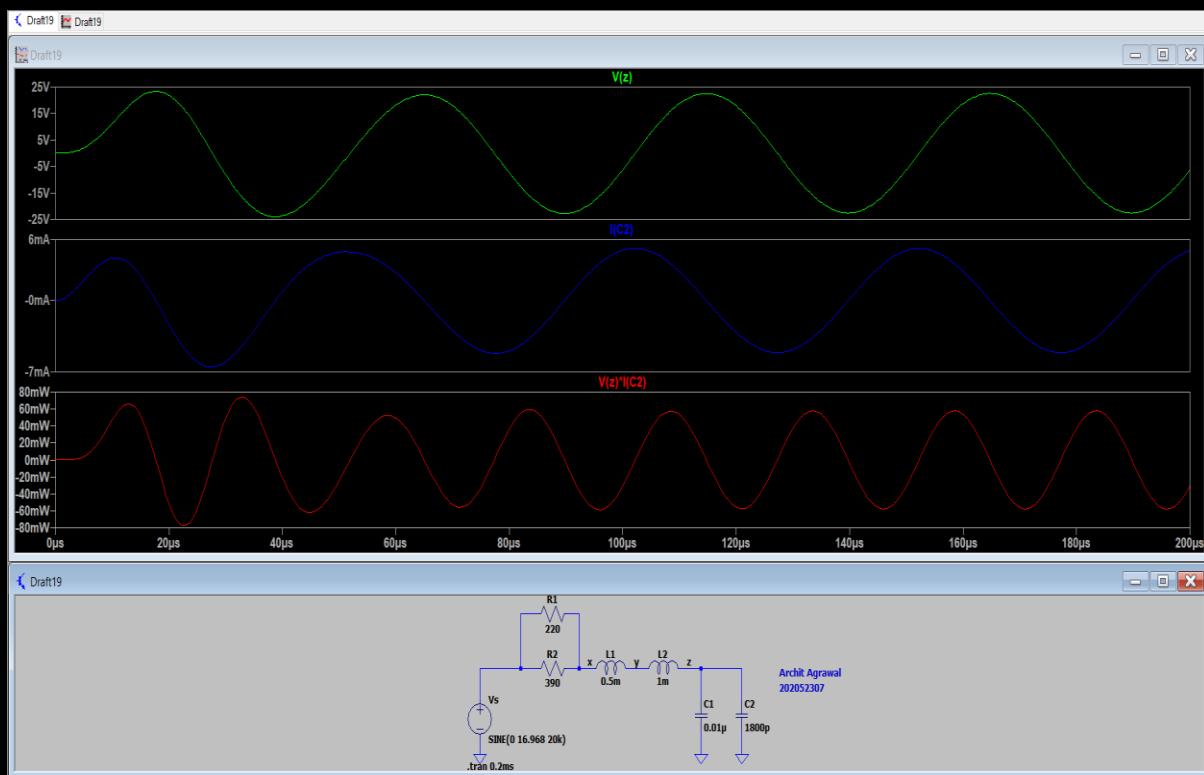
## Voltage, current and Power across Capacitor $C_2$



# EE160 : Experiment 3

## AC Analysis

```
| --- AC Analysis ---  
  
frequency: 20000      Hz  
V(n001):   mag:      12 phase: 2.12037e-015°      voltage  
V(x):      mag:    11.5267 phase: -16.1447°      voltage  
V(y):      mag:    13.0173 phase: -16.1448°      voltage  
V(z):      mag:    15.9984 phase: -16.1449°      voltage  
I(C2):     mag: 0.00361875 phase: 73.8551°      device_current  
I(C1):     mag: 0.0201042 phase: 73.8551°      device_current  
I(L2):     mag: 0.0237229 phase: 73.8551°      device_current  
I(L1):     mag: 0.0237229 phase: 73.8551°      device_current  
I(R2):     mag: 0.00855582 phase: 73.8551°      device_current  
I(R1):     mag: 0.0151671 phase: 73.8551°      device_current  
I(Vs):     mag: 0.0237229 phase: -106.145°      device_current
```

*EE160 : Experiment 3*

**VIRTUAL**

**LAB**

**SIMULATIONS**


## EE160 : Experiment 3

*Keeping inductance and  
capacitance constant and  
varying the resistance.*

# R-L-C Circuit Analysis
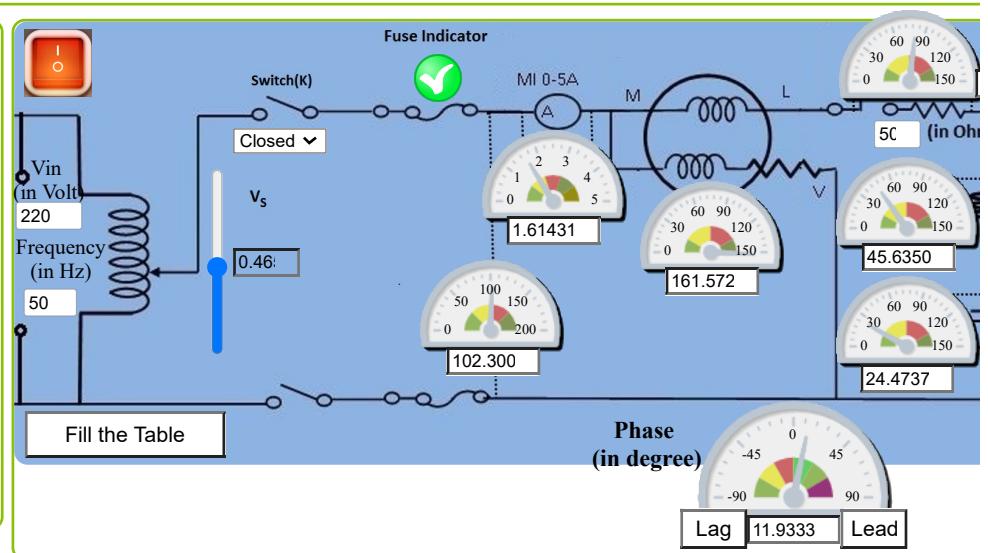
## Procedure: (For Balanced Load)

- Closed the Switch(K). Set Input Voltage  $V_{in}=220V$ .
- Set power supply voltage ( $V_S$ ) at=0V. Keep all the resistance, Inductance, capacitance at maximum position.
- Adjust the voltage across the circuit ( $V_S$ ) to about 70 V and note current( $I$ ),  $V_s$ ,  $V_L$ ,  $V_C$ ,  $V_R$  and power( $W$ ) from the meters.
- Adjust the rheostat for several settings and repeat step 2.
- Adjust the rheostat to the maximum setting and change the capacitance to 0uF, 140 uF, 70uF and change the inductance to 0mH, 30 mH, 60mH repeat step 2.
- Draw phasor diagrams showing  $VR$ ,  $VL$ ,  $VC$ ,  $VS$ , &  $I$  for different sets of readings.



Observation Table

Serial no. of Observation	Power Supply $V_s$ (in Volt)	Current $I$ (in Amp)	Power (in Watt)	$VR$ (in Volt)	$VL$ (in Volt)	$VC$ (in Volt)	Theta (in degree)	Power factor (in degree)
1	102.300000i	3.62403056	170.736767i	47.1123973i	102.447719i	54.9420197i	27.6587351i	27.6587351i
2	102.300000i	2.73717974i	172.319518i	62.9551342i	77.3773343i	41.4969413i	20.5241377	20.5241377
3	102.300000i	2.09657848i	153.847446i	73.3802469i	59.2681771i	31.7851227i	15.5777724i	15.5777724i
4	102.300000i	1.84097842i	142.346465i	77.3210938i	52.0426191i	27.9101048i	13.6391587i	13.6391587i
5	102.300000i	1.61431315i	130.300348i	80.7156578i	45.6350186i	24.4737520i	11.9333075i	11.9333075i


## EE160 : Experiment 3

*Keeping resistance and  
capacitance constant and  
varying the inductance.*

# R-L-C Circuit Analysis
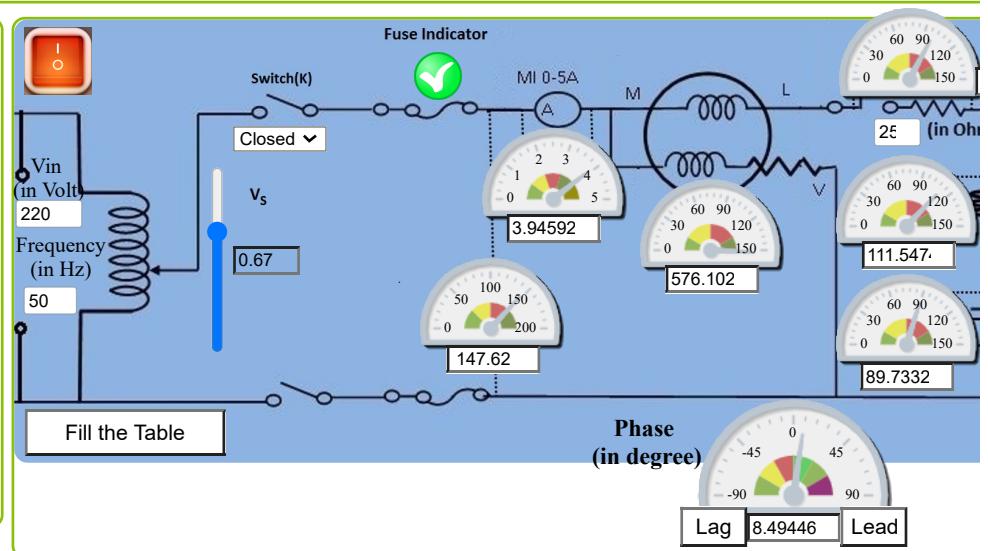
## Procedure: (For Balanced Load)

- Closed the Switch(K). Set Input Voltage  $V_{in}=220V$ .
- Set power supply voltage ( $V_S$ ) at=0V. Keep all the resistance, Inductance, capacitance at maximum position.
- Adjust the voltage across the circuit ( $V_S$ ) to about 70 V and note current( $I$ ),  $V_s$ ,  $V_L$ ,  $V_C$ ,  $V_R$  and power( $W$ ) from the meters.
- Adjust the rheostat for several settings and repeat step 2.
- Adjust the rheostat to the maximum setting and change the capacitance to 0uF, 140 uF, 70uF and change the inductance to 0mH, 30 mH, 60mH repeat step 2.
- Draw phasor diagrams showing  $VR$ ,  $VL$ ,  $VC$ ,  $VS$ , &  $I$  for different sets of readings.



Observation Table

Serial no. of Observation	Power Supply $V_s$ (in Volt)	Current $I$ (in Amp)	Power (in Watt)	$VR$ (in Volt)	$VL$ (in Volt)	$VC$ (in Volt)	Theta (in degree)	Power factor (in degree)
1	147.62	4.36802934	476.992008	109.200733	0	99.3320904	-42.273531	42.2735310
2	147.62	4.62587863	534.968827	115.646965	43.5896543	105.195766	-24.6561486	24.6561486
3	147.62	4.44250035	493.395235	111.062508	83.7233617	101.025614	-6.72829034	6.72829034
4	147.62	3.94592777	389.258650	98.6481944	111.547432	89.7332009	8.49446422	8.49446422
5								


# EE160 : Experiment 3

*Keeping resistance and  
inductance constant and  
varying the capacitance.*

# R-L-C Circuit Analysis
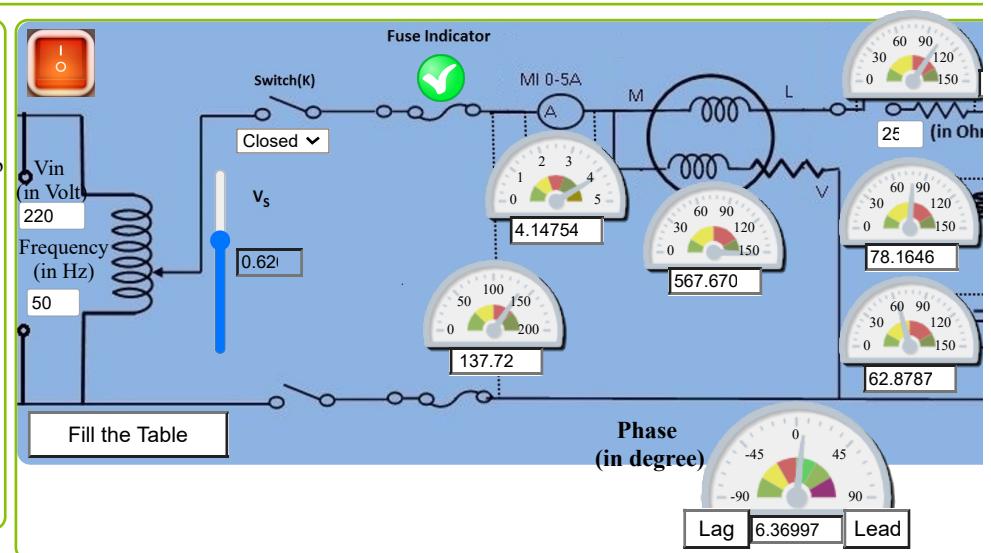
## Procedure: (For Balanced Load)

- Closed the Switch(K). Set Input Voltage  $V_{in}=220V$ .
- Set power supply voltage ( $V_S$ ) at=0V. Keep all the resistance, Inductance, capacitance at maximum position.
- Adjust the voltage across the circuit ( $V_S$ ) to about 70 V and note current( $I$ ),  $V_s$ ,  $V_L$ ,  $V_C$ ,  $V_R$  and power( $W$ ) from the meters.
- Adjust the rheostat for several settings and repeat step 2.
- Adjust the rheostat to the maximum setting and change the capacitance to 0uF, 140 uF, 70uF and change the inductance to 0mH, 30 mH, 60mH repeat step 2.
- Draw phasor diagrams showing  $VR$ ,  $VL$ ,  $VC$ ,  $VS$ , &  $I$  for different sets of readings.



Observation Table

Serial no. of Observation	Power Supply $V_s$ (in Volt)	Current $I$ (in Amp)	Power (in Watt)	$VR$ (in Volt)	$VL$ (in Volt)	$VC$ (in Volt)	Theta (in degree)	Power factor (in degree)
1	137.72	0	0	0	0		-89.963789e	
2	137.72	3.24749398i	263.655430	81.1873497	61.2022717	147.700640i	-38.892523e	38.8925235
3	137.72	4.14456814i	429.436127	103.614203i	78.1085312	94.2504239i	-6.72829034	6.72829034
4	137.72	4.14754729i	430.053714	103.688682	78.1646763	62.8787813	6.36997139	6.36997139
5								