


## EE160: Experiment 1

Objective - Design and simulate the given circuits in SPICE. Plot the voltages (across each element), currents (through each element), and total current. Find the phase difference between source/input voltage ( $V_s$ ) and all other voltages and currents from your simulations. Calculate the voltages and currents theoretically.

Draw the phasor diagram from your theoretical calculations. Compare the theoretical results with the simulation results. Also, plot the total power ( $V_s \times I_{\text{total}}$ ) of the circuit.

### Mathematical Expressions and Theoretical Calculations

#### CIRCUIT 1 :

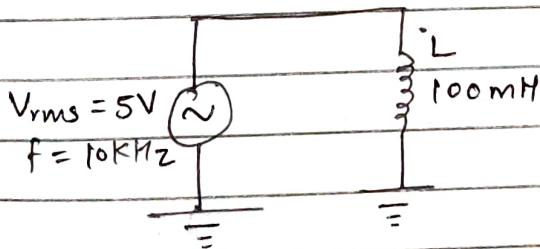

$$Z = jX_L$$

$$\begin{aligned} X_L &= \omega L = 2\pi(10k)(100m) \\ &= 6.28\text{ k}\Omega \end{aligned}$$

$$\therefore Z = j(6.28\text{k})\Omega$$

$$\therefore \bar{I}_S = \frac{\bar{V}_S}{Z} = \frac{5 \angle 0^\circ}{(6.28k) \angle 90^\circ}$$

$$\bar{I}_S = 0.796 \angle -90^\circ \text{ mA}$$

$$\bar{V}_S = 5 \angle 0^\circ$$


$\therefore I_S$  lags  $V_S$  by  $90^\circ$  or  $V_S$  leads  $I_S$  by  $90^\circ$ .

The current through inductor is equal to  $I_S$  and voltage across it is  $V_L$  in this circuit.

$$\therefore \bar{I}_L = \bar{I}_S$$

$$\bar{V}_L = \bar{V}_S$$

### Phasor Diagram

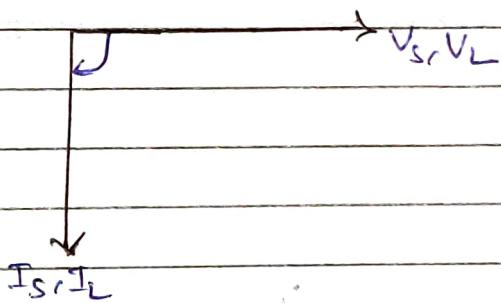


### Time Domain

$$V_L = V_S = 5\sqrt{2} \sin(\omega t + 0^\circ) \quad (\text{as } V_{rms} = 5V)$$

$$I_L = I_S = 0.796\sqrt{2} \sin(\omega t - 90^\circ)$$


Name: Archit Agrawal  
Student ID: 201082307

Date: \_\_\_\_\_  
Page: 3

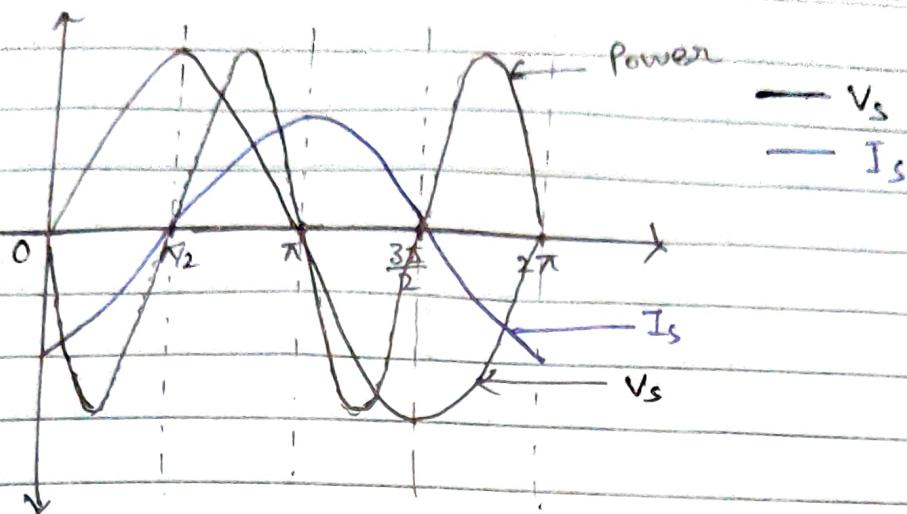


In 1st and 3rd <sup>quarter</sup> half of power cycle, energy is returned to the circuit while in 2nd and 4<sup>th</sup> ~~half~~ quarter of power cycle, energy is stored.


## CIRCUIT

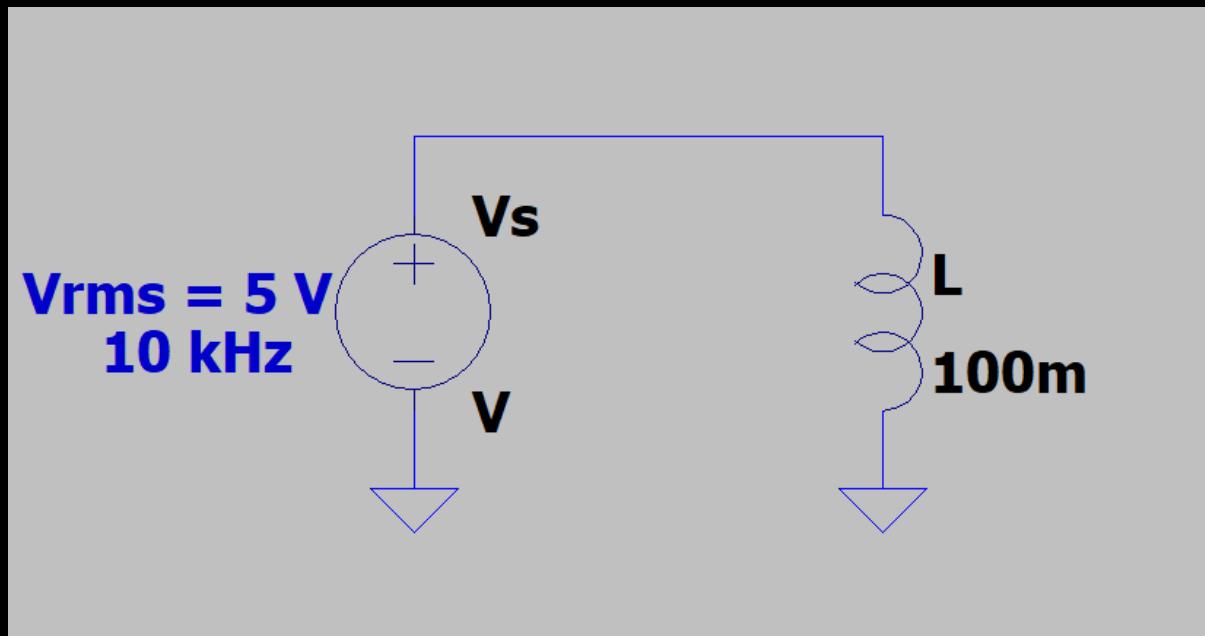
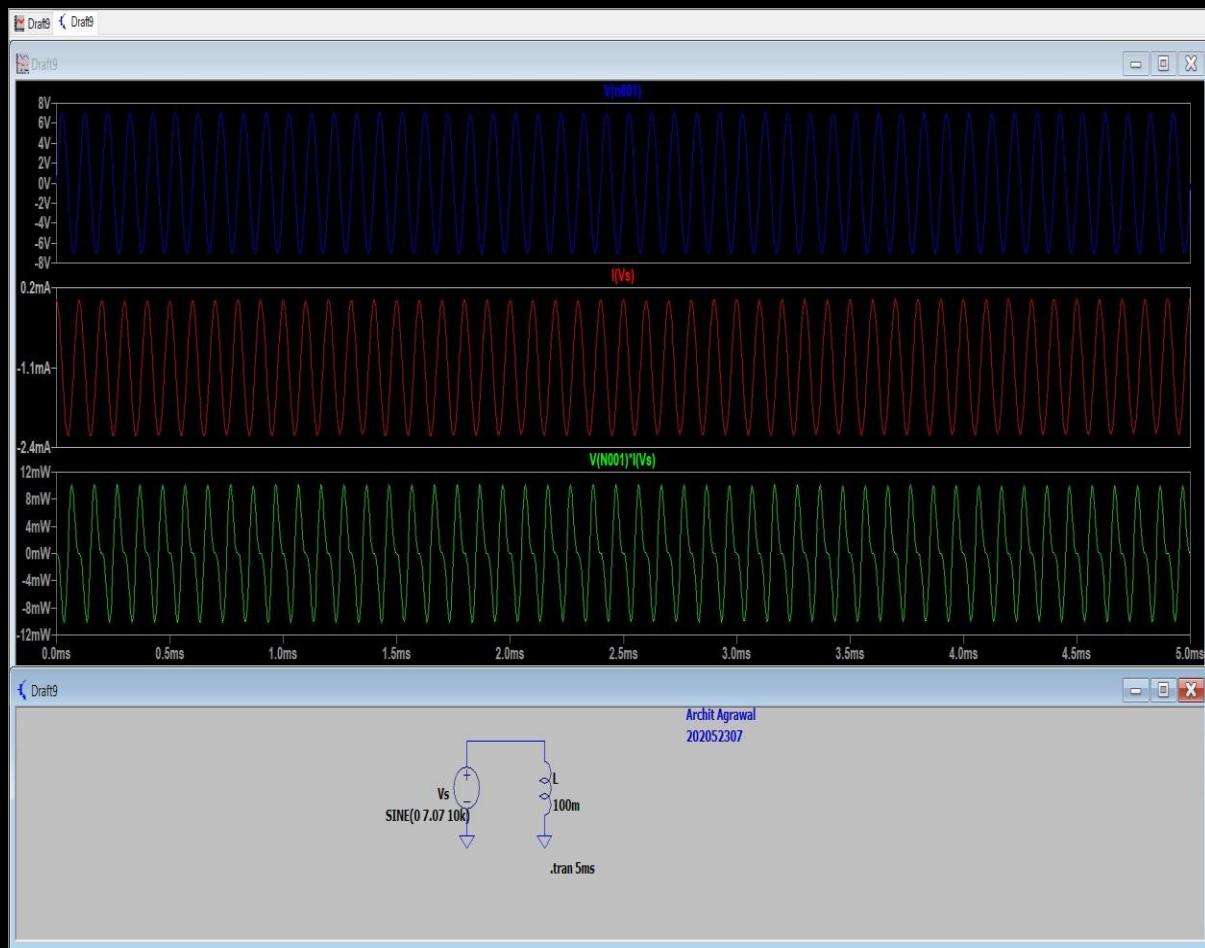
## Source Voltage, total current and total power


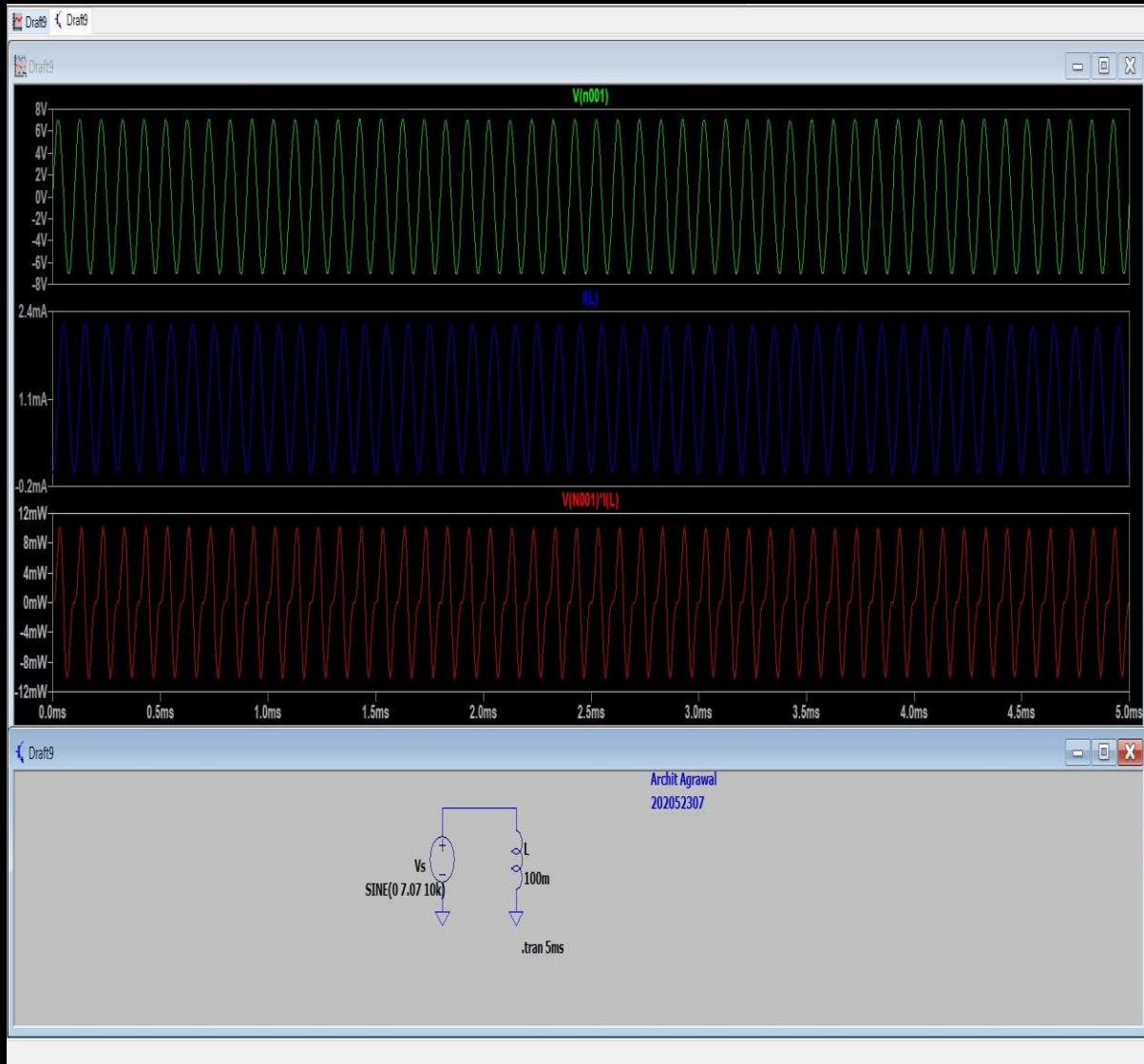
## Voltage, Current and Power across Inductor




## AC Analysis

```
* C:\Users\Archit\Documents\LTspiceXVII\Draft9.asc
--- AC Analysis ---
frequency:      10000      Hz
V(n001)::       mag:          5 phase:        0°      voltage
I(L)::          mag: 0.000795775 phase: -90°    device_current
I(Vs)::         mag: 0.000795775 phase: 90°    device_current
```

Name: Archit Agarwal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 4

## CIRCUIT 2 :

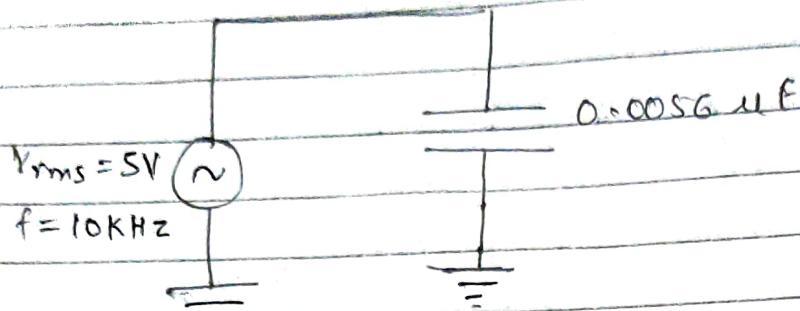

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi(10\text{K})(0.0056\mu)} = 28.42\text{ k}\Omega$$

$$Z = -j(28.42\text{k})$$

$$\bar{Z} = 28.42 \angle -90^\circ \text{ k}\Omega$$

$$\therefore \bar{I}_S = \frac{\bar{V}_S}{Z} = \frac{5 \angle 0^\circ}{28.42 \angle -90^\circ}$$

$$\bar{I}_S = 0.176 \angle 90^\circ \text{ mA}$$

$$\bar{V}_S = 5 \angle 0^\circ \text{ V}$$

$I_S$  leads  $\bar{V}_S$  by  $90^\circ$

In this circuit  $I_C = I_S$  and  $V_C = V_S$ .


### Phasor Diagram

$I_S, I_C$

$90^\circ$

$\rightarrow V_S, V_C$

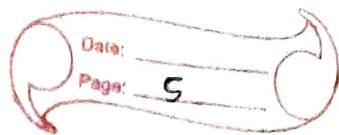
Name: Archit Agrawal  
Student ID: 202052307


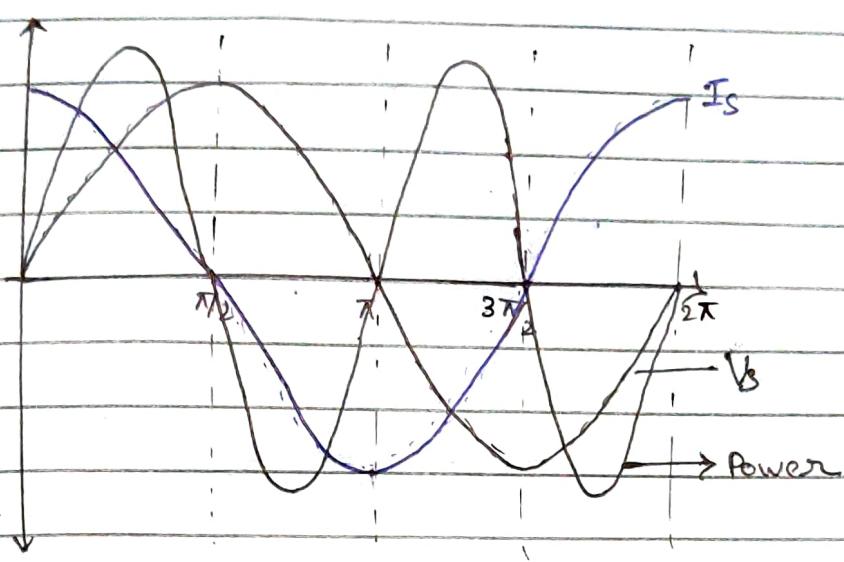
### Time Domain


$$V_C = V_S = 5\sqrt{2} \sin(\omega t) \text{ V}$$

$$I_C = I_S = 0.176\sqrt{2} \sin(\omega t + 90^\circ) \text{ mA}$$




In 1st and 3rd quarter of power cycle, energy is stored while in 2nd and 4th quarter of cycle, energy is released.


## CIRCUIT

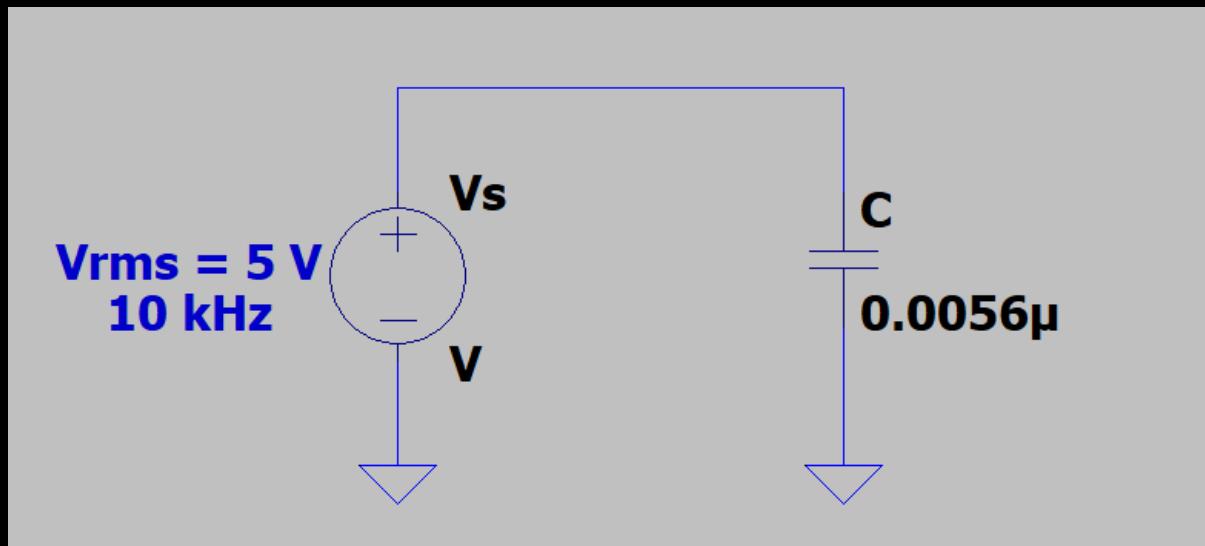
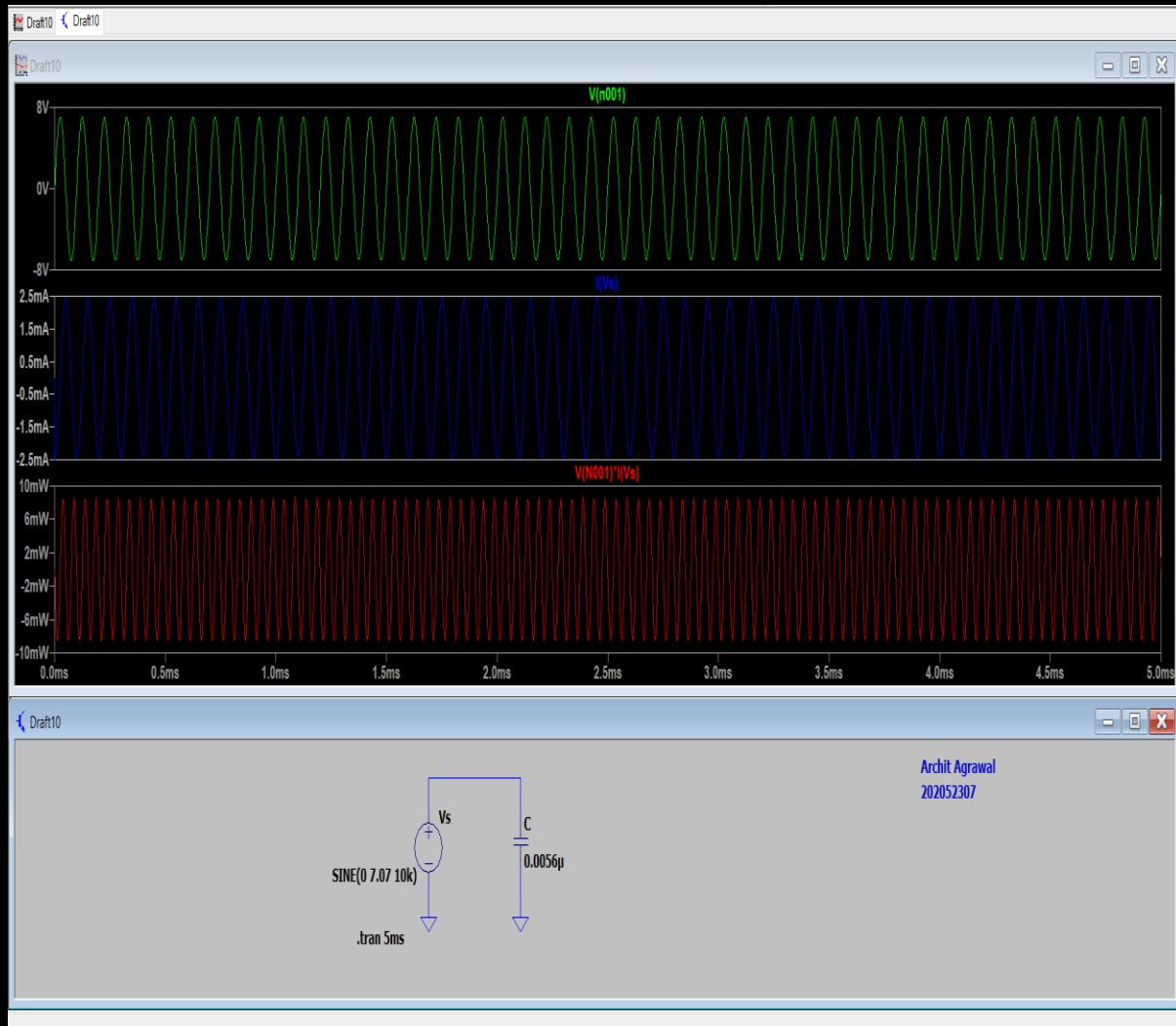
## Source Voltage, total current and total power


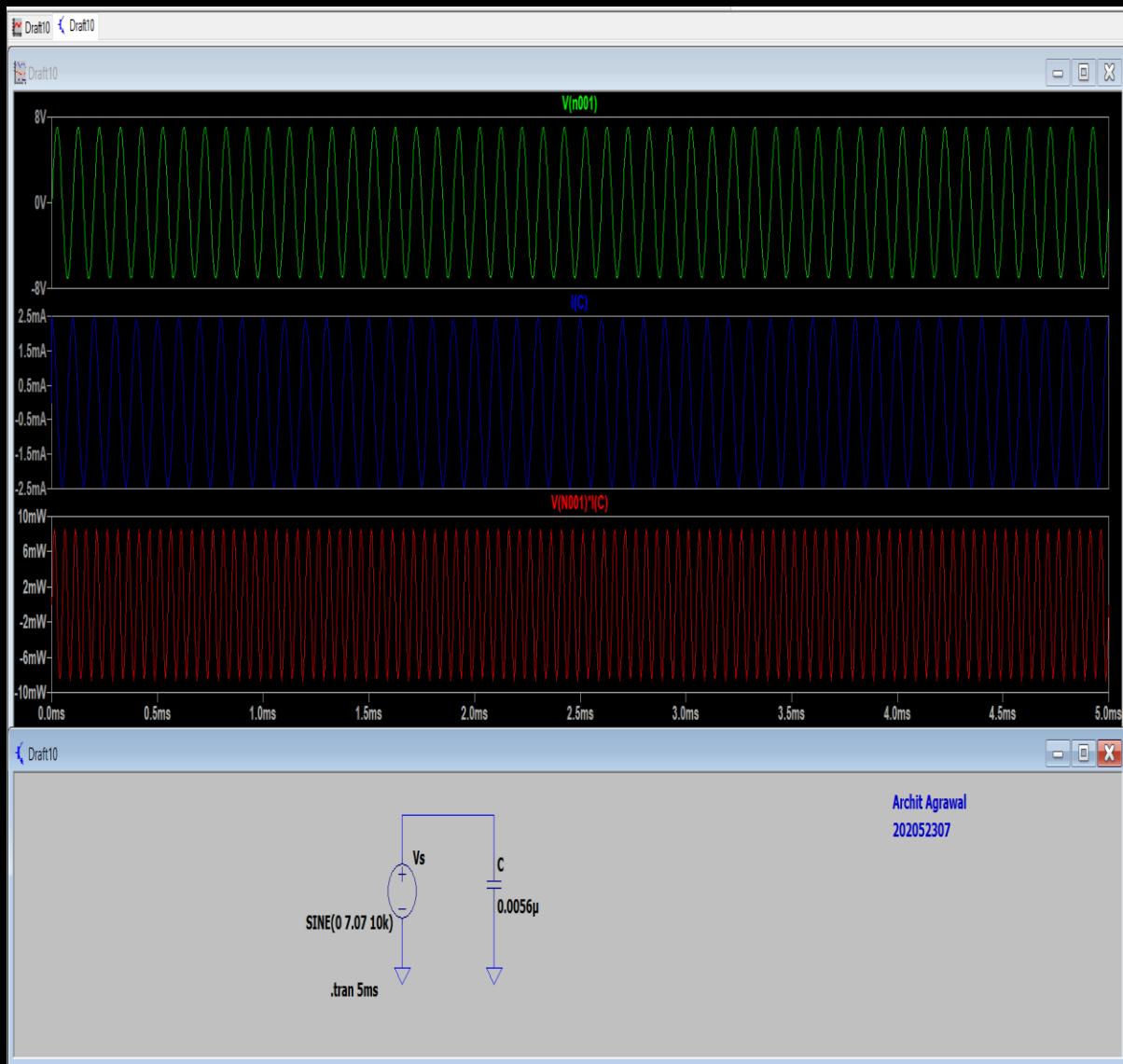
## Voltage, Current and Power across Capacitor



## AC Analysis

```
* C:\Users\Archit\Documents\LTspiceXVII\Draft10.asc
--- AC Analysis ---
frequency:      10000      Hz
V(n001):        mag:          5 phase:       0°      voltage
I(C):           mag: 0.00175929 phase:   90°      device_current
I(Vs):          mag: 0.00175929 phase: -90°      device_current
```


Name: Archit Agarwal  
Student ID: 207052307

Date:

Page:

6

### CIRCUIT 3:

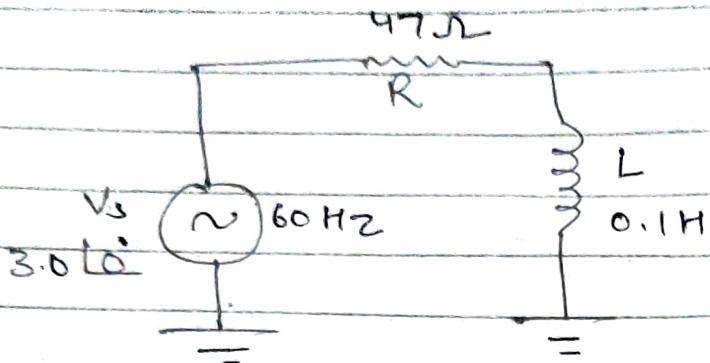

$$X_L = \omega L = 2\pi(60) \times 0.1 \\ = 37.68 \Omega$$

$$\therefore Z = 47 + j(37.68) \Omega$$
$$\underline{Z} = 60.24 \angle 38.69^\circ$$


$$\overline{I}_s = \frac{\overline{V}_s}{Z} = \frac{3 \angle 0^\circ}{60.24 \angle 38.69^\circ}$$

$$\overline{I}_R = \overline{I}_L = \overline{I}_s = 49.8 \angle -38.69^\circ \text{ mA}$$

$$\overline{V}_R = \overline{I}_s \cdot Z_R \\ = 49.8 \angle -38.69^\circ \times 47 \angle 0^\circ \text{ mV} \\ = 2.34 \angle -38.69^\circ \text{ V}$$

$$\overline{V}_L = \overline{I}_s \cdot Z_L \\ = 49.8 \angle -38.69^\circ \times 37.68 \angle 90^\circ \text{ mV} \\ = 1.877 \angle 51.31^\circ$$

### Phasor Diagram

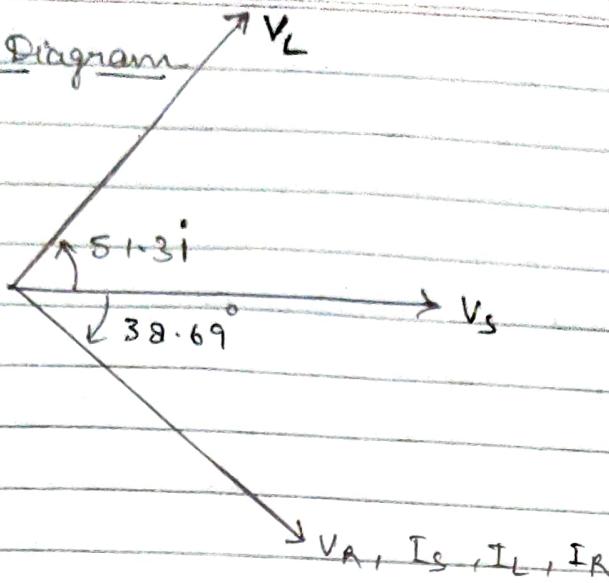

- ⇒  $I_s$  lags  $V_s$  by  $38.69^\circ$ .
- ⇒  $V_L$  leads  $V_s$  by  $51.31^\circ$ .
- ⇒  $V_R$  lags  $V_s$  by  $38.69^\circ$ .
- ⇒  $V_R$  is in phase with  $I_R$ .


### Time Domain

$$I_s = 49.8\sqrt{2} \sin(\omega t - 38.69^\circ) \text{ mA}$$

$$V_R = 2.34\sqrt{2} \sin(\omega t - 38.69^\circ) \text{ V}$$

$$V_L = 1.877\sqrt{2} \sin(\omega t + 51.31^\circ) \text{ V}$$
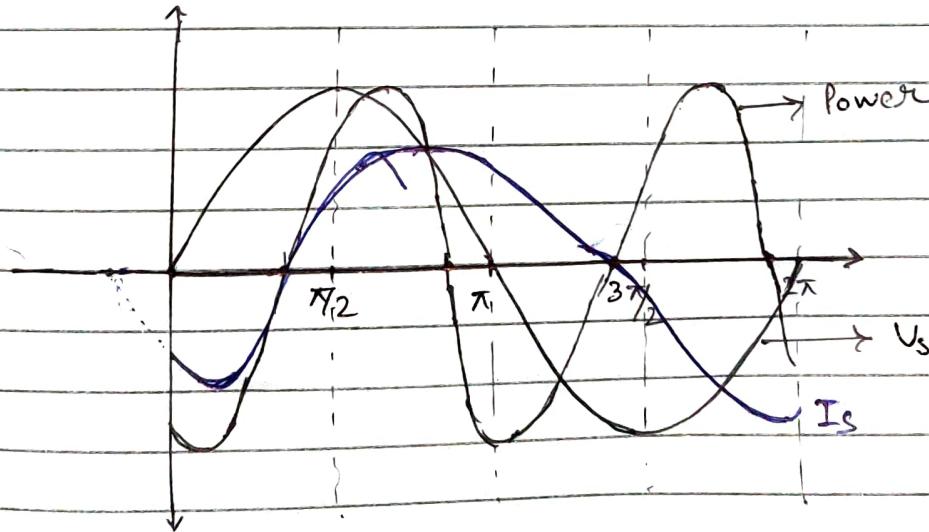
$$V_s = 3\sqrt{2} \sin(\omega t) \text{ V}$$



Name: Archit Agrawal  
Student ID: 202052307



$$(I_s)_m = 49.8 \sqrt{2} \text{ mA} = 70.42 \text{ mA}$$


$$(V_s)_m = 4.24 \text{ V}$$

$$\begin{aligned}\text{True Power (P)} &= I_{\text{rms}}^2 R \\ &= (49.8)^2 \times 47 \text{ mW} \\ &= 116.56 \text{ mW}\end{aligned}$$


$$\begin{aligned}\text{Reactive Power (Q)} &= I_{\text{rms}}^2 X_L \\ &= (49.8)^2 \times (37.68) \\ &= \cancel{116.56 \text{ mVAR}} \\ &= 93.45 \text{ mVAR}\end{aligned}$$

$$\begin{aligned}\text{Apparent Power (S)} &= I_{\text{rms}}^2 Z \\ &= 149.4 \text{ mVA}\end{aligned}$$


## CIRCUIT

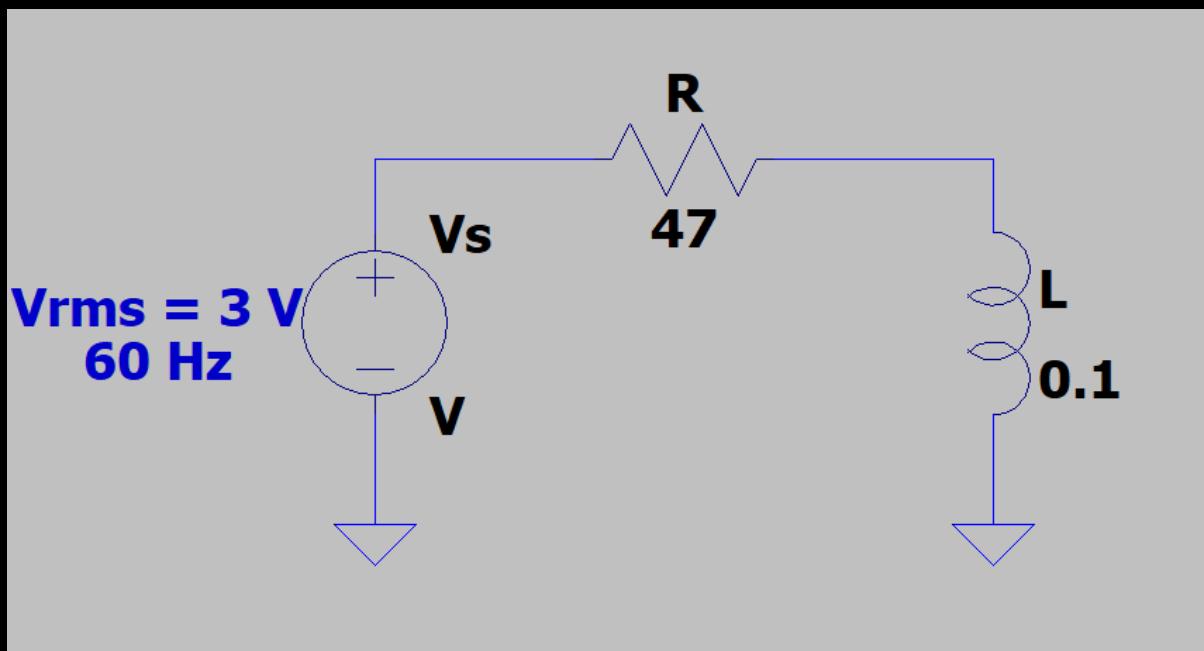

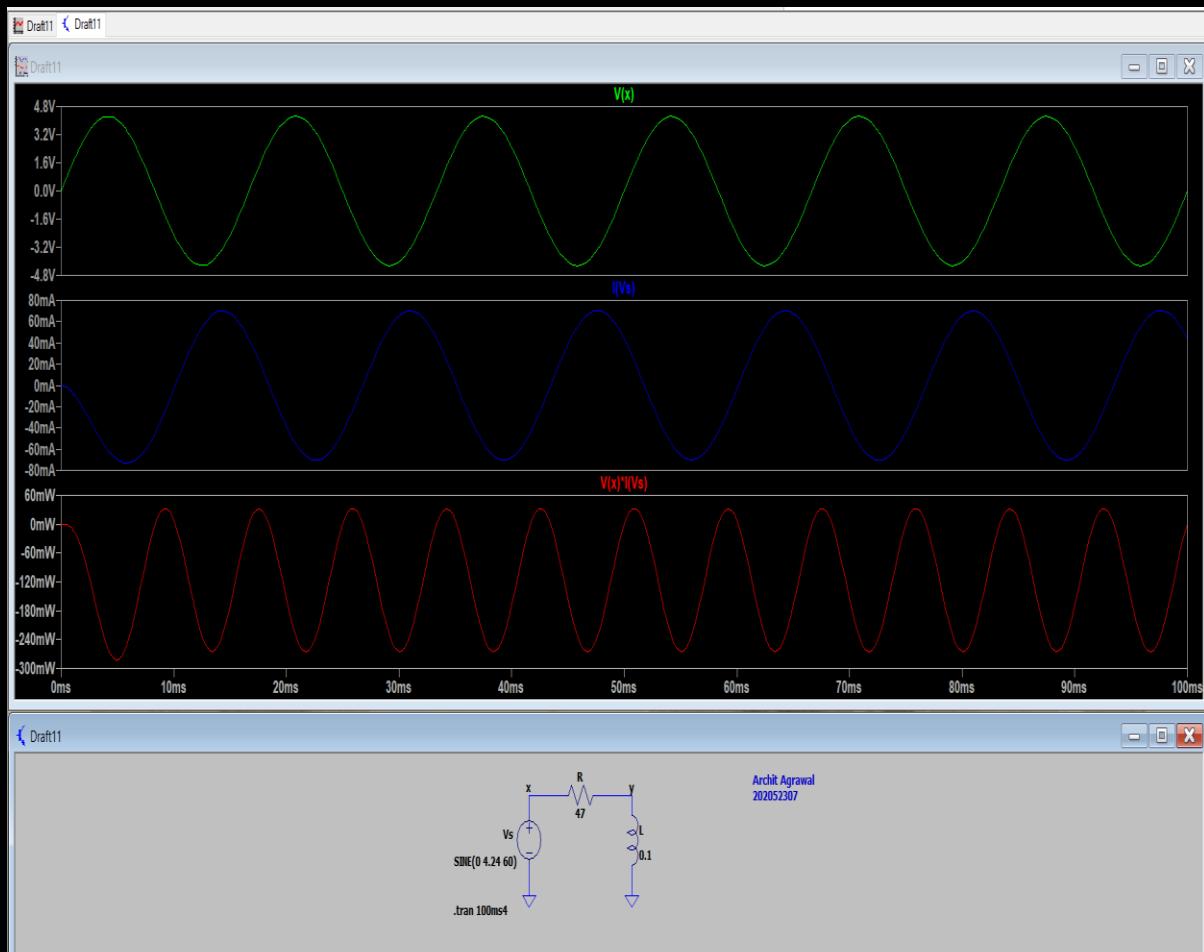
## Source Voltage, total current and total power


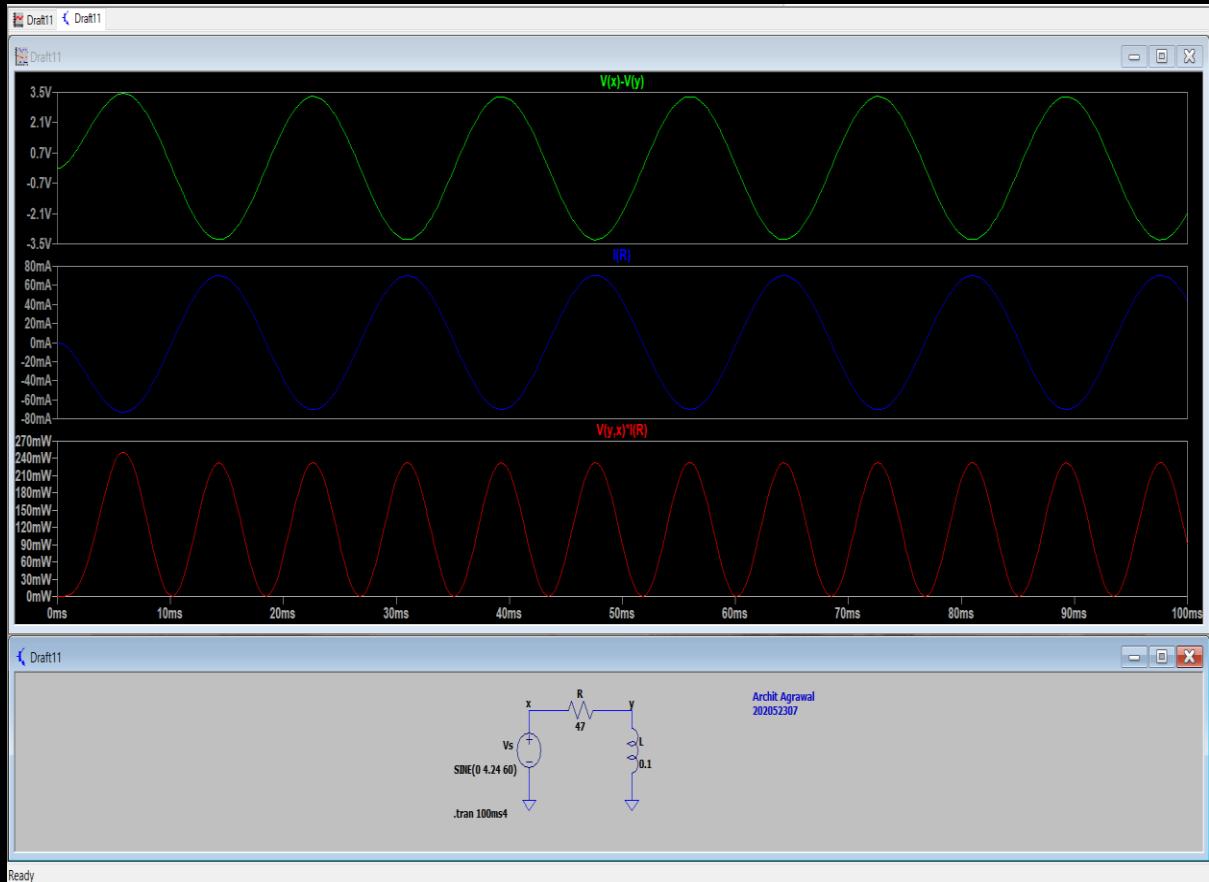
## Voltage, Current and Power across Resistor



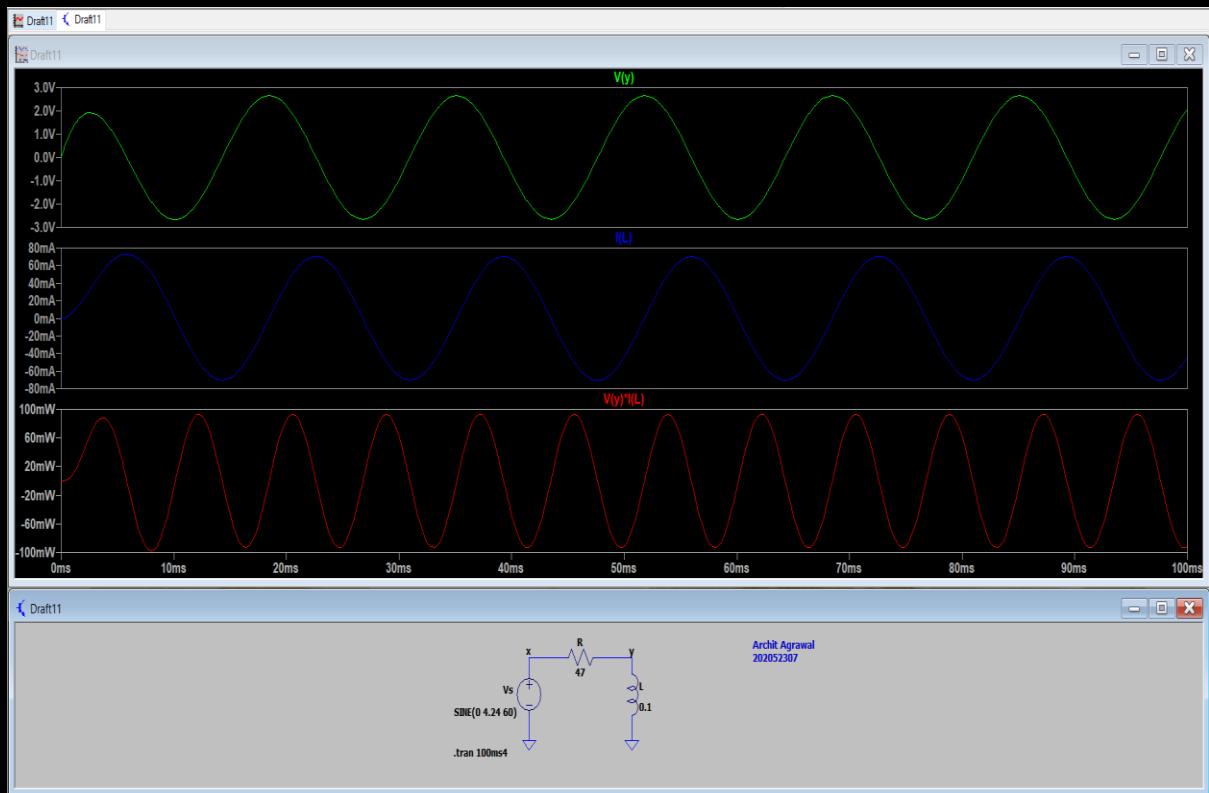
## Voltage, Current and Power across Inductor



## AC Analysis

```
* C:\Users\Archit\Documents\LTspiceXVII\Draft11.asc
--- AC Analysis ---
frequency:      60          Hz
V(y) :        mag:  1.87707 phase:  51.2657°      voltage
V(x) :        mag:  3 phase: 4.24074e-015°      voltage
I(L) :        mag: 0.0497908 phase: -38.7328°    device_current
I(R) :        mag: 0.0497908 phase: 141.267°      device_current
I(Vs) :       mag: 0.0497908 phase: 141.267°      device_current
```

## CIRCUIT 4 :

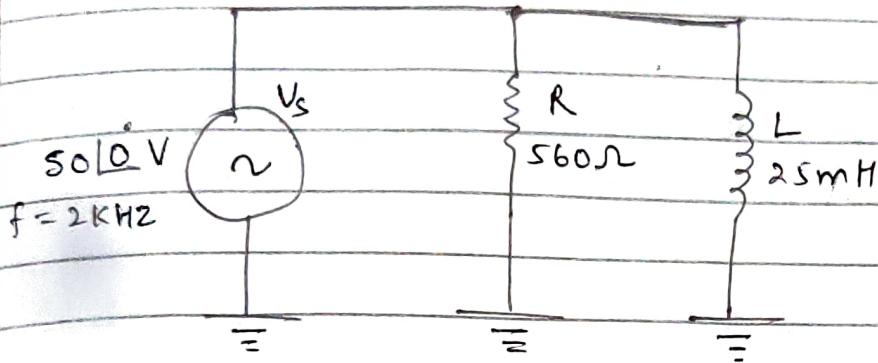

$$X_L = \omega L = 2\pi (2\text{K}) (25\text{m}) \\ = 314.2 \Omega$$

$$Z_R = 560 \angle 0^\circ \Omega = 560 + j(0) \Omega$$

$$Z_L = 314.2 \angle 90^\circ \Omega = 0 + j(314.2) \Omega$$

$$Z = Z_R \parallel Z_L$$

$$= \frac{Z_R \cdot Z_L}{Z_R + Z_L} = \frac{560 \angle 0^\circ \times 314.2 \angle 90^\circ}{560 + j(314.2)}$$

$$Z = \frac{175952 \angle 90^\circ}{642.12 \angle 29.29^\circ}$$

$$\bar{Z} = 274 \angle 60.71^\circ \Omega$$

$$\bar{V}_R = \bar{V}_L = \bar{V}_s = 50 \angle 0^\circ \text{ V}$$


$$I_s = \frac{\bar{V}_s}{\bar{Z}} = \frac{50 \angle 0^\circ}{274 \angle 60.71^\circ} = 0.182 \angle -60.71^\circ \text{ A}$$

$$I_R = \frac{\bar{V}_A}{Z_R} = \frac{50 \angle 0^\circ}{560 \angle 0^\circ} = 0.09 \angle 0^\circ A$$

$$I_L = \frac{\bar{V}_L}{Z_L} = \frac{50 \angle 0^\circ}{314.2 \angle 90^\circ} = 0.159 \angle -90^\circ A$$
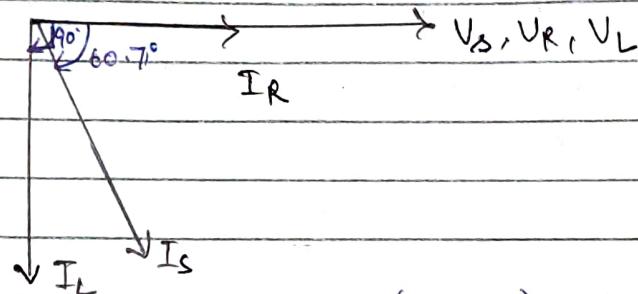
### Phasor Diagram

- ⇒  $I_S$  lags  $V_S$  by  $60.7^\circ$ .
- ⇒  $V_R$  is in phase with  $I_R$ .
- ⇒  $I_L$  lags  $V_S$  by  $90^\circ$ .



$$Z = 134.04 + j(238.9) \Omega$$

$$\begin{aligned} \text{True power (P)} &= I_{\text{rms}}^2 Z_R \\ &= (0.182)^2 \times 134.04 \\ &= 4.39 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Reactive power (Q)} &= I_{\text{rms}}^2 Z_{X_L} \\ &= (0.182)^2 \times (238.9) \\ &= 7.826 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{Apparent Power (S)} &= I_{\text{rms}}^2 Z \\ &= (0.182)^2 \times 274 \\ &= 8.976 \text{ W} \end{aligned}$$

Name: Ankit Agrawal  
Student ID : 202052307




## Time Domain

$$V_s = 50\sqrt{2} \sin(\omega t + 0^\circ) \text{ V}$$


$$I_s = 0.182\sqrt{2} \sin(\omega t - 60^\circ) \text{ A}$$

$$I_R = 0.09\sqrt{2} \sin(\omega t + 0^\circ) \text{ A}$$


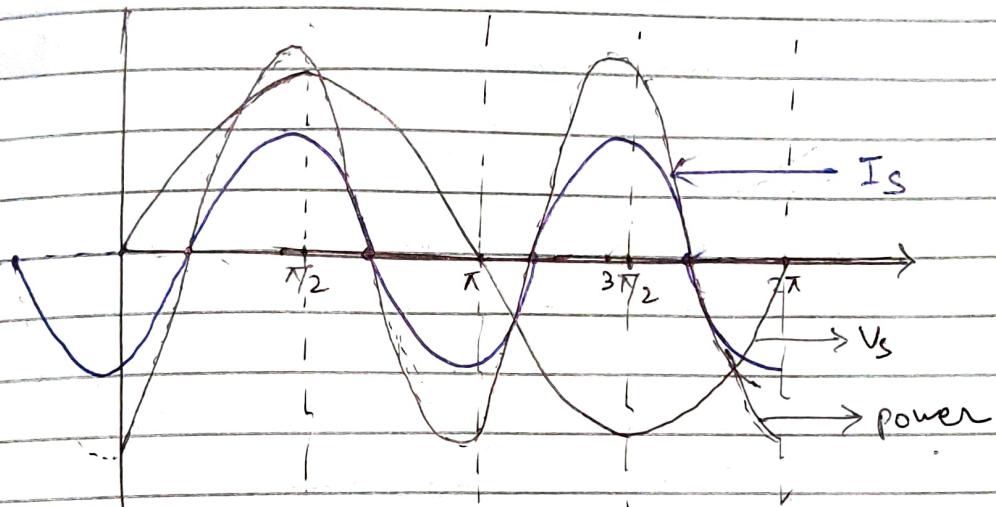
$$I_L = 0.159\sqrt{2} \sin(\omega t - 90^\circ) \text{ A}$$




## CIRCUIT

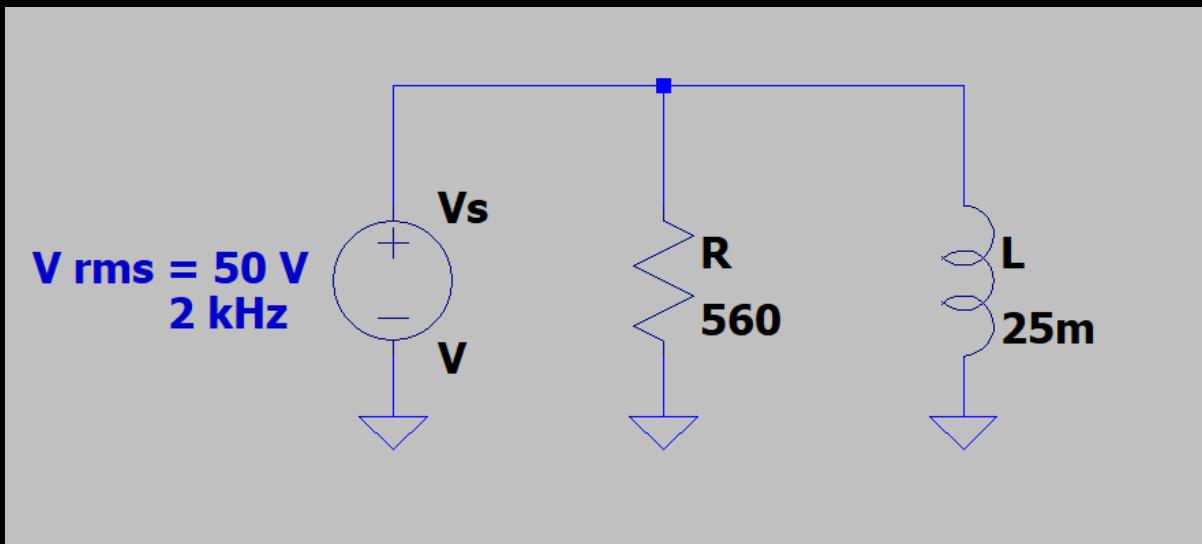

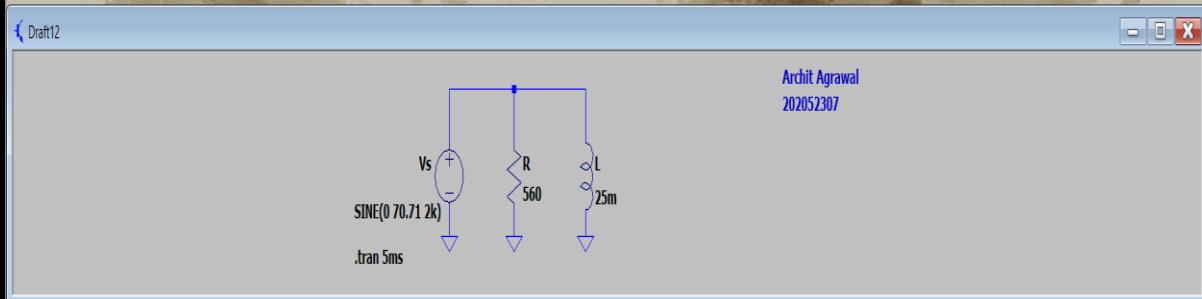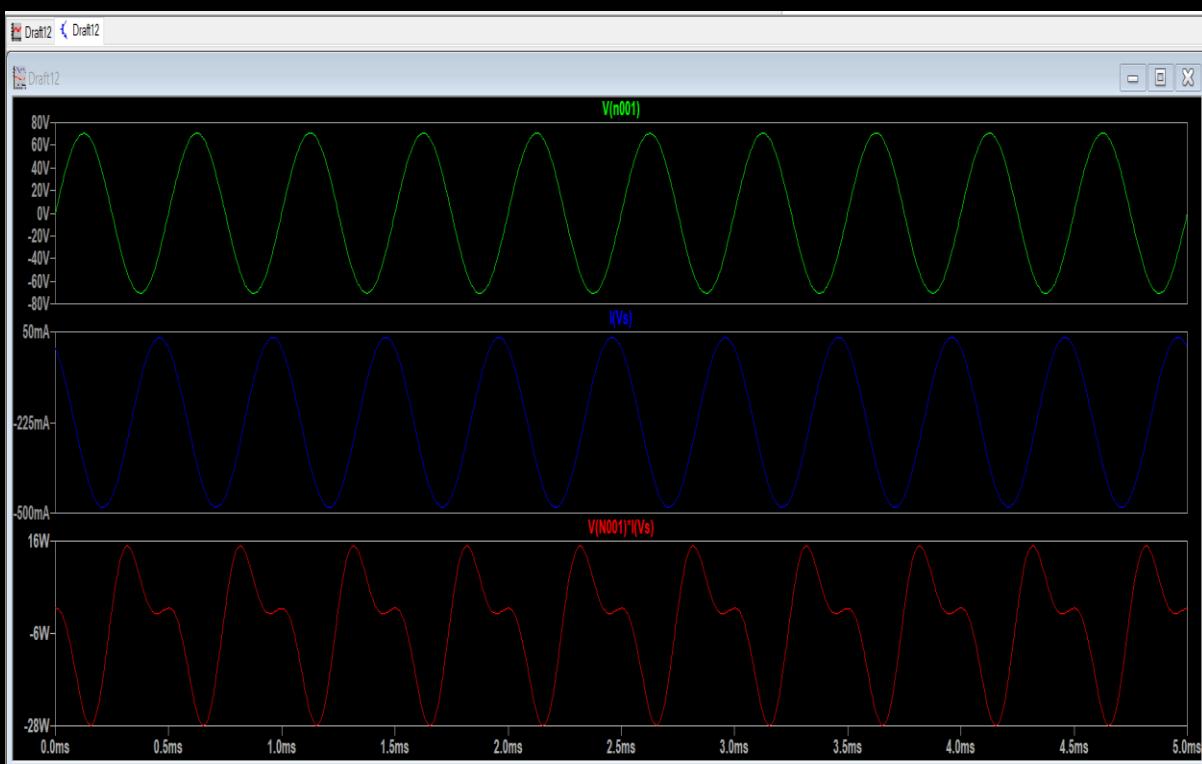
## Source Voltage, total current and total power


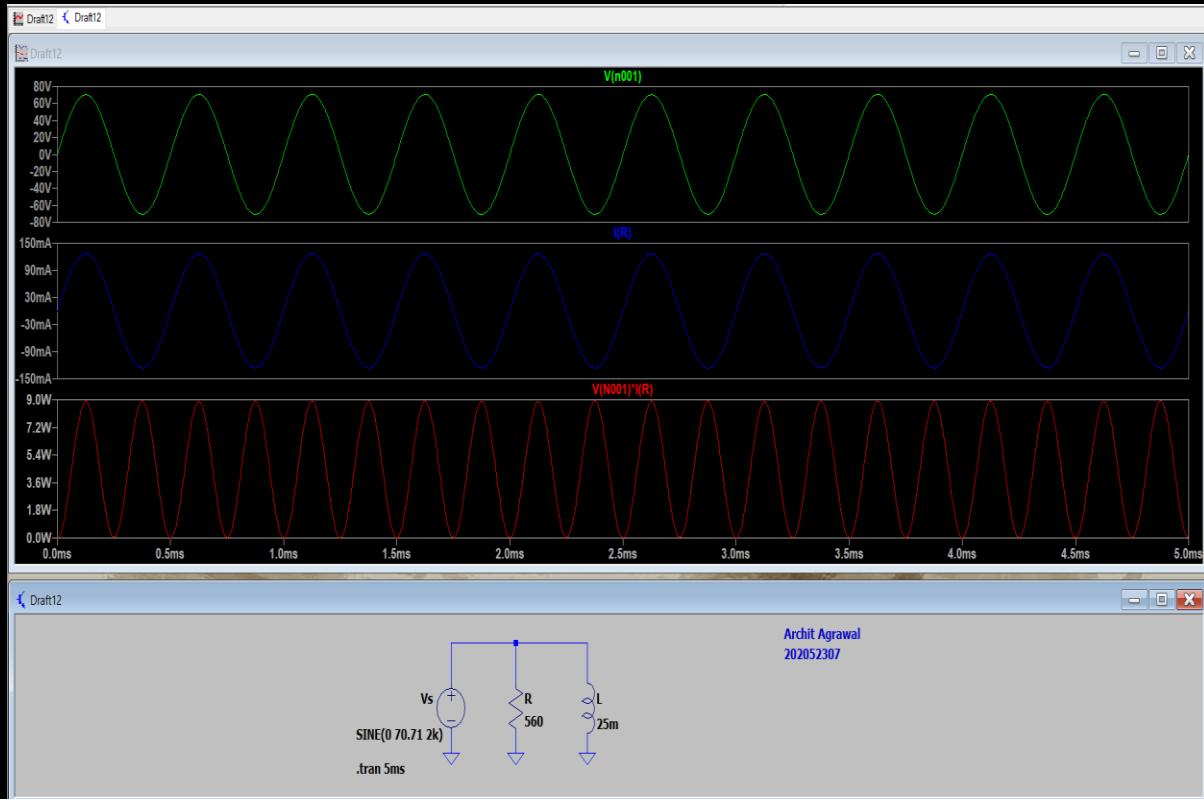
## Voltage, Current and Power across Resistor


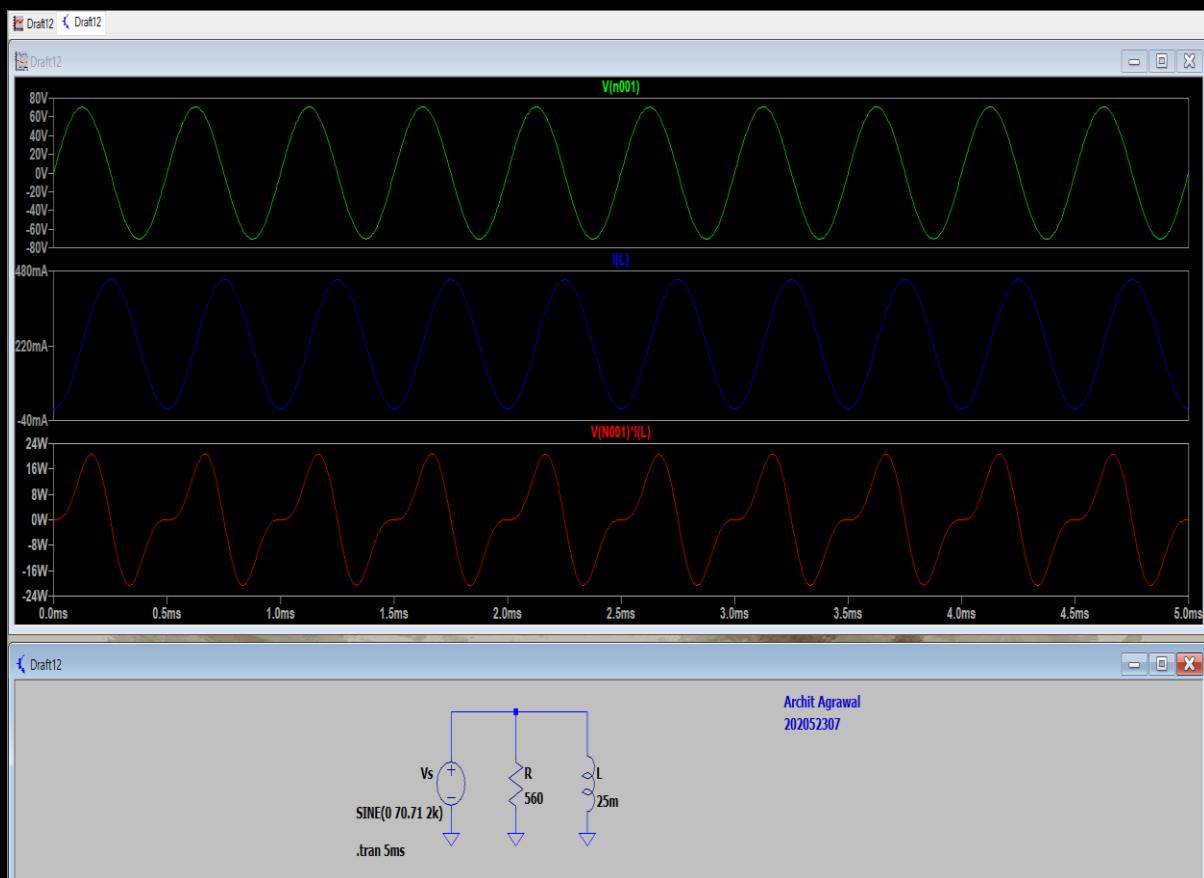
## Voltage, Current and Power across Inductor



## AC Analysis


```
LT * C:\Users\Archit\Documents\LTspiceXVII\Draft12.asc X
--- AC Analysis ---

frequency:      2000      Hz
V(n001):        mag:      50 phase:      0°      voltage
I (L) :         mag:  0.159155 phase: -89.9998° device_current
I (R) :         mag:  0.0892857 phase:      0° device_current
I (Vs) :        mag:  0.182489 phase: 119.293° device_current
```

Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 12

### CIRCUIT 5:

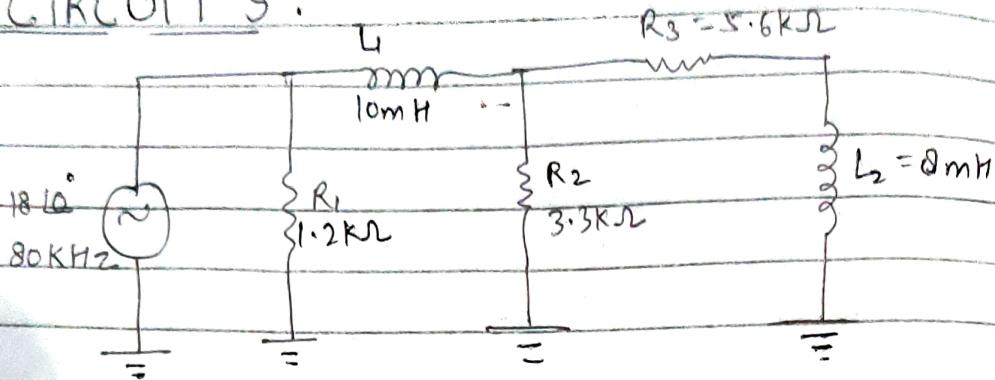

$$X_L_1 = \omega L_1 = 2\pi f L_1 = 2\pi (80\text{K})(10\text{m}) = 5.026\text{k}\Omega$$

$$X_L_2 = \omega L_2 = 2\pi (80\text{K}) (8\text{m}) = 4.021\text{k}\Omega$$

$$Z_1 = Z_{R_2} + Z_{R_3}$$

$$\begin{aligned} &= 5.6\text{k} + j(4.021\text{k}) \cdot \text{j}\Omega \\ &= 6.894 \angle 35.68^\circ \text{k}\Omega \end{aligned}$$

$$Z_2 = Z_{R_2} \parallel Z_1$$

$$= \frac{Z_{R_2} \cdot Z_1}{Z_1 + Z_{R_2}}$$

$$= \frac{3.3\text{k} \angle 0^\circ \times 6.894\text{k} \angle 35.68^\circ}{(5.6\text{k} + j(4.021\text{k})) + (3.3\text{k})}$$

$$= \frac{22.75 \times 10^6 \angle 35.68^\circ}{9.766\text{k} \angle 24.31^\circ}$$

$$= 2.33\text{k} \angle 11.37^\circ \text{k}\Omega$$

$$Z_2 = 2.284\text{k} + j(0.46\text{k})\text{k}\Omega$$

Name: Archit Agrawal  
Student ID: 202052307



$$\begin{aligned}Z_3 &= Z_2 + jX_L \\&= 2.284\text{K} + j(0.46\text{K}) + j(5.486\text{K}) \\&= 2.284\text{K} + j(5.486\text{K}) \\&= 5.942\text{K} \angle 67.4^\circ \text{ } \Omega\end{aligned}$$

$$Z = Z_{R1} \parallel Z_3$$

$$\begin{aligned}&= \frac{Z_{R1} \cdot Z_3}{Z_{R1} + Z_3} \\&= \frac{1.2\text{K} \angle 0^\circ \times 5.942\text{K} \angle 67.4^\circ}{2.284\text{K} + j(5.486\text{K}) + 1.2\text{K}} \\&= \frac{7.13 \angle 67.4^\circ \times 10^6}{6.5 \angle 57.6^\circ \times 10^3} \\Z &= 1.096\text{K} \angle 9.8^\circ \text{ } \Omega\end{aligned}$$

$$Z = 1.08\text{K} + j(0.187\text{K}) \text{ } \Omega$$

$$\therefore \bar{I}_S = \frac{\bar{V}_S}{Z} = \frac{18 \angle 0^\circ}{1.096\text{K} \angle 9.8^\circ} = 16.42 \angle -9.8^\circ \text{ mA}$$

$$\bar{I}_S = 16.18 - j(2.794) \text{ mA}$$

From the circuit we know,  $V_{R1} = V_S$

$$\therefore \bar{I}_{R1} = \frac{\bar{V}_S}{Z_{R1}} = \frac{18 \angle 0^\circ}{1.2\text{K} \angle 0^\circ} = 15 \angle 0^\circ \text{ mA}$$

Name: Archit Agrawal  
Student ID: 202052367

Date:  
Page:

14

$$\bar{I}_L = \bar{I}_S - \bar{I}_{A_1}$$

$$= 16.18 - j(2.794) - 15$$

$$= 1.18 - j(2.794) \text{ mA}$$

$$= 3.032 \angle -67.10^\circ \text{ mA}$$

$$\therefore \bar{V}_L = \bar{I}_L \times \bar{Z}_L$$

$$= 15.18$$

$$= 3.032 \angle -67.10^\circ \text{ mA} \times 5.026 \text{ K. } 19^\circ$$

$$= 15.18 \angle 22.6^\circ \text{ V}$$

$$V_L = 14.01 + j(5.83) \text{ V}$$

$$\bar{V}_{R_2} = \bar{V}_S - \bar{V}_{L_1}$$


$$V_{R_2} = 18 - (14.01 + j(5.83))$$

$$= 3.99 - j(5.83) \text{ V}$$


$$\bar{V}_{R_2} = 7.07 \angle -55.6^\circ \text{ V}$$

$$\bar{I}_{R_2} = \frac{\bar{V}_{R_2}}{Z_{R_2}} = \frac{7.07 \angle -55.6^\circ}{3.3 \text{ K } 10^\circ}$$
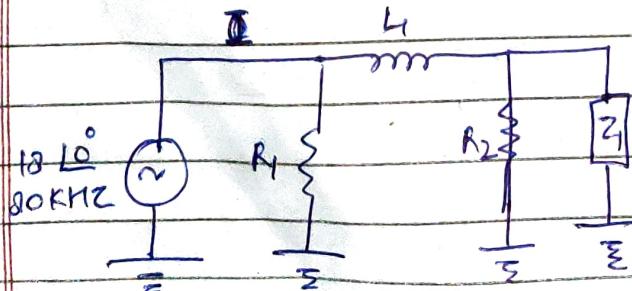
$$\bar{I}_{R_2} = 2.142 \angle -55.6^\circ \text{ mA}$$



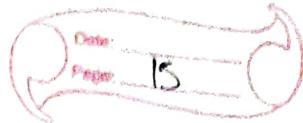Name: Archit Agrawal  
Student ID: 202052307



$$\overline{I}_{Z_1} = \frac{\overline{V}_{Z_1}}{Z_1} = \frac{7.07}{6.894K} \angle -55.6^\circ \quad (\because \overline{V}_{Z_1} = \overline{V}_S - \overline{V}_{L_1})$$

$$\overline{I}_{Z_1} = 1.025 \angle -91.28^\circ \text{ mA}$$

$$\overline{I}_{R_3} = \overline{I}_{L_2} = \overline{I}_{Z_1} = 1.025 \angle -91.28^\circ \text{ mA}$$

$$\overline{V}_{R_3} = \overline{I}_{R_3} \times Z_{R_3}$$

$$= 1.025 \angle -91.28^\circ \text{ mA} \times 5.6K \angle 0^\circ$$

$$\overline{V}_{R_3} = 5.734 \angle -91.28^\circ \text{ V}$$

and,  $\overline{V}_{L_2} = \overline{I}_{L_2} \times Z_{X_{L_2}}$

$$= 1.025 \angle -91.28^\circ \text{ mA} \times 4.021K \angle 90^\circ$$
$$= 4.117 \angle -1.25^\circ \text{ V}$$

The values calculated are

$$\overline{V}_S = 18 \angle 0^\circ \text{ V}$$

$$\overline{I}_S = 16.42 \angle -9.8^\circ \text{ mA}$$

$$\overline{V}_{R_1} = \overline{V}_S = 18 \angle 0^\circ \text{ V}$$

$$\overline{I}_{R_1} = 15 \angle 0^\circ \text{ mA}$$

$$\overline{V}_{L_1} = 15.18 \angle 22.6^\circ \text{ V}$$

$$\overline{I}_{L_1} = 3.032 \angle -67.10^\circ \text{ mA}$$

$$\overline{V}_{R_2} = 7.07 \angle -55.6^\circ \text{ V}$$

$$\overline{I}_{R_2} = 2.142 \angle -55.6^\circ \text{ mA}$$

Name: Archit Agrawal  
Standard ID : 202052307

Date: \_\_\_\_\_  
Page: 16

$$\frac{\bar{V}_{R_3}}{\bar{I}_{R_3}} = 5.734 \angle -91.28^\circ V$$
$$\bar{I}_{R_3} = 1.025 \angle -91.28^\circ mA$$

$$\frac{\bar{V}_{L_2}}{\bar{I}_{L_2}} = 4.117 \angle -1.25^\circ V$$
$$\bar{I}_{L_2} = 1.025 \angle -91.28^\circ mA$$

Now,

$$V_s = 18 \angle 0^\circ V$$

$$I_s = 16.42 \angle -9.8^\circ mA$$

phase difference ( $\phi$ ) =  $9.8^\circ$   
power factor ( $\cos\phi$ ) =  $\cos(9.8^\circ) = 0.985$

$$\begin{aligned}\text{Apparent Power (S)} &= \bar{I}_{ms} \cdot \bar{V}_{ms} \\ &= 16.42 \times 18 \\ &= 0.295 W\end{aligned}$$


$$\begin{aligned}\text{True Power (P)} &= S \times \cos\phi \\ &= 0.295 \times 0.985 \\ &= 0.291 W\end{aligned}$$

$$\begin{aligned}\text{Reactive power (Q)} &= S \times \sin\phi \\ &= 0.295 \times \sin(9.8^\circ) \\ &= 0.0503 W\end{aligned}$$

Name: Archit Agrawal  
Student ID: 202052307

Date: \_\_\_\_\_  
Page: 17

## Phasor Diagram

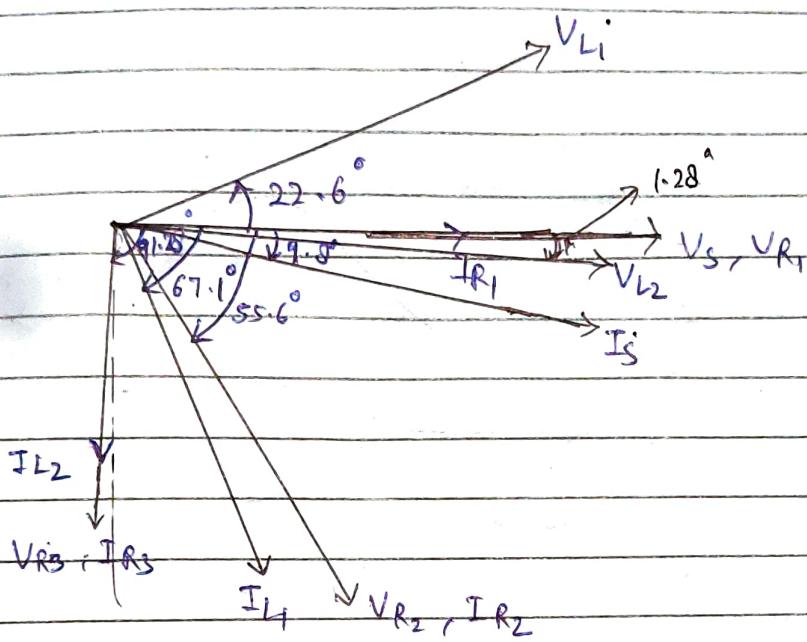

## Time Domain

$$V_s = 18\sqrt{2} \sin(\omega t) \text{ V}$$

$$I_3 = 16.42\sqrt{2} \sin(\omega t - 9.8^\circ) \text{ mA}$$

$$V_{R_1} = 18\sqrt{2} \sin(\omega t) \text{ V}$$

$$I_{R_1} = 15\sqrt{2} \sin(\omega t) \text{ mA}$$

$$V_{R_2} = 7.07 \sqrt{2} \sin(\omega t - 55.6^\circ) V$$

$$I_{R_2} = 2.142 \sqrt{2} \sin(\omega t - 55.6^\circ) V$$

$$V_{R_3} = 5.734 \sqrt{2} \sin(\omega t - 91.28^\circ) V$$

$$I_{R_3} = 1.025 \sqrt{2} \sin(\omega t - 91.28^\circ) \text{ mA}$$

Name: Archit Agrawal  
Student ID: 202052307


Date: \_\_\_\_\_  
Page: \_\_\_\_\_ 18

$$V_{L_1} = 15.18\sqrt{2} \sin(\omega t + 22.6^\circ) V$$


$$I_{L_1} = 3.032\sqrt{2} \sin(\omega t - 67.4^\circ) mA$$

$$V_{L_2} = 4.117\sqrt{2} \sin(\omega t - 1.25^\circ) V$$


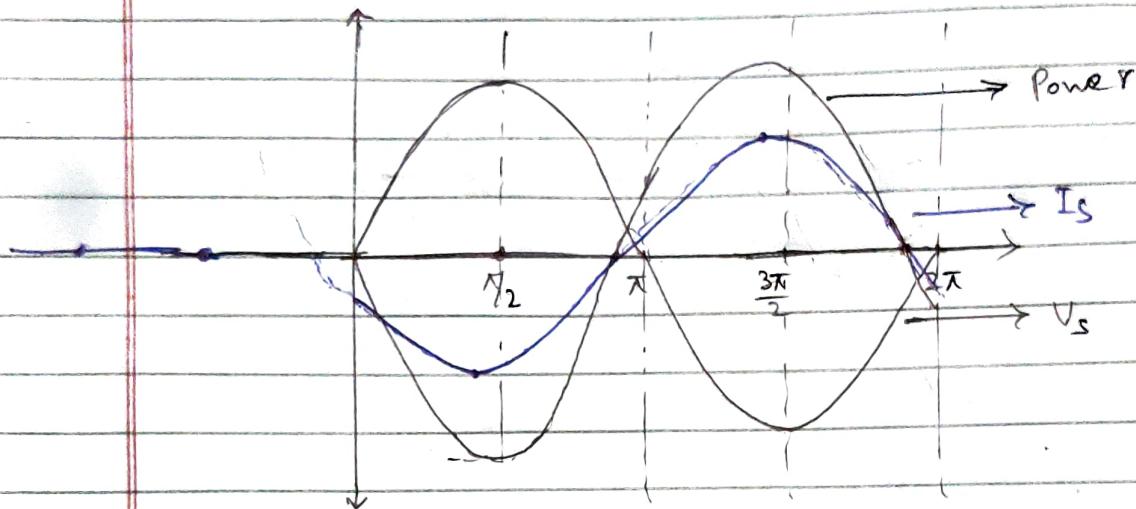
$$I_{L_2} = 1.025\sqrt{2} \sin(\omega t - 91.25^\circ) mA$$




## CIRCUIT

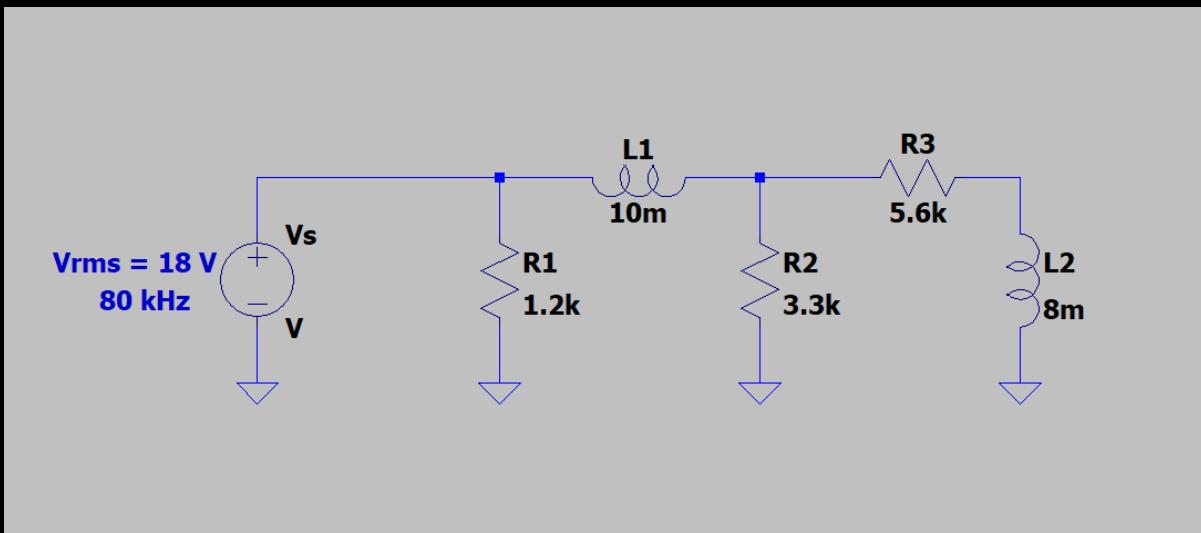

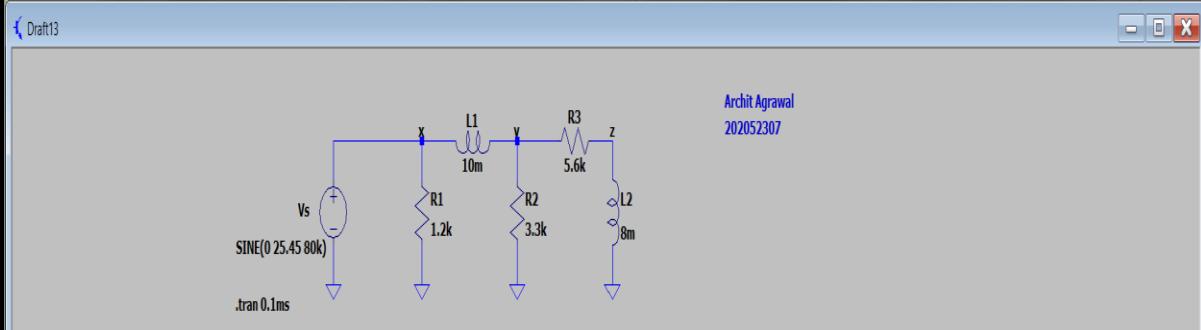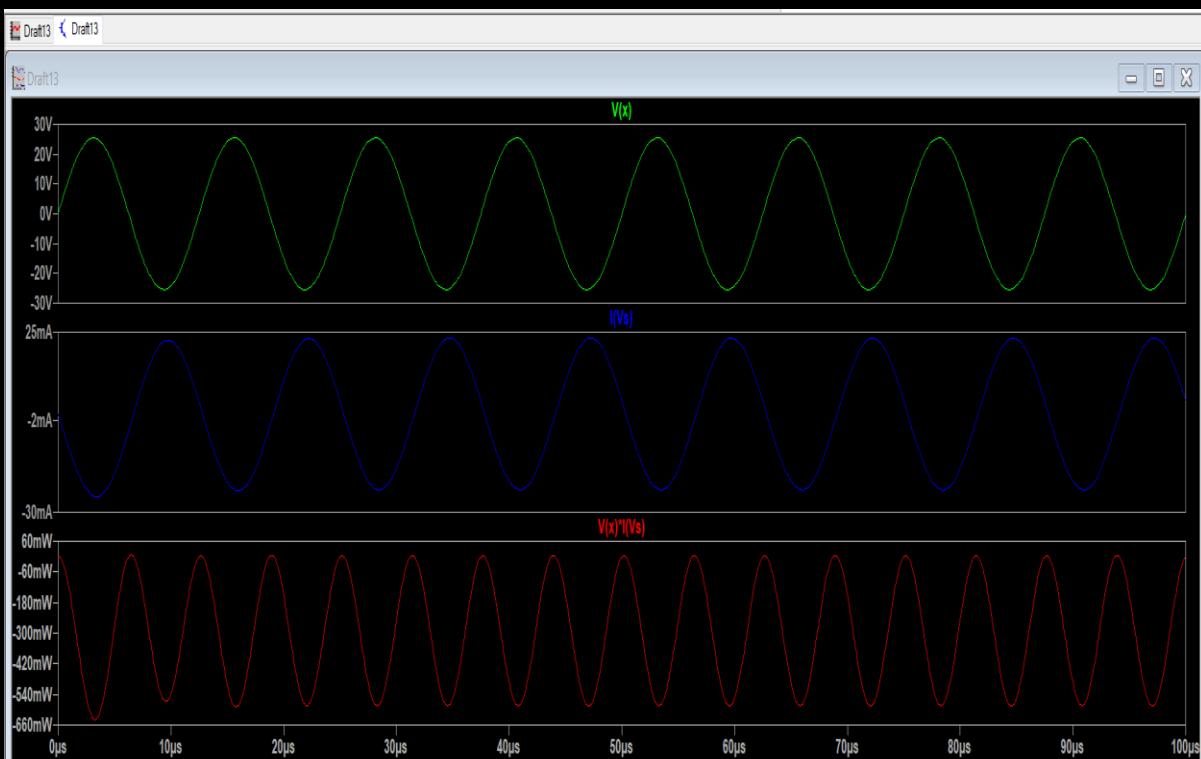
## Source Voltage, total current and total power



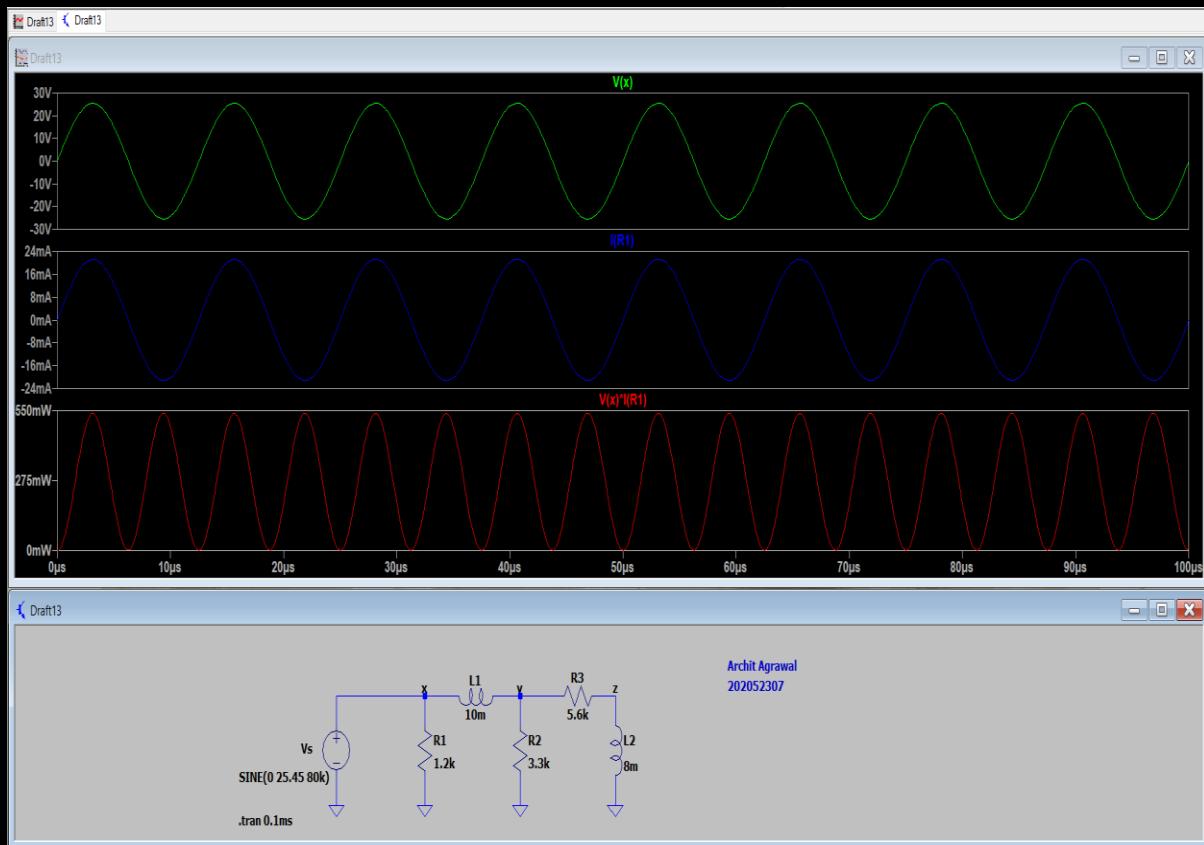
## Voltage, Current and Power across Resistance $R_1$



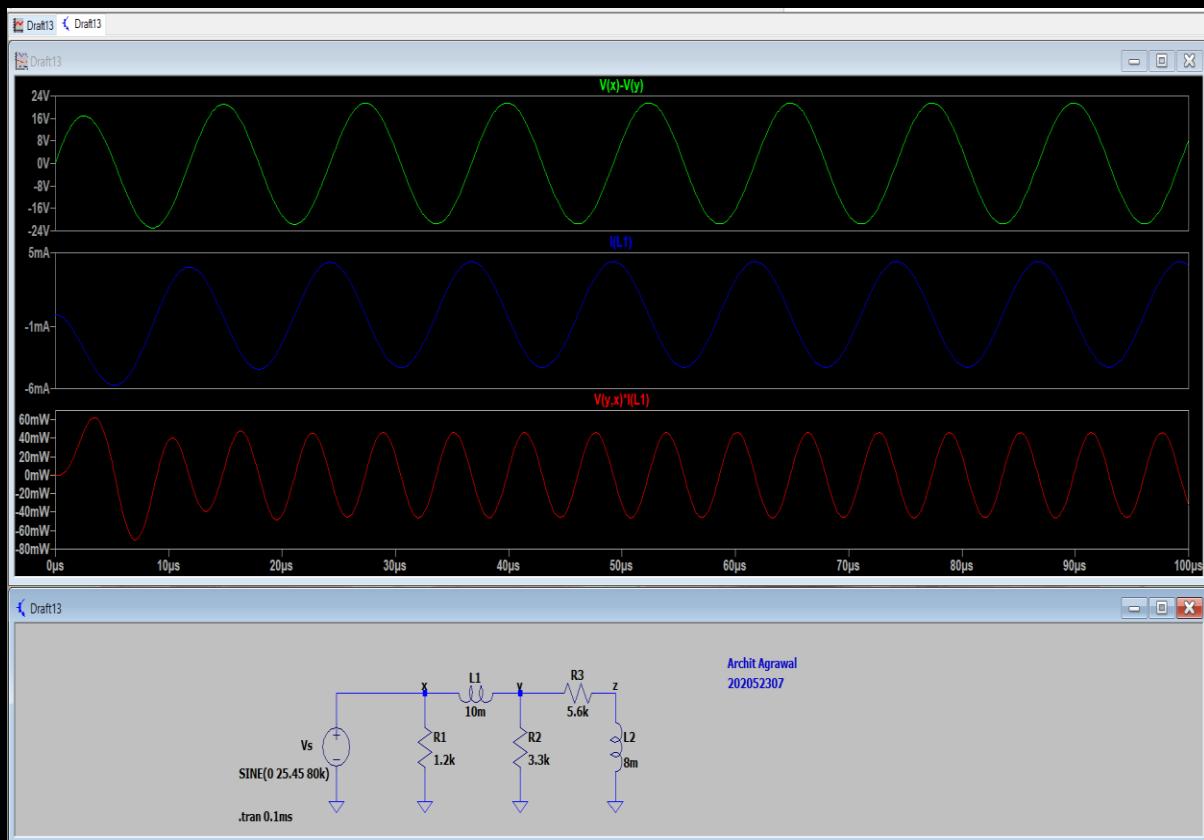
## Voltage, Current and Power across Inductance $L_1$



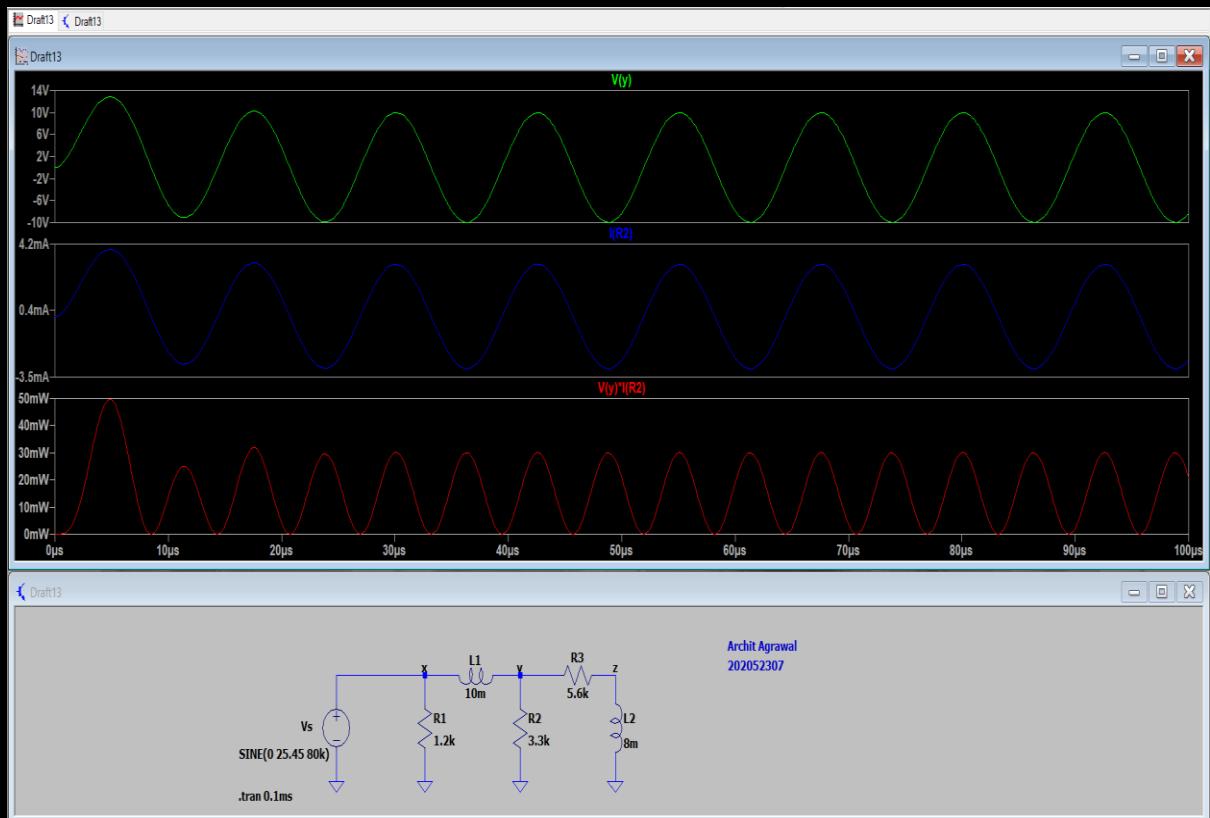
## Voltage, Current and Power across Resistance $R_2$


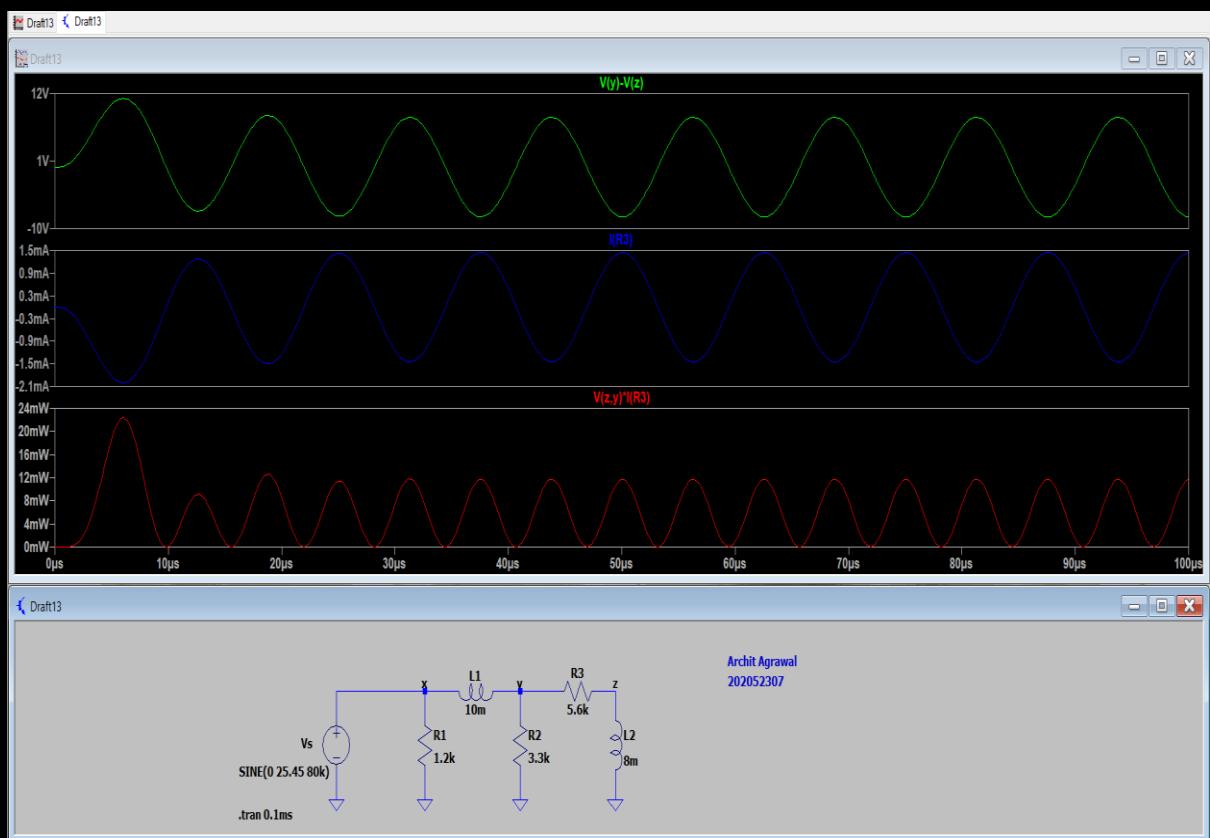
## Voltage, Current and Power across Resistance $R_3$


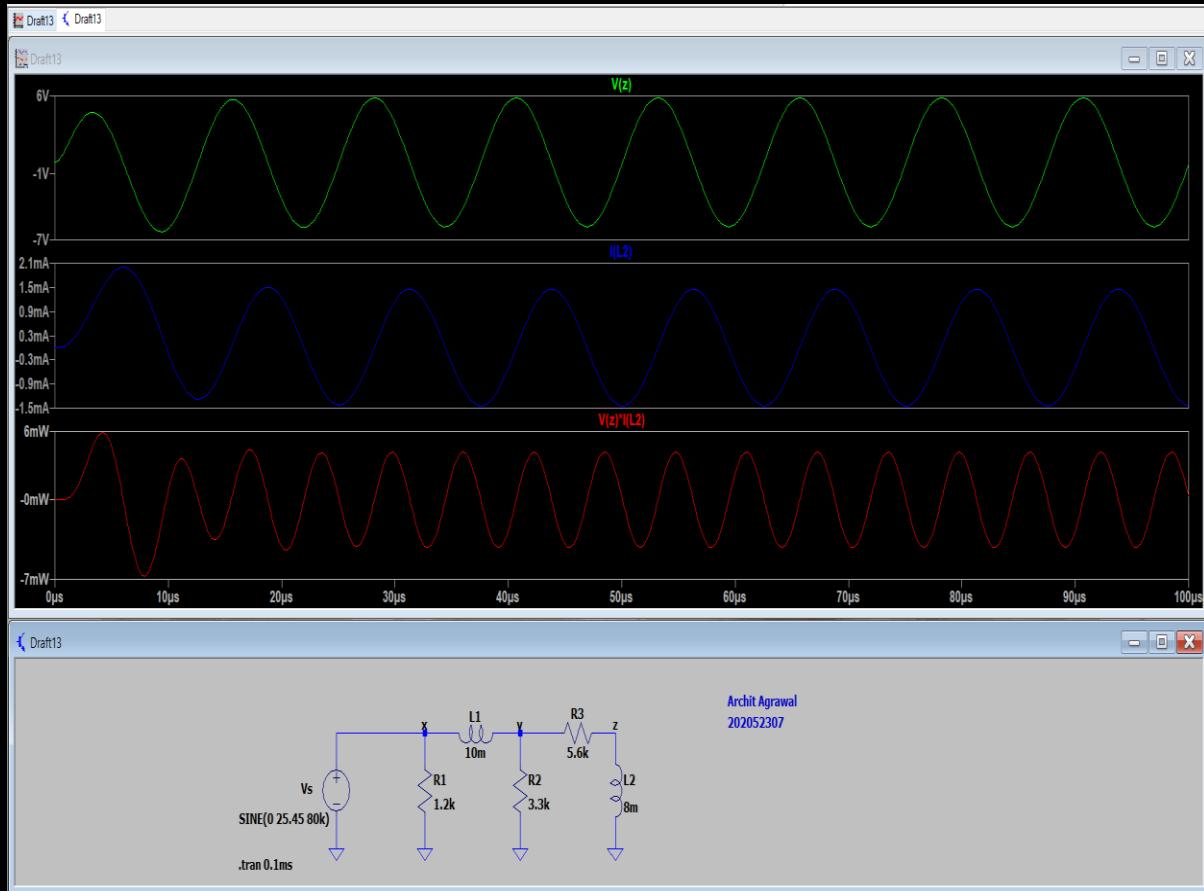
## Voltage, Current and Power across Inductance $L_2$



## AC Analysis

```

* C:\Users\Archit\Documents\LTspiceXVII\Draft13.asc
--- AC Analysis ---

frequency:      80000      Hz
V(z) :          mag:  4.11601 phase: -1.71121°      voltage
V(x) :          mag:     18 phase: 1.41358e-015°      voltage
V(y) :          mag:  7.05672 phase: -56.0299°      voltage
I(L1) :         mag: 0.00302923 phase: 112.603°      device_current
I(L2) :         mag: 0.00102357 phase: -91.7112°      device_current
I(R3) :         mag: 0.00102357 phase: 88.2888°      device_current
I(R2) :         mag: 0.0021384 phase: -56.0299°      device_current
I(R1) :         mag: 0.015 phase: 1.41358e-015°      device_current
I(Vs) :         mag: 0.0164044 phase: 170.185°      device_current

```

### Observations and Conclusions

Performing the experiment we have drawn following conclusions :-

- (i) the current through a resistor is in phase of the voltage across it.
- (ii) the current through an inductor lags by the voltage across it by  $90^\circ$ .
- (iii) the current through an capacitor leads by the voltage across it by  $90^\circ$ .
- (iv) the phase angle is equal to the difference between phase of source voltage and total current.
- (v) A resistor is a power-dissipating device while an inductor and capacitor only stores and release energy in an AC circuit.