
 


## Assignment 6

 1. Realize the circuit shown below contains two comparators



We know that, in comparator,



$V_{out} = 1$  when  $V_+ > V_-$   
and  $V_{out} = 0$  when  $V_+ \leq V_-$

Therefore, in the above given circuit, the comparator at top outputs 0 and the comparator at bottom also outputs 0.

$\therefore$  in the latch, we have  $R=0$  and  $S=0$ , and this is the memory still in a ~~latch~~ SR latch. Hence, the circuit will retain the previous output i.e. it will retain its memory.

2. A new clocked A-B flip flop is defined with two inputs X AND Y in addition to the clock input. The flip flop function as follows:

- If  $AB = 00$ , the flip flop changes state with each clock pulse
- If  $AB = 01$  the flip flop state Z becomes 1 with the next clock pulse.
- If  $AB = 10$ , the flip flop state Z becomes 0 with next clock pulse.
- If  $AB = 11$ , the change of state occurs with the clock pulse.


Write the truth-table for the A-B flip flop.

Let  $Q$  be the present state of the circuit and  $Q^*$  be the next state. The truth table ~~will be~~ for the flip flop will be.

X	Y	$Q^*$
0	0	$\overline{Q}$
0	1	1
1	0	0
1	1	$Q$

Assignment 7

 3. Find the mode of a counter and also find that it is up counter or down counter.




clock is not neglected  $\Rightarrow$  up counter

$\rightarrow \bar{Q}_0 = 1, Q_1 = 1 < \bar{Q}_2 = 1$ , then the counter again reaches to 111 or initial value.

$\rightarrow$  Therefore, the last value of the counter will be 010 or 2.

 4. It is desired to design a binary ripple counter of the type shown in fig. that is capable of counting the number of items passing on a conveyor belt. Each time an item passes at given point, a pulse is generated that can be used as clock signal. If the maximum number of items to be counted is 6000, determine the no. of flipflops required.



From the figure, it can be seen (also given in question) that it is a asynchronous counter. Asynchronous counters (binary) can store  $2^n$  number if there are  $n$  - flip-flops present. (0 to  $2^n - 1$ )

We need to count ~~the~~ a maximum number of 6000 items.

$$\therefore 2^n \geq 6000$$

$$\therefore 2^n - 1 \geq 6000$$


$$2^n \geq 6000$$



the smallest integer that satisfies this condition is 13. Hence, a total of 13 flip-flops will be required to design a counter the given counter.

### Assignment 8

 5. A 4-bit shift register configured for right-shift operation i.e.  $D_{in} \rightarrow A, A \rightarrow B, B \rightarrow C, C \rightarrow D$ , is shown. If the present state of the register is  $ABCD = 1101$ , how many number of clock cycles are required to reach the state = 1111?




Since, A is XOR of previously stored A and D. New inputs to B, C, D are shown below. as a table for each pulse of clock.

Let clock pulse 0 denotes the present state i.e. 1101,

clk	A (A ⊕ D)	B	C	D	
0	1	1	0	1	← present state
1	0	1	1	0	
2	0	0	1	1	
3	1	0	0	1	
4	0	1	0	0	
5	0	0	1	0	
6	0	0	0	1	
7	1	0	0	0	
8	1	1	0	0	
9	1	1	1	0	
10	1	1	1	1	required state

Hence, 10 clock cycles will be required to reach the state 1111.

 Q.6 - Assume that all the digital gates in the circuit shown in figure are ideal, the resistor  $R = 10\text{K}\Omega$  and the supply voltage is 5V. The D flip-flops  $D_1, D_2, D_3, D_4$  and  $D_5$  are initialized with logic values 0, 1, 1 and 0, respectively. The clock has a 30% duty cycle.



Find out the average power dissipated (in mW) in the resistor R?

Let us first analyze the circuit and try to configure the output waveform.


the output ~~is~~  $Y = D_3 + D_5$ .

→ output of  $D_1$  is input to  $D_2$ , output of  $D_2$  is input to  $D_3$  and so on. The output of  $D_5$  is input to  $D_1$  also. Let us try to find the time period of output waveform.

	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$Y = D_3 + D_5$
Present state	0	1	0	1	0	0
1→	0	0	1	0	1	1
2→	1	0	0	1	0	0
3→	0	1	0	0	1	1
4→	1	0	1	0	0	1
5→	0	1	0	1	0	0

In the 5<sup>th</sup> clock pulse, the flip flops reached their initial state; and hence, the output will repeat for each 5 clock pulses.

The output waveform is:

 

∴ average power dissipated will be:

$$P_{avg} = \frac{V^2}{R} \times \text{duty cycle}$$

$$= \frac{V^2}{R} \times \frac{T_{high}}{T_{total}}$$

$$= \frac{V^2}{R} \times \frac{3}{5}$$


$$P_{avg} = \frac{5 \times 5}{10K} \times \frac{3}{5}$$

$$P_{avg} = 1.5 \text{ mW}$$

Hence, the average power dissipated will be 1.5 mW.

### Assignment-9

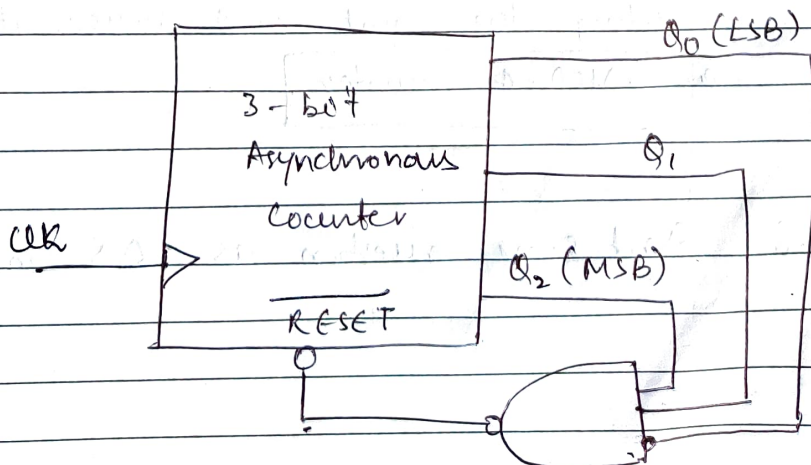Q.7. For the circuit in the figure, the delay of bubbled NAND gate is 2 ns. and that of the counter is assumed to be zero.





If the clock (clk) frequency is 1 GHz, then the counter behaves as a — ?

Let us try analyzing the counter circuit table.

clk	current states			o/p of NAND	next states		
	$Q_2$	$Q_1$	$Q_0$		$Q_2^k$	$Q_1^k$	$Q_0^k$
0	0	0	0	1	0	0	0
1	0	0	1	1	0	1	0
2	0	1	0	1	0	1	1
3	0	1	1	1	1	0	0
4	1	0	0	1	1	0	1
5	1	0	1	1	1	1	0
6	1	1	0	0	0	0	0

As in 6<sup>th</sup> cycle, preset input received 0 as input. Hence, it resets the counter.

When, there was no propagation delay, then the counter was acting as MOD-6 counter. But since, there is a propagation delay of 2ns in NAND gate and frequency of clock is 1 GHz, the NAND gate will allow 2 extra clock pulses before resetting the count and hence, it is a MOD-8 counter.

Q.8. Exact same question as Q.5 in Assignment 8.

# Assignment 10

## Q.9

### *Code of Design*

```
design.vhd
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3
4 entity full_adder is
5 port(
6     A: in std_logic;
7     R: in std_logic;
8     C: in std_logic;
9     s: out std_logic;
10    co: out std_logic
11 );
12 end full_adder;
13
14 architecture rtl of full_adder is
15 begin
16     process(A, R, C) is
17     begin
18         s <= A xor (R xor C);
19         co <= (A and R) or (C and (A xor R));
20     end process;
21 end rtl;
```


### *Code of Testbench*

```
testbench.vhd
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3
4 entity testbench is
5 -- empty
6 end testbench;
7
8 architecture tb of testbench is
9
10 -- DUT component
11 component full_adder is
12 port(
13     A: in std_logic;
14     R: in std_logic;
15     C: in std_logic;
16     s: out std_logic;
17     co: out std_logic);
18 end component;
19
20 signal a_in, b_in, c_in, s_out, c_out: std_logic;
21
22 begin
23
24 -- Connect DUT
25 DUT: full_adder port map(a_in, b_in, c_in, s_out, c_out);
26
27 process
28 begin
29     a_in <= '0';
30     b_in <= '0';
31     c_in <= '0';
32     wait for 1 ns;
33
34     a_in <= '0';
35     b_in <= '1';
36     c_in <= '0';
37     wait for 1 ns;
38
39     a_in <= '1';
40     b_in <= '0';
41     c_in <= '0';
42     wait for 1 ns;
43
44 ..
```

# Assignment 10

```
44
45     a_in <= '1';
46     b_in <= '1';
47     c_in <= '0';
48     wait for 1 ns;
49
50     a_in <= '0';
51     b_in <= '0';
52     c_in <= '1';
53     wait for 1 ns;
54
55     a_in <= '0';
56     b_in <= '1';
57     c_in <= '1';
58     wait for 1 ns;
59
60     a_in <= '1';
61     b_in <= '0';
62     c_in <= '1';
63     wait for 1 ns;
64
65     a_in <= '1';
66     b_in <= '1';
67     c_in <= '1';
68     wait for 1 ns;
69
70     -- Clear inputs
71     a_in <= '0';
72     b_in <= '0';
73     c_in <= '0';
74
75     wait;
76 end process;
77 end tb;
```

## Output

 

Note: To revert to EPWave opening in a new browser window, set that option in your user page.

# Assignment 10

## Q.10

### Code of Design

design.vhd



```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3
4 entity circuit is
5 port(
6     A: in std_logic;
7     R: in std_logic;
8     o: out std_logic
9 );
10 end circuit;
11
12 architecture rtl of circuit is
13 begin
14     process(A, R, o) is
15     begin
16         o <= (A or R) and (not (A and R));
17     end process;
18 end rtl;
```

### Code of testbench

testbench.vhd



```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 entity testbench is
4     -- empty
5 end testbench;
6
7 architecture tb of testbench is
8
9     -- DUT component
10    component circuit is
11    port(
12        A: in std_logic;
13        R: in std_logic;
14        o: out std_logic);
15    end component;
16
17    signal a_in, b_in, c_out: std_logic;
18
19    begin
20
21        -- Connect DUT
22        DUT: circuit port map(a_in, b_in, c_out);
23
24        process
25        begin
26            a_in <= '0';
27            b_in <= '0';
28            wait for 1 ns;
29
30            a_in <= '0';
31            b_in <= '1';
32            wait for 1 ns;
33
34            a_in <= '1';
35            b_in <= '0';
36            wait for 1 ns;
37
38            a_in <= '1';
39            b_in <= '1';
40            wait for 1 ns;
41
42            -- Clear inputs
43            a_in <= '0';
44            b_in <= '0';
```



# Assignment 10

```
45  
46     wait;  
47     end process;  
48 end tb;
```

## *Output*

