 


# EC201 : Assignment 3

## Problems with simulations

1. Draw two truth tables illustrating the outputs of a half-adder, one table for the sum output and the other for the output and Design in Logisim

Solution:




a	b	Sum	Carry
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

a	b	Carry
0	0	0
0	1	1
1	0	1
1	1	0

a	b	Sum
0	0	0
0	1	0
1	0	0
1	1	1

 2. Fill in the truth table at right for the following circuit. Ignore rows not included in the table, then design in Logisim.




a	b	c	x	y
0	1	1		
1	0	1		
1	1	0		
1	1	1		

Name: Archit Agrawal  
Student ID: 202052307

# EC201 : Assignment 3

Solution:

 

a	b	c	x	y
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	0

Problems Without Simulations

Name: Archit Agrawal  
Student ID: 202052307

### EC Assignment 3

#### Problems without Simulations

3. Two 1's with no carry-in are added using a full adder. What are the outputs?

given  $A = 1$ ,  $B = 1$ ,  $C_{in} = 0$

$$\begin{aligned}\therefore S &= A \oplus B \oplus C_{in} \\ &= 1 \oplus 1 \oplus 0 \\ S &= 0\end{aligned}$$

$$\begin{aligned}C_{out} &= AB + C_{in}(A \oplus B) \\ &= 1 + 0(1 \oplus 1) \\ C_{out} &= 1\end{aligned}$$

$\therefore$  Outputs are  $S = 0$  and  $C_{out} = 1$

4. Two 1's with a carry-in of 1 are added using a full adder. What are the outputs?

$A = 1$ ,  $B = 1$ ,  $C_{in} = 1$


$$\begin{aligned}S &= A \oplus B \oplus C_{in} \\ &= 1 \oplus 1 \oplus 1 \\ S &= 1\end{aligned}$$

$$\begin{aligned}C_{out} &= A \cdot B + C_{in}(A \oplus B) \\ &= 1 + 1(1 \oplus 1) \\ C_{out} &= 1\end{aligned}$$


$\therefore$  Outputs are:  $S = 1$  and  $Count = 1$

5. A half adder is implemented with XOR and AND gates. A full adder is implemented with two half adders and one OR gate. The propagation delay of an XOR gate is twice that of an AND/OR gate. The propagation delay of AND/OR gate is  $1.2 \mu s$ . A 4-bit ripple carry binary adder is implemented by using full adders. Find out total propagation time of this 4-bit binary adder in  $\mu s$ .

### Half Adder

 

### Full Adder

 

- from A or B to  $C_{out}$ : 4 gate delays ( $XOR \rightarrow AND \rightarrow OR$ )
- from A ~~or~~ B to S: 4 gate delays ( $XOR \rightarrow XOR$ )
- from  $C_{in}$  to  $C_{out}$ : 2 gate delays ( $AND \rightarrow OR$ )
- from  $C_{in}$  to S: 2 gate delay ( $XOR$ )

because  $C_{out}$  of one stage is  $C_{in}$  for the next input:

- 4-gate delays from generating first carry signal (A or B to  $C_{out}$ ).
- 2-gate delays per intermediate stage ( $C_i$  to  $C_{i+1}$ )
- 2-gate delays at last stage to produce both the sum and carry-out outputs ( $C_{n-1}$  to  $C_n$  and  $S_{n-1}$ )

For an n-bit full adder, total propagation delay

$t_p = 4 + 2(n-2) + 2$ $t_p = 2n + 2$
---------------------------------------

for 1-bit full adder,  $t_p = 4$  ~~ms~~




∴ total delay of a 1-bit full adder is

$$t = 4 \times 12$$

$$= 4.8 \mu s$$

Diagram of 4-bit ripple adder using full adder.

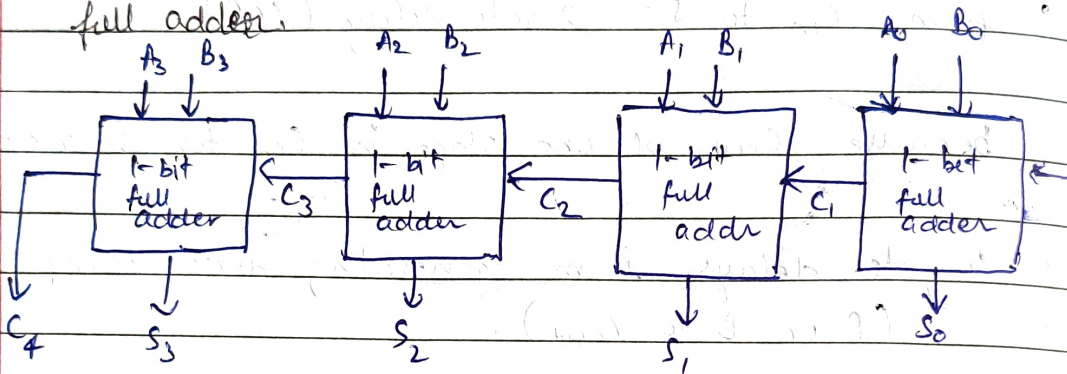

delay of 4 full adders  $= 4 \times 4.8 \mu s$

$= 19.2 \mu s$