

EC160: Experiment 9 RC Differentiator and Integrator

- Objective :-
- (i) to understand charging and discharging of RC circuit
 - (ii) to understand square wave response of RC circuit
 - (iii) to understand RC circuit as integrator and differentiator


Theory :-

Charging of a capacitor

When a capacitor is connected to a battery, positive charge appears on one plate and negative charge on other. The potential difference between the plates ultimately becomes equal to emf of the battery.

The whole process takes some time and during this time there is an electric current through the connecting wires and the battery.

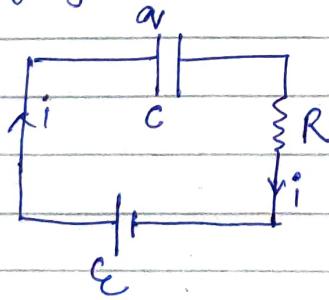A charging circuit of a capacitor is shown



Suppose a capacitor of capacitance C , a resistor R and a battery of emf E is connected as shown at $t=0$.

Suppose the charge on the capacitor and the current in the circuit are q and i respectively at time t .

∴ the potential drop across the capacitor is $\frac{qV}{C}$

and across the resistor is iR .

also, charge deposited on capacitor plate in time dt is

$$dq = i dt$$

Using Kirchoff's Loop law,

$$\frac{qV}{C} + Ri - \epsilon = 0$$

$$R \frac{dq}{dt} = \epsilon - \frac{qV}{C}$$

$$\frac{dq}{\epsilon C - q} = \frac{1}{RC} dt$$

Integrating using proper limits

$$\int_0^q \frac{dq}{\epsilon C - q} = \int_0^t \frac{1}{CR} dt$$

After solving,

$$q_V = \epsilon C (1 - e^{-t/RC})$$


This gives charge on the capacitor at time t .

Also, the current i in the circuit at time t is,

$$i = \frac{dq}{dt} = \frac{\epsilon}{R} e^{-t/RC}$$

Discharging of capacitor

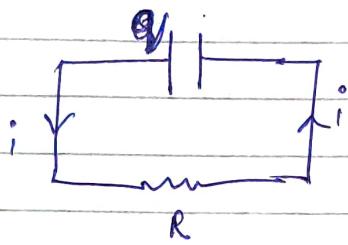If the plates of a charged capacitor are connected through a conducting wire, the capacitor gets discharged. Again there is a flow of charge through the wires and hence there is a current. Suppose a capacitor of capacitance C has a charge Q . At $t=0$, the plates are connected through a resistance R as shown.



Let the charge on capacitor be q and current in the circuit be i at a time t .

Using Kirchoff's loop law

$$\frac{qV}{C} - Ri = 0$$

Here $i = -\frac{dq}{dt}$ because the charge q decreases as time passes,

Thus,

$$R \frac{dq}{dt} = -\frac{qV}{C}$$

$$\frac{dq}{q} = -\frac{1}{CR} dt$$
$$\int \frac{dq}{q} = \int_0^t -\frac{1}{CR} dt$$

$$\ln \frac{Q}{Q_0} = -\frac{t}{CR}$$


$$Q = Q_0 e^{-t/CR}$$

This gives the value of charge on capacitor at instant t :

$$i = -\frac{dQ}{dt} = \frac{Q_0}{CR} e^{-t/CR}$$

This gives the value of current in the circuit at any instant t :

RC Integrator circuit

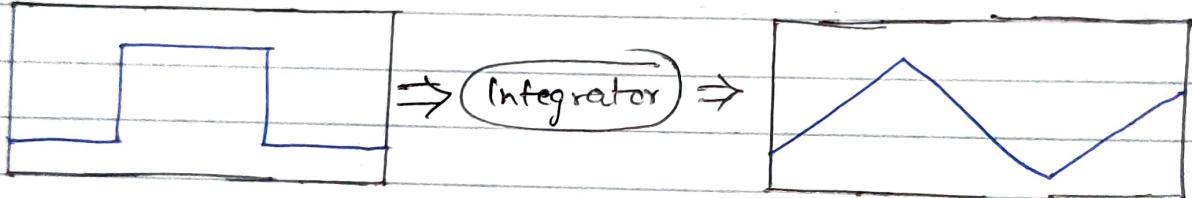


An integrator is a circuit that converts or 'integrates' a square wave input signal into triangular waveform output:

for a passive RC integrator circuit the input is connected to a resistance while the output voltage is taken from across a capacitor.

The capacitor charges up when the input is high and discharges when the input is low.

If the signal is a sine wave, an RC integrator will simply act as a simple low pass filter (LPF) above its cut-off point with the cut-off or corner frequency corresponding to the RC

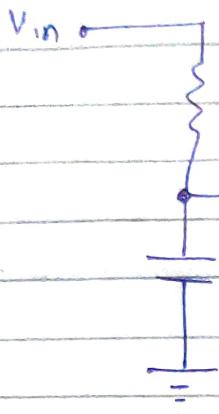
time constant (τ), thus reducing its output above the cut-off frequency point.



$$i_{C(t)} = C \frac{dV_C(t)}{dt}$$

$$V_{out} = V_C$$

RC Differentiator Circuit:

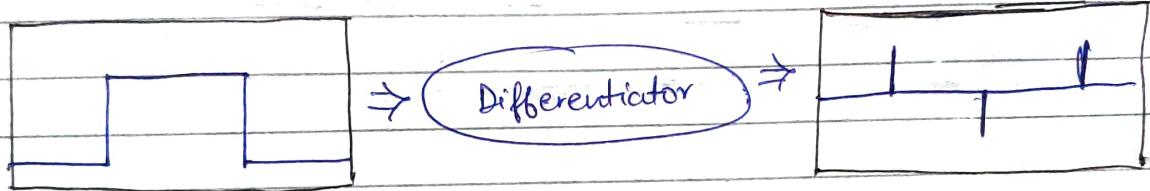


The differentiator circuit converts a square wave input signal into high frequency spikes as its output.

For a passive RC differentiator circuit, the input is connected to a capacitor while the output voltage is taken across a resistance being the exact opposite to RC integrator circuit.

A passive RC differentiator circuit is nothing more than a capacitance in series with a resistance, that is a frequency dependent device which has reactance in series with a fixed resistance.

At low input frequencies, the reactance X_C is high blocking any D.C voltage or slowly varying inputs. While at high frequencies, the capacitors reactance is low allowing rapidly varying pulses.

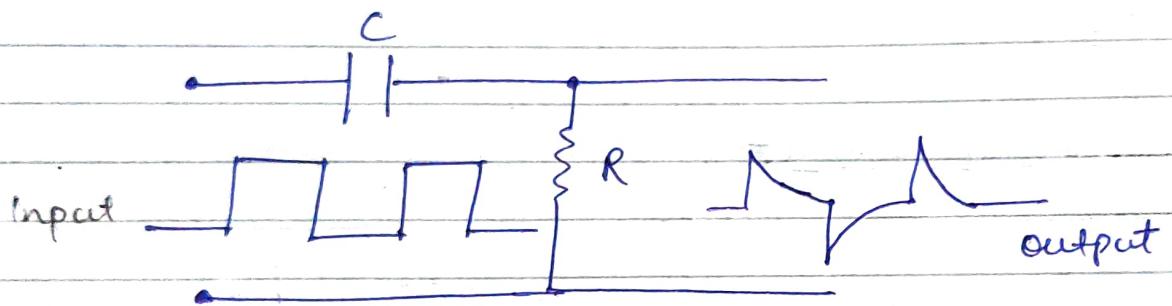An RC differentiator will simply act as a simple High Pass Filter (HPF) with a cut-off or corner frequency corresponding to RC time constant (T).



Procedure for the experiment:-

For RC Integrator and Differentiator Circuit:-

Step 1: Set Resistance $R = 10\text{ k}\Omega$ and capacitance $C = 0.1\text{ }\mu\text{F}$.

Step 2: Click on 'ON' button to start the experiment.

Step 3: Click on 'square wave' button to generate the input waveform.

Step 4: Click on 'oscilloscope' button to get the output waveform.

Step 5: Vary the amplitude, frequency and volt/div using controllers.

Step 6: Click on 'Dual' button to observe both the waveforms.

channel 1 shows input waveform and channel 2 shows output waveform.

Step 7: Observe the waveforms for Integrator and Differentiator circuits.

Simulation Results




An MoE Govt of India Initiative

RC Integrator

INSTRUCTION


OSCILLOSCOPE

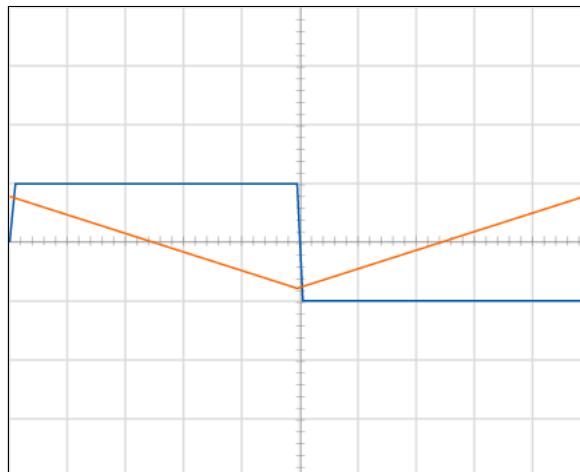


Channel 1 Channel 2 Ground Dual



CIRCUIT

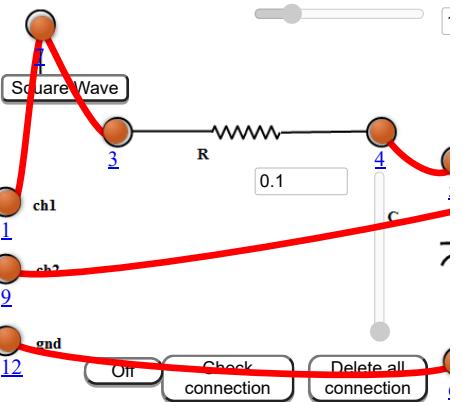

CONTROLS

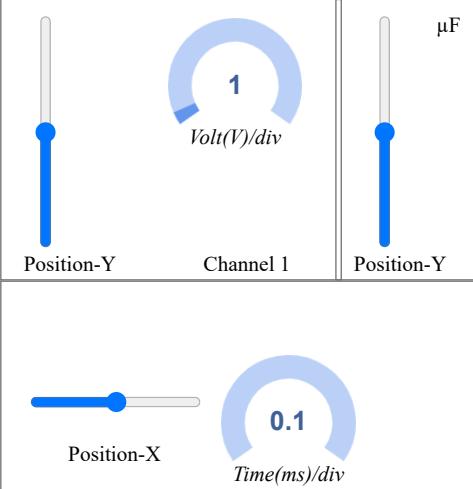




An MoE Govt of India Initiative


RC Integrator

INSTRUCTION


OSCILLOSCOPE

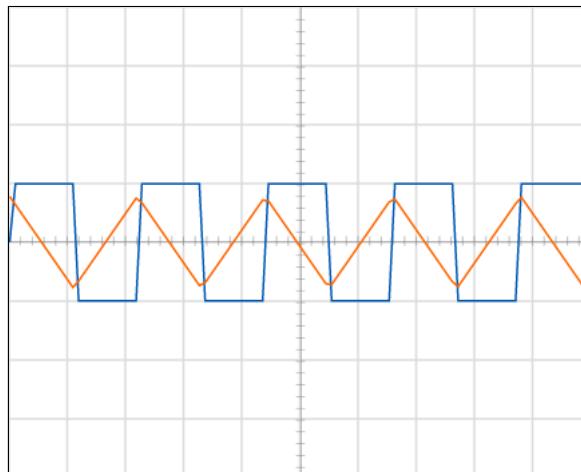

CIRCUIT

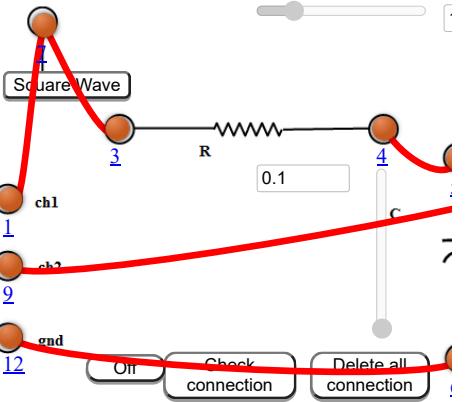

CONTROLS

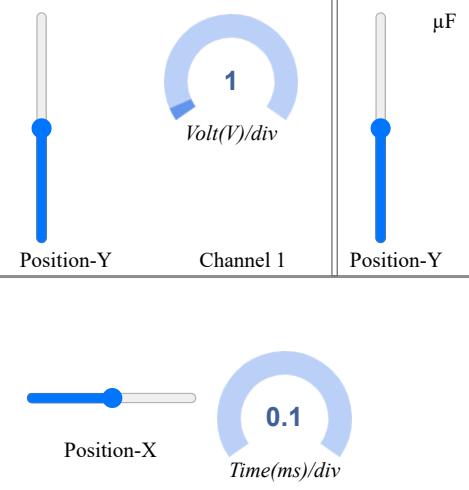




An MoE Govt of India Initiative


RC Integrator

INSTRUCTION


OSCILLOSCOPE

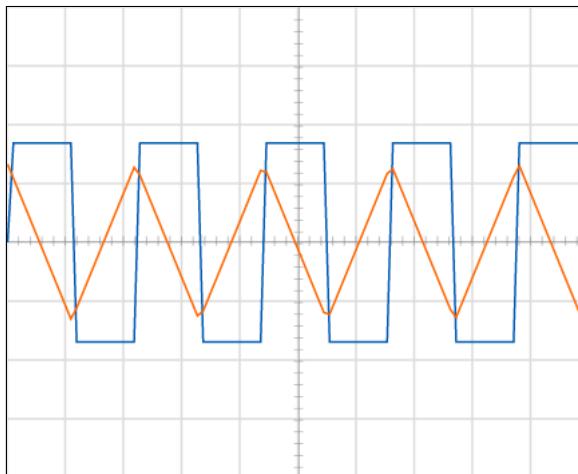

CIRCUIT

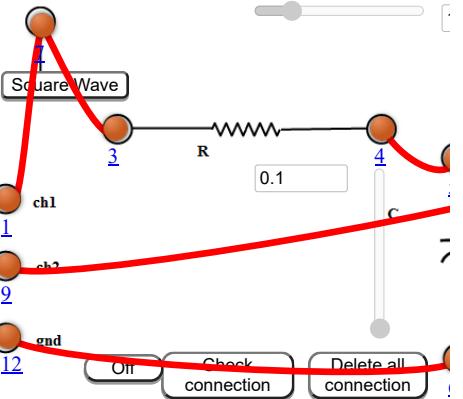

CONTROLS

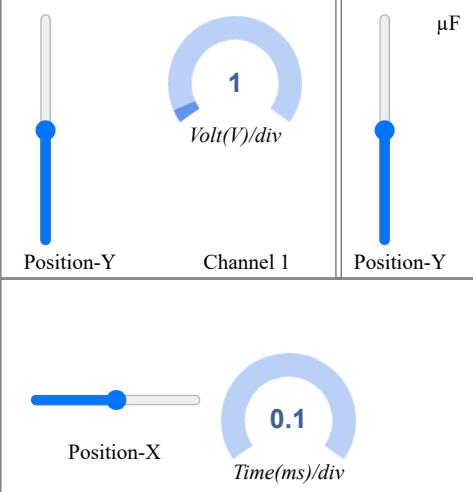




An MoE Govt of India Initiative

RC Integrator

INSTRUCTION

OSCILLOSCOPE

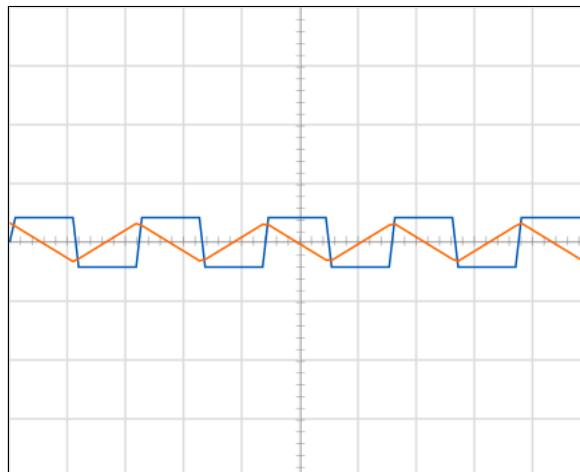


Channel 1 Channel 2 Ground Dual


4500
Frequency(Hz)

2
Amplitude(Volt)

CIRCUIT

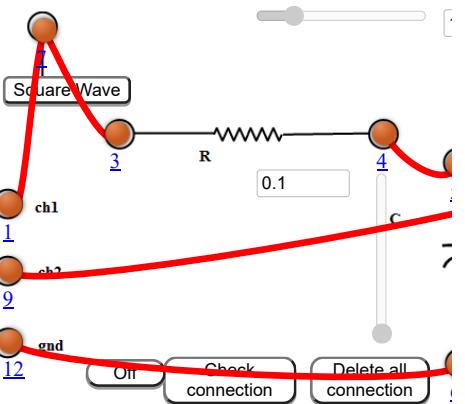

CONTROLS

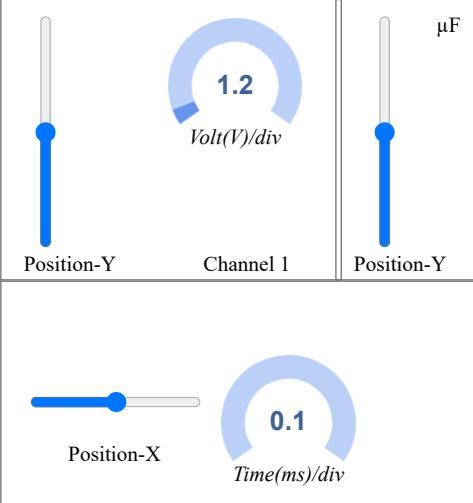




RC Differentiator

INSTRUCTION

OSCILLOSCOPE

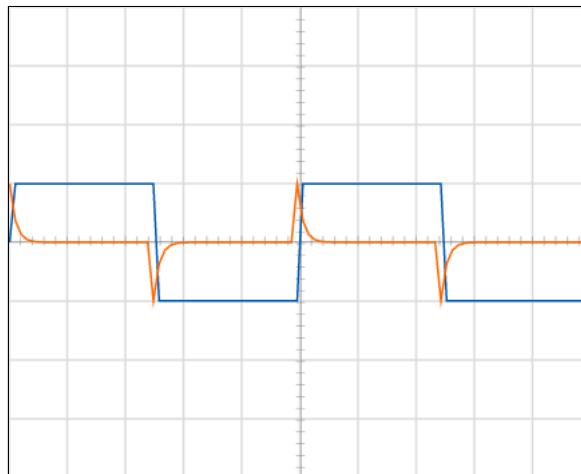


Channel 1 Channel 2 Ground Dual


2000
Frequency(Hz)

1
Amplitude(Volt)

CIRCUIT

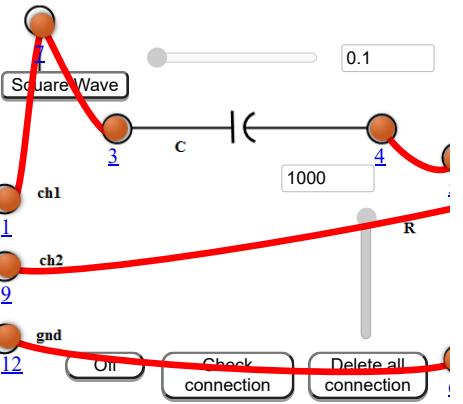

CONTROLS

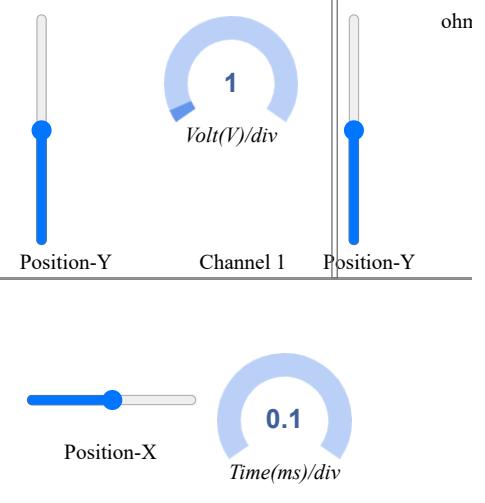


Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)



RC Differentiator

INSTRUCTION


OSCILLOSCOPE

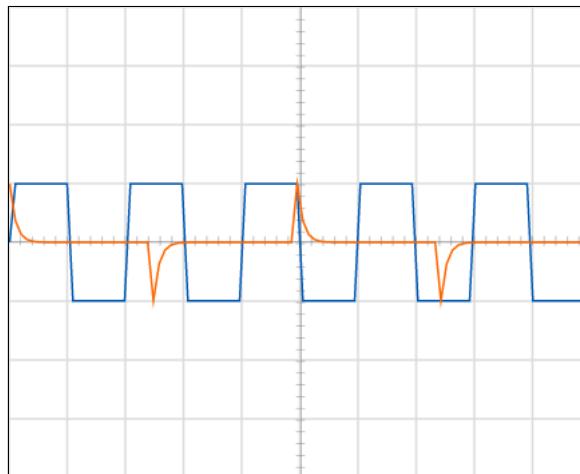


Channel 1 Channel 2 Ground Dual



CIRCUIT

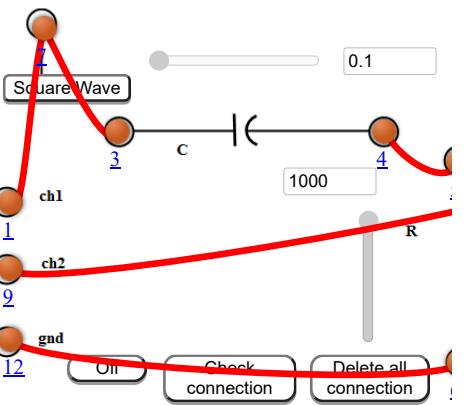

CONTROLS

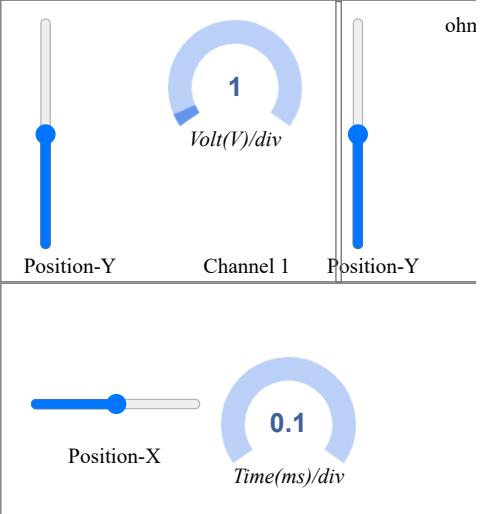


Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)



RC Differentiator

INSTRUCTION

OSCILLOSCOPE

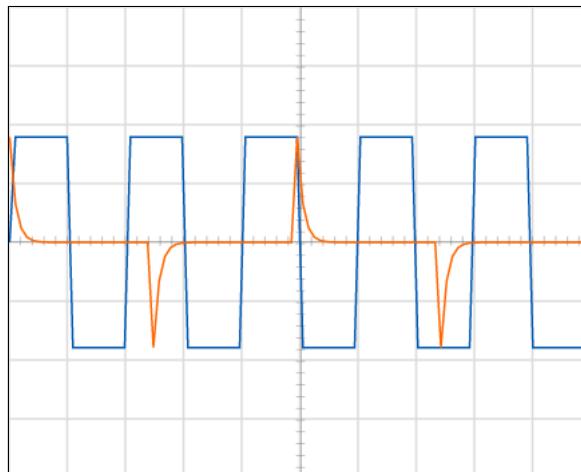


Channel 1 Channel 2 Ground Dual


5000
Frequency(Hz)

2
Amplitude(Volt)

CIRCUIT

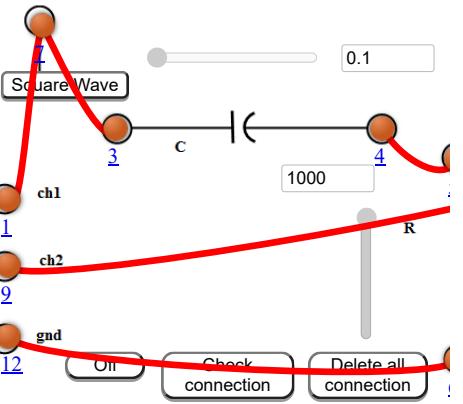

CONTROLS

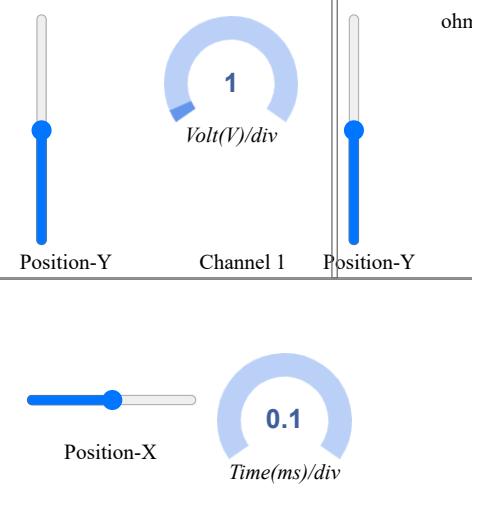


Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)



RC Differentiator

INSTRUCTION

OSCILLOSCOPE

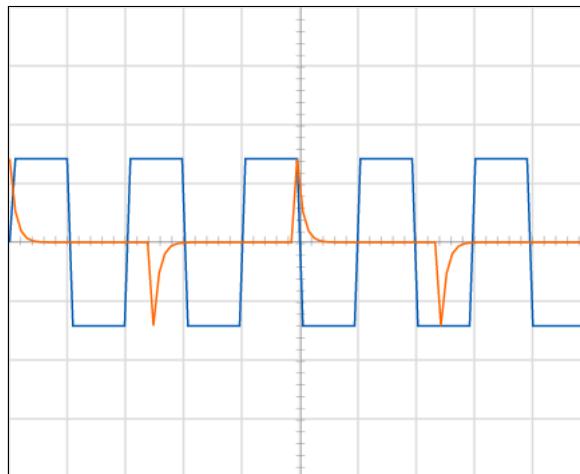


Channel 1 Channel 2 Ground Dual


5000
Frequency(Hz)

2
Amplitude(Volt)

CIRCUIT

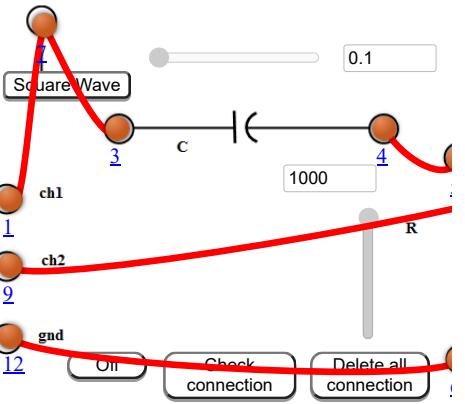

CONTROLS

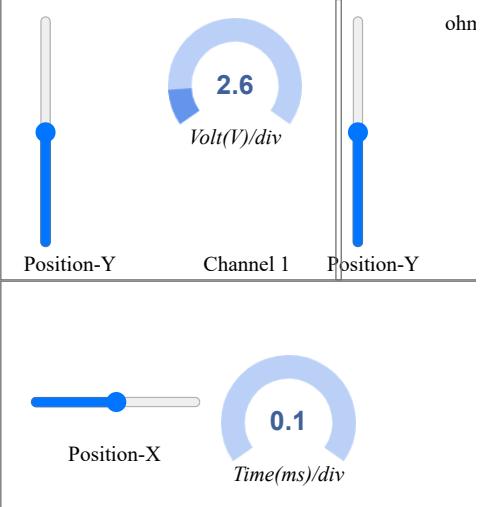

Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)

Name: Archit Agrawal
Student ID: 202052307

Page 8

Conclusion :- Performing the experiment, we can draw following conclusions -

- (i) A RC integrator circuit converts a square wave into a triangular wave as output.
- (ii) A RC differentiator circuit converts a square wave into high frequency spikes as output.
- (iii) The procedure that how an RC integrator and RC differentiator circuit works.

Quiz Performance

BASIC ELECTRONICS VIRTUAL LABORATORY (../INDEX.HTML)

Home (../index.html) > Basic Electronics Lab (./index.html) > RC Differentiator and Integrator (index.html)

RC Differentiator and Integrator


[THEORY \(#\)](#)

[PROCEDURE \(#\)](#)

[OSCILLOSCOPE](#)

[SIMULATION \(#\)](#)

[QUIZ \(#\)](#)

[REFERENCES \(#\)](#)
[TUTORIAL \(#\)](#)

Quiz

Test Your Knowledge!!

- ✓ 1. Which statement about a series RC circuit is true?

voltage drop



The capacitor's voltage drop is in phase with the resistor's



The current leads the source voltage




The current lags the source voltage



The resistor voltage lags the current

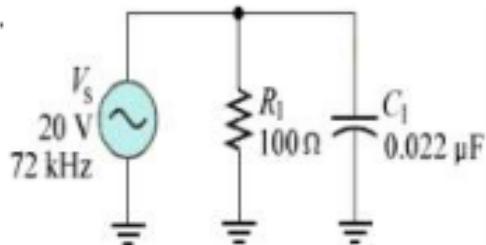- ✓ 2. If the frequency increases in the given circuit, how would the total current change?



total current would change



The total current would increase



The total current would decrease



The total current would remain the same



More information is needed in order to predict how the

- ✓ 3. What is the effect of increasing the resistance in a series RC circuit?

There will be no effect at all



The current will increase



The input voltage will increase



The phase shift will decrease



Copyright © 2011 Indian Institute
of Technology Kharagpur,
[Licensing Terms](#)
([..//license/index.html](#))