

Name: Archit Agrawal
Student ID: 202052307



Date:

Page: 1


EE100 Assignment 1

1 Problem from Section 16-3

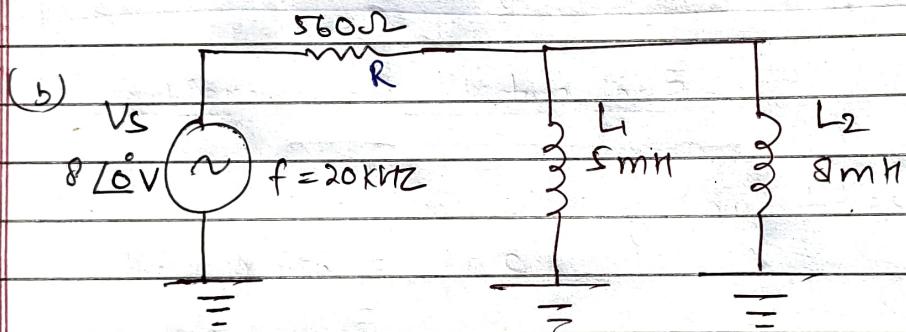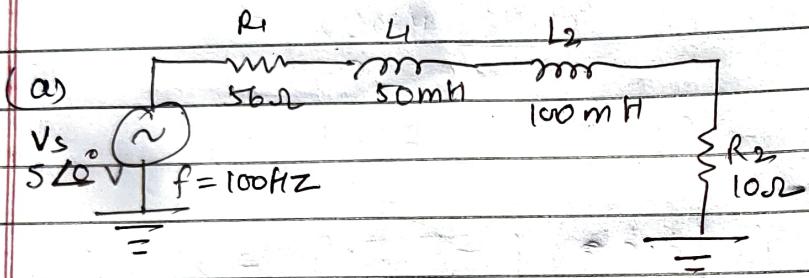1. Express the total current in the following circuits in rectangular and polar form



(a) The circuit can be redrawn as

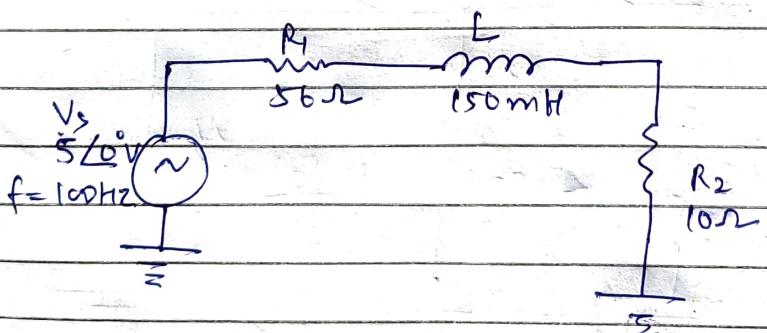

$$L = L_1 + L_2 = 150 \text{ mH}$$

$$\omega L = 2\pi f L = 2\pi \times 100 \times 150 \text{ mH} \\ = 94.2 \Omega$$

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 2

$$\therefore Z = (56 + 10) + j(94.2) \Omega$$

$$Z = 115.02 \angle 54.98^\circ \Omega$$

$$\therefore \text{total current } \bar{I} = \frac{V_s}{Z}$$


$$\bar{I} = \frac{5 \angle 0^\circ}{115.02 \angle 54.98^\circ} A$$

$$\bar{I} = 43.47 \angle -54.98^\circ \text{ mA}$$

$$\therefore T = 24.946 - j(35.6) \text{ mA}$$

Answer

(b) The circuit can be redrawn as

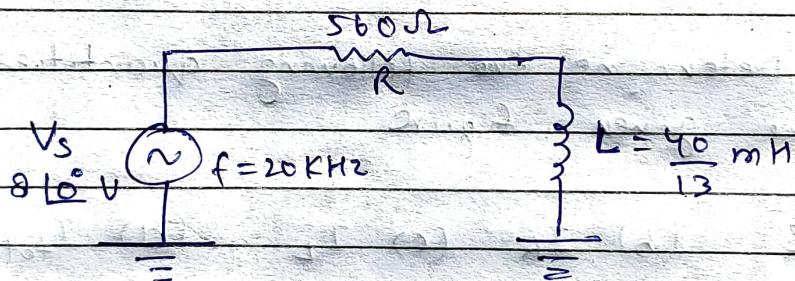

where, $L = L_1 \parallel L_2$

$$L = \frac{L_1 \times L_2}{L_1 + L_2} = \frac{(5 \text{ mH}) \times (8 \text{ mH})}{13 \text{ mH}}$$

$$L = \frac{40 \text{ mH}}{13}$$

$$\therefore X_L = 2\pi f X_L = 2 \times \pi \times (20 \text{ k}) \left(\frac{40 \text{ m}}{13} \right)$$

$$X_L = 386.46 \Omega$$

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 3

$$\therefore z = 560 + j386.46 \Omega$$

$$z = 680.41 \angle 34.19^\circ \Omega$$

$$\therefore \text{total current } I_s = \frac{V_s}{z} = \frac{8}{680.41 \angle 34.19^\circ} = 11.76 \angle -34.19^\circ \text{ mA}$$

$$I_s = 11.76 \angle -34.19^\circ \text{ mA}$$

$$\therefore I_s = 9.727 - j(6.61) \text{ mA}$$


Answer

1 Problem from section 16-5

25. Determine the following quantities in the given figure

(a) Z (b) I_R (c) I_L (d) I_{tot}

(e) θ

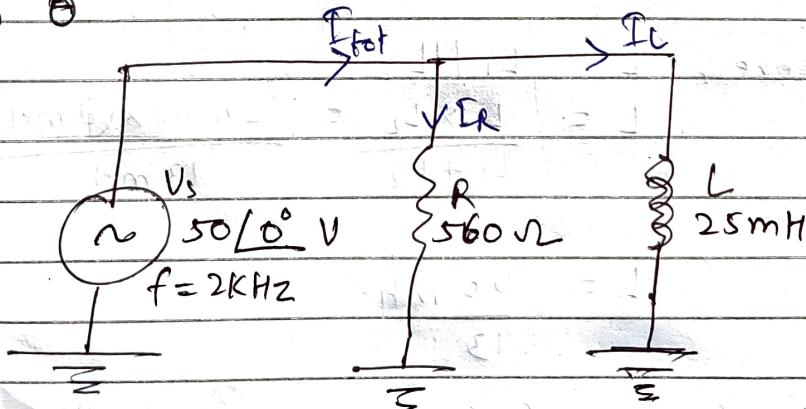

$$(a) X_L = \omega L = 2\pi(2\text{K})(25\text{m}) \\ = 314 \Omega$$

Name: Archit Agrawal
Student ID: 202052507

Date:

Page:

4

$$\therefore Z_R = 560 \Omega \Rightarrow \bar{Z}_R = 560 \angle 0^\circ$$

$$Z_{XL} = j(314 \Omega) \Rightarrow \bar{Z}_{XL} = 314 \angle 90^\circ$$

$$\text{and } Z = Z_R \parallel Z_{XL}$$

$$Z = \frac{Z_R \cdot Z_{XL}}{Z_R + Z_{XL}}$$

$$\bar{Z} = \frac{560 \angle 0^\circ \times 314 \angle 90^\circ}{560 + j314} \Omega$$

$$\bar{Z} = \frac{175840 \angle 90^\circ}{642.02 \angle 29.279} \Omega$$

$$\bar{Z} = 273.80 \angle 60.721^\circ \Omega$$

$$\therefore Z = 133.945 + j(238.89) \Omega$$

Answer

$$(b) \quad \bar{I}_R = \frac{\bar{V}_S}{\bar{Z}_R}$$

$$= \frac{50 \angle 0^\circ}{560 \angle 0^\circ}$$

$$\bar{I}_R = 89.286 \angle 0^\circ \text{ mA}$$

$$\therefore I_R = 89.286 \text{ mA} + j(0)$$

Answer

$$(c) \quad \bar{I}_L = \frac{\bar{V}_S}{\bar{Z}_{XL}} = \frac{50 \angle 0^\circ}{314 \angle 90^\circ}$$

$$\bar{I}_L = 159.236 \angle -90^\circ \text{ mA}$$

$$I_L = 0 - j(159.236 \text{ mA})$$

Answer

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 5

(d) $I_{\text{tot}} = I_R + I_L$

$$I_{\text{tot}} = 89.286 \text{ mA} - j(159.236 \text{ mA})$$

$$\bar{I}_{\text{tot}} = 182.56^{\circ} \text{ } |-60.72^{\circ} \text{ mA}$$

Answer

(e) $\theta = \phi_V - \phi_{I_{\text{tot}}}$

$$= 0 - (-60.72^{\circ})$$


$$\theta = 60.72^{\circ}$$

Answer

3B/1 Problem from Section 16-6:

33. For the circuit determine the following

(a) I_{tot} (b) V_L (c) V_{AB}

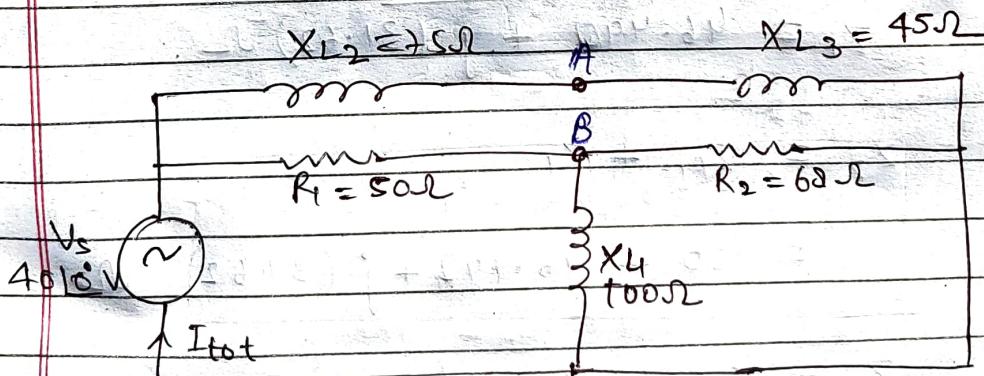


Name: Archit Agrawal
Student ID: 202052307

Date:

Page:

6

The circuit can be redrawn as

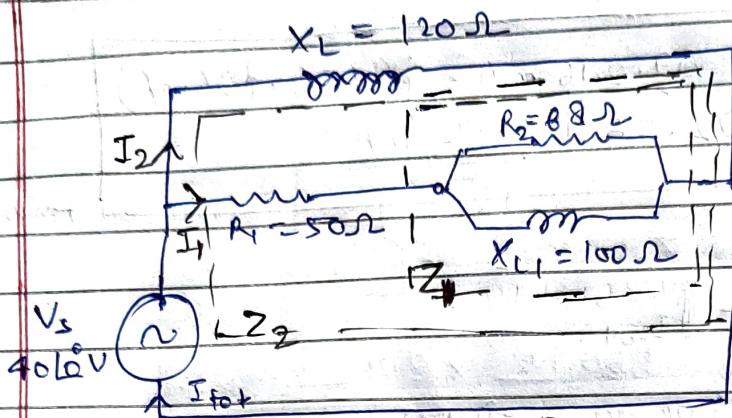

$$Z_1 = R_2 \parallel Z_{X_4}$$

$$= \frac{68 \angle 0^\circ \times 100 \angle 90^\circ}{68 + j(100)}$$

$$\bar{Z}_1 = \frac{6800 \angle 90^\circ \Omega}{120.93 \angle 55.785}$$

$$\bar{Z}_1 = 56.23 \angle 34.215^\circ \Omega$$

$$Z_1 = 46.49 \Omega + j(31.62) \Omega$$

$$Z_2 = Z_{R_1} + Z_1$$

$$= 50 + 46.49 \Omega + j(31.62) \Omega$$

$$Z_2 = 96.49 \Omega + j(31.62) \Omega$$

$$\bar{Z}_2 = 101.569 \angle 18.194^\circ \Omega$$

$$Z = Z_{X_L} \parallel Z_2$$

$$Z = \frac{Z_{X_L} \cdot Z_2}{Z_{X_L} + Z_2}$$

Name: Archit Agrawal

Student ID: 2020S2307

Date:

Page:

7

$$\bar{Z} = \frac{120 [90^\circ] \times 101.564 [18.149^\circ]}{j(120) + \cancel{101.564} 96.498 + j(31.62)}$$

$$\bar{Z} = \frac{12187.68 [108.149^\circ]}{179.72 [57.52^\circ]}$$

$$\bar{Z} = 67.815 [50.624^\circ] \Omega$$

Ans

$$\therefore \bar{I}_{\text{tot}} = \frac{\bar{V}_s}{\bar{Z}}$$

$$\bar{I}_{\text{tot}} = \frac{40 [0^\circ]}{67.815 [50.624^\circ]}$$

$$\bar{I}_{\text{tot}} = 589.84 [-50.624^\circ] \text{ mA}$$

$$I_{\text{tot}} = 374.2 - j(455.95) \text{ mA}$$

Answer

$$(b) \quad \bar{I}_1 = \frac{\bar{I}_{\text{tot}} \cdot Z_{XL}}{Z_{XL} + Z_2}$$

$$\bar{I}_1 = \frac{589.84 [-50.624^\circ] \times 120 [90^\circ] (\text{mA} \cdot \Omega)}{j(120) + 96.498 + j(31.62)}$$

$$= \frac{589.84 \times 120 [39.376^\circ]}{179.72 [57.52^\circ]} \text{ mA}$$

$$\bar{I}_1 = 393.84 [-18.344^\circ] \text{ mA}$$

Q Q

$$I_1 = 373.82 - j(123.95) \text{ mA}$$

Name: Archit Agrawal
Student ID: 202052307

Date:

Page: 8

$$\bar{V}_L \neq \bar{V}_S + \bar{V}_R$$

$$V_L = V_S - V_R$$

$$\bar{V}_R = \bar{I}_1 \times Z_R$$

$$= 393.84 | -18.344^\circ \times 50 | 0^\circ \text{ mV}$$

$$\bar{V}_R = 19.69 | -18.344^\circ \text{ V}$$

$$V_R = 19.69 - j(6.197) \text{ V}$$

$$\therefore V_L = 40 - (19.69 - j6.197)$$

$$V_L = 21.31 + j6.197 \text{ V}$$

Answer

$$(c) V_A = V_S - V_{Z_{L_2}} = V_S - I_2 Z_{X_{L_2}}$$

$$\text{Now, } I_2 = I_{\text{tot}} - I_1$$

$$I_2 = 374.2 - j(455.95) - (373.82 - j(123.95))$$

$$I_2 = 0.38 - j332 \text{ mA}$$

$$\bar{I}_2 = 332 | -89.93^\circ \text{ mA}$$

$$\therefore V_{Z_{L_2}} = 332 | -89.93^\circ \times 75 | 90^\circ \text{ mV}$$

$$V_{Z_{L_2}} = 24.9 | 0.07^\circ \text{ V}$$

$$V_{Z_{L_2}} \approx 24.9 \text{ V}$$

Name: Archit Agrawal
Student ID: 202052307



$$\therefore V_A = 40 - 24.9V \\ = 15.1V$$

$$\text{and } V_B = V_L = 21.31 + j(6.197)V$$

$$\therefore V_{AB} = V_A - V_B$$


$$V_{AB} = -6.21 - j(6.197)V$$

Answer

1 Problem from Section 15-4:

33. For the circuit, determine the following
in polar form

- (a) Z (b) I_{tot} (c) V_R (d) V_C

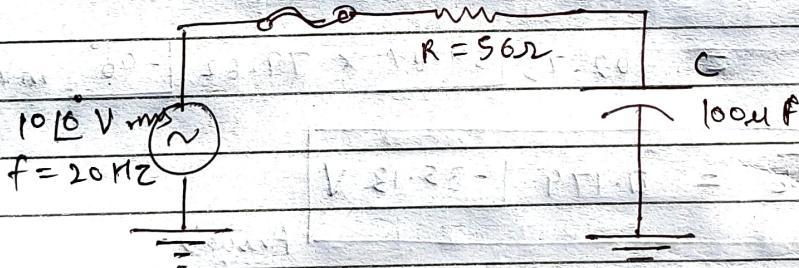

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi(3.14) \times 20 \times (100\mu)}$$

$$X_C = 79.62 \Omega$$

$$\therefore Z = 56 + j(-79.62) \Omega$$

$$(a) \quad \bar{Z} = 97.34 - 54.87 \Omega$$

Answer

Name: Archit Agrawal

Student ID: 202052307

Date:

Page:

10

$$(b) \overline{I_{\text{tot}}} = \frac{\overline{V_s}}{\overline{Z}}$$

$$= 10 \angle 0^\circ \\ 97.34 \angle -54.87^\circ$$

$$\boxed{\overline{I_{\text{tot}}} = 102.73 \angle 54.87^\circ \text{ mA}}$$

Answer

$$(c) \overline{V_R} = \overline{I_{\text{tot}}} \times \overline{Z_R}$$

$$= 102.73 \angle 54.87^\circ \times 56 \angle 0^\circ \text{ mV}$$

$$\boxed{\overline{V_R} = 5.754 \angle 54.87^\circ \text{ V}}$$

Answer

$$(d) \overline{V_C} = \overline{I_{\text{tot}}} \times \overline{Z_C}$$

$$= 102.73 \angle 54.87^\circ \times 79.62 \angle -90^\circ \text{ mV}$$

$$\boxed{\overline{V_C} = 8.179 \angle -35.13^\circ \text{ V}}$$

Answer

1 Problem from Section 15-6 :-

46. For the parallel circuit, find the magnitude of each branch current and total current. What is the phase angle between the applied voltage and total current?


Name: Archit Agrawal

Student ID: 202052307

Date:

Page:

11

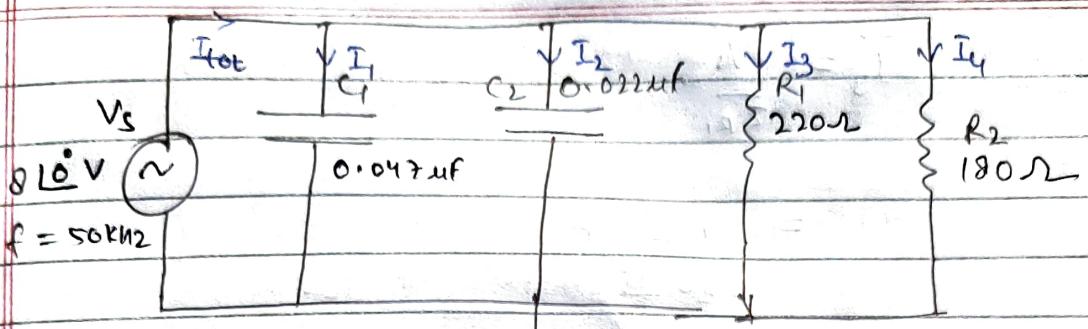

$$\overline{I}_1 = \frac{\overline{V}_s}{\overline{Z}_{C_1}}$$

$$\frac{x_{C_1}}{Z_{C_1}} = \frac{1}{\omega C} = \frac{1}{2 \times 3.14 \times (50\text{K}) \times (0.047\mu)} \quad \text{--- (1)}$$

$$x_{C_1} = 67.76 \Omega$$

$$\therefore \overline{Z}_{C_1} = 67.76 \angle -90^\circ \Omega$$

$$\therefore \overline{I}_1 = \frac{8 \angle 0^\circ}{67.76 \angle -90^\circ}$$

$$\overline{I}_1 = 118.06 \angle 90^\circ \text{ mA}$$

$$I_1 = j(118.06) \text{ mA}$$

$$x_{C_2} = \frac{1}{2\pi f C_2} = 144.75 \Omega$$

$$Z_{C_2} = 144.75 \angle -90^\circ \Omega$$

$$\therefore \overline{I}_2 = \frac{\overline{V}_s}{\overline{Z}_{C_2}} = \frac{8 \angle 0^\circ}{144.75 \angle -90^\circ}$$

$$\overline{I}_2 = 55.26 \angle 90^\circ \text{ mA}$$

$$I_2 = j(55.26) \text{ mA}$$

Name: Archit Agrawal

Student ID: 202052307

Date:

Page:

12

$$\overline{I}_3 = \frac{\overline{V}_S}{\overline{Z}_{R_1}}$$

$$= 8 \angle 0^\circ A$$

$220 \angle 0^\circ$

$$\overline{I}_3 = 36.36 \angle 0^\circ mA$$

$$I_3 = 36.36 mA$$

$$\overline{I}_4 = \frac{\overline{V}_S}{\overline{Z}_{R_2}}$$

$$= 8 \angle 0^\circ A$$

$180 \angle 0^\circ$

$$\overline{I}_4 = 44.44 \angle 0^\circ mA$$

$$I_4 = 44.44 mA$$

Using KCL, we know

$$I_{tot} = I_1 + I_2 + I_3 + I_4$$

$$\therefore I_{tot} = (36.36 + 44.44) + j(118.06 + 55.26) mA$$

$$I_{tot} = 80.8 + j(173.32) mA$$

$$I_{tot} = 191.25 \angle 65^\circ mA$$

phase angle between applied voltage and total current is

$$\phi = 6 - 65^\circ = -65^\circ$$


Answer

1 Problem from Section 15.7


54. For the circuit in the figure, determine

(a) I_{tot} (b) θ (c) V_{R_1} (d) V_{R_2}

(e) V_{R_3} (f) V_C

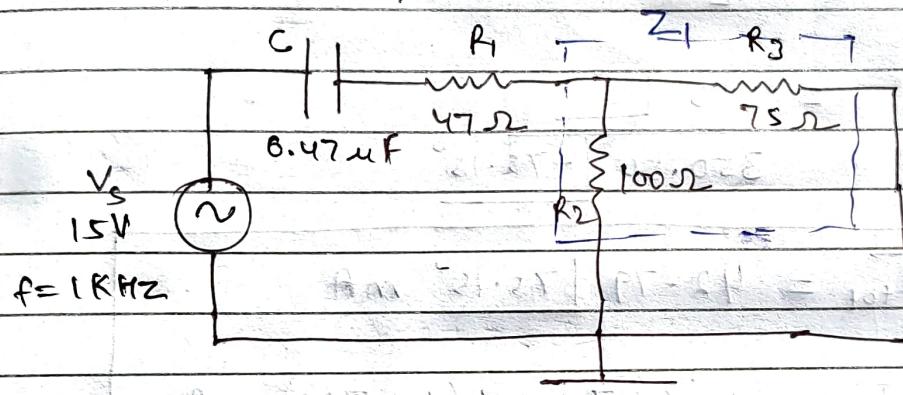

the circuit can be redrawn as

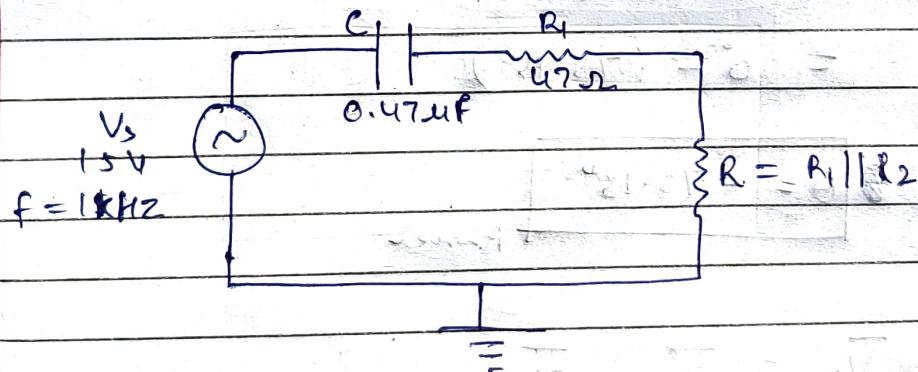

$$R = \frac{3}{75 \times 100} = 42.057 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2 \times (3.14) \times (1K) \times (0.47\mu)} = 338.8 \Omega$$

$$X_C = 338.8 \Omega$$

Name: Archit Agrawal

Student ID: 202052307

Date:

Page:

14

$$z = (47 + 42.857) - j(338.8) \Omega$$

$$z = (89.857) - j(338.8) \Omega$$

$$\bar{z} = 350.50 \angle -75.15^\circ \Omega$$

(a) $\overline{I}_{\text{tot}} = \frac{\overline{V}_S}{\bar{z}}$

$$= 15 \angle 0^\circ$$

$$350.50 \angle -75.15^\circ$$

$$\overline{I}_{\text{tot}} = 42.79 \angle 75.15^\circ \text{ mA}$$

$$I_{\text{tot}} = 10.967 + j(41.361) \text{ mA}$$

Answer

(b) $\theta = \phi_V - \phi I_{\text{tot}}$

$$= 0^\circ - (-75.15^\circ)$$

$$\theta = -75.15^\circ$$

Answer

(c) $\overline{V}_{R_1} = \overline{I}_{\text{tot}} \times \bar{Z}_{R_1}$

$$= 42.79 \angle 75.15^\circ \times 47 \angle 0^\circ \text{ mV}$$

$$\overline{V}_{R_1} = 2.011 \angle 75.15^\circ \text{ V}$$

$$V_{R_1} = 0.515 + j(1.944) \text{ V}$$

Answer

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 15

(d) $\bar{V}_{R_2} = \bar{I}_{\text{tot}} \times \bar{V}_R$
 $= 42.79 |75.15^\circ \times 42.857 |0^\circ \Omega$

$$\boxed{\bar{V}_{R_2} = 1.834 |75.15^\circ V}$$
$$\boxed{V_{R_2} = 0.47 + j(1.773) V}$$

Answer

(e) Since R_2 and R_3 are in parallel

$$\therefore V_{R_3} = V_{R_2}$$
$$V_{R_3} = 0.47 + j(1.773) V$$

Answer

(f) $\bar{V}_c = \bar{I}_{\text{tot}} \times \bar{Z}_{xc}$
 $= 42.79 |75.15^\circ \times 338.8 |-90^\circ mV$

$$\boxed{\bar{V}_c = 14.497 |-14.85^\circ V}$$

$$\boxed{V_c = 14.013 - j(3.715) V}$$


Answer

Name: Archit Agrawal
Student ID: 202052307



5 Questions from Home work

Ques.

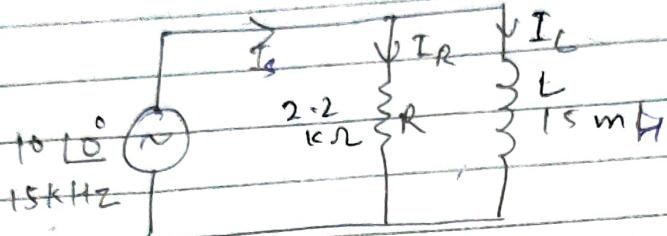

Find \bar{I} , \bar{I}_R , \bar{I}_L , P , S . Plot time domain and phasor for. Draw KCL.

$$Z_R = 2.2 \text{ k} \Omega$$

$$\begin{aligned} Z_L &= 2\pi(15 \text{ m})(15 \text{ m}) \\ &= 1.413 \text{ k} \Omega \end{aligned}$$

$$\therefore Z_L = j(1.413) \text{ k} \Omega$$

$$\therefore Z = Z_R \parallel Z_L$$

$$Z = \frac{2.2 \text{ k } 0^\circ \times 1.413 \text{ k } 90^\circ}{2.2 \text{ k } + j(1.413 \text{ k })}$$


$$\bar{Z} = \frac{3.12 \text{ } 90^\circ}{2.615 \text{ } 32.71^\circ} \text{ k} \Omega$$

$$\boxed{\begin{aligned} \bar{Z} &= 1.193 \text{ } 57.29^\circ \text{ k} \Omega \\ Z &= 0.72 + j(1.003) \text{ k} \Omega \end{aligned}}$$

$$I_S = \frac{\bar{U}_S}{\bar{Z}} = \frac{10 \text{ L0}^\circ}{1.193 \text{ } 57.29^\circ \text{ k} \Omega}$$

$$\boxed{\bar{I}_S = 8.382 \text{ } -57.29^\circ \text{ mA}}$$

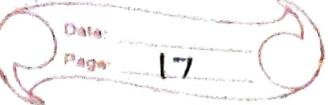Name : Archit Agrawal
Student ID : 202052307



$$\bar{I}_R = \frac{\bar{V}_S}{\bar{Z}_R} = \frac{10 \angle 0^\circ}{2.2k \angle 0^\circ}$$

$$\boxed{\bar{I}_R = 4.545 \angle 0^\circ \text{ mA}}$$

$$\bar{I}_L = \frac{\bar{V}_S}{\bar{Z}_L} = \frac{10 \angle 0^\circ}{1.413k \angle 90^\circ}$$

$$\boxed{\bar{I}_L = 7.08 \angle -90^\circ \text{ mA}}$$

$$\therefore \phi = \phi_{V_S} - \phi_{I_S}$$

$$\phi = 0 - (-57.29^\circ)$$

$$\phi = 57.29^\circ$$

$$\therefore P = V_S I_S \cos \phi \\ = 10 \times 8.382 \cos(57.29^\circ) \text{ MW}$$

$$\boxed{P = 45.295 \text{ mW}}$$

$$Q = V_S I_S \sin \phi$$

$$Q = 10 \times 8.382 \sin(57.29^\circ)$$


$$\boxed{Q = 70.53 \times 10^3 \text{ VAR}}$$

$$S = \sqrt{P^2 + Q^2}$$


$$= \sqrt{(45.295)^2 + (70.53)^2}$$

$$\boxed{S = 83.82 \times 10^3 \text{ VA}}$$

Phasor Diagrams

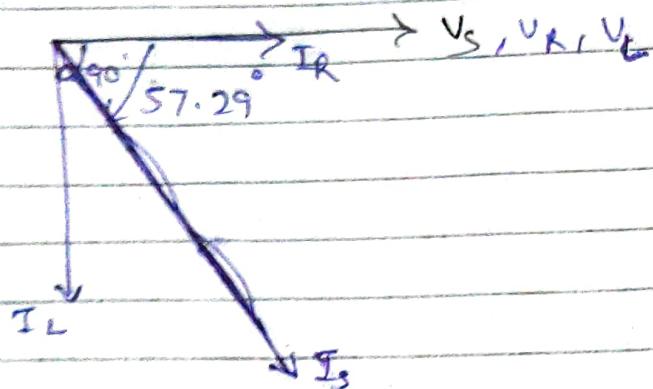

Time Domain

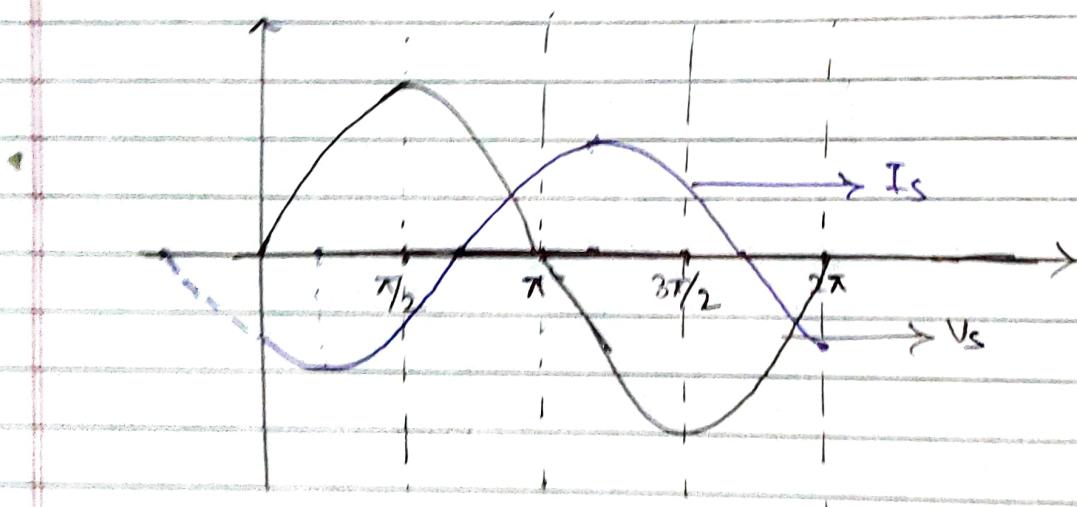

$$V_S = 10 + j(0) \text{ V}$$

~~Ans~~

$$V_S = 10 \sin(\omega t) \text{ V}$$

$$I_S = 0.782 \sin(\omega t - 57.29^\circ) \text{ mA}$$

$$I_S = 4.529 - j(7.052) \text{ mA}$$


$$I_R = 4.545 + j0 \text{ mA}$$

$$I_L = 0 - j(7.08) \text{ mA}$$

Clearly $I_S = I_R + I_L$, hence KCL is proved

Name: Archit Agrawal
Student ID: 202052307

Page 19

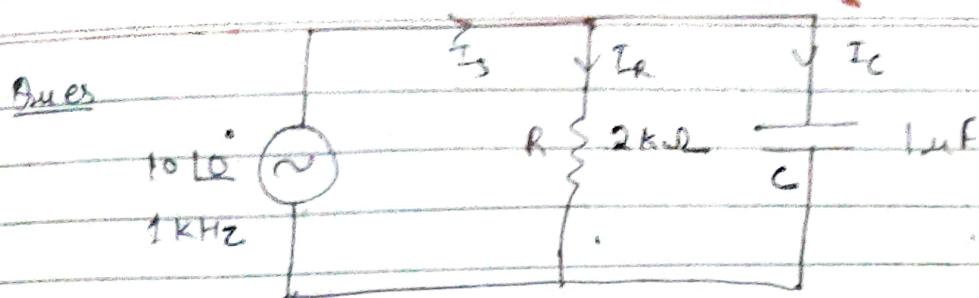

Find \bar{I}_R , \bar{I}_c , \bar{I}_s , P , θ , S .

Plot the phasor diagram and time domain diagram

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2 \times 3.14 \times 1\text{K} \times 1\mu} = 0.159\text{ k}\Omega$$

$$Z_C = -j(0.159\text{ k}) \Omega$$

$$Z_R = 2\text{k} \Omega$$

$$\therefore \bar{I}_R = \frac{\bar{V}_s}{Z_R} = \frac{10\text{ }10^\circ}{2\text{k }10^\circ}$$

$$\bar{I}_R = 5\text{ mA } 10^\circ$$

$$I_R = 5\text{ mA} + j(0)$$

$$\bar{I}_c = \frac{\bar{V}_s}{Z_C} = \frac{10\text{ }10^\circ}{0.159\text{ k }[-90^\circ]}$$

$$\bar{I}_c = 62.89\text{ }[-90^\circ]\text{ mA}$$

$$I_c = 0 + j(62.89)\text{ mA}$$

Using KCL,

$$\bar{I}_s = I_R + I_c$$

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 20

$$I_s = 5 + j(62.89) \text{ mA}$$

$$I_s = 63.088 \angle 85.454^\circ \text{ mA}$$

$$\begin{aligned}\phi &= \phi_{vs} - \phi_{I_s} \\ &= 0 - 85.454^\circ \\ \phi &= -85.454^\circ\end{aligned}$$


$$\begin{aligned}\therefore P &= I_s V_s \cos \phi \\ &\approx 50 \text{ mW}\end{aligned}$$

$$\begin{aligned}Q &= I_s V_s \sin \phi \\ Q &= -628.89 \times 10^{-3} \text{ VAR}\end{aligned}$$


$$\begin{aligned}S &= \sqrt{P^2 + Q^2} \\ &= \sqrt{(50)^2 + (-628.89)^2}\end{aligned}$$

$$S = 630.874 \times 10^{-3} \text{ VA}$$

Phasor Diagram

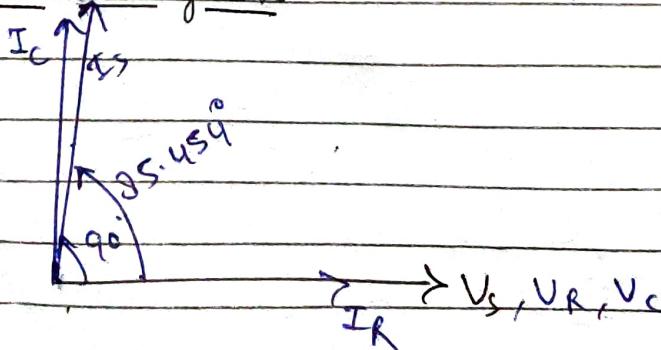


Time Domain

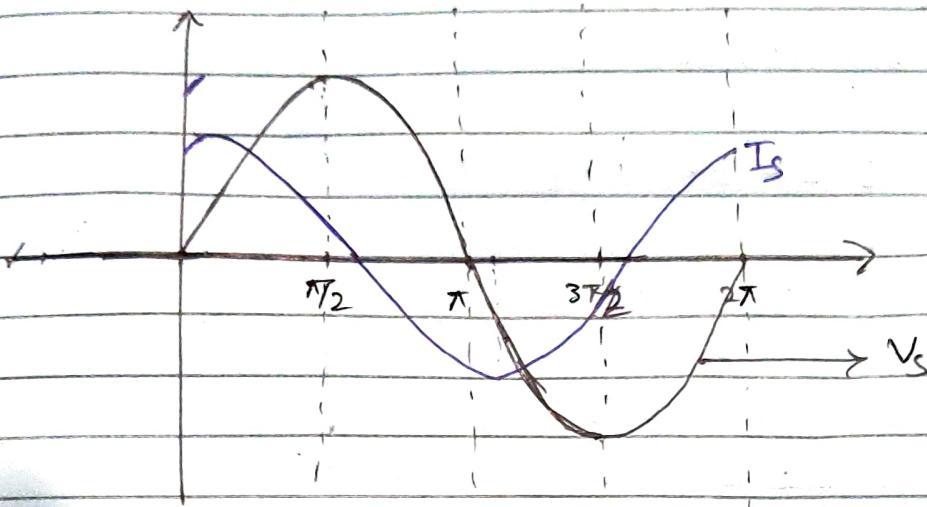

Ques 3 For the series RL circuit. determine magnitude of total impedance and phase angle at each of the following frequencies

- (a) 10 kHz (b) 20 kHz (c) 30 kHz

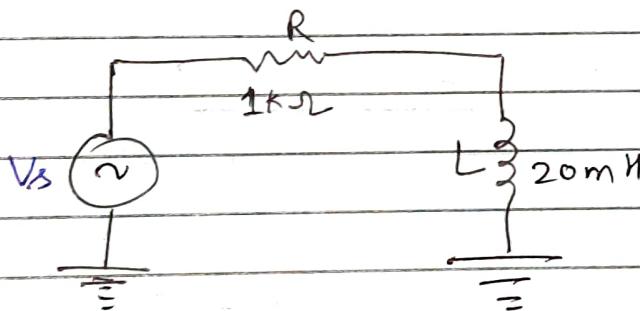

$$(a) f = 10 \text{ kHz}$$

$$X_L = 2\pi f L = 2\pi (10 \text{ k}) (20 \text{ m}) = 1.26 \text{ k}\Omega$$

$$\therefore Z = 1k + j(1.26k) \Omega$$

$Z = 1.61k \angle 51.5^\circ \Omega$

$\phi = 51.5^\circ$

(b) $f = 20 \text{ kHz}$

$$X_L = 2\pi f X_L = 2\pi (20\text{K})(20\text{m}) \approx 2.51 \text{ k}\Omega$$

$$\therefore Z = 1\text{k} + j(2.51\text{k})\Omega$$

$$\bar{Z} = 2.70\text{k} \angle 68.3^\circ \Omega$$

$$\therefore \phi = 68.3^\circ$$

(c)

$$f = 30 \text{ kHz}$$

$$X_L = 2\pi f X_L = 2\pi (30\text{K})(20\text{m}) = 3.77 \text{ k}\Omega$$

$$Z = 1\text{k} + j(3.77\text{k})\Omega$$

$$\bar{Z} = 3.90 \angle 75.1^\circ \text{ k}\Omega$$

$$\phi = 75.1^\circ$$

Ques 4. Given two voltages

$$V_1(t) = 10 \sin(\omega t + 30^\circ)$$

$$V_2(t) = 15 \sin(\omega t + 60^\circ)$$

Find $V_1(t) + V_2(t)$ and $V_1(t) \cdot V_2(t)$


$$\bar{V}_1 = 10 \angle 30^\circ \text{ V}$$

$$\bar{V}_2 = 15 \angle 60^\circ \text{ V}$$

$$V_1 = 8.66 + j(5) \text{ V}$$

$$V_2 = 7.5 + j(12.99) \text{ V}$$

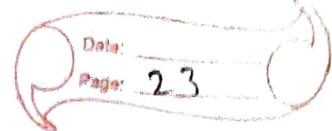Name: Archit Agrawal
 Student ID: 202082307



$$V_1 + V_2 = (8.66 + 7.5) + j(5 + 12.99)$$

$$V_1 + V_2 = 16.16 + j(17.99) \text{ V}$$

$$\underline{V_1 + V_2} = 24.18 \angle 48.06^\circ \text{ V}$$

$$V_1(t) + V_2(t) = 24.18 \sin(\omega t + 48.06^\circ) \text{ V}$$


$$\begin{aligned} \overline{V_1 \cdot V_2} &= \overline{V_1} \cdot \overline{V_2} \\ &= 10 \angle 30^\circ \times 15 \angle 60^\circ \\ &= 150 \angle 90^\circ \text{ V} \end{aligned}$$

$$V_1 \cdot V_2 = 150 \angle 90^\circ \text{ V}$$

$$V_1 \cdot V_2 = j(150) \text{ V}$$

$$V_1(t) \cdot V_2(t) = 150 \sin(\omega t + 90^\circ) \text{ V}$$

Q.S

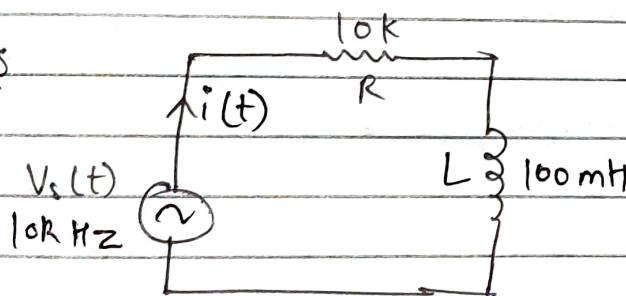

$I_s = 0.2 \angle 0^\circ \text{ mA}$. Find \overline{V}_s , $V_s(t)$, \overline{V}_R , \overline{V}_b , $V_R(t)$, $V_s(t)$. Plot phasor diagram.

$$\begin{aligned} X_L &= 2\pi (10k) (100m) \\ &= 6.28 \text{ k}\Omega \end{aligned}$$

$$\therefore Z = 10k + j(6.28k)$$

$$\underline{Z} = 11.8 \angle 32.1^\circ \text{ k}\Omega$$

Name: Archit Agarwal
Student ID: 202052307

Date: _____
Page: 24

$$\bar{V}_S = \bar{I}_S \cdot \bar{Z}$$

$$\bar{V}_S = 0.2 [0^\circ] \text{ mA} \times 11.8 [32.1^\circ] \text{ k}\Omega$$

$$\bar{V}_S = 2.36 [32.1^\circ] \text{ V}$$

$$V_S(t) = 2.36 \sin(\omega t + 32.1^\circ) \text{ V}$$

$$\begin{aligned}\bar{V}_R &= \bar{I}_S \cdot \bar{Z}_R \\ &= 0.2 [0^\circ] \text{ mA} \times 10 [6^\circ] \text{ k}\Omega\end{aligned}$$

$$\bar{V}_R = 2 [0^\circ] \text{ V}$$

$$V_R(t) = 2 \sin(\omega t + 0^\circ) \text{ V}$$

$$\bar{V}_L = \bar{I}_S \cdot \bar{Z}_L$$

$$\approx 0.2 [0^\circ] \text{ mA} \times 6.28 \text{ k} [90^\circ] \text{ }\Omega$$

$$\approx 1.256 [90^\circ] \text{ V}$$

$$\boxed{\bar{V}_L = 1.256 [90^\circ] \text{ V}}$$

$$\boxed{V_L(t) = 1.256 \sin(\omega t + 90^\circ)}$$

