

EE100: Basic Electrical EngineeringRemote End-Semester Exam

1.(a) Rated voltage and rated current for high voltage side,

$$\boxed{\text{rated voltage (HV side)} = 1000 \text{ V}} \quad (\text{given})$$

$$\text{rated current (HV side)} = \frac{\text{rated Power}}{\text{rated voltage (HV side)}}$$

$$= \frac{100 \times 10^3 \text{ VA}}{10^3 \text{ V}}$$

$$\boxed{\therefore \text{rated current (HV side)} = 100 \text{ A}}$$

② rated voltage and rated current for low-voltage side,

$$\boxed{\text{rated voltage (LV side)} = 100 \text{ V}} \quad (\text{given})$$

$$\text{rated current (LV side)} = \frac{\text{rated Power}}{\text{rated Voltage (LV side)}}$$

$$= \frac{100 \times 10^3 \text{ VA}}{100 \text{ V}}$$

$$\boxed{\text{rated current (LV side)} = 1000 \text{ A}}$$



(b) OC - test (secondary - side)

$$|Y_{ex}| = \frac{I_{oc}}{V_{oc}}$$

$$= \frac{6 \text{ A}}{100 \text{ V}}$$

$$|Y_{ex}| = 0.06 \text{ S}$$

$$\phi = \cos^{-1} \left(\frac{P_{oc}}{I_{oc} \cdot V_{oc}} \right)$$

$$\phi = \cos^{-1} \left(\frac{400}{100 \cdot 6} \right)$$

$$\phi = 48.189^\circ$$

$$\therefore Y_{ex} = \frac{0.06}{\cancel{48.189^\circ}} \angle -48.189^\circ \text{ S}$$

$$Y_{ex} = 0.04 - j(0.0447) \text{ S}$$

$$\therefore Y_{ex} = \frac{1}{R_c} - \frac{j}{X_m}$$

$$\therefore R_{cp} = \frac{1}{0.04} = 25 \Omega$$

$$X_{mp} = \frac{1}{0.0447} = 22.371 \Omega$$

SC - test (primary side)

$$|Z_{eq}| = \frac{V_{sc}}{I_{sc}} = 0.5 \Omega$$

$$\phi = \cos^{-1} \left(\frac{P_{sc}}{I_x \cdot V_{sc}} \right)$$

$$\phi = \cos^{-1} \left(\frac{1800}{50 \times 100} \right)$$

$$\phi = 68.899^\circ$$


$$Z_{eq} = 0.5 \angle 68.899^\circ \Omega$$

$$= 0.18 + j 0.47 \Omega$$

$$\therefore R_{eq,p} = 0.18 \Omega$$

$$X_{eq,p} = 0.47 \Omega$$

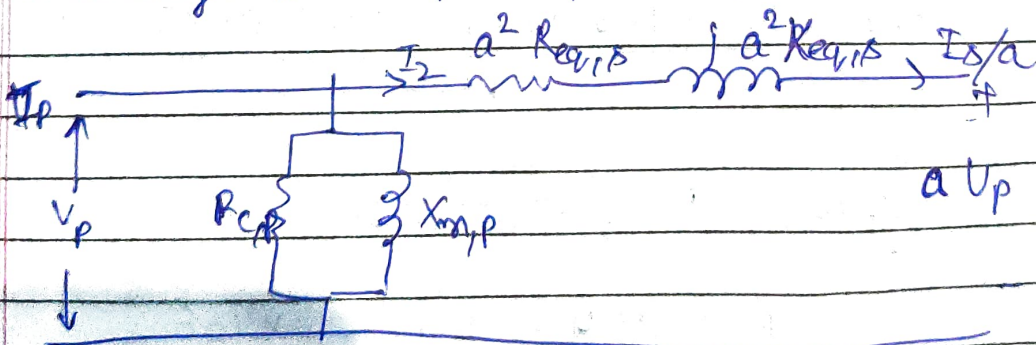equivalent circuit referred to high voltage side (primary side)



$$R_{sp} = \left(\frac{1000}{100}\right)^2 R_{c,p}$$
$$= 2500 \Omega$$

$$X_{m,p} = \left(\frac{1000}{100}\right)^2 X_{m,p}$$

$$X_{m,p} = 2237.1 \Omega$$

$$V_p = 1000 \text{ V}$$

at full load $I_2 = \frac{100 \times 10^3}{1000} = 100 \text{ A}$

and power factor $\cos \phi_2 = 0.8$
 $\therefore \sin \phi_2 = 0.6$

$$\therefore VR = \frac{I_2 R_{eq} \cos \phi_2 + I_2 X_{eq} \sin \phi_2}{E_2}$$

$$\% R = \frac{I_2 R_{eq} \cos \phi_2 + I_2 X_{eq} \sin \phi_2 \times 100}{E_2}$$


$$\% R = \frac{100 \times 1.8 \times 0.8 + 100 \times 0.47 \times 0.6 \times 100}{1000}$$

~~$$\% R = 14.4 + 13.056$$~~

$$\% R = \frac{14.4 + 28.2 \times 100}{1000 \text{ } 10}$$

$$\% R = 4.26\%$$

2-

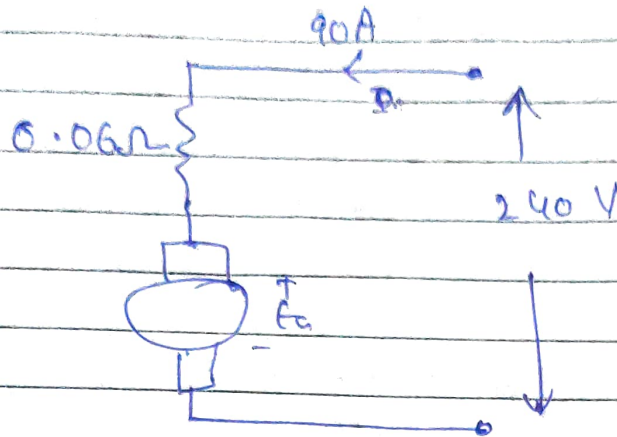

(a) So, $E_a = 240 - 90 \times 0.6$

$$E_a = 234.6 \text{ V}$$

and, $\omega_m = \frac{1200 \times 2\pi}{60} = 40\pi \text{ rad/s}$

$$\therefore \text{torque} = \frac{E_a I_a}{\omega_m} = \frac{234.6 \times 90}{40\pi}$$

$$\boxed{\tau = 168.02 \text{ N-m}}$$

(b) Since, $\text{torque} = K \phi I_a$

$$\therefore 168.02 = K \phi \times 90$$

$$\therefore K \phi = \frac{168.02}{90} \quad \text{--- (1)}$$

Now, $\text{torque} = 280 \text{ N-m}$

$$\therefore 280 = K \phi I_{a_2}$$

Archi's Agreement
202052307
Archi's Agreement



Mahabir

Date

Page

6

$$I_{a2} = \frac{280 \times 90}{168.02} = 149.9 \text{ A}$$

$$\therefore I_{a2} = 149.9 \text{ A}$$

$$\therefore E_a = 290 - 0.06 \times 149.9$$

$$E_a = 231.006 \text{ V}$$

$$\therefore E_a = K \phi \omega_m$$

$$\omega_m = \frac{231.006 \times 90}{168.02}$$

$$= 123.738 \text{ rad/s}$$

$$= 123.738 \times \frac{60}{2\pi} \text{ rpm}$$

$$\omega_m = 1181 \text{ rpm}$$

3. (a) at starting, slip $s = 1$.

$$\begin{aligned}\text{current } I_2 &= \frac{E_2}{\sqrt{R_2^2 + X_2^2}} \\ &= \frac{460/\sqrt{3}}{\sqrt{(0.2)^2 + (0.5)^2}}\end{aligned}$$

$$= \frac{265.5889}{\sqrt{0.29}}$$

$$I_2 = \frac{265.5889}{0.5385} = 493.201 \text{ A}$$

\therefore starting current is 493.201 A.

(b) for maximum torque, we know that

$$s_{\max} = \frac{R_2}{X_2} = \frac{0.2}{0.5} = 0.4$$

$$\therefore s_{\max} = 0.4$$

torque at s_{\max}

$$T_{\max} = \frac{3 \times 60}{2\pi N_s} \cdot \frac{(s_{\max})^2 E_2^2 R_2}{R_2^2 + (s_{\max} X_2)^2}$$

$$T_{max} = 0.0159 \cdot \frac{(0.4) \left(\frac{460}{\sqrt{3}} \right)^2 \cdot (0.2)}{(0.2)^2 + (0.4 \times 0.5)^2}$$

$$T_{max} = \frac{89.723 \text{ N-m}}{0.2828}$$

$$T_{max} = 317.26 \text{ N-m}$$

(c) at full load

$$\text{slip } \% S = \frac{N_s - N_o}{N_s} \times 100$$

$$N_s = \frac{120 \times f_e}{P} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$

$$\therefore S = \frac{1800 - 1740}{1800}$$

$$S = 0.033$$

$$\therefore \text{efficiency of motor} = (1 - S) \times \frac{N_o}{N_s} \times 100\%$$

$$= \frac{1740}{1800} \times 100$$

$$\text{efficiency of motor} = 96.67\%$$