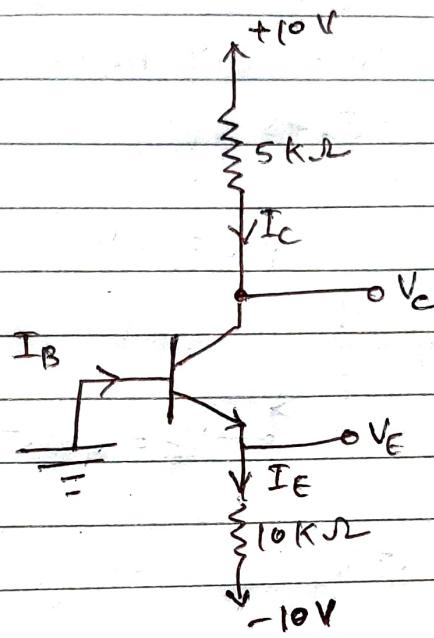


## EC100: Assignment 4

Q1 (3.10 of 4.1) In the circuit shown, the voltage at the emitter was measured and found to be  $-0.7$  V. If  $\beta = 50$ , find  $I_C$ ,  $I_B$ ,  $I_E$  and  $V_C$ .



The given transistor is npn type, and given  $V_E = -0.7$  V.

Assuming, the ~~given~~ transistor to be operating in active mode.

$$\therefore I_E = \frac{V_E - (-10)}{10\text{ k}\Omega} = \frac{9.3}{10\text{ k}} = 0.93\text{ mA}$$

$$\therefore I_C = (\beta + 1) I_B$$

$$\therefore I_B = \frac{0.93\text{ mA}}{51} \quad (\text{as } \beta = 50)$$


$$I_B = 0.01823\text{ mA} = 18.23\mu\text{A}$$

and  $\therefore I_c = \beta I_B + I_{Co}$  ( $I_{Co}$  is negligible)

$$\begin{aligned} \therefore I_c &= \beta I_B \\ &= 50 \times 18.23 \mu A \\ &= 0.91 \text{ mA} \end{aligned}$$

$$\begin{aligned} \text{and } V_c &= 10 - I_c (5 \text{ k}\Omega) \\ &= 10 - (0.91 \text{ mA}) (5 \text{ k}\Omega) \\ &= 5.45 \text{ V} \end{aligned}$$

Now,

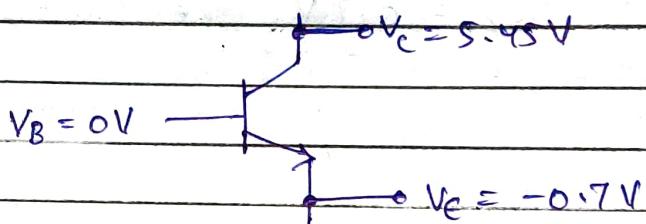


Since  $V_B - V_E \geq 0.7 \text{ V}$ , the emitter junction is forward biased and  $V_C - V_B \geq 0.7 \text{ V}$ . The collector junction is reverse biased.

Hence, our assumption is correct that the transistor is working in active mode.

$$\begin{aligned} \text{Hence, } I_C &= 0.91 \text{ mA} \\ I_B &= 18.23 \mu A \\ I_C &= 0.91 \text{ mA} \\ V_C &= 5.45 \text{ V} \end{aligned}$$

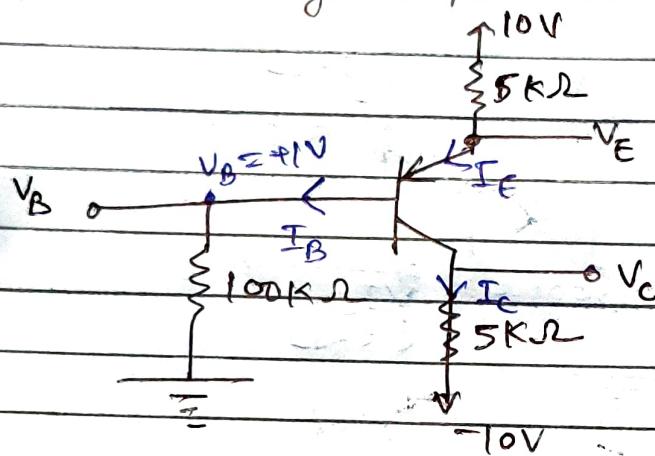Q.2 (3.11 of 4.1) In the circuit shown, the measurements indicates  $V_B$  to be 1 V and  $V_C$  to be 1.7 V. What are the values of  $\alpha$  and  $\beta$  for this transistor? What voltage  $I_C$  do you expect at the collector?



The given transistor is pnp type. Assuming it to be operating in active mode.

Given,  $V_B = +1\text{V}$  and  $V_C = +1.7\text{V}$ .

$$\therefore I_B = \frac{V_B - 0}{100K} = \frac{1}{100K} = 0.01\text{mA}$$

$$\text{and } I_E = \frac{10 - 1.7}{5K} = \frac{8.3}{5K} = 1.66\text{mA}$$

$$\therefore I_C = (\beta + 1) I_B$$

$$\therefore \beta + 1 = \frac{I_E}{I_B} = \frac{1.66\text{ mA}}{0.01\text{ mA}}$$

$$\beta + 1 = 166$$

$$\beta = 165$$

$$\therefore \alpha = \frac{\beta}{\beta+1} = \frac{165}{166}$$

$$\alpha = 0.994$$

$$\therefore I_C = \beta I_B + I_{C0} \quad (I_{C0} \text{ is negligible})$$

$$I_C = 165 \times 0.01 \text{ mA}$$

$$I_C = 1.65 \text{ mA}$$


$$\therefore V_C = -10 + I_C R_C$$

$$V_C = -10 + (1.65 \text{ mA})(5 \text{ k}\Omega)$$

$$V_C = -10 + 8.25$$

$$V_C = -1.75 \text{ V}$$

Now,

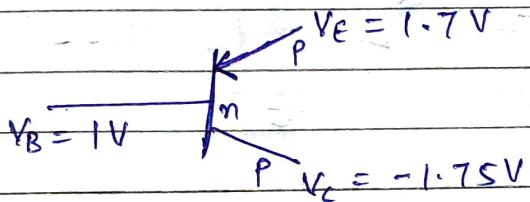


$\therefore V_C - V_B \geq 0.7 \text{ V}$ , emitter junction is forward biased.

and since,  $V_B - V_C = 2.75 \text{ V} \geq 0.7 \text{ V}$ , the collector junction is reverse biased. Hence, our assumption is correct and  $\alpha = 0.994$


$$\beta = 165$$

$$\text{and, } V_C = -1.75 \text{ V.}$$

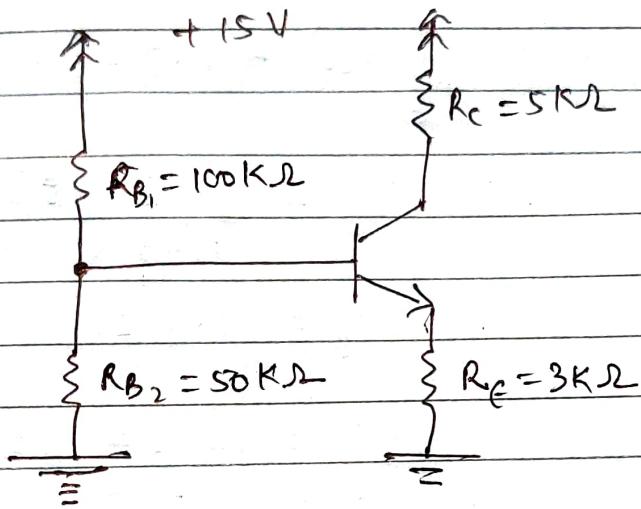Q.3 (3.27 of 4.1) If the transistor in the circuit is replaced with another having  $\beta = 50$  ( $\beta = 100$  before), find new value of  $I_C$ , and express the change in  $I_C$  as percentage



The circuit can be redrawn as

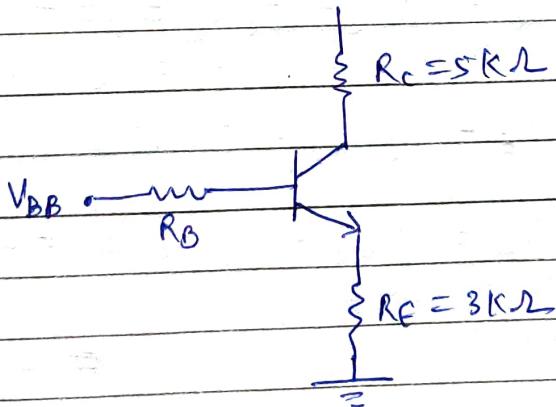

$$V_{BB} = V_{cc} \times \frac{50\text{ k}}{150\text{ k}} \quad (\text{voltage divider})$$

$$V_{BB} = 15 \times \frac{50}{150} = 5\text{ V}$$

$$\text{and } R_B = R_B1 \parallel R_B2 = 100\text{ k} \parallel 50\text{ k} \\ = \frac{100\text{ k}\cdot 50\text{ k}}{3} = 16.67\text{ k}$$

If  $B = 100$  and assuming that transistor is in active mode.

$$5 - I_B R_B - V_{BE} - I_C R_E = 0$$

$$5 - I_B \left( \frac{100 \text{ k}\Omega}{3} \right) - 0.7 - (\beta + 1) I_B (3 \text{ k}\Omega) = 0$$

$$I_B = \frac{4.3 \times 0.3}{100 \times 1000}$$

$$I_B = 0.0128 \text{ mA}$$

$$\therefore I_C = \beta I_B = 1.28 \text{ mA}$$

$$I_E = 1.2928 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C = 15 - (1.28 \text{ mA})(5 \text{ k}\Omega)$$

$$= 8.6 \text{ V}$$

$$V_E = I_E R_E = 3.878 \text{ V}$$

$$V_B = V_{BB} - I_B R_B = 5 - (0.0128 \text{ mA}) \left( \frac{100 \text{ k}\Omega}{3} \right)$$

$$= 5 - 0.427$$

$$= 4.573 \text{ V}$$

$$V_B = 4.573 \xrightarrow[P]{\quad} n V_C = 8.6 \text{ V}$$

$$\xrightarrow{\quad} n V_E = 3.878 \text{ V}$$

Since, the emitter junction is in FB and collector junction is in RB, our assumption is correct.

$$\text{and } I_C \text{ (at } \beta = 100) = 1.28 \text{ mA}$$

If  $\beta = 50$ , and assuming that transistor is in active mode.

$$I_B = \frac{4.3 \times 3}{559 \times 1000}$$

$$I_B = 0.0230 \text{ mA}$$

$$\therefore I_C = 50 \times 0.023 = 1.15 \text{ mA}$$

$$I_E = 1.173 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C = 15 - (1.15 \text{ mA})(5 \text{ k}\Omega)$$


$$V_C = 9.25 \text{ V}$$

$$V_E = I_E R_E = 3.519 \text{ V}$$

$$V_B = V_{BB} - I_B R_B = 5 - (0.023 \text{ mA}) \left( \frac{100 \text{ k}\Omega}{3} \right)$$

$$= 5 - 0.77$$

$$= 4.23 \text{ V}$$

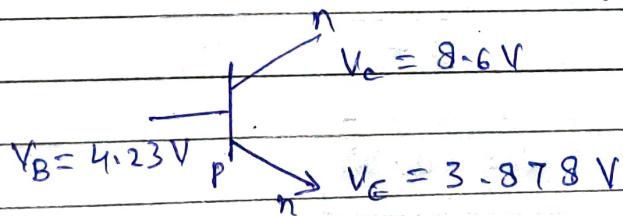

Since, the emitter junction is in FB and collector junction is in RB, our assumption is correct. and,

$$I_C (\text{at } \beta = 50) = 1.15 \text{ mA.}$$

$$\therefore \text{change in } I_C = \frac{1.15 - 1.28 \times (100\%)^-}{1.28}$$

$$\approx -10\%$$

Q 4 (8.5 ex of 4.2) The collector and base current are measured as  $I_c = 5\text{mA}$ ,  $I_B = 50\text{\mu A}$ , and  $I_{CBO} = 1\text{\mu A}$ :

- Determine  $\alpha$ ,  $\beta$  and  $I_E$ .
- Determine new level of  $I_B$  required to produce  $I_c = 10\text{mA}$

$$I_B = 50\text{\mu A}, I_c = 5\text{mA}, I_{CBO} = 1\text{\mu A}$$

$$\begin{aligned} \text{(i)} \quad \beta &= \frac{I_c}{I_B} \\ &= \frac{5 \times 10^{-3}}{50 \times 10^{-6}} = 100 \end{aligned}$$

$$\boxed{\beta = 100}$$

$$\text{(ii)} \quad \therefore \alpha = \frac{\beta}{\beta + 1} = \frac{100}{101}$$

$$\boxed{\alpha = 0.99}$$

$$\begin{aligned} \therefore I_E &= I_B + I_c \\ I_E &= 5.05\text{ mA} \end{aligned}$$

$$\text{(iii)} \quad \therefore I_c = \beta I_B + I_{CBO}$$


$$10\text{ mA} = 100(I_B) + 1\text{\mu A}$$

$$\therefore I_B = \frac{(10 - 0.001)\text{ mA}}{100}$$

$$I_B = 0.0999 \text{ mA}$$

$I_B = 99.9 \mu\text{A}$

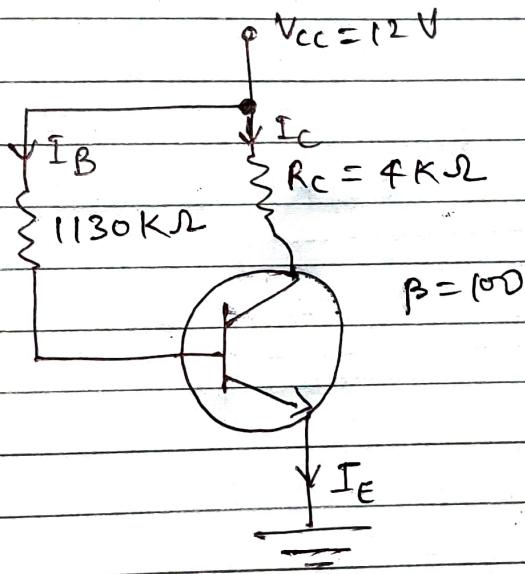Q5 (4S of 4.2) Figure shows the circuit of fixed bias using a silicon transistor with  $\beta = 100$ . Determine (i) base current, (ii) collector current (iii) operating point  $V_C$ ,  $V_B$  and  $V_{EB}$  (iv) operating point (v) stability factor  $S$ .



The transistor is n-p-n. Assuming it to be operating in active mode.

$$\because V_B - V_{BE} = 0$$

$$\therefore V_B = 0.7V$$

$$\therefore I_B = \frac{V_{CC} - V_B}{1130 \text{ k}\Omega} = \frac{12 - 0.7}{1130 \text{ k}\Omega}$$

$$I_B = 0.01 \text{ mA}$$

$$\therefore I_c = \beta I_B + I_{Co} \quad (I_{Co} \text{ is negligible})$$

$$\therefore I_c = 100 \times 0.01 \text{ mA} \\ = 1 \text{ mA}$$

$$\therefore I_E = I_B + I_c = 1.01 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C$$


$$= 12 - (1 \text{ mA})(4 \text{ k}\Omega) \\ = 8 \text{ V}$$

(i)  $I_B = 10 \mu\text{A}$

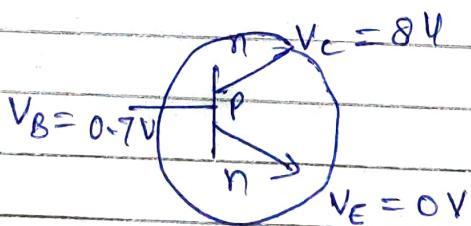(ii)  $I_c = 1 \text{ mA}$

(iii)

$V_C = 8 \text{ V}$
$V_B = 0.7 \text{ V}$
$V_{CB} = 7.3 \text{ V}$



Clearly, emitter junction is FB and base-collector junction is RB. Hence, our assumption is correct.

(iv) operating point is  $(V_C, I_C)$


∴ operating point is  $(8V, 1mA)$

(v) stability factor  $S \approx \beta + 1$

$$S = 100 + 1 = 101$$

(Ex 11.27 of 4.2)

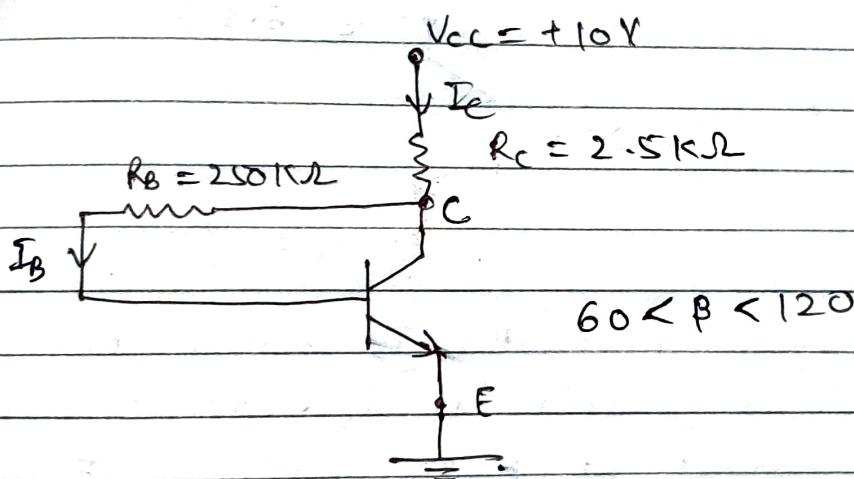Q.6. calculate the maximum and minimum collector current in the circuit



Assuming the transistor to be operating in active region.

Applying KVL,

$$V_{CC} - I_c R_c - I_B R_B - V_{BE} = 0$$

$$I_c R_c + I_B R_B = V_{CC} - V_{BE}$$

$$\beta R_c I_B + I_B R_B = V_{CC} - V_{BE} \quad (\because I_c = \beta I_B)$$

$$I_B = \frac{V_{CC} - V_{BE}}{\beta R_c + R_B}$$

If  $\beta = 60$

$$I_B (\text{at } \beta=60) = \frac{10 - 0.7}{\{(60 \times 2.5) + 250\} K}$$


$$= \frac{9.3}{400K}$$

$$I_B (\text{at } \beta=60) = 0.02325 \text{ mA}$$

$$\therefore I_C (\text{at } \beta=60) = 1.395 \text{ mA}$$

$$\therefore V_C (\text{at } \beta=60) = 10 - (1.395 \text{ mA})(2.5 \text{ k}\Omega)$$

$$= 6.51 \text{ V}$$

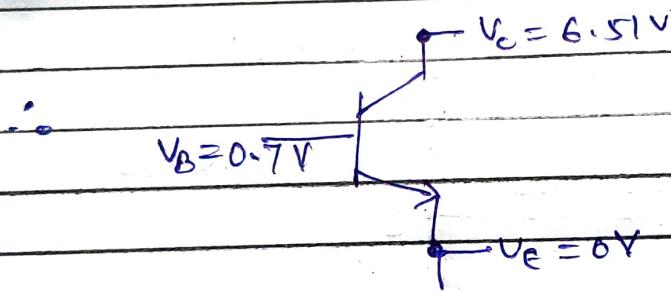

Clearly, the emitter junction if (FB) and collector junction is  $R_B$ . Hence, our assumption is correct at  $\beta=60$  and  $I_C = 1.395 \text{ mA}$

If  $\beta = 180$

$$I_B (\text{at } \beta=180) = \frac{10 - 0.7}{\{(180 \times 2.5) + 250\} K}$$

$$= \frac{9.3}{700K}$$

$$= 0.0133 \text{ mA}$$

$$\therefore I_C (\text{at } \beta=180) = 2.39 \text{ mA}$$

$$\therefore V_C (\text{at } \beta=180) = 4.02 \text{ V}$$

$$\therefore V_B = 0.7V$$


$V_C = 4.02V$

$V_E = 0V$

Similarly, emitter junction is (FB) and collector junction is (RB). Our assumption is correct.

Hence, the minimum and maximum value of  $I_C$  are 1.395 mA and 2.39 mA.

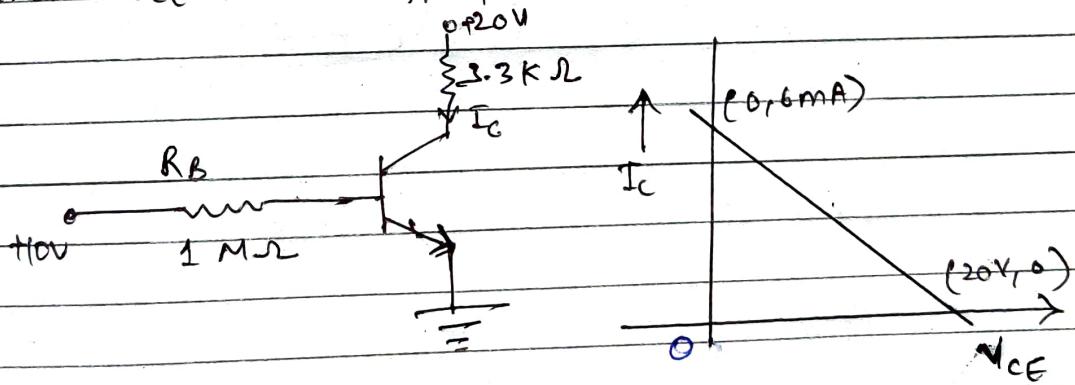Q.7 (Q.15 of 4.2) Draw the load line for the following figure - what is  $I_C$  at saturation point?  
find  $V_{CE}$  at cut-off point.




When  $V_{CE} = 0$ ,

$$I_C = \frac{20 - 0}{3.3k} = 6.06 \text{ mA}$$

When  $I_C = 0$ ,  $V_{CE} = V_{CE} = 20V$

Hence, load line is given in the graph.

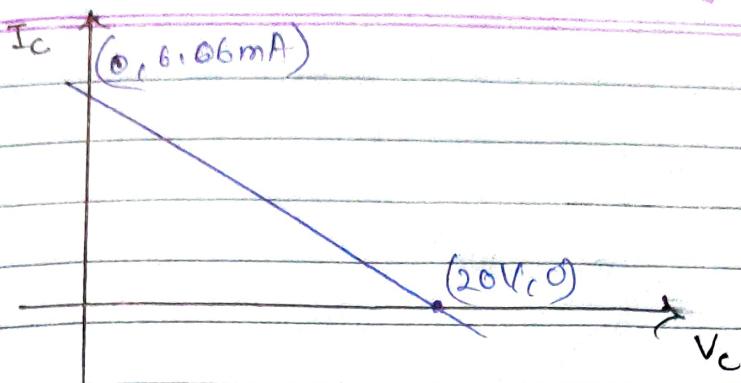


Hence, at saturation point, i.e.  $V_c = 0$ , current  $I_c = 6.06\text{mA}$ .

and, at cutoff point, i.e. at  $I_c = 0$ , the voltage  $V_{CE}$ ,

$$\because I_c = 0, \quad V_{CE} = V_{CC} = 20\text{V}$$

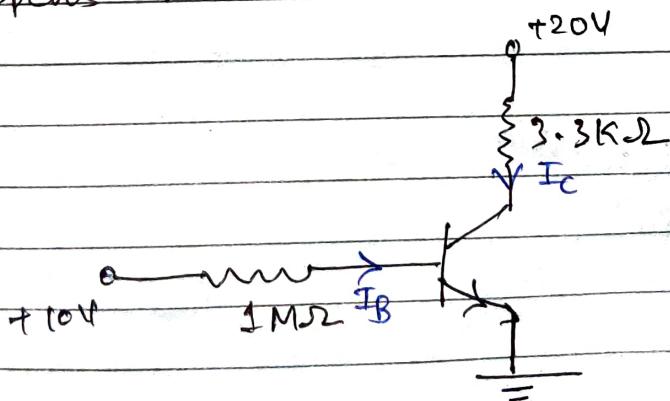
Q.8 (7-6) of 4.1) If the collector supply voltage is increased to 25V in the figure, what happens to the load line?



From the given circuit,

When  $I_c = 0$ ,  $V_c = V_{CE} = 20\text{V}$   
and when  $V_c = 0$ ,  $I_c = \frac{20-0}{3.3\text{k}\Omega} = 6.06\text{mA}$

Hence, the load line is

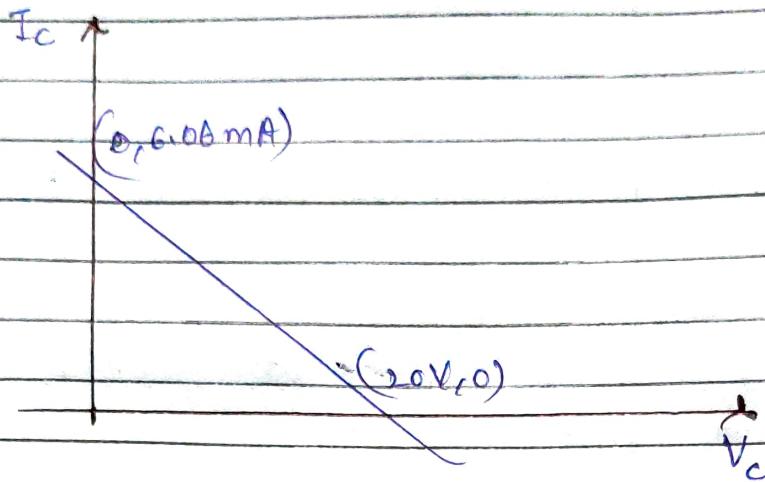


When collector supply voltage is increased to  $25\text{V}$ , i.e.  $V_{CC} = 25\text{V}$ , in the circuit,

When  $I_C = 0$ ,  $V_C = V_{CC} = 25\text{V}$ .


When  $V_C = 0$ ,  $I_C = \frac{25 - 0}{3.3\text{K}\Omega} = 7.57\text{mA}$

therefore, the new load line is

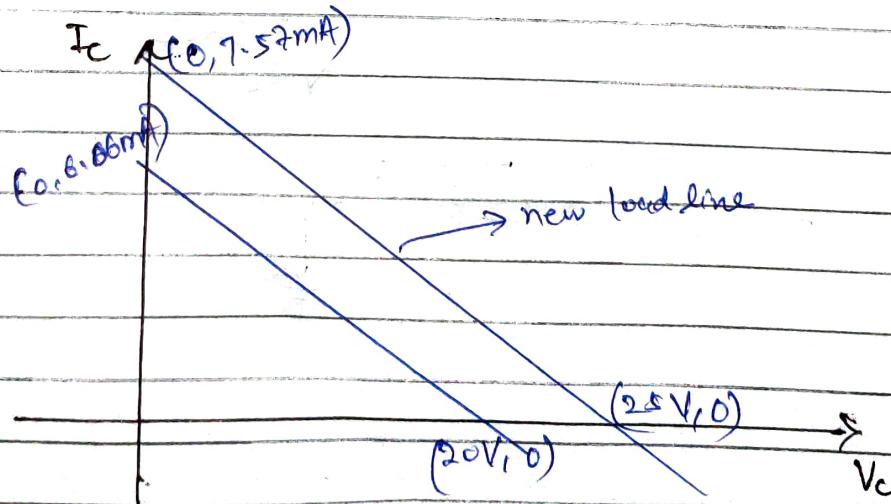


Hence, the slope of load line remains same but its intercept changes.

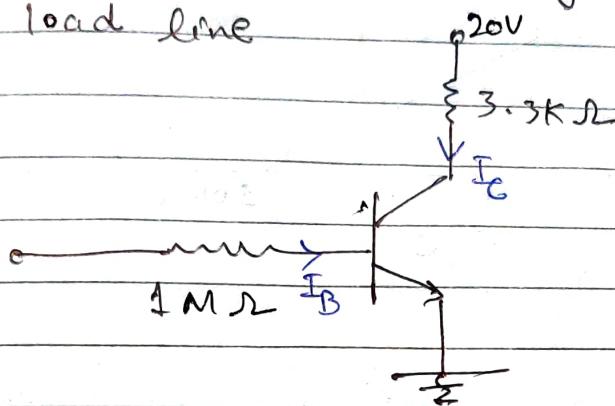Q.9 (7-5 of 4.1) If the collector resistance is increased to  $4.7\text{ k}\Omega$  in Fig. what happens to the load line



From the given circuit,  
when  $I_c = 0$ ,  $V_c = V_{cc} = 20\text{V}$   
and when  $V_c = 0$ ,  $I_c = \frac{20 - 0}{3.3\text{k}\Omega} = 6.06\text{mA}$


therefore the load line is,

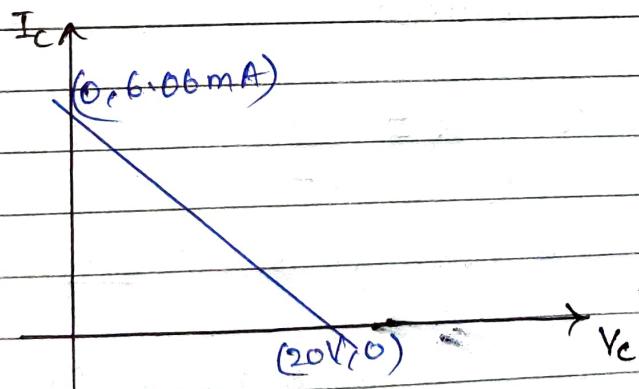

Now, if the collector resistance  $R_c$  is changed to  $4.7\text{ k}\Omega$ .

When  $I_c = 0$ ,  $V_c = V_{cc} = 20\text{V}$   
and when  $V_c = 0$ ,  $I_c = \frac{20 - 0}{4.7\text{k}} = 4.25\text{mA}$

therefore, the new load line is

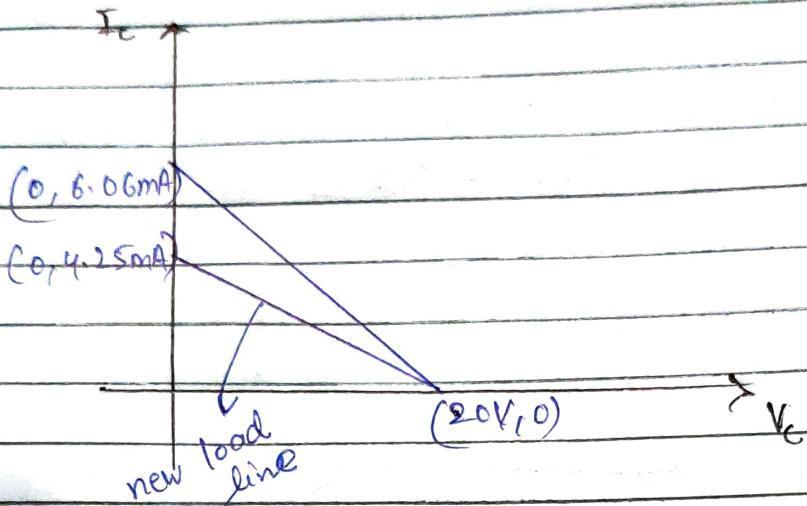

the slope of the <sup>load</sup> line is changed and its intercept on  $I_C$  axis is reduced.

Q.10 (3-2 of 4-1) Transistors of a certain type are specified to have  $\beta$  values in the range 50 to 150. Find the range of their  $\alpha$  values.

$$\therefore \alpha = \frac{\beta}{\beta + 1}$$

$$\alpha (\text{when } \beta = 50) = \frac{50}{51}$$


$$\alpha (\text{at } \beta = 50) = 0.9804$$

$$\alpha (\text{at } \beta = 150) = \frac{150}{151}$$


$$= 0.9934$$

$\therefore$  Range of  $\alpha$  is from 0.9804 to 0.9934.

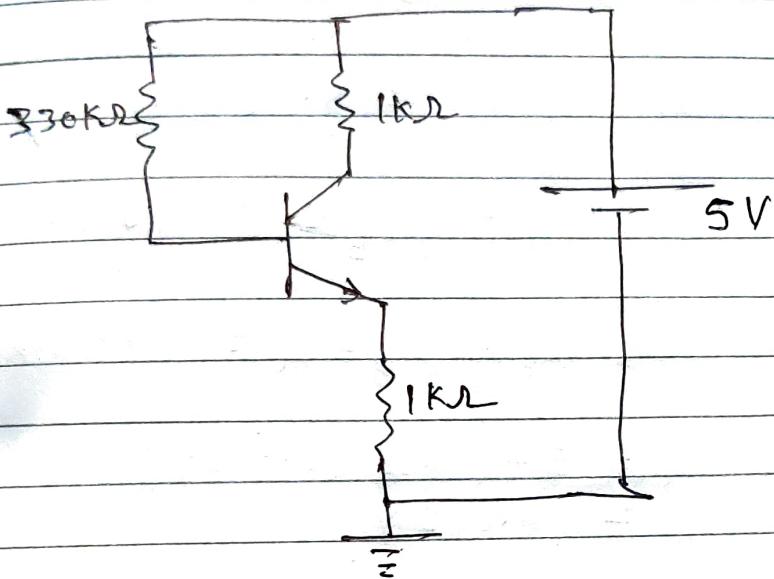Q.11 (1 of 4-2) In the circuit, the transistor has  $\beta = 100$ , and its  $I_{CO}$  is negligible. Determine the transistor currents.



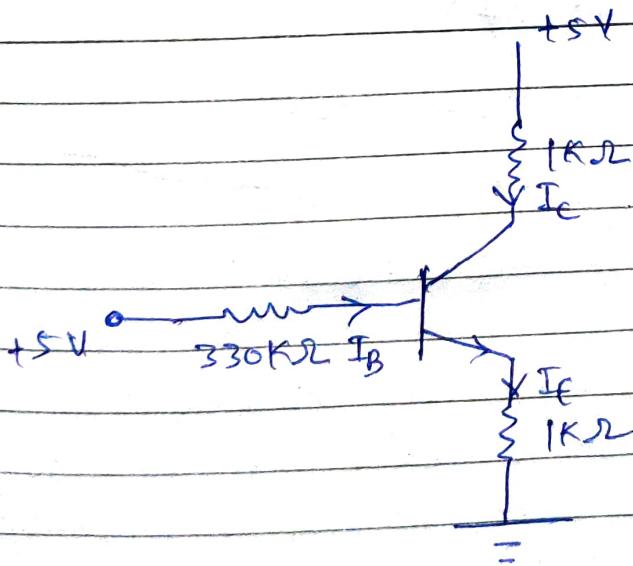Assuming the given npn transistor to be operating in active mode. The circuit can be drawn as



$$\therefore (5V) - (330k\Omega)I_B - V_{BE} - (1k\Omega)I_E = 0$$

Archit Agrawal  
202052307

PAGE: 19  
DATE:

$$(330\text{ k}\Omega) I_B + (10\text{k}\Omega) I_B = 5 - 0.7 \quad \{ \because I_E = (\beta + 1) I_B \}$$

$$\therefore I_B = \frac{4.3}{430\text{ k}\Omega}$$

$$I_B = 0.00998\text{ mA} \\ = 9.98\text{ }\mu\text{A}$$


$$\therefore I_C = \beta I_B = 0.998\text{ mA}$$

$$\text{and } I_E = I_B + I_C = 1.008\text{ mA}$$

$$\therefore V_C = 5 - (1\text{k}\Omega)(0.998\text{ mA}) \\ = 4.002\text{ V}$$

$$\text{and } V_E = I_E R_C = 1.008\text{ V}$$
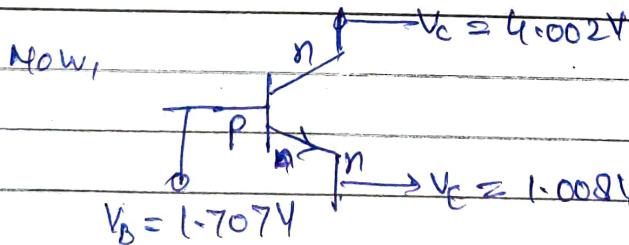
$$\text{and } V_B = 5 - (330\text{k})(0.00998\text{ mA}) \\ = 1.707\text{ V}$$




Clearly, emitter junction is forward biased  
and ~~the~~ collector junction is reverse  
biased. Hence, our assumption is correct.

$$\text{and } I_B = 9.98\text{ }\mu\text{A}$$

$$I_C = 0.998\text{ mA}$$

$$I_E = 1.008\text{ mA}$$

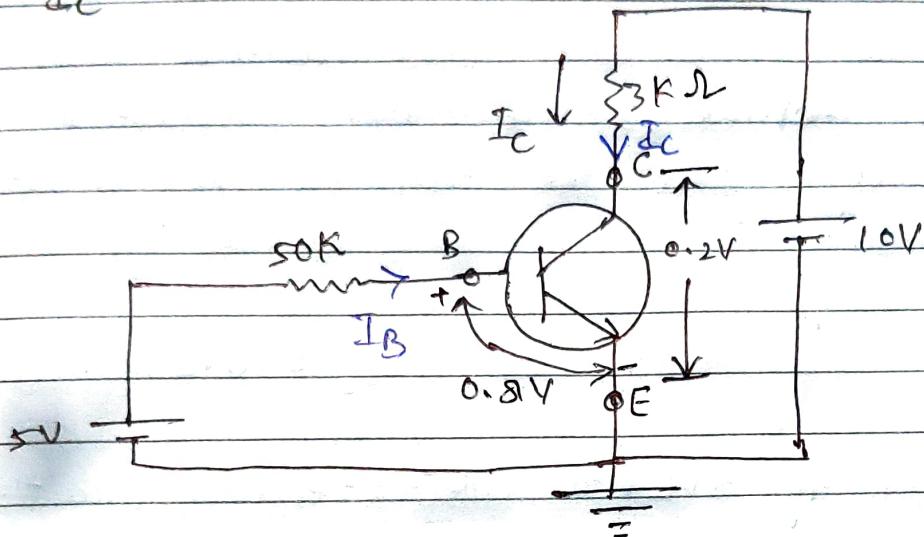Q.12 (Q.4(a) of 4.2) In the figure, if  $B = 100$ , determine whether or not the silicon transistor is in saturation mode and find  $I_B$  and  $I_C$ .



Assuming the transistor to be in ~~saturation~~<sup>active</sup> mode,

Applying KVL to base circuit,

$$5 - (50k)I_B - 0.8 = 0$$

$$I_B = \frac{4.2}{50k} = 0.084 \text{ mA}$$

$$\therefore I_C = B I_B = 8.4 \text{ mA}$$


$$\text{and } I_E = I_B + I_C = 8.484 \text{ mA}$$

$$\therefore V_C = 10 - (3k)I_C = -15.2 \text{ V}$$

$$V_B = 0.8 \text{ V}$$

$$V_E = 0 \text{ V}$$

Now,

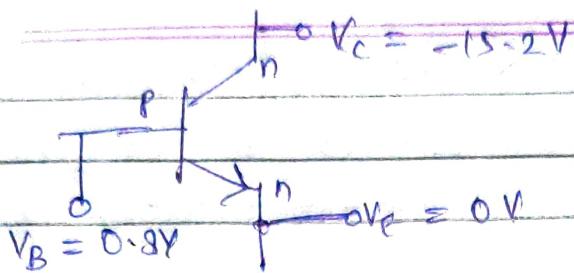

As the emitter-base and collector-base junctions are forward biased, our assumption is wrong and the transistor is in saturation mode.

In saturation mode,  $V_{CE} = 0.2\text{ V}$

Applying KVL to collector-emitter circuit;

$$10 - I_C R_C - 0.2 = 0$$


$$I_C = \frac{9.8}{3k\Omega} = 3.27\text{ mA}$$

$$\therefore I_B = \frac{I_C}{\beta} = \frac{3.27\text{ mA}}{100} = 0.0327\text{ mA}$$

$$I_B = 32.7\text{ }\mu\text{A}$$

$\therefore I_B = 32.7\text{ }\mu\text{A}$  and  $I_C = 3.27\text{ mA}$ .

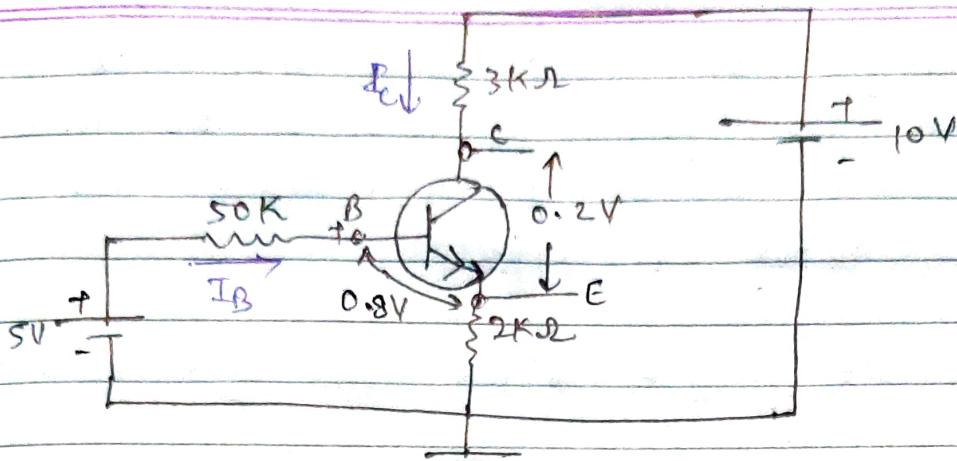Q. 13 (4c) of 4.2) In the figure, if  $\beta = 100$ , determine if transistor is in saturation mode or not and find  $I_B$  and  $I_C$ .



Assuming the transistor to be in active mode,

Applying KVL to base circuit

$$5V - (50k) I_B - 0.8 - (2k\Omega) I_E = 0$$

$$\therefore I_B = \frac{4.2}{(2k)(\beta+1) + 50k} \quad (\because I_E = (\beta+1) I_B)$$

$$I_B = \frac{4.2}{252k} = 0.0167 \text{ mA}$$

$$\therefore I_C = \beta I_B = 1.67 \text{ mA}$$


$$\therefore I_E = 1.6867 \text{ mA}$$

$$\therefore V_E = I_E R_E = 3.373 \text{ V}$$

$$V_C = 10 - I_C R_C = 4.99 \text{ V}$$

$$V_B = V_E + 0.8 = 4.173 \text{ V}$$

Now,

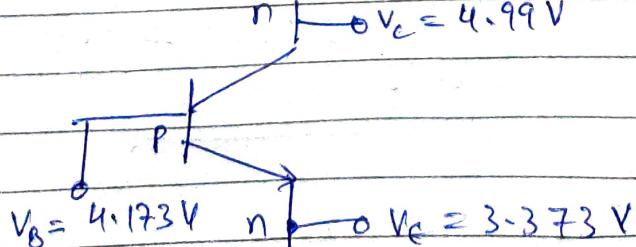

Clearly,  $V_{BE} \geq 0.7$  and  $V_{CB} \geq 0.7$ .  
 Hence, the emitter junction is EB and  
 collector junction is RB. Hence, our  
 assumption is correct.

Therefore,  $I_C = 1.67\text{ mA}$  and  $I_B = 16.7\text{ }\mu\text{A}$ .

Q.14 (Ex 8-3 of 4.2) Determine the values of  
 emitter current and collector current  
 of a transistor having  $\alpha_{DC} = 0.98$  and  
 collector to base leakage current

$I_{CBO} = 4\text{ }\mu\text{A}$ . The base current is  $50\text{ }\mu\text{A}$ .

$$\text{Given } \alpha = 0.98$$

$$\therefore \beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{0.02} = 49$$

$$\text{given } I_{CBO} = 4\text{ }\mu\text{A} \text{ and } I_B = 50\text{ }\mu\text{A}$$

$$\therefore I_C = (\beta + 1)I_{CBO} = 50 \times 4\text{ }\mu\text{A} = 200\text{ }\mu\text{A}$$

$$\text{collector current, } I_C = I_B + I_{CBO}$$

$$= 49 \times 50\text{ }\mu\text{A} + 200\text{ }\mu\text{A}$$

$$= 2650\text{ }\mu\text{A}$$

$$I_C = 2.650\text{ mA}$$

$$\therefore \text{emitter current} = I_B + I_{CBO}$$

$$= 2.650 + 0.05$$

$$I_E = 2.7\text{ mA}$$

Q.15 Calculate  $\beta$  for two transistors for which  $\alpha = 0.99$  and  $0.98$ . For collector currents of  $10mA$ , find the base current of each transistor.

If  $\alpha = 0.99$ ,

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{0.01} = 99$$

$$I_B \text{ (at } \beta=99) = \frac{I_C}{\beta} = \frac{10mA}{99} = 0.101mA$$

$$I_B \text{ (at } \beta=99) = 101\mu A$$

If  $\alpha = 0.98$ ,

$$\beta = \frac{0.98}{0.02} = 49$$

$$I_B \text{ (at } \beta=49) = \frac{I_C}{\beta} = \frac{10mA}{49} = 0.204mA$$

$$I_B \text{ (at } \beta=49) = 204\mu A$$