

[Dashboard](#) / [Courses](#) / [Winter 2021-22](#) / [BTech Semester 4](#) / [CS268](#) / [Assignment 3-25-02-2022](#) / [Assignment 3-25-02-2022](#)

**Started on** Friday, 25 February 2022, 1:50 PM

**State** Finished

**Completed on** Friday, 25 February 2022, 1:54 PM

**Time taken** 4 mins 11 secs

**Marks** 2.00/4.00

**Grade** 5.00 out of 10.00 (50%)

Question **1**

Complete

Mark 1.00 out of 1.00

**Two 1's with a carry-in of 1 are added using a ripple carry adder. What are the outputs?**

- ☒ a. 1,1
- ☐ b. 0,1
- ☐ c. 1,0
- ☐ d. 0,0

Question **2**

Complete

Mark 0.00 out of 1.00

**For  $X = (A \oplus B)C + (A \oplus B)C$  &  $Y = AB + (A \oplus B)C$ , choose the correct option.**

- ☐ a. Are the expressions for the carry look ahead adder
- ☐ b. Are the expressions for the Full subtractor
- ☐ c. Are the expressions for the ripple carry adder
- ☒ d. None of the mentioned

Question **3**

Complete

Mark 0.00 out of 1.00

What is true for the look ahead carry adder?

- ☐ a. All of the mentioned
- ☐ b. **They work by creating two signals P and G known to be Carry Propagator and Carry Generator.**
- ☐ c. **To reduce the computation time, there are faster ways to add two binary numbers by using carry lookahead adders**
- ☒ d. **The carry propagator is propagated to the next level whereas the carry generator is used to generate the output carry ,regardless of input carry.**

Question **4**

Complete

Mark 1.00 out of 1.00

**A half adder is implemented with XOR and AND gates. A full adder is implemented with two half adders and one OR gate. The propagation delay of an XOR gate is twice that of an AND/OR gate. The propagation delay of an AND/OR gate is 1.2 microseconds. A 4-bit ripple-carry binary adder is implemented by using full adders.What is the total propagation time of this 4-bit binary adder in microseconds.**

- ☐ a. **19.5 ms**
- ☒ b. **19.2 ms**
- ☐ c. **19.8 ms**
- ☐ d. **20 ms**

[◀ Assignment 2-18-02-2022](#)

Jump to...

[Assignment 4-04-03-2022 ▶](#)