

EG160: Experiment 2

Ohm's Law

Objective :- To understand Ohm's law, to verify Ohm's law for a simple circuit. To understand and verify Ohm's law for series and parallel combination of resistances.


- To understand Non-ohmic devices.

Theory :- The Ohm's law states that the current through a conductor is directly proportional to the voltage across its terminals.

$$V \propto I$$

where, R is the proportionality constant known as resistance of the conductor.

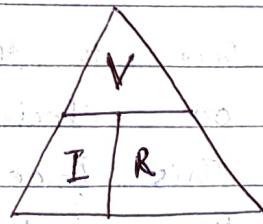In the given figure, the horizontal line represents fraction and vertical line represents multiplication. To find Ohm's law equation in different form, it is convenient to use this figure known as Ohm's law Triangle.



To find V , put V on left hand side of equal to and use other two with the sign between them (represented by line)

this gives, $V = I.R.$

Repeat same to find I and R in terms of other two factors corresponding to them.

Mathematical Proof of Ohm's Law:

To proof Ohm's law mathematically, we have to proof that $\frac{V}{I} = \text{constant}$.

Consider a cylindrical conductor of length l and cross-sectional area A , having n number of electrons per unit volume. Let a potential difference of V be applied at its end.

Assuming the potential drop throughout the conductor is uniform, therefore, electric field E built inside the conductor is

$$E = \frac{V}{l} \quad \text{--- (1)}$$

Due to this electric field a force eE acts on electron in opposite direction to the field. This force produces an acceleration of $\frac{eE}{m}$ and the electron slowly reaches a velocity (v_a) which is almost constant (due to collisions with other electrons and positive ions). Let us assume the average distance and time between two collisions be d and T .

$$\therefore d = \frac{1}{2} \left(\frac{eE}{m} \right) T^2 \quad \text{--- (1)}$$

$$\text{and, } v_a = \frac{d}{T}$$

$$\therefore V_d = \frac{e E T}{2m}$$

(11)

$$V_d = \frac{e T V}{2m l} \quad \text{--- (IV)} \quad \left(\text{from (1) } E = \frac{V}{l} \right)$$

Now, consider a length $V_d \Delta t$ of the conductor.

The volume of this portion is $A V_d \Delta t$. Since free electron density is n , therefore number of free electrons in this region is $n A V_d \Delta t$.

Thus, the charge ΔQ in this area is,

$$\Delta Q = n e A V_d \Delta t$$

Since this charge crosses area A in time Δt , the current is given by,

$$i = \frac{\Delta Q}{\Delta t} = n e A V_d$$


$$i = \frac{n e A e T V}{2m l} \quad \left(\text{from (IV)} \right)$$

$$V = \left(\frac{2m l}{n e^2 T A} \right) i$$

Since, n and T remains constant at a particular temperature, the quantity $\frac{2m l}{n e^2 T A}$ is constant.

Hence, $\frac{V}{i}$ is constant and Ohm's law is proved.

Ohm's law for resistances in Series

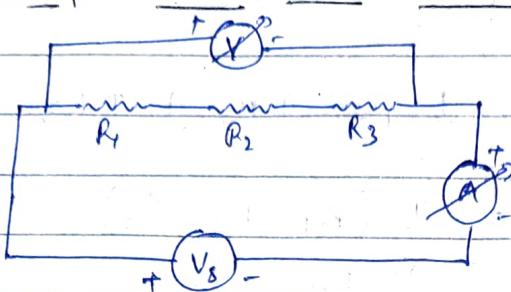

Three resistors are connected in series to a source voltage V_s . Since current in each resistor in a series circuit is same, let this current be I .

The equivalent resistance of the circuit is,

$$R_{eq} = R_1 + R_2 + R_3 \quad (1)$$

$$\therefore \text{current } I = \frac{V_s}{R_{eq}} \Rightarrow V_s = I R_{eq} \quad (II)$$

The source voltage should be equal to the sum of voltage drops across each resistor.

From Ohm's Law,

$$V_1 = IR_1$$

$$V_2 = IR_2$$

$$V_3 = IR_3$$

$$\therefore V_1 + V_2 + V_3 = I(R_1 + R_2 + R_3)$$


$$V_1 + V_2 + V_3 = I R_{eq} \quad (\text{from (1)})$$

$$V_1 + V_2 + V_3 = V_s \quad (\text{from (II)})$$

Hence, Ohm's law is verified for series combination

of resistors.

Ohm's Law for resistances in parallel

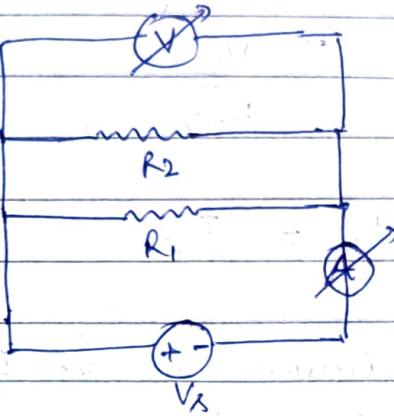

Two resistors are connected in parallel to a source voltage V_s. Since voltage across each resistor in parallel circuit is same, voltage across R₁ and R₂ is V_s.

The equivalent resistance of the circuit is

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (1)$$

∴ total current supplied by source V_s is (I_T) = $\frac{V_s}{R_{\text{eq}}}$ (11)

Let the current through R₁ and R₂ be I₁ and I₂ respectively,

From Ohm's law,

$$I_1 = \frac{V_s}{R_1}$$

$$I_2 = \frac{V_s}{R_2}$$

The total current I_T should be equal to current sum through each resistor,

$$\begin{aligned}\therefore I_1 + I_2 &= \frac{V_s}{R_1} + \frac{V_s}{R_2} \\ &= V_s \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \\ &= \frac{V_s}{R_{eq}}\end{aligned}$$

(from ①)

$$\therefore I_1 + I_2 = I_T \quad \{ \text{from ②} \}$$

Hence, Ohm's law is verified for parallel combination of resistors.

Note-: The devices which do not obey Ohm's law are known as Non-Ohmic devices. In the case of Non-Ohmic devices, the V versus I graph is not linear. Examples of such devices are diodes, thermistors etc.

Procedure to perform the experiment :-

Step-1: Set the value of resistance. Keep it constant throughout the experiment.


Step-2: The voltmeter must be connected in parallel to resistor and ammeter must be connected in series with the resistor.

Step-3: Vary the source voltage and note the readings of Voltage and current using voltmeter and ammeter.

Step-4: Plot the V-I graph for observed readings.

Step-5: V-I graph will come out to be a straight line, which verifies the Ohm's law.

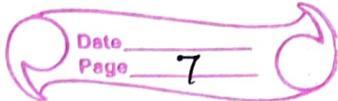Name: Archit Agrawal
Student ID: 202052307
Group: A1



For series combination, voltmeter will be placed parallel to the combination of resistors and ammeter will be in series with resistors.

We have to keep the resistances values fixed and note down the readings to plot the graph.

For parallel combination, ammeter will be placed in series with the combination of resistors and voltmeter will be placed parallel to resistors.

We have to keep the resistances values fixed and note down the readings to plot the graph.

Simulation Results

Virtual Labs
An MHRD Govt of India Initiative

INDIAN INSTITUTE OF TECHNOLOGY
Kharagpur
संस्थान विद्यालय
वर्धन
1951
योग: कर्मसु कौशलम्

INSTRUCTION

Ohm's Law

CONTROLS


DC volt : Volt
 Resistance : Kohms

Add to Table Plot Clear
 Check connection Delete all connection

EXPERIMENTAL TABLE

Resistance: 35 KΩ


4	8	0.229
5	10	0.286
6	13	0.371
7	16	0.457
8	19	0.543
9	22	0.629
10	24	0.686
11	29	0.829

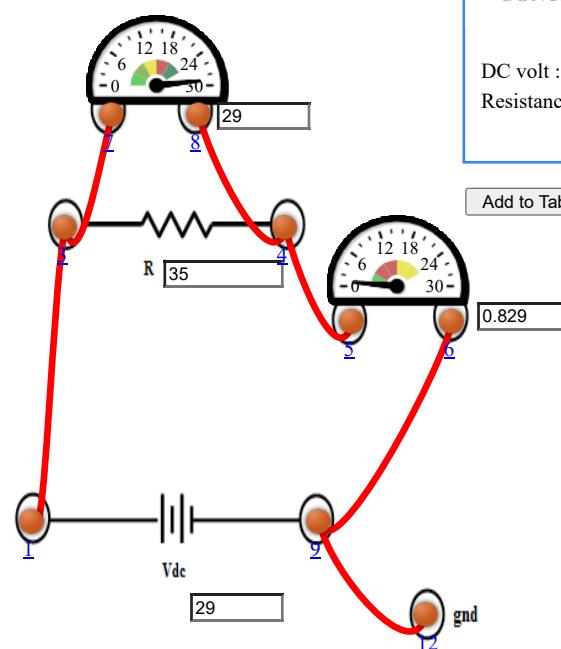

GRAPH PLOT

V-I Plot

Print

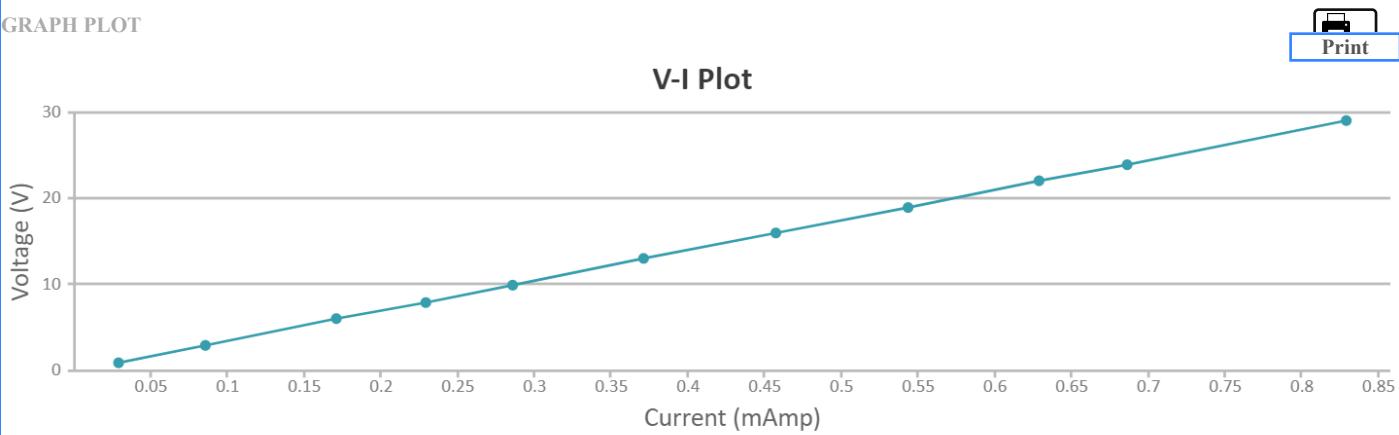

**Virtual
Labs**
An MHRD Govt of India Initiative

INDIAN INSTITUTE OF TECHNOLOGY KHARAGPUR
1951
योगः कर्मसु कारणम्

INSTRUCTION

Ohm's Law Series

CONTROLS


DC volt : Volt
 Resistance1 : Kohr
 Resistance2 : Kohr

 Add to Table Plot Clear Check connection Delete all connection

EXPERIMENTAL TABLE


Resistance(R_1): K Ω Resistance(R_2): K Ω Resistance(R_{eq}): K Ω


3	8	0.167
4	10	0.208
5	13	0.271
6	17	0.354
7	19	0.396
8	23	0.479
9	27	0.563
10	30	0.625

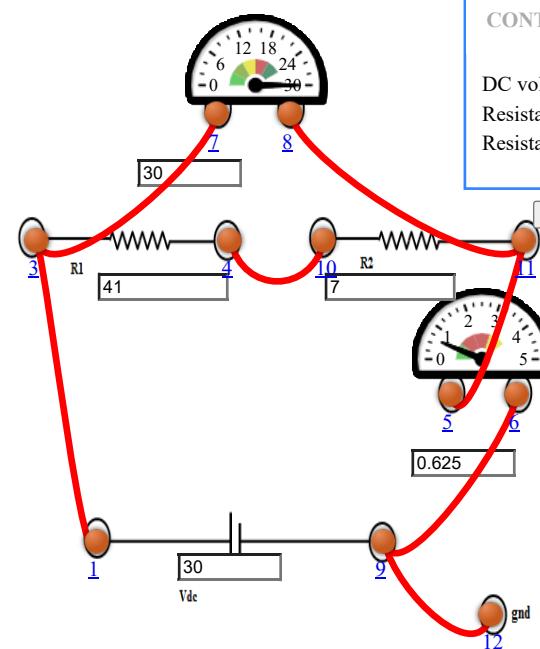

GRAPH PLOT

V-I Plot

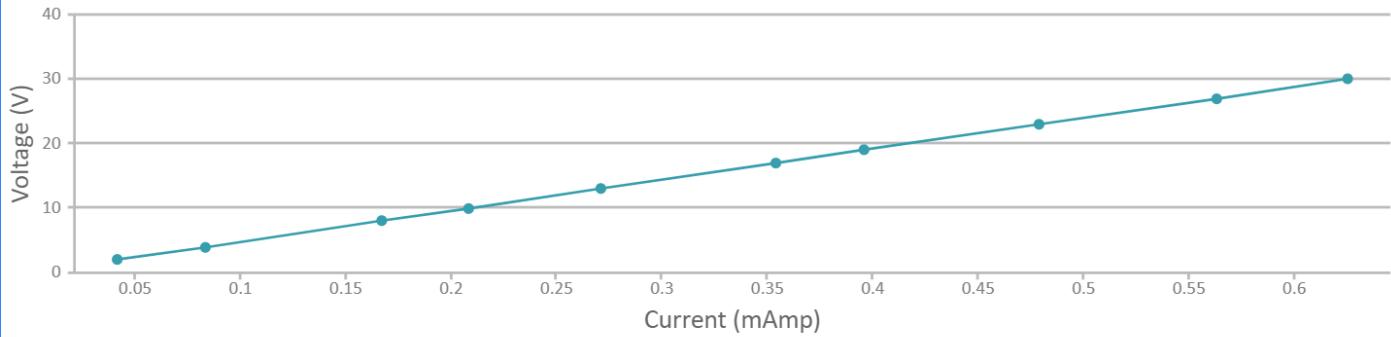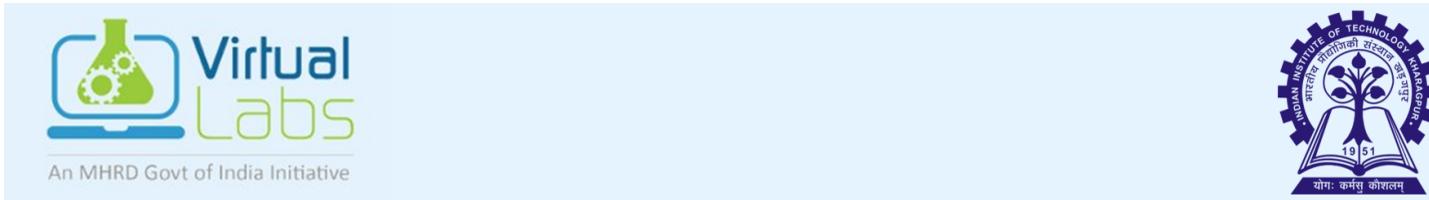 PrintCopyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)




INSTRUCTION

EXPERIMENTAL TABLE

Resistance(R_1): 1110 Ω Resistance(R_2): 13 K Ω Resistance(R_{eq}): 0.129984 Ω

3	6	5.87
4	9	8.80
5	13	12.7
6	17	16.6
7	21	20.5
8	25	24.4
9	28	27.4
10	30	29.3

Ohm's Law Parallel

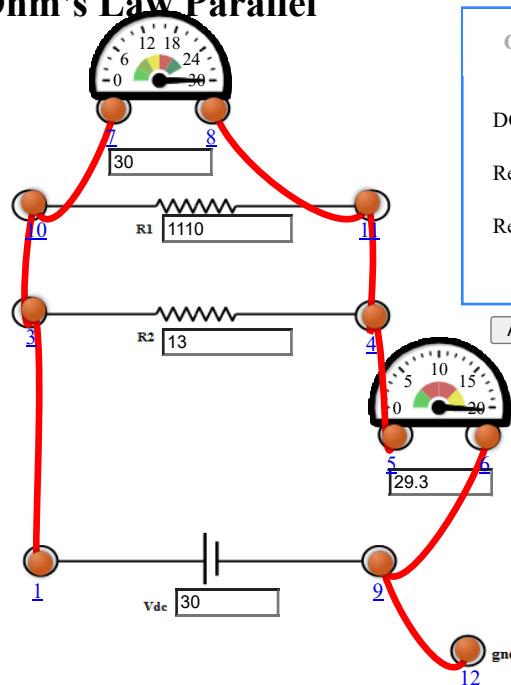


CONTROLS

DC volt : VResistance1 : Resistance2 :

GRAPH PLOT

V-I Plot

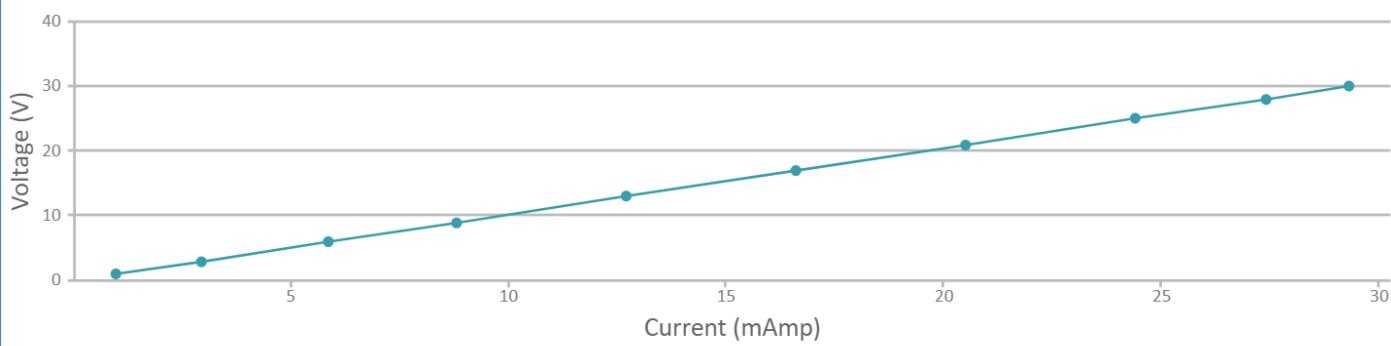

Copyright © 2011 Indian Institute of
Technology Kharagpur, [Licensing Terms](#)

Virtual Labs
An MHRD Govt of India Initiative


INSTRUCTION**Non Ohmic Device****CONTROLS**

DC volt : Vol
 Resistance : Ko


Add to Table Plot C

EXPERIMENTAL TABLE

5	0.487	0.135	37
6	0.483	0.119	42
7	0.479	0.102	49
8	0.477	0.0926	54
9	0.474	0.0820	61
10	0.471	0.0735	68
11	0.469	0.0685	73

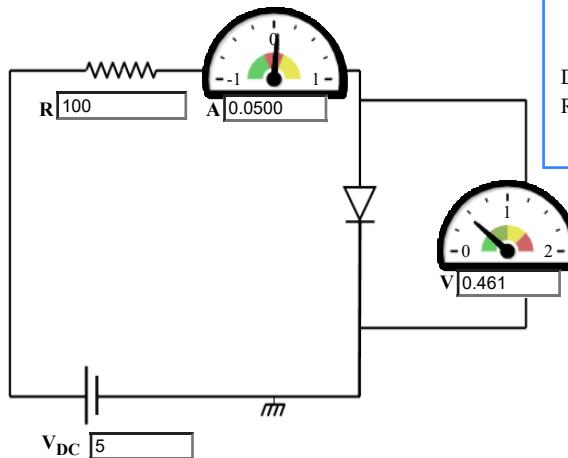**GRAPH PLOT****V-I Plot**

Print

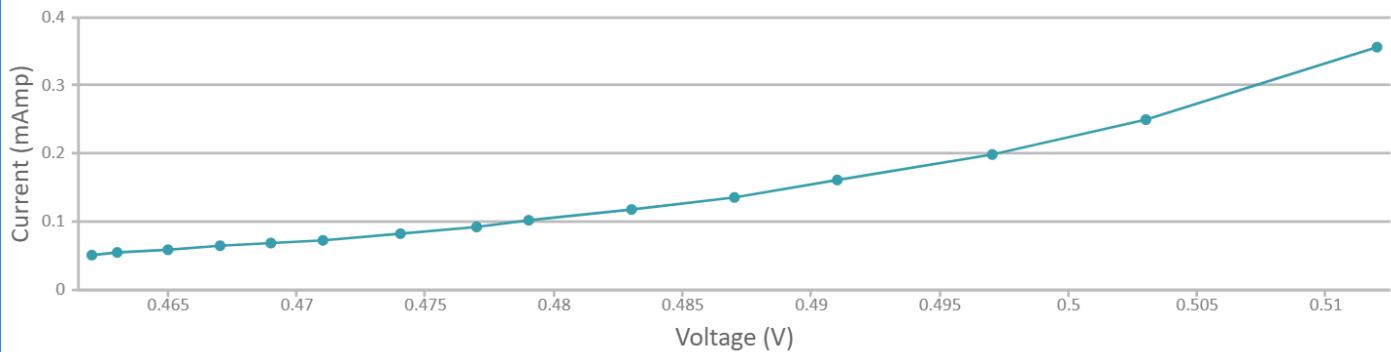

Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)

Conclusion:- Performing the experiment in the simulator, following conclusions can be drawn,

- The V-I graph is observed to be linear for resistor, which verifies that the current through a resistor is directly proportional to the voltage difference across its terminals. Hence, resistor is an Ohmic device.
- The V-I graph is observed to be a curve for a diode. Hence, current through a diode is not directly proportional to the voltage across its terminals. Hence, diode is a Non-ohmic device.

Quiz Performance

BASIC ELECTRONICS VIRTUAL LABORATORY (../INDEX.HTML)

Home (../index.html) > Basic Electronics Lab (./index.html) > Ohms Law (index.html)

Ohms Law


[THEORY \(#\)](#)

[PROCEDURE \(#\)](#)

[SIMULATION \(#\)](#)

[QUIZ \(#\)](#)


[ASSIGNMENT \(#\)](#)

[REFERENCES \(#\)](#)

Quiz

Test Your Knowledge!!

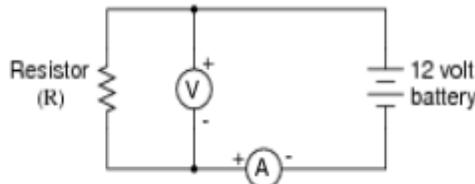- ✓ 1. What is the value of this resistor, in ohms



Voltmeter indication = 12.3 volts
Ammeter indication = 4.556 millamps


270 Ω

27 k Ω

2700 k Ω

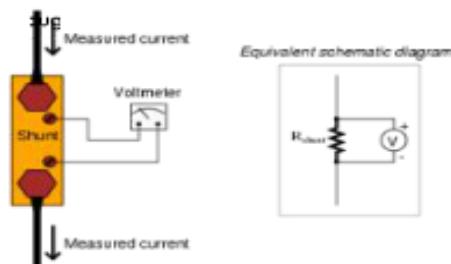2.7 k Ω

- ✓ 2. Shunt resistance is labeled with the following rating: 150 A , 50 mV. What is the resistance of this shunt, in ohms?



Shunt resistors are often used as current-measuring devices, in that they are designed to drop very precise amounts of voltage as large electric currents pass through them. By measuring the amount of voltage dropped by a shunt resistor, you will be able to determine the amount of current going through it:

333.3 $\mu\Omega$

33.33 m Ω

3.333 Ω



3.333 mΩ

- ✓ 3. If doubling the voltage across a resistor doubles the current through the resistor then



the resistor value decreased



the resistor value did not change



the resistor value increased



it is impossible to determine the change in the resistor

value

- ✓ 4. If the voltage across a fixed value of resistance is increased five times, what does the current do?



Not enough information



It decreases by a factor of five.




It stays the same.



It increases by a factor of five

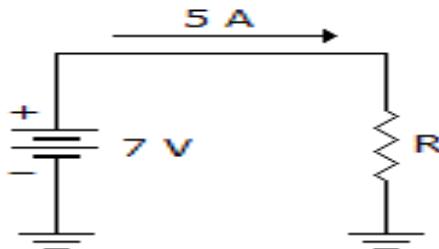- ✓ 5. What is the power in the given circuit?



3.6 W



245 W




175 W



35 W

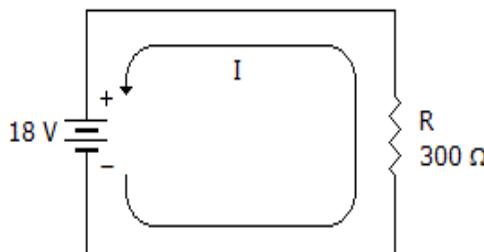- ✗ 6. If the voltage in the given circuit was cut in half, what would the current equal?



30 mA



60 mA



10 mA




90 mA

- ✓ 7. Resistance and current are _____.



inversely proportional

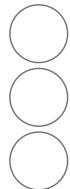

directly proportional

not related

similar to voltage

Submit

Copyright © 2011 Indian Institute
of Technology Kharagpur,
[Licensing Terms](#)
([..//license/index.html](#)).