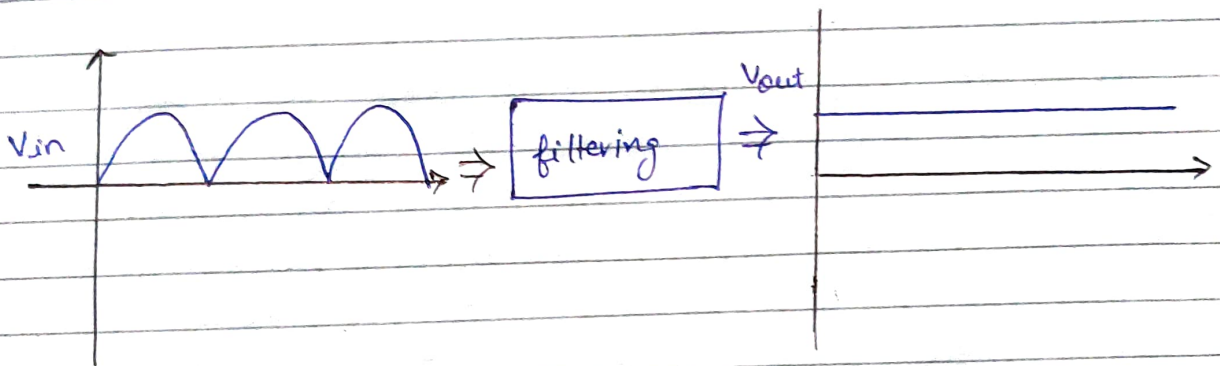


## EC160: Experiment 6 Capacitive Rectification

Objectives - i) to learn and understand filtering of rectified signal.

- (ii) to study ripple voltage and ripple factor.
- (iii) to understand capacitive filtering.

Theory: Filtering in rectifiers -




~~After~~ After filtering the pulsating input is converted to a constant DC power supply. Thus, we would like to "filter" the pulsating input signal.

We can do this by splitting the input waveform into AC (high frequency) and the DC components (very low frequency) and by then "rejecting" the high frequency components.

Capacitor filter circuit and its working:

When a capacitor is connected across the output of a rectifier, the AC components will face a low impedance path to ground and, therefore,

will not appear in the output.

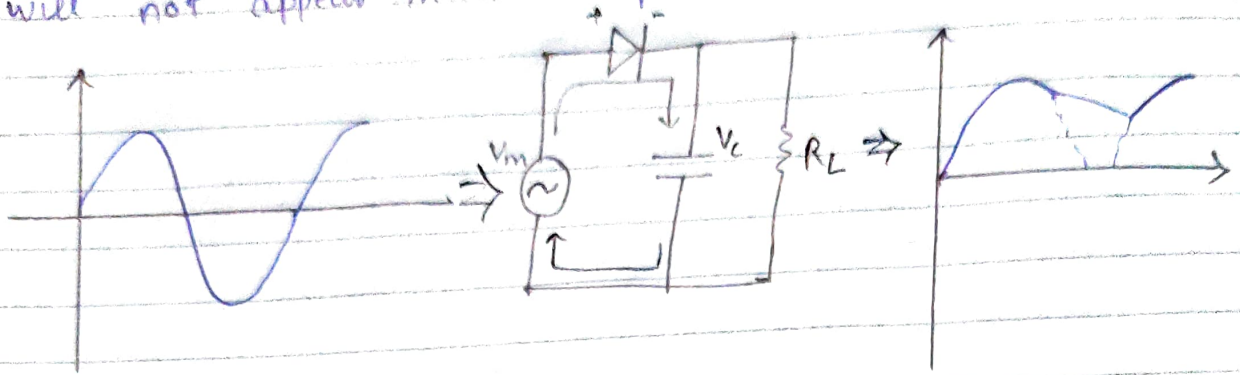


Working:-

In forward bias-


a) When the input begins to decrease below its peak, the capacitor retains its charge and the diode becomes reverse biased during the remaining part, the capacitor can discharge only through load resistance at a rate determined by RC time constant. Larger the time constant, the less the capacitor will discharge.

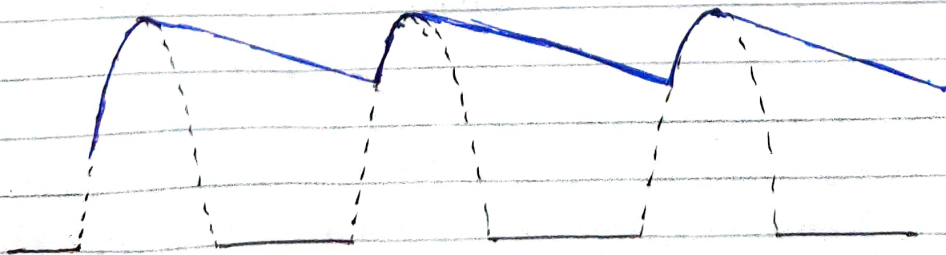b) The diode will again become forward biased when the input voltage exceeds the capacitor voltage by approximately 0.7V.

Half-Wave VS Full-Wave Capacitive Rectification



Half wave rectification + filtering

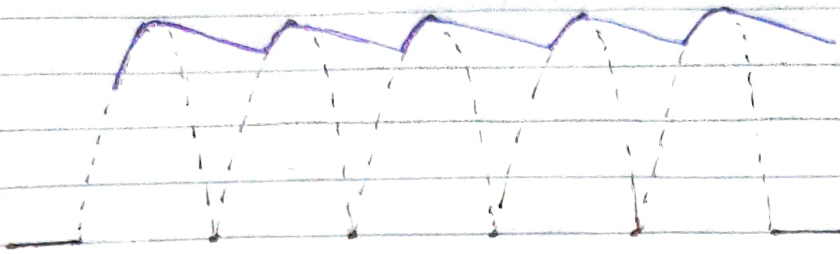

### Full-Wave Rectification + Filtering

The advantage of a full-wave rectifier over a half-wave is quite clear. The capacitor can more effectively reduce the ripple factor when the time between the peaks is shorter.

### Mathematical Expressions:-

For half-wave rectification

$$V_{av} = \frac{V_m}{\pi} \quad \text{and} \quad I_{av} = \frac{I_m}{\pi}$$

$$\text{Form factor (FF)} = \frac{V_{rms}}{V_{av}} = \frac{\pi}{2} = 1.57$$

$$\text{Ripple factor } (\gamma) = \sqrt{(FF)^2 - 1} = 1.21$$

$$\text{RMS load voltage} = \frac{V_m}{2}$$

$$\text{RMS load current} = \frac{I_m}{2}$$

$$\text{Efficiency} = \frac{P_{out}}{P_{in}} \times 100\% = 40.56\%$$



for full-wave rectification

$$V_{av} = \frac{2V_m}{\pi} \quad \text{and} \quad V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{av} = I_{dc} = \frac{2I_m}{\pi} \quad \text{and} \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\text{Form factor (FF)} = 1.11$$

$$\text{Ripple factor } (\gamma) = \sqrt{(FF)^2 - 1} = 0.482$$

$$\begin{aligned} \text{Efficiency } (\eta) &= \frac{P_{out}}{P_{in}} \times 100\% \\ &= 81.3\% \end{aligned}$$

Procedure for the Experiment:-

for half-wave rectification:-

- Step 1: Take a diode, a load resistor of  $1\text{ k}\Omega$  and a capacitor of  $102\text{ }\mu\text{F}$ .
- Step 2: Connect to AC voltage source of  $50\text{ Hz}$ ,  $2\text{ V}$ .
- Step 3: Click on 'ON' button to make the circuit on.
- Step 4: Click on 'sine wave' button to observe the input waveform.
- Step 5: Click on 'Run Simulation' button to observe the filtered waveform.
- Step 6: Observe the corresponding waveform.  
Channel 1 shows input waveform, 'channel 2' shows output waveform and 'Dual' shows both of them simultaneously.


### For full-wave rectifier

- Step 1: Take 4 diodes, load resistance of  $1\text{K}\Omega$  and capacitor of  $102\text{ }\mu\text{f}$ .
- Step 2: Connect to AC voltage source of  $50\text{ Hz}$ ,  $220\text{ V}$ .
- Step 3: Click on 'ON' button to make circuit on.
- Step 4: Click on 'sine wave' to get input waveform.
- Step 5: Click on 'Run Simulation' to observed filtered waveform.
- Step 6: Observe the waveforms.

## Simulation Results

## Capacitive Rectification for Half Wave Rectifier

### INSTRUCTION

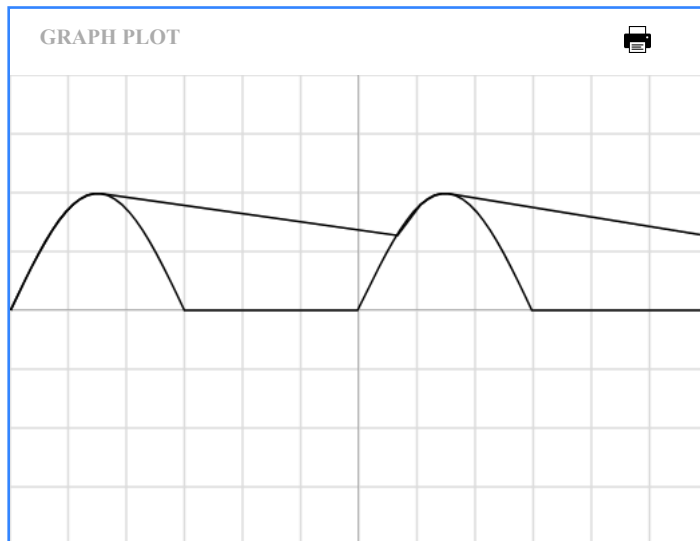

### CALCULATION


Measure the  $V_m$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{dc} = \frac{V_m}{\pi}$$

$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \frac{\sqrt{(V_{rms}^2 - V_{dc}^2)}}{V_{dc}}$$

### CIRCUIT

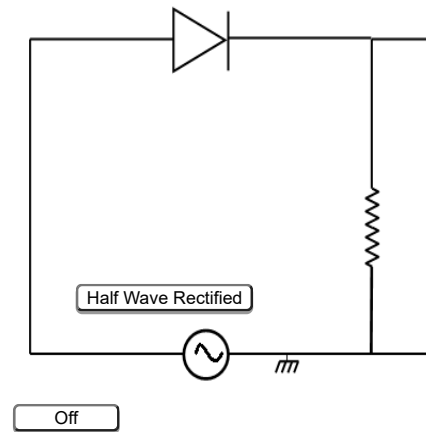


### CONTROLS

$V_{Pch1}$ :  1  
 Position Y-Axis:  0  
 Phase:  0  
 Frequency:  1000  
 $V_{Pch2}$ :  1  
 Position Y-Axis:  0  
 Phase:  0  
 Frequency:  1000

## Capacitive Rectification for Half Wave Rectifier

### INSTRUCTION

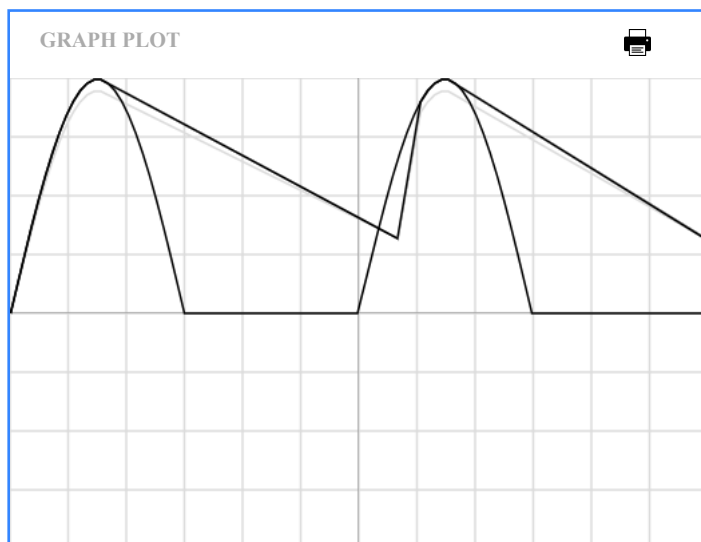

Channel 1

Channel 2

Ground

Dual

### CALCULATION




Measure the  $V_m$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{dc} = \frac{V_m}{\pi}$$

$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \frac{\sqrt{(V_{rms}^2 - V_{dc}^2)}}{V_{dc}}$$

### CIRCUIT

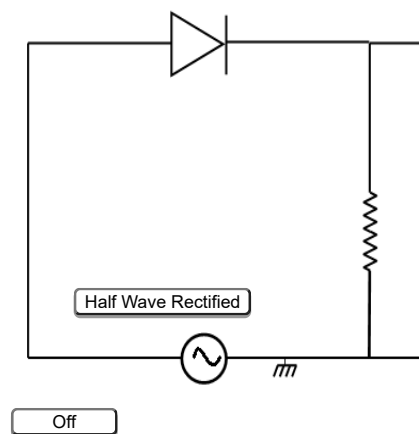

### CONTROLS

$V_{Pch1}$ :  2

Position Y-Axis:  0

Phase:  0

Frequency:  1000

$V_{Pch2}$ :  2


Position Y-Axis:  0

Phase:  0

Frequency:  1000

## Capacitive Rectification for Full Wave Rectifier

### INSTRUCTION

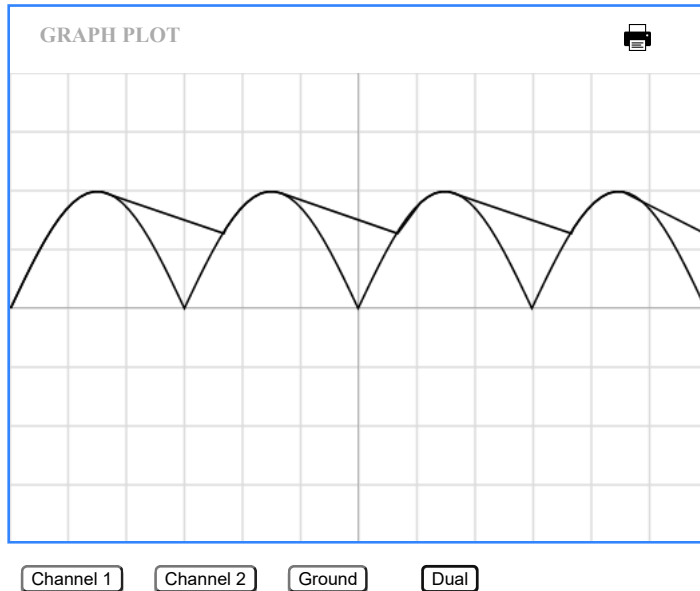

### CALCULATION


Measure the  $V_m$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{dc} = \frac{V_m}{\pi}$$

$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \frac{\sqrt{(V_{rms}^2 - V_{dc}^2)}}{V_{dc}}$$

### CIRCUIT

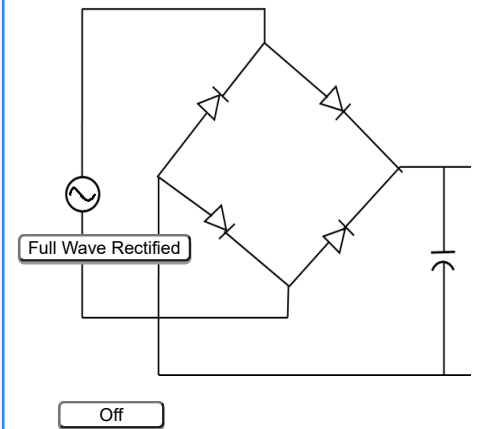


### CONTROLS

$V_{Pch1}$ :  1  
 Position Y-Axis:  0  
 Phase:  0  
 Frequency:  1000  
 $V_{Pch2}$ :  1  
 Position Y-Axis:  0  
 Phase:  0  
 Frequency:  1000



## Capacitive Rectification for Full Wave Rectifier

### INSTRUCTION

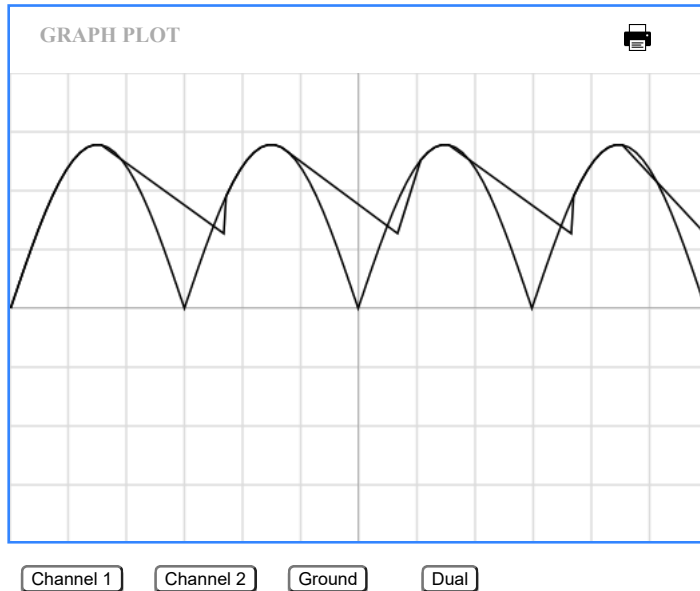

**CALCULATION**


Measure the  $V_m$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{dc} = \frac{V_m}{\pi}$$

$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \frac{\sqrt{(V_{rms}^2 - V_{dc}^2)}}{V_{dc}}$$

### CIRCUIT

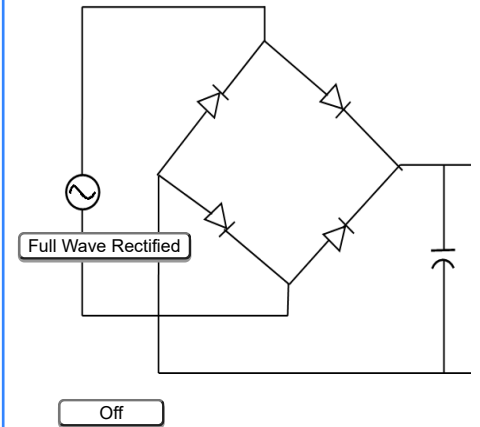

### CONTROLS

$V_{Pch1}$ :  1.4

Position Y-Axis:  0

Phase:  0

Frequency:  1000

$V_{Pch2}$ :  1.4

Position Y-Axis:  0

Phase:  0

Frequency:  1000

Conclusion:- Performing the experiment, following conclusions can be drawn:-

- (i) Filtering implies converting pulses to a constant dc supply.
- (ii) Filtering can be done using a capacitor.
- (iii) The efficiency of rectifiers increases on using capacitive filters.
- (iv) In full-wave bridge rectifiers, when capacitor filter is used, the current ripple is reduced more than then in a half-wave rectifier.
- (v) The capacitor can reduce the ripple factor more efficiently when the time between peaks is lesser.

# Quiz Performance

## BASIC ELECTRONICS VIRTUAL LABORATORY (../INDEX.HTML)

Home (../../index.html)\_0 &gt; Basic Electronics Lab (../index.html) &gt; Capacitive Rectification (index.html)

# Capacitive Rectification

[THEORY \(#\)](#)[PROCEDURE \(#\)](#)[SIMULATION \(#\)](#)[QUIZ \(#\)](#)[REFERENCES \(#\)](#)

## Quiz

Test Your Knowledge!!

- ✓ 1. A half wave rectifier circuit produces a peak rectified voltage output  $V_{RM} = 9V$ . The AC signal frequency  $f = 50Hz$ . The load Resistance = 12 k?. If the ripple voltage  $V_r$  is to be limited to 0.2V, then the filter capacitor C is

☐25 $\mu$ F☐50 $\mu$ F☒75 $\mu$ F☐100 $\mu$ F

- ✓ 2. A full wave rectifier circuit produces a peak rectified voltage output  $V_{RP} = 10V$ . The AC signal frequency is 50Hz. The load resistance is 10 k?. If the ripple voltage is to be limited to  $V_r = 0.1V$  then the filter capacitor C is

☐10 $\mu$ F☐20 $\mu$ F☐50  $\mu$ F☒100 $\mu$ F