

Student ID: 202082307

Name: Ankit Agarwal

Sign: ankit agarwal

Page No. 1

Date: 24/3/2021

End Sem Exam: Basic Electronic Circuit

i. Given $R_f = 120\Omega$

peak to peak of input sine wave = 24 V

∴ peak input voltage $V_m = 12 V$

and $R_L = 1.76 k\Omega$

v_c , cut-in voltage for $S^o = 0.7 V$

$$(i) \therefore \text{DC output voltage} = \frac{2(V_m - 2v_c) \times R_L}{(R_s + 2R_f + R_L)}$$

$$= \frac{2(12 - 1.4) \times 1760\Omega}{(240\Omega + 1760\Omega)}$$

$$\boxed{\text{dc output voltage} = 5.94 V}$$

$$(ii) \text{rms output voltage} = \frac{I_m R_L}{\sqrt{2}}$$

$$= \frac{(V_m - 2v_c) \times R_L}{\sqrt{2}(R_s + 2R_f + R_L)}$$

$$= \frac{(12 - 1.4) \times 1760\Omega}{\sqrt{2}(240\Omega + 1760\Omega)}$$

$$= 6.59 V$$

$$(iii) \text{rectification efficiency} \eta = \frac{81.2\%}{1 + \frac{R_s + 2R_f}{R_L}}$$

Student ID: 202052307

Name: Archit Agrawal

Sign: /fclt agrawal

Page No. 2

Date: 24/3/2021

$$\eta = \frac{81.2\%}{\left(1 + \frac{240}{1760}\right)}$$

$$\text{Value of } \eta = 71.456\%$$

V.P. 1 - V.P. 2 = initial height - final height

Initial height = 4.5 m

Final height = 3.5 m

$$71.456\% \times (4.5 - 3.5) = \text{initial height} - \text{final height}$$

$$71.456\% \times (4.5 - 3.5) = 8.1\%$$

Initial height = 4.5 m

| V.P. 2 - initial height |

Initial height = 4.5 m

3.5

$$71.456\% \times (4.5 - 3.5)$$

$$(4.5 - 3.5) \times 71.456\%$$

$$71.456\% \times (4.5 - 3.5) =$$

$$(4.5 - 3.5) \times 71.456\%$$

| V.P. 2 |

4.5 m

(4.5 - 3.5) m

1 m

Student ID : 2020S2307

Name : Archit Agrawal

sign : felut agrawal

Page No. 3

Date : 24/3/2021

(2)



the diode is reverse biased

let resistance of the diode be R .

given reverse saturation current = 100nA .

$$\therefore i = 100\text{nA}$$

$$2 - iR - i(10M) = 0$$


$$(R + 10M) = \frac{2}{100\text{nA}}$$

$$R + 10^7 = 2 \times 10^7$$

$$R = 10^7 \Omega$$

Answer

3.

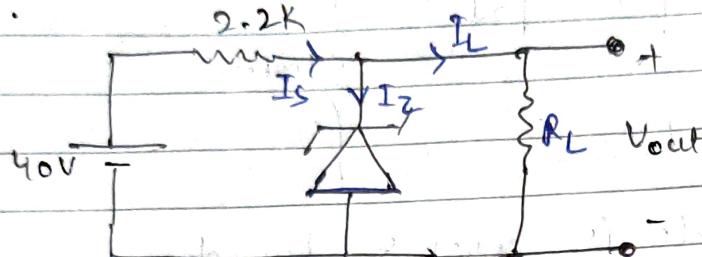

Given: $V_Z = 8V$

$$I_{Z(\min)} = 500 \mu A = 0.5mA$$

$$I_{Z(\max)} = 12mA$$

Voltage across zener diode = 8V

$$\therefore I_s = \frac{(40 - 8)}{2.2K} = 14.545mA$$

Using KVL,

$$I_s = I_Z + I_L$$

The maximum current through load resistor is

$$\begin{aligned} I_{L(\max)} &= I_s - I_{Z(\min)} \\ &= 14.545mA - 0.5mA \\ &= 14.045mA \end{aligned}$$

and minimum current through load resistor is

$$I_{L(\min)} = I_s - I_{Z(\max)}$$

$$\begin{aligned} &= 14.545mA - 12mA \\ &= 2.545mA \end{aligned}$$

Name: Archit Agrawal

Setor: archit agrawal

$$\text{Since } I_L = \frac{V_Z}{R_L} \Rightarrow R_L = \frac{V_Z}{I_L}$$

$$\therefore R_{L(\min)} = \frac{V_Z}{I_{L(\max)}} = \frac{8}{14.045 \text{ mA}}$$

$$= 569.59 \Omega$$


$$\text{and } R_{L(\max)} = \frac{V_Z}{I_{L(\min)}} = \frac{8}{2.545 \text{ mA}}$$

$$= 3.143 \text{ k}\Omega$$


Hence, the range of load resistor so that the zener diode operates in breakdown region is 569.59Ω to $3.143 \text{ k}\Omega$.

4.

(i) DC analysis of first stage

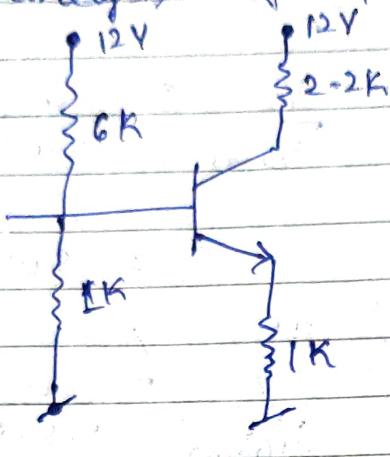


The circuit can be redrawn as

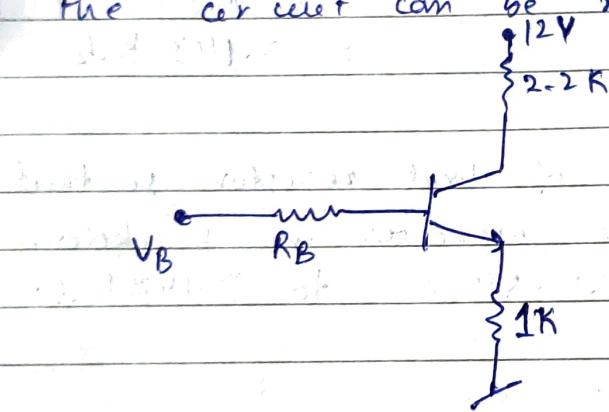

$$V_B = \frac{12 \times 1k}{1k + 6k} = \frac{12}{7} V$$
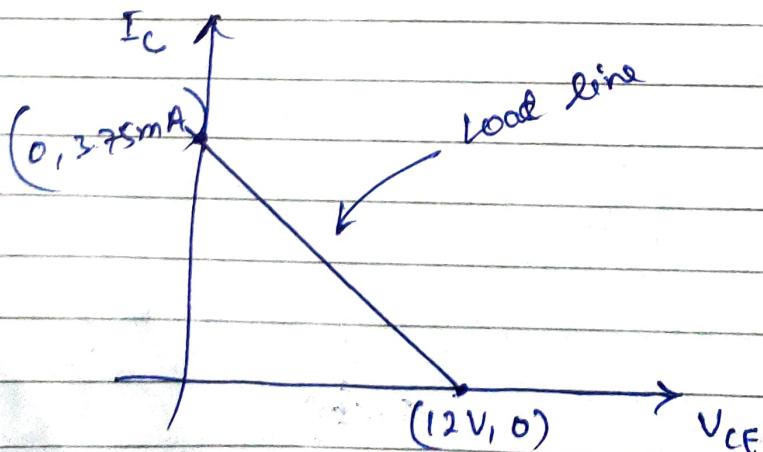
$$R_B = (1k \parallel 6k) = \frac{6}{7} k\Omega$$



Name: Archit Agrawal
 Sigma & faculty formulae

In the circuit if $V_{CE} = 0$,

$$I_C = \frac{12}{3.2\text{ k}} = 3.75 \text{ mA}$$

and if $I_C = 0$,

$$V_{CE} = 12 \text{ V}$$

Hence, load line is shown in figure.

(ii) Using KVL in base-emitter circuit,

$$V_B - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_B = \frac{\frac{12}{7} - \frac{7}{10}}{\frac{6\text{ k} + (10)(1\text{ k})}{7}}$$

$$I_B = \frac{1.014}{101.85\text{ k}} = 0.00995 \text{ mA}$$

$$\therefore I_C = 0.995 \text{ mA}$$

$$I_E = 1.0049 \text{ mA}$$

$$\therefore V_C = 12 - (2.2\text{ k})(0.995 \text{ mA}) \\ = 9.811 \text{ V}$$

$$V_E = (1\text{ k})(1.0049 \text{ mA}) = 1.0049 \text{ V}$$

$$V_B = \frac{12}{7} - (0.00995)(\frac{6}{7}\text{ k}) \\ = 1.7057 \text{ V}$$


Clearly, transistor is in active region.

and Q point is (V_{CE}, I_C)

$$\begin{aligned} V_{CE} &= 9.811 - 1.0049 \\ &= 8.8061 \text{ V} \end{aligned}$$

∴ Q point is $(8.8061 \text{ V}, 0.995 \text{ mA})$

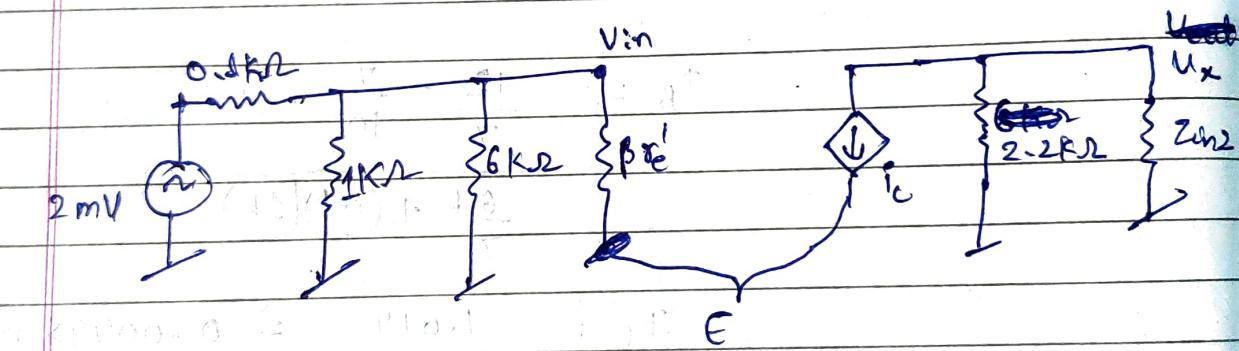(iii) Using AC analysis and π model of transistor the circuit can be redrawn as



Input resistance


$$R_{in} = \beta n V_T = 5174.6 \Omega$$

Input impedance for Stage 1.

$$Z_{in1} = (1 \text{ k}\Omega) \parallel (6 \text{ k}\Omega) \parallel (5.174 \text{ k}\Omega)$$

$$(1 \text{ k}\Omega) \parallel (6 \text{ k}\Omega) = 0.73 \text{ k}\Omega$$

Student ID: 202052307

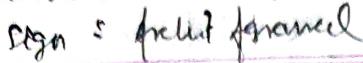Name: Archit Agrawal
Sign: 

Page No. 9
Date 24/3/2021

(iv) $A_v = \frac{R_C || Z_{in2}}{r_e}$

$$Z_{in2} = \frac{(8\text{ k}\Omega) || (1\text{ k}\Omega) || (\beta \times r_e)}{= 0.73\text{ k}\Omega}$$

$$\therefore A_v = \frac{(2.2\text{ k}) || (0.73\text{ k})}{51.746}$$

$$A_v = \frac{0.5482\text{ k}}{51.746}$$

$$A_v = 10.59$$

RW,

$$0.4545 \\ + 1.3698$$

$$1.824$$

∴ for first stage $A_v = 10.59$


(v) voltage at input (V_{in}) $= \frac{2\text{ mV} \times (Z_{in})_1}{(Z_{in})_1 + R_B}$

$$= 0.948\text{ V}$$

$$\therefore V_{in} = 10.59 \times 0.948$$

~~10.81?~~

$$= 10.039\text{ V}$$

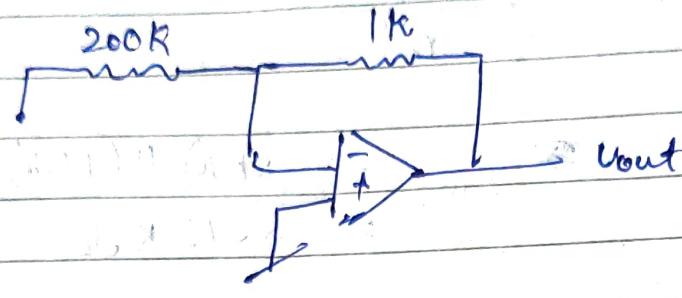5.

$$A_{oi} = 2 \times 10^5$$

For non ideal Op Amp

$$R_2 = 1K$$

$$R_1 = 200K$$

$$A = \frac{U_{out}}{V_{in}} = \frac{R_2 / R_1}{1 + \left[\left(1 + \frac{R_2}{R_1} \right) / A_{oi} \right]}$$

$$\frac{1K}{200K} = \frac{-1K}{200K} \cdot \frac{1 + \left(\left(1 + \frac{1K}{200K} \right) / 2 \times 10^5 \right)}{1 + \left(\left(1 + \frac{1K}{200K} \right) / 2 \times 10^5 \right)}$$

$$= \frac{5 \times 10^{-3}}{1 + (5.025 \times 10^{-6})}$$

$$= 4.999 \times 10^{-3}$$

student ID : 202052307


Name : Archit Agrawal

Regn : archit agrawal

Page No. U

Date 24/3/2021

Q.

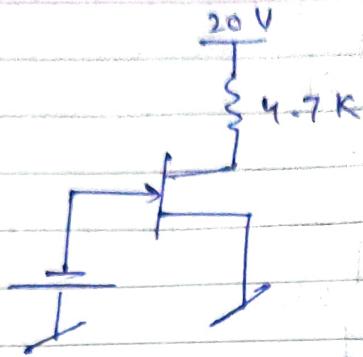

The drain current.

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = (10 \text{ mA}) \left(1 - \frac{2}{4} \right)^2$$

$$I_D = 2.5 \text{ mA}$$

$$\text{and } V_P = 20 - (4.7 \text{ k}) (2.5 \text{ mA}) \\ = 8.25 \text{ V}$$