

## EC160: Experiment 4

### Half-Wave Rectification

Objective :- To understand rectification and to study the working of a half-wave rectifier.


Theory :- A rectifier is a device that converts an oscillating two-directional alternating current (AC) into a single-directional direct current (DC).

Rectifiers are essentially of two types:-


- (i) Half-Wave Rectifier
- (ii) Full-Wave Rectifier
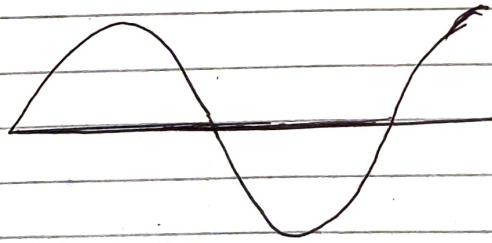
#### Half-Wave Rectifier

The diagram below illustrates the basic principle of a half-wave rectifier.



Input Signal

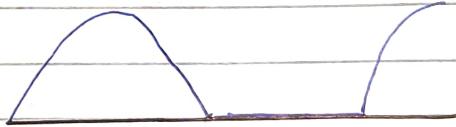


Output signal

Half-wave rectifiers allow only one half of AC voltage through and will block the other half-cycle.


A half-wave rectifier consists of three main parts

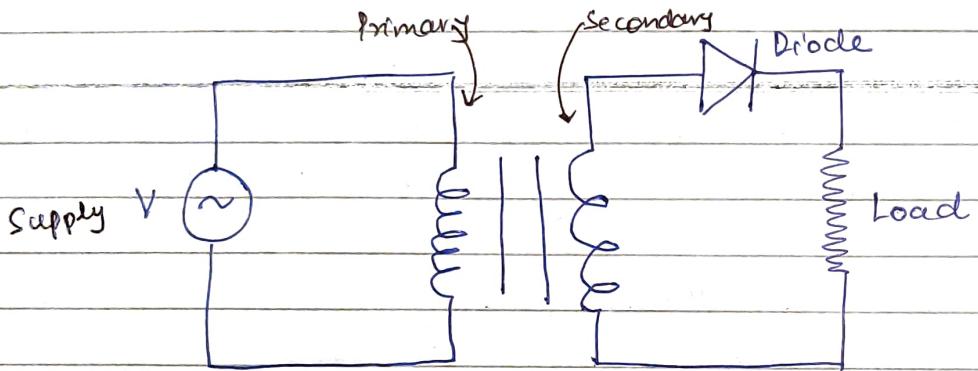- i) A transformer
- ii) A diode
- iii) A resistive load


A half-wave circuit diagram looks like this:



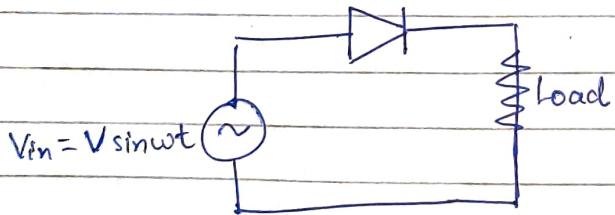An AC voltage is applied to the primary of transformer and an AC voltage  $V_{in}$  is available across the diode. Therefore, the circuit can be redrawn as



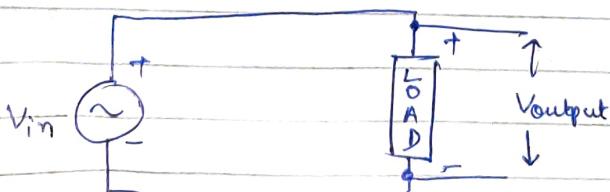
For the positive half-cycle of the AC source voltage, the equivalent circuit effectively becomes



Name: Archit Agrawal  
Student ID: 2020852307


This is because the diode is forward biased and hence allowing current to pass through. Therefore, for positive half-cycle the output voltage across the load ( $V_{output}$ ) is equal to input voltage.

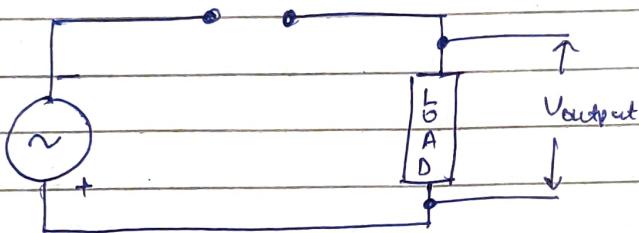But for the negative half-cycle of AC source voltage, the equivalent circuit becomes



this is because the diode is now reverse biased and hence no current flows through it. Therefore, for negative half-cycle the output voltage across the load ( $V_{output}$ ) is zero.

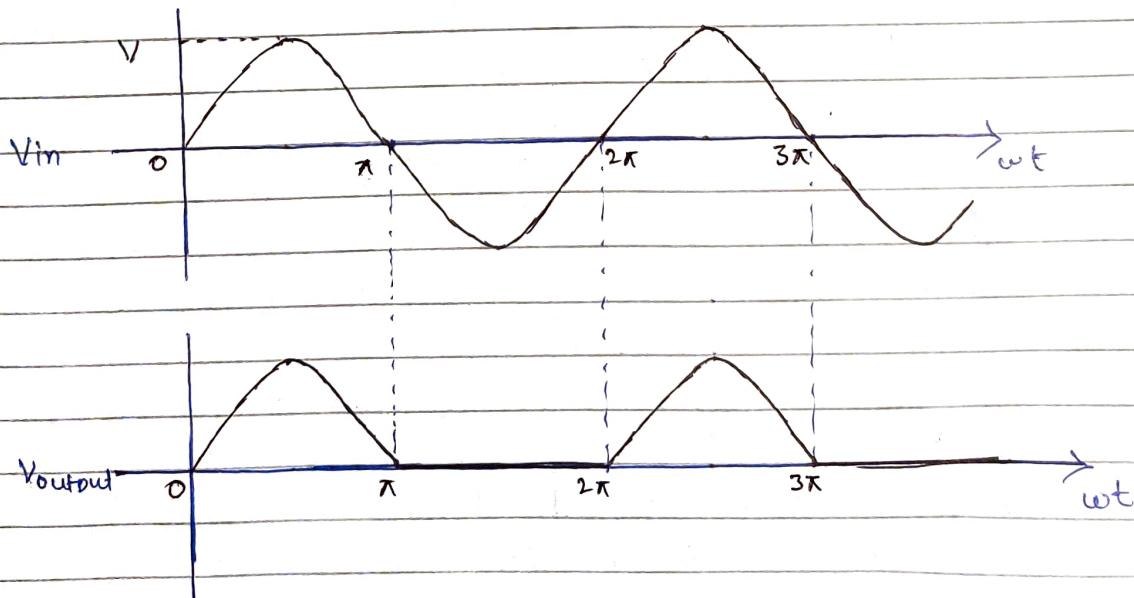The waveform of input and output voltage is drawn below



The waveform drawn is of a positive half-wave rectifier. A positive half-wave allows only positive half-cycles to flow through the diode while a negative half-wave rectifier allows only negative half-cycles to flow through the diode.

### Mathematical Expressions

for an ideal half-wave rectifier,

output voltage ( $V_{\text{output}}$ ) in positive half-cycle =  $V_{\text{in}}$

output voltage ( $V_{\text{output}}$ ) in negative half-cycle = 0

$$V_{\text{output}} = \begin{cases} V \sin \omega t & : \text{for positive half-cycles} \\ 0 & : \text{for negative half-cycles} \end{cases}$$

- Average output voltage :- It is the average voltage across the load for one cycle.

$$\text{average output voltage} = \frac{\int_0^{\pi} V \sin \theta d\theta + \int_{\pi}^{2\pi} 0 d\theta}{2\pi}$$

$$= -V \left[ (\cos \theta) \right]_0^{\pi}$$

$$= \frac{2V}{2\pi} = \frac{V}{\pi}$$

$$V_{\text{avg}} = 0.318 V$$

Hence, the average output voltage is 0.318 times of the maximum voltage  $V$ .

• RMS Load Voltage :-

$$V_{rms} = \sqrt{\frac{\int_0^{\pi} V^2 \sin^2 \theta d\theta + \int_0^{\pi} 0 d\theta}{2\pi}}$$

$$V_{rms} = \sqrt{\frac{V^2 \int_0^{\pi} \left(\frac{1 + \cos 2\theta}{2}\right) d\theta}{2\pi}}$$

$$= \sqrt{\frac{V^2}{2} \left( \theta + \frac{\sin 2\theta}{2} \right) \Big|_0^{\pi}}$$

$$= \sqrt{\frac{V^2}{4\pi} (\pi)}$$

$$= \frac{V}{2}$$

$$\therefore V_{rms} = \frac{V}{2}$$

• Average load current :-

$$I_{avg} = V_{avg}/R$$

where R is resistance of load.

$$\therefore I_{avg} = 0.318 V/R$$

• RMS load current :-

$$I_{rms} = \frac{V_{rms}}{R}$$

$$= \frac{V}{2R}$$

Name: Archit Agrawal  
Student ID: 202052307

- Form factor of Half Wave Rectifier

Form factor (F.F.) is the ratio between RMS value and average value (either of voltage or current)

$$\therefore F.F. = \frac{V_{rms}}{V_{avg}}$$

$$= \frac{0.5V}{0.318V} = 1.57$$

Hence, FF for a half-wave rectifier is 1.57.

- Ripple factor: The ripple is the ratio between the RMS value of AC voltage (on the input side) and the DC Voltage (on the output side) of the rectifier.

$$\delta = \sqrt{\left(\frac{V_{rms}}{V_{DC}}\right)^2 - 1}$$

The ripple factor for half-wave rectifier is 1.21.

- Efficiency: Rectifier efficiency is the ratio between output DC power and input AC power.

$$\text{Efficiency } (\eta) = \frac{\text{Output Power}}{\text{Input power}}$$

The efficiency of a half-wave rectifier is equal to 40.6%.

Name: Archit Agrawal  
Student ID: 202052307

- Peak Inverse Voltage: Peak Inverse Voltage (PIV) is the maximum voltage that the diode can withstand during reverse bias condition.

$$\text{Peak Inverse Voltage (PIV)} \geq V$$

### Procedure for the Experiment:

Step 1: Set the resistance  $R_L$ .

Step 2: Click on 'ON' Button to start the experiment.

Step 3: Click on 'sine wave' button to generate input waveform.

Step 4: Click on 'Oscilloscope' button to get rectified output.

Step 5: Vary the amplitude, frequency, volt/div using the controllers.

Step 6: Click on 'dual' to observe both waveforms.

(Channel 1 shows input waveform and channel 2 shows output rectified waveform)

## Simulation Results


&lt;




## Half Wave Rectifier

### INSTRUCTION

#### OSCILLOSCOPE

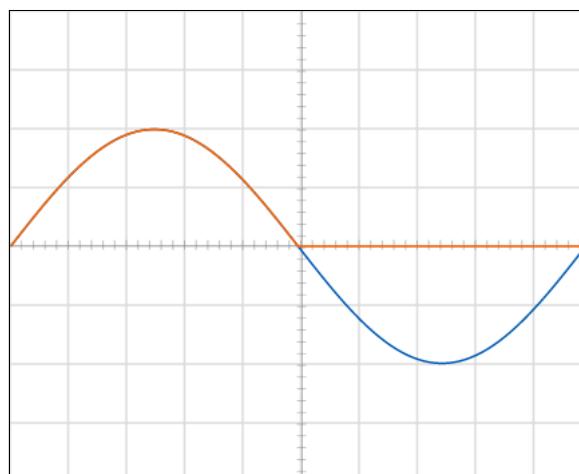

Channel 1 Channel 2 Ground Dual

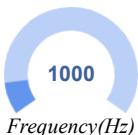

#### CALCULATION


$$V_{rms} = \frac{V_m}{2}, V_m \text{ is the peak voltage}$$

$$V_{dc} = \frac{V_m}{\pi}$$


$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$$

Peak Current: 6.49999989269141 mA

### CIRCUIT

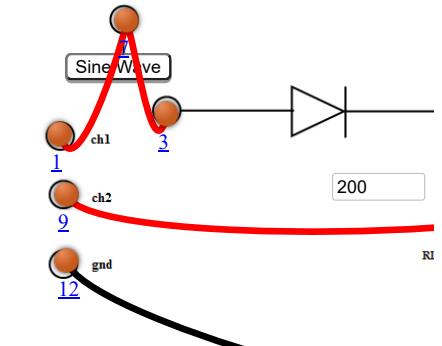

### CONTROLS

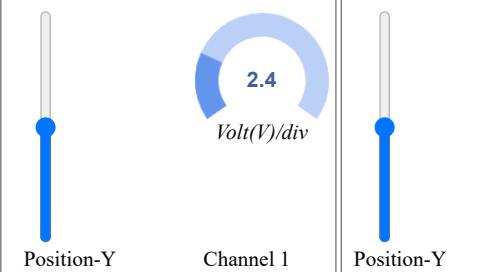

Virtual Oscilloscope Tutorial : [Virtual Osc](#)

Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)


&lt;



## Half Wave Rectifier

### INSTRUCTION

#### OSCILLOSCOPE

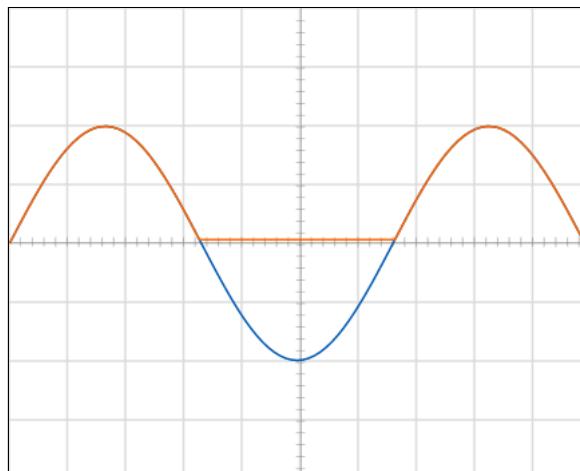

Channel 1 Channel 2 Ground Dual

1500  
Frequency(Hz)

2  
Amplitude(Volt)

#### CALCULATION


$$V_{rms} = \frac{V_m}{2}, V_m \text{ is the peak voltage}$$

$$V_{dc} = \frac{V_m}{\pi}$$



$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$$

Peak Current: 6.49999989269141 mA

### CIRCUIT

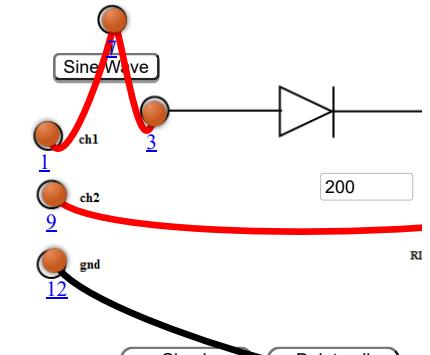

### CONTROLS

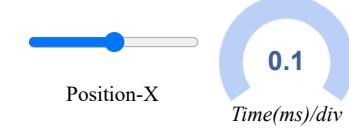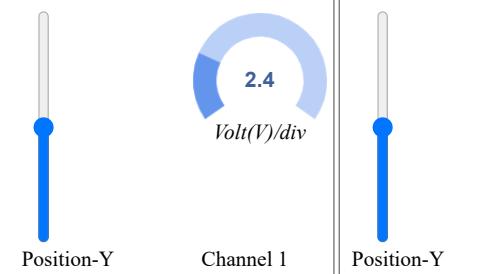

Virtual Oscilloscope Tutorial : [Virtual Osc](#)

Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)


&lt;




## Half Wave Rectifier

### INSTRUCTION

#### OSCILLOSCOPE

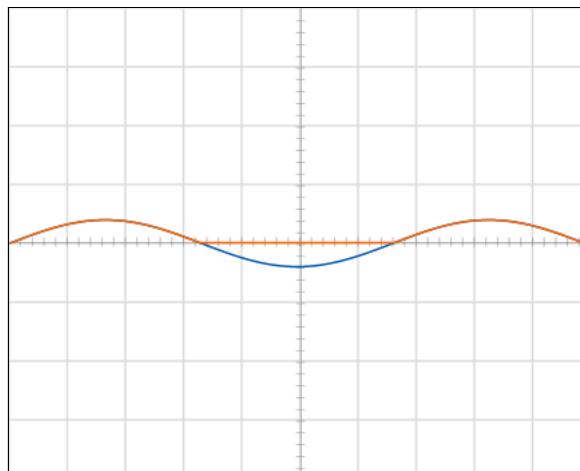

Channel 1 Channel 2 Ground Dual

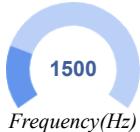

#### CALCULATION

$$V_{rms} = \frac{V_m}{2}, V_m \text{ is the peak voltage}$$


$$V_{dc} = \frac{V_m}{\pi}$$

$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$$



Peak Current: 6.49999989269141 mA



### CIRCUIT

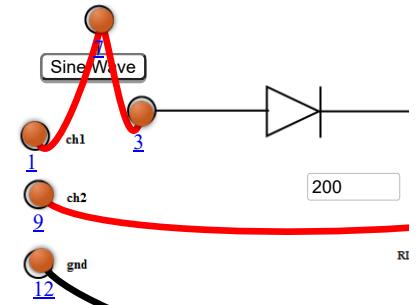

### CONTROLS

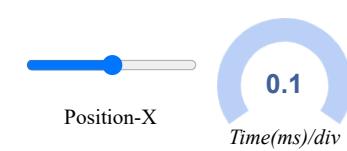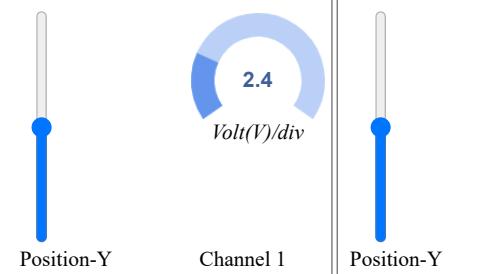

Virtual Oscilloscope Tutorial : [Virtual Osc](#)

Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)


&lt;



## Half Wave Rectifier

### INSTRUCTION

#### OSCILLOSCOPE

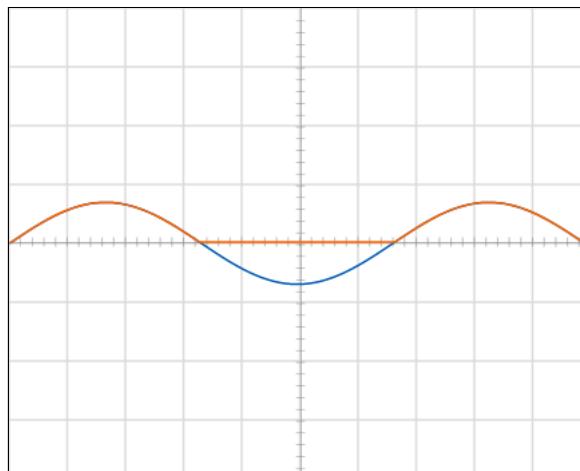

Channel 1 Channel 2 Ground Dual

**1500**  
Frequency(Hz)

**1**  
Amplitude(Volt)

#### CALCULATION




$$V_{rms} = \frac{V_m}{2}, V_m \text{ is the peak voltage}$$

$$V_{dc} = \frac{V_m}{\pi}$$


$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$$

Peak Current: **6.49999989269141** mA

### CIRCUIT

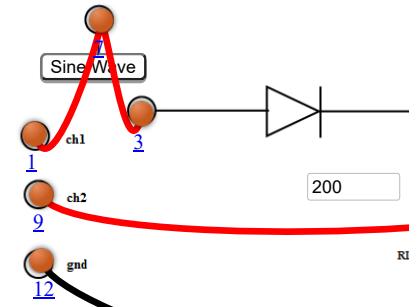

### CONTROLS

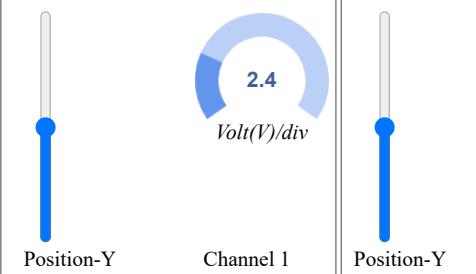

Virtual Oscilloscope Tutorial : [Virtual Osc](#)

Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)


&lt;



## Half Wave Rectifier

### INSTRUCTION

#### OSCILLOSCOPE

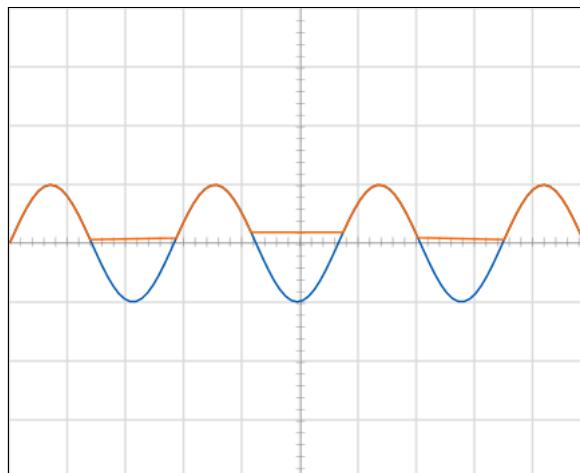

Channel 1 Channel 2 Ground Dual



#### CALCULATION


$$V_{rms} = \frac{V_m}{2}, V_m \text{ is the peak voltage}$$

$$V_{dc} = \frac{V_m}{\pi}$$

$$\text{Ripple Factor} = \frac{V_{ac}}{V_{dc}} \quad \text{Since, } V_{ac} = \sqrt{(V_{rms}^2 - V_{dc}^2)}$$

Peak Current: 6.49999989269141 mA

### CIRCUIT

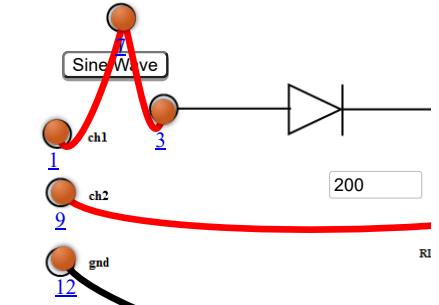

### CONTROLS



Position-Y



Channel 1

Position-Y

Virtual Oscilloscope Tutorial : [Virtual Osc](#)

Copyright © 2011 Indian Institute of Technology Kharagpur, [Licensing Terms](#)

Name: Archit Agrawal  
Student ID: 202052307

Conclusion :- Performing the above experiment we came to following conclusions:-

- i) Rectifier is a device which converts an AC current/voltage to a DC current/voltage.
- ii) Half-wave rectifier is a device which converts half of the input <sup>AC</sup> signal to an output DC signal.
- (iii) The form factor and ripple factor of an ideal half-wave rectifier are 1.57 and 1.21 respectively.
- (iv) The efficiency of an ideal half-wave rectifier is 40.6%.

## Quiz Performance

## BASIC ELECTRONICS VIRTUAL LABORATORY (../INDEX.HTML)

Home (../index.html) > Basic Electronics Lab (../index.html) > Half Wave Rectification (index.html)

# Half Wave Rectification


[THEORY \(#\)](#)

[PROCEDURE \(#\)](#)

[OSCILLOSCOPE](#)

[SIMULATION \(#\)](#)

[QUIZ \(#\)](#)

[REFERENCES \(#\)](#)
[TUTORIAL \(#\)](#)

### Quiz

Test Your Knowledge!!

- ✓ 1. What is the Ripple factor of a half wave rectifier?

0.31

0.48

0.707

1.21;

- ✓ 2. The peak applied signal voltage is  $V_m$  then for a half wave rectifier circuit the PIV(Peak Inverse Volatge) of the diode should be:

$> 2V_m$

$\leq 2V_m$

$\geq V_m$

$< V_m$

- ✓ 3. An ideal Si diode is used in a half wave rectifier circuit with peak input sinusoidal signal amplitude of 5V ( $V_m = 5V$  &  $V_T = 0.7V$ ). The average dc voltage is

$< 1.27V$

$= 1.37V$

$> 1.87V$