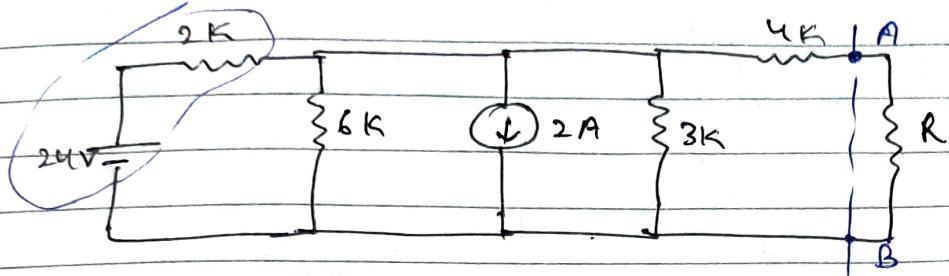


Student ID : 202052307
Name : Archit Agrawal
Sign : archit agrawal

Page No. 1
Date : 28/11/2021


EC Remote Exam




Roll Number is 202052307

$$\therefore R = 17 \text{ k}\Omega$$

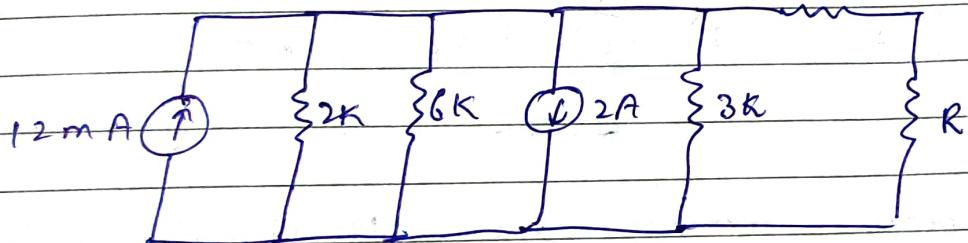Let's perform source transformation as shown




This can be transformed to

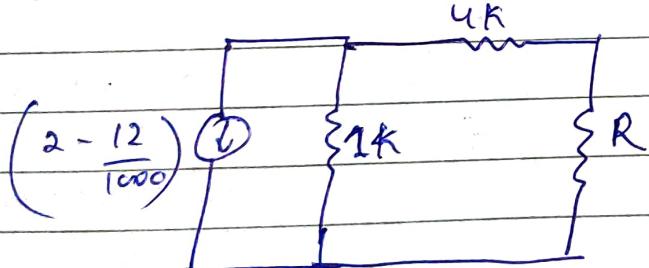



Now we get current equivalent $I_N = \left(2 - \frac{12}{1000}\right)$ A

and the R_N will be calculated by doing


Voltage \rightarrow short circuit, open circuit \rightarrow current

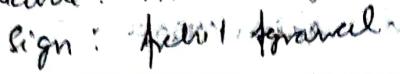Student ID : 202052307
Name : Archit Agrawal.
Sign : 

Page No. 2
Date : 28/1/2021

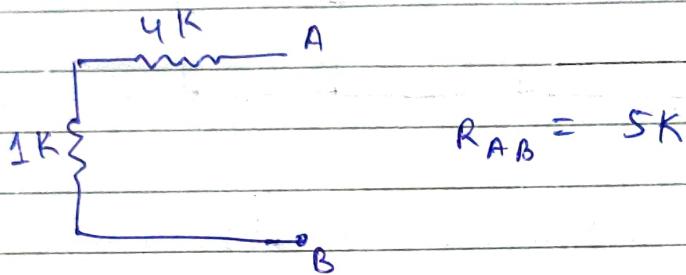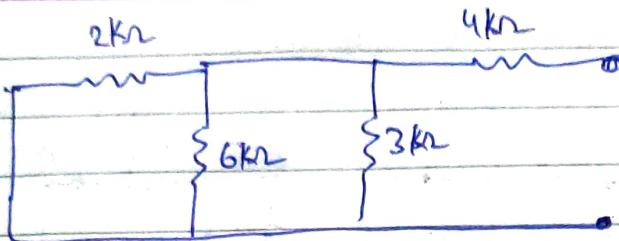


so we can write norton equivalent

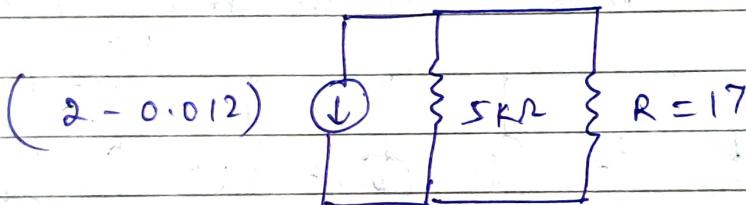

Now, voltage across $17k\Omega$ is 1.988 V
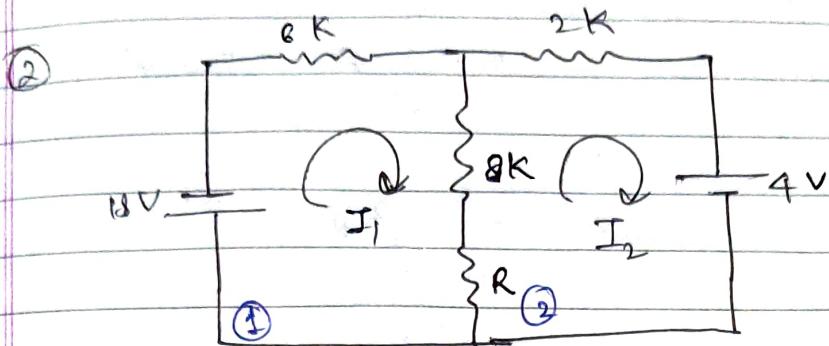
$$\begin{aligned}\therefore \text{current } I &= \frac{V}{R} \\ &= \frac{1.988}{17 \times 10^3} = 0.11694 \text{ A} \\ &= 116.94 \text{ mA}\end{aligned}$$



Let I_1 and I_2 be current in mesh 1 and mesh 2.

Applying KVL in mesh 1,

$$-18 - 6I_1 - (8+R)(I_1 - I_2) = 0 \quad \textcircled{I}$$

Applying KVL in mesh 2,

$$-2I_2 - 4 - (I_2 - I_1)(R+8) = 0 \quad \textcircled{II}$$

earn ①, ($\because R = 17\text{K}$)

$$18 + 6I_1 + 25(I_1 - I_2) = 0$$

$$31I_1 - 25I_2 + 18 = 0 \quad \textcircled{III}$$

earn ④,

$$2I_2 + 4 + (I_2 - I_1)(25) = 0$$

$$-25I_1 + 27I_2 + 4 = 0 \quad \textcircled{IV}$$


Solving ③ and ④,

$$I_1 = \frac{-293}{106}$$

$$\text{and } I_2 = \frac{-287}{106}$$

Student ID: 20210352307

Name: Archit Agrawal

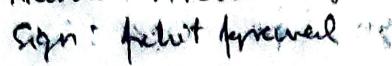Sign: 

Page No. 4

Date: 20/1/2021

$$\text{current through } R_1 = I_1 - I_2 \\ = \frac{-6}{106} A = \frac{-3}{53} A$$

$$\therefore \text{Power consumed} = I^2 R \\ = \frac{9}{53 \times 53} \\ = 0.0544 W \\ = 54.4 \text{ mW}$$

④



25 μm → Si doped with N_D

$$J = \alpha m A / (\mu m)^2$$
$$= 17 \text{ mA} / (\mu m)^2$$

$$V_{ext} = 21 \text{ V}$$

$$J = q n_D \mu E$$

$$\mu_D = \frac{J}{q n_D E} = \frac{17 \times 10^{-3} \text{ A}/(\mu\text{m})^2}{1.6 \times 10^{-19} \times 1300 \times 10^{-6} (\mu\text{m})^2 / \text{V} \times \frac{21}{25 \mu\text{m}}}$$

$$N_D = \frac{17 \times 10^{-3} \times 25}{1.6 \times 10^{-19} \times 1300 \times 10^{-6} \times 21}$$

$$N_D = 0.0097 \times 10^{22}$$

$$N_D = 9.7 \times 10^{19} \text{ atoms/cm}^3$$

Student ID: 202052307

Name: Archit Agrawal

Sign: Archit Agrawal

Page No. 6

Date: 28/1/2021

(5)

$$X \text{ is } = 5 + 2 + 3 + 0 + 7 = 17$$

$$\text{Now, } V_o = V_T \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

$$\text{So } V_o' = V_T \left(\frac{N_A \times 17 N_D}{n_i^2} \right)$$

$$V_o' - V_o = V_T \ln \left(\frac{N_A \cdot N_D}{n_i^2} \right) \quad \{ \ln 17 + 1 \}$$

$$= V_T \ln \left(\frac{N_A \cdot N_D}{n_i^2} \right) (1.83)$$

$$V_o' - V_o = V_T \ln \left(\frac{N_A + N_D}{n_i^2} \right) + V_T \ln(17) - V_T \ln \left(\frac{N_A + N_D}{n_i^2} \right)$$

$$= V_T \ln(17)$$

$$= 2.83 V_T$$

$$V_T \text{ at } 300K = 0.026 V$$

$$\boxed{V_o' - V_o = 0.026 \times 2.83 \\ = 0.07358 V}$$

- 10 Given V_1, V_2, V_3, V_4, V_5 are inputs
 V_o is output

We know that for an inverting circuit we have

$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

Again applying the inverting circuit :-

$$V_o = \frac{R_f}{R_1} \left(\frac{R_c}{R_b} \right) + V_2 \frac{R_c}{R_b} \frac{R_f}{R_2} - V_3 \frac{R_c}{R_3} - V_4 \frac{R_c}{R_4}$$

Given that $R_f = R_2 = 10 \text{ k}\Omega$

Given,

$$V_o = \frac{V_1}{X} - 3V_2 + 10V_3 - \frac{V_4}{X} + 6V_5$$

$$V_o = \frac{V_1}{X} + 10V_3 + 6V_5 - 3V_2 - \frac{V_4}{X}$$

where,


$$\frac{R_c}{R_b} = 3, \quad \frac{R_c}{R_b} = \frac{1}{X} \quad (02) \quad \frac{1}{15}$$

$$\frac{R_c}{R_a} \times \frac{10 \text{ k}\Omega}{R_1} = \frac{1}{X} \quad (02) \quad \frac{1}{15}$$

$$\frac{R_c}{R_a} \times \frac{10 \text{ k}\Omega}{R_3} = 10$$


$$\frac{R_c}{R_a} \times \frac{10 \text{ k}\Omega}{R_5} = 6$$

Circuit would be something like this

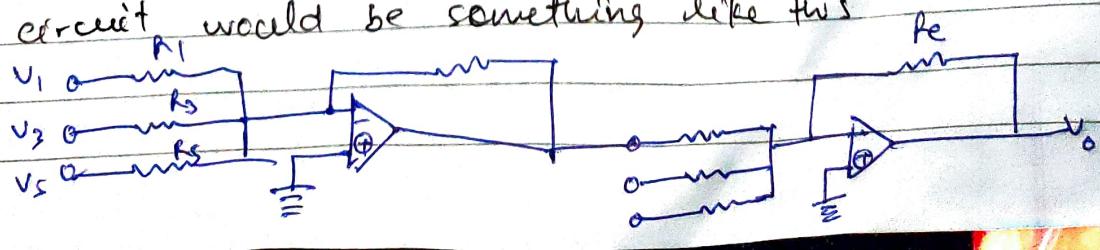

Student ID: 202052307


Name: Archit Agrawal

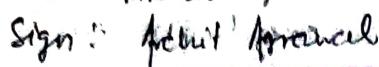Sign: 

Page No. 8

Date: 28/11/2021

(3) $R = 17 \text{ k}\Omega$

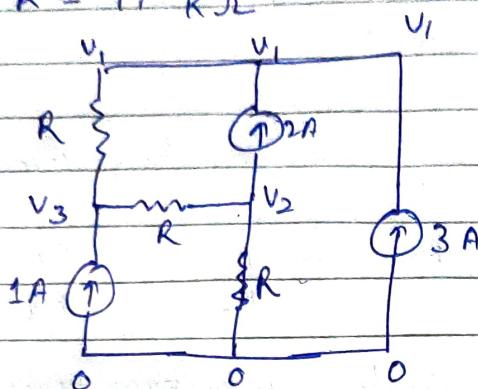

$$\frac{V_2 - V_3}{R} - \frac{V_2}{R} = 2 \text{ A} \quad (I)$$

$$\frac{V_1 - V_3}{R} + \frac{V_2 - V_3}{R} = 1 \text{ A} \quad (II)$$

$$\frac{V_2}{R} = 1 + 3 = 4 \text{ A}$$

$$\Rightarrow V_2 = 4 \times 18 \\ = 72 \text{ KV}$$

$$\Rightarrow 72 - V_3 - 72 = 2 \times 18$$

$$- V_3 = 36 \text{ KV}$$

$$V_3 = -36 \text{ KV}$$

$$\Rightarrow V_1 - 36 + 72 - 36 = 18 \text{ KV}$$

$$V_1 = 18 \text{ KV}$$

$$P_{BA} = 17 \text{ KV} \times 3 \text{ A} \\ = 51 \text{ KW}$$

(6)

Roll No. is 202052307

$$\therefore x = 17$$

So reverse saturation = 17 nA

forward voltage = 0.72 V

Diffusion capacitance = $\frac{C I}{n V_T}$

$$T = 5 \text{ nsec}$$

$$T = 360 \text{ K}$$

$$V_T = \frac{360}{116 \text{ mV}} = 0.031$$

$$\text{Now, } I_D = I_0 (e^{\frac{V}{nT}} - 1)$$

 $\eta = 2 \text{ for Si}$

$$I_0 = 17 \times 10^{-9} \text{ A}$$

$$I_D = 17 \times 10^{-9} \left(e^{\frac{0.72}{2 \times 0.031}} - 1 \right)$$

$$\therefore C_D = \frac{(5 \times 10^{-6}) \times (17 \times 10^{-9})}{2 \times (0.031)} \left(e^{\frac{0.72}{2 \times 0.031}} - 1 \right)$$