
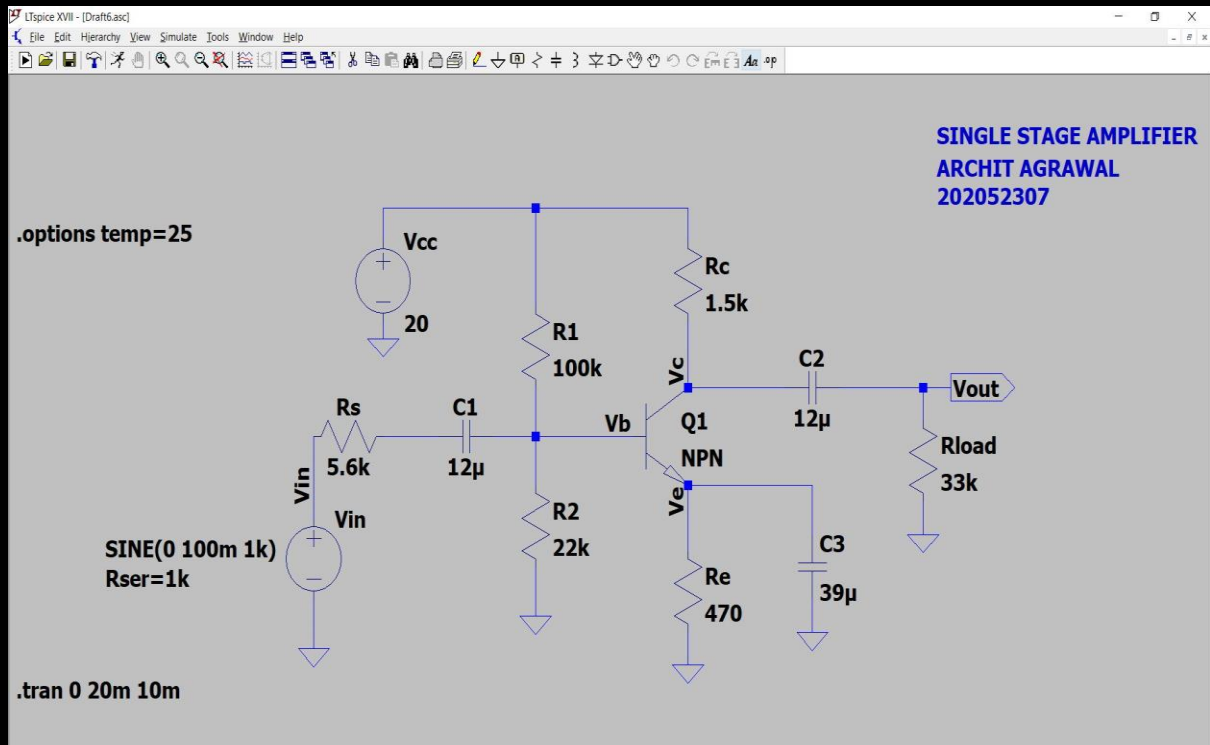


SPICE EXPERIMENT 2 : SINGLE STAGE AMPLIFIER

Single Stage Amplifier Circuit

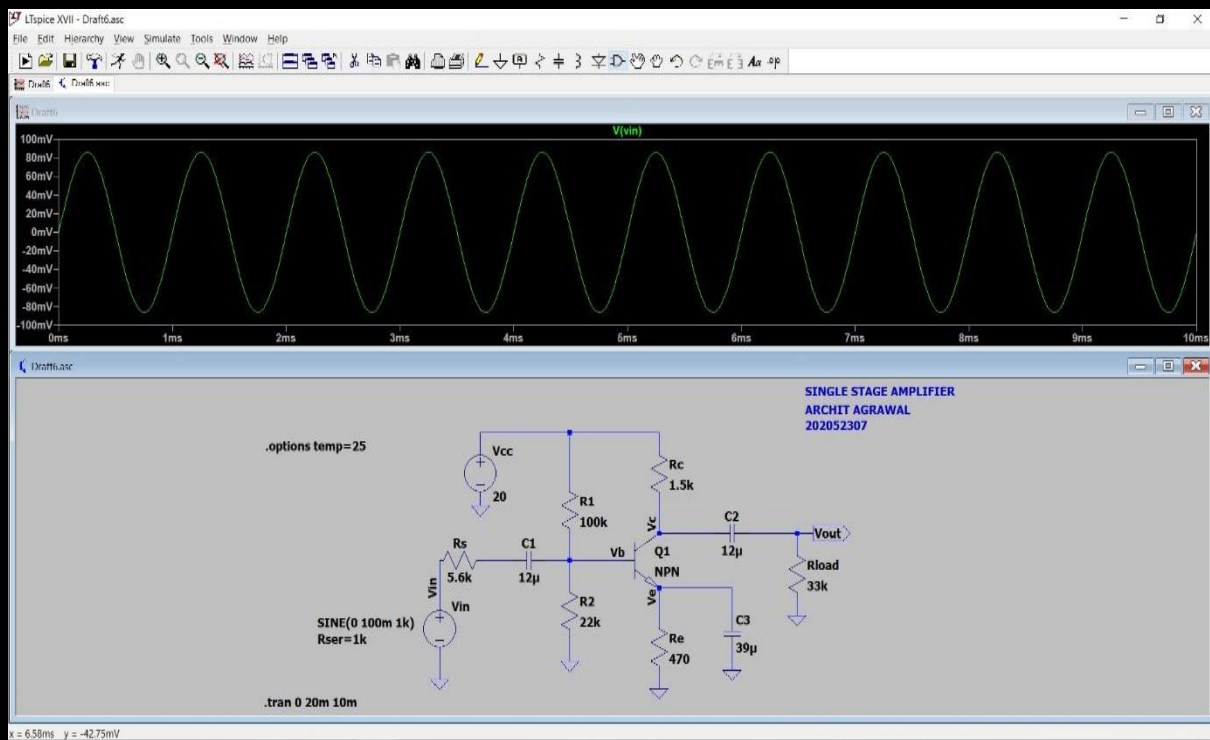


Input Voltage (V_{in})




SPICE EXPERIMENT 2 : SINGLE STAGE AMPLIFIER

Output Voltage (V_{out})

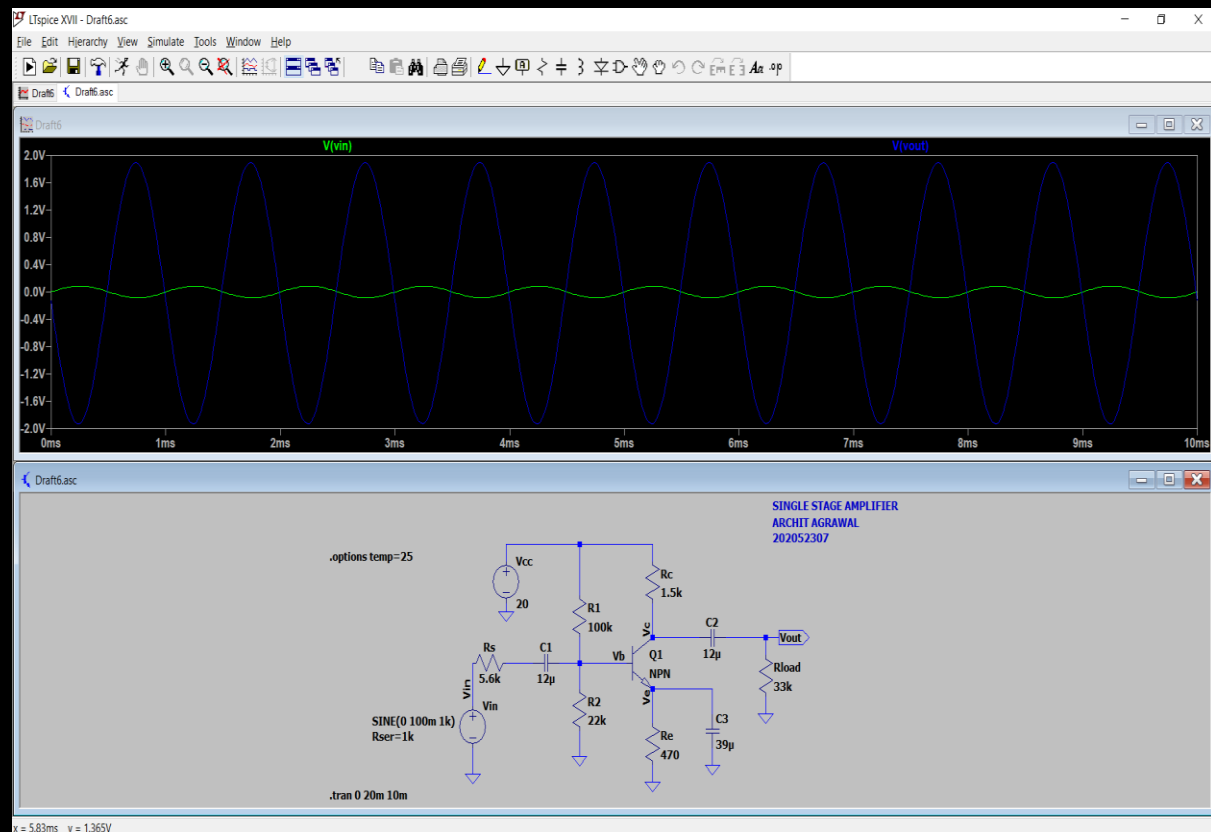


Collector Voltage (V_c)

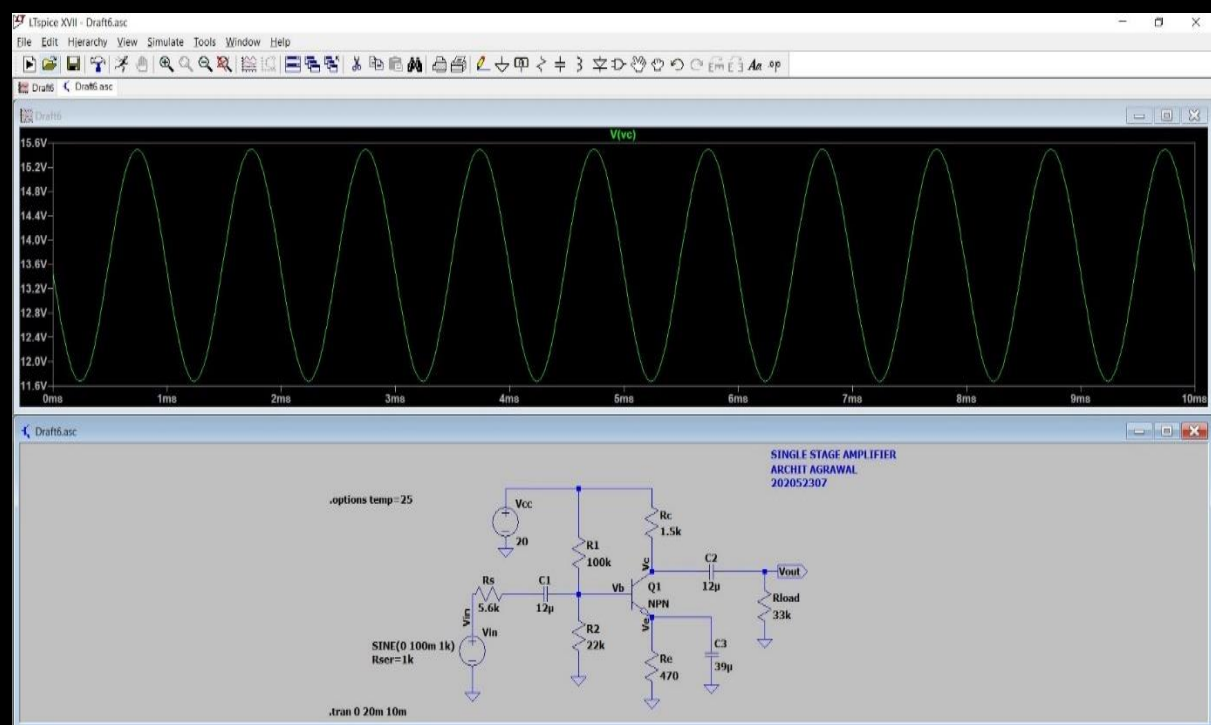


SPICE EXPERIMENT 2 : SINGLE STAGE AMPLIFIER

Emitter Voltage (V_E)

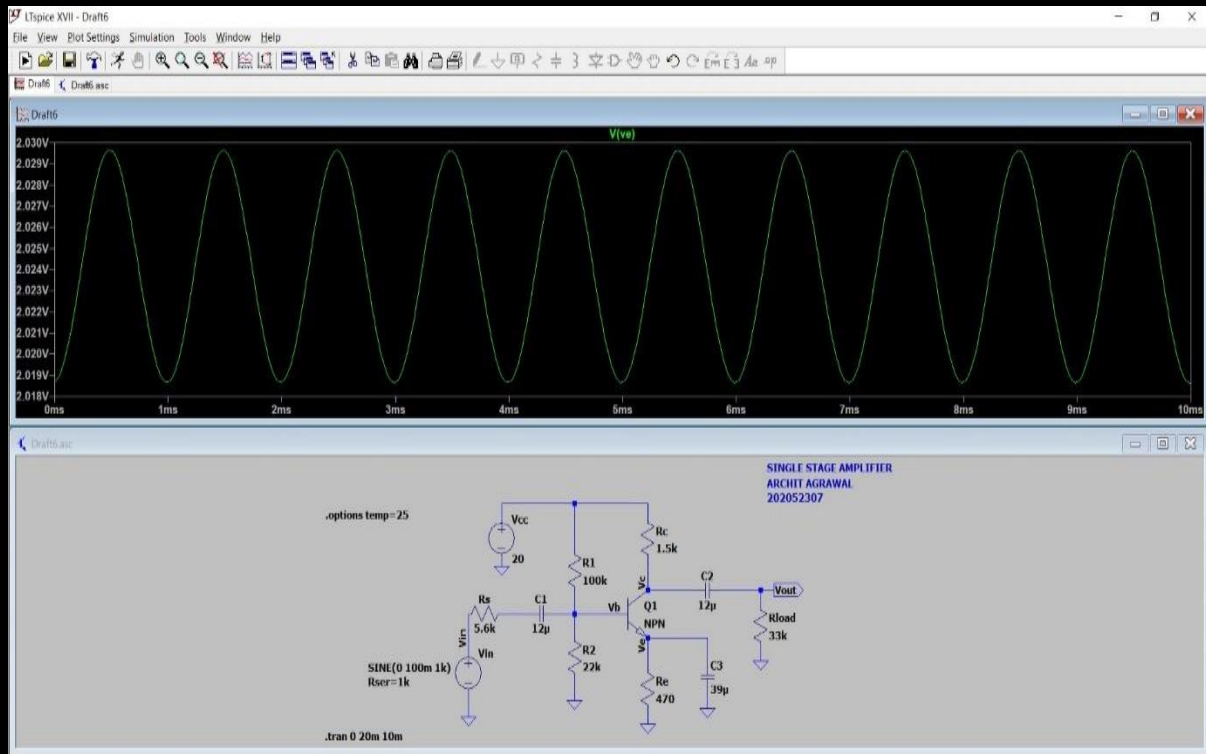


Base Voltage (V_B)

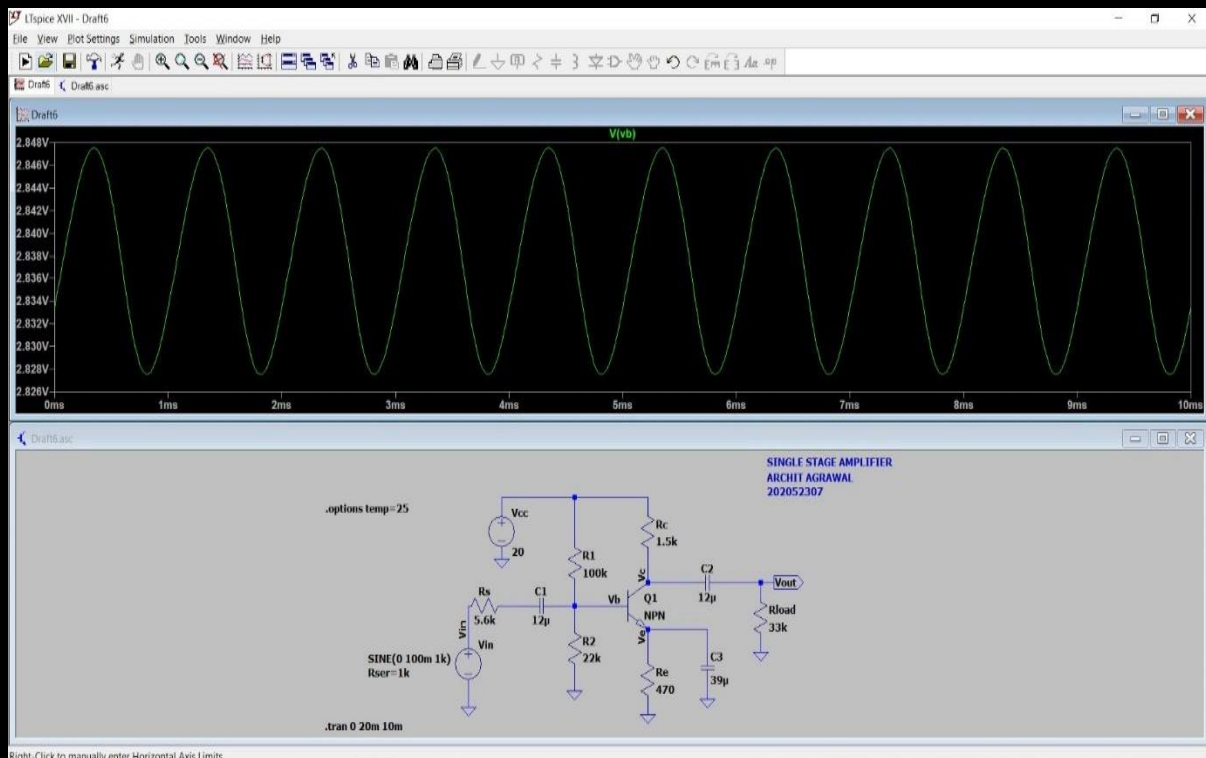


SPICE EXPERIMENT 2 : SINGLE STAGE AMPLIFIER

Collector Current (I_C)

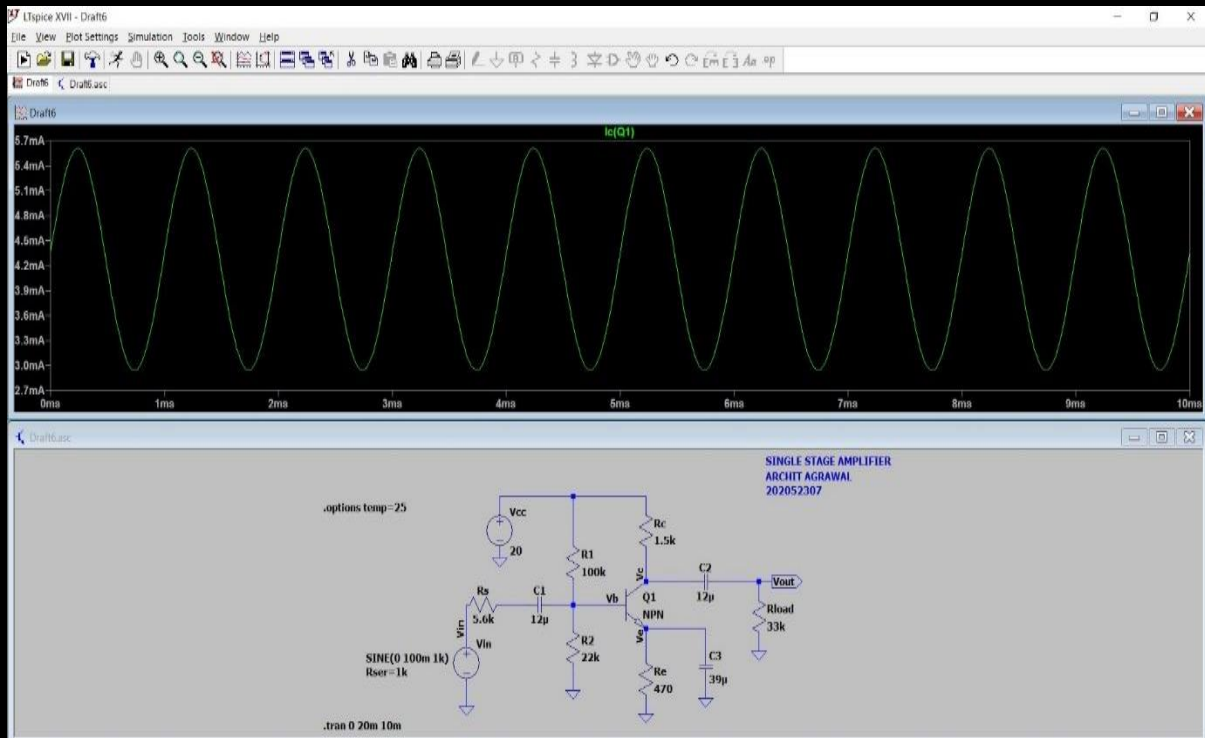

Emitter Current (I_E)

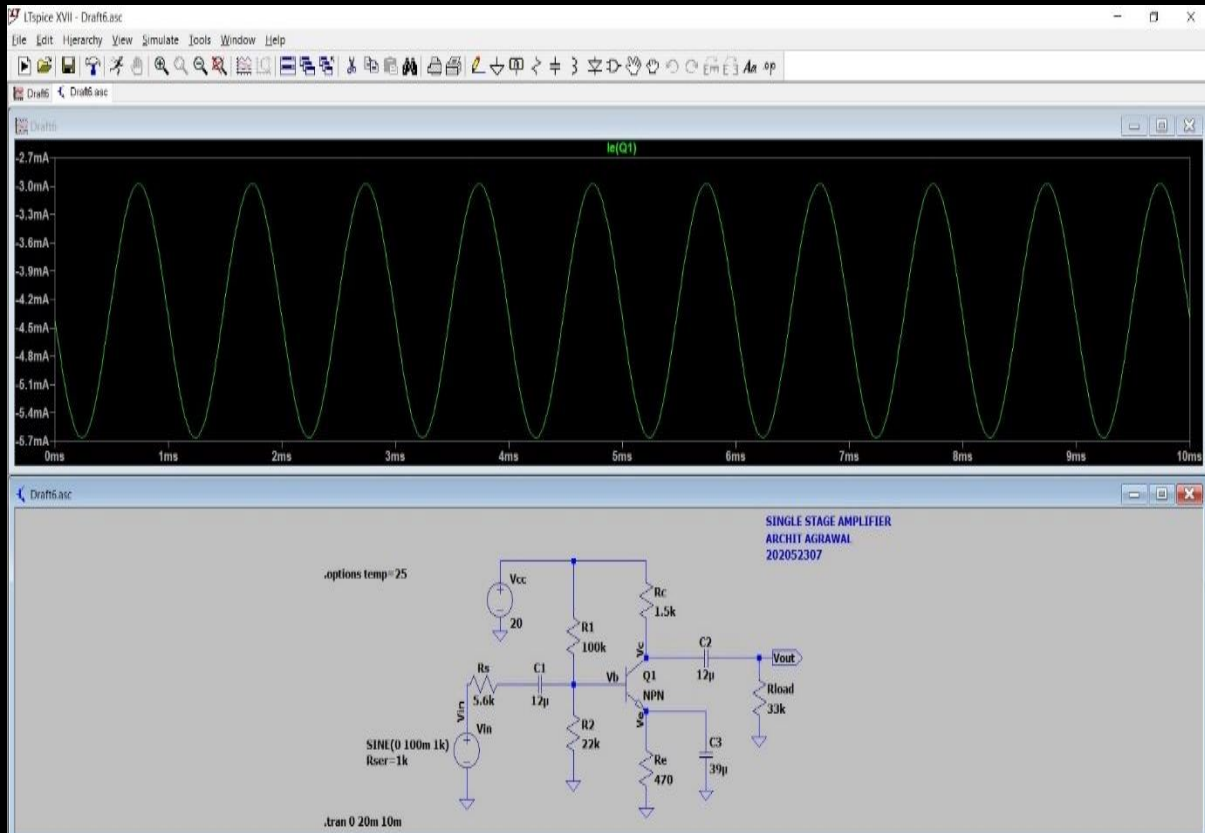

SPICE EXPERIMENT 2 : SINGLE STAGE AMPLIFIER

Base Current (I_B)

