


Name: Archit Agrawal
Student ID: 202052307



Basic Electrical Engineering (EE100)
Assignment No. 2

Problem from Section 17-2

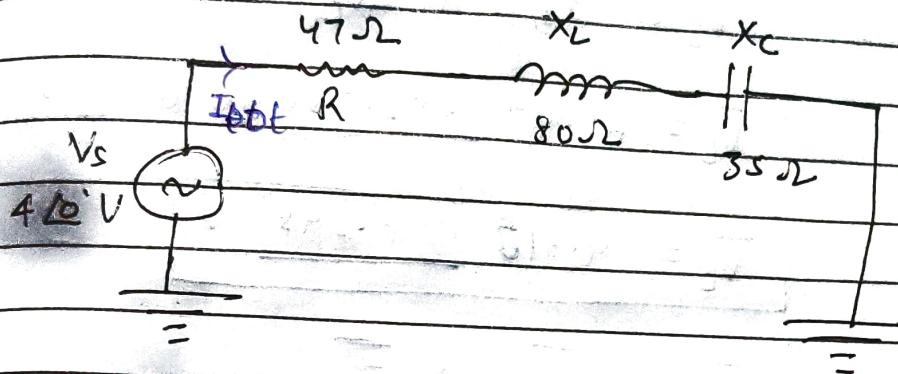5. For the circuit shown in figure, find I_{tot} , V_A , V_L and V_C in polar form.



$$Z = R + j(X_L - X_C)$$

$$Z = 47 + j(80 - 35)$$

$$Z = 47 + j45 \Omega$$

$$Z = 65.069 \angle 43.755^\circ \Omega$$

$$\therefore \bar{I}_{tot} = \frac{\bar{V}_s}{\bar{Z}}$$

$$\bar{I}_{tot} = 410^\circ \text{ A}$$
$$65.069 \angle 43.755^\circ$$

$$I_{tot} = 61.47 \angle -43.755^\circ \text{ mA}$$

Name: Archit Agrawal
Student ID: 202052307



$$\therefore \bar{V}_R = \bar{I}_{tot} \times \bar{Z}_B$$

$$= 61.47 [-43.755^\circ] \times 47 [0^\circ] \text{ mV}$$

$$\boxed{\bar{V}_R = 2.889 [-43.755^\circ] \text{ V}}$$

and, $\bar{V}_L = \bar{I}_{tot} \times \bar{Z}_{xc}$

$$\bar{V}_L = 61.47 [-43.755^\circ] \times 80 [90^\circ] \text{ mV}$$

$$\boxed{\bar{V}_L = 4.918 [46.245^\circ] \text{ V}}$$


and, $\bar{V}_C = \bar{I}_{tot} \times \bar{Z}_{xc}$

$$\bar{V}_C = 61.47 [-43.755^\circ] \times 35 [-90^\circ] \text{ mV}$$

$$\boxed{\bar{V}_C = 2.151 [-133.755^\circ] \text{ V}}$$

1 Problem from Section 17-3

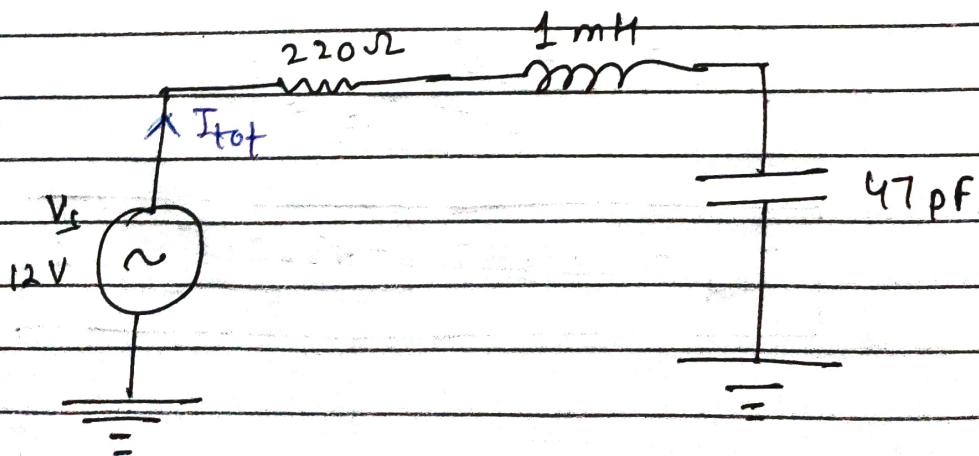10. Find X_L , X_C , Z and I_{tot} at the resonant frequency in the figure



Name: Archit Agrawal
Student ID: 202052307



As we know resonance frequency is given by

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi\sqrt{10^{-3} \times 47 \times 10^{-12}}}$$

$$f_r = \frac{1}{2\pi\sqrt{470 \times 10^{-8}}}$$

$$f_r = 734.5 \text{ kHz}$$

$$\therefore X_L = 2\pi f_r L \\ = 2 \times 3.14 \times 734.5 \text{ K} \times 1 \text{ m}$$

$$X_L = 4.613 \text{ k}\Omega$$

$$\text{and, } X_C = \frac{1}{2\pi f_r C} \\ = \frac{1}{2\pi \times 734.5 \text{ K} \times 47 \text{ p}}$$

$$X_C = 4.613 \text{ k}\Omega$$

$$\therefore Z = R + j(X_L - X_C)$$


$$Z = 220 \Omega$$

$$\bar{Z} = 220 \angle 0^\circ \Omega$$

$$\therefore \bar{I}_{\text{tot}} = \frac{\bar{V}_S}{\bar{Z}} = \frac{12 \angle 0^\circ}{220 \angle 0^\circ} \Rightarrow \bar{I}_{\text{tot}} = 54.55 \angle 0^\circ \text{ mA}$$

1 Problem from Section 17-5

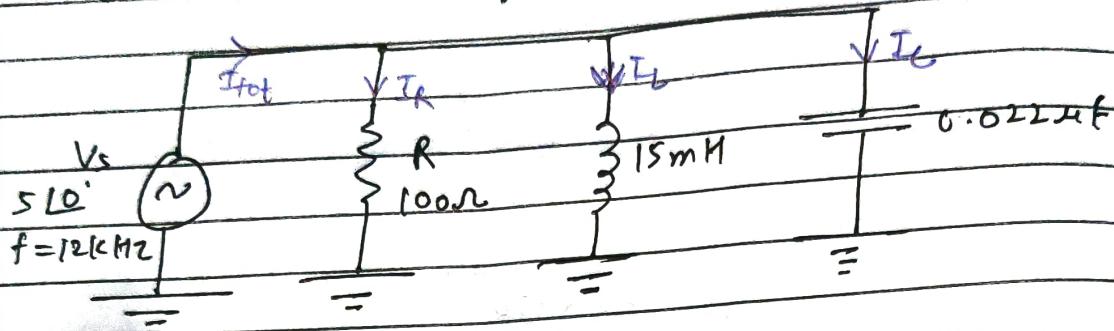19. For the given circuit + find all currents and voltages in polar form.



clearly, $\bar{V}_R = \bar{V}_L = \bar{V}_C = \bar{V}_s = 5\angle 0^\circ \text{ V}$

$$X_L = 2\pi f L \\ = 2 \times 3.14 \times 12 \text{ K} \times 15 \text{ m}$$

$$X_L = 1130.4 \Omega$$

and $X_C = \frac{1}{j} \frac{1}{2 \times 3.14 \times 12 \text{ K} \times 0.022 \mu\text{F}}$

$$X_C = 603.165 \Omega$$

Now, $\bar{I}_R = \frac{\bar{V}_s}{Z_R}$

$$= \frac{5\angle 0^\circ}{100\angle 0^\circ}$$

$\bar{I}_R = 50\angle 0^\circ \text{ mA}$

$I_R = 50 + j0 \text{ mA}$

Name: Archit Agrawal
Student ID: 202052307



and, $\bar{I}_L = \frac{\bar{V}_L}{Z_L}$

$$\bar{I}_L = \frac{5.10^\circ}{130.4190^\circ} A$$

$$\begin{aligned}\bar{I}_L &= 4.42 | -90^\circ \text{ mA} \\ I_L &= 0 - j(4.42) \text{ mA}\end{aligned}$$

and, $\bar{I}_C = \frac{\bar{V}_C}{Z_C}$

$$= \frac{5.10^\circ}{603.165 | -90^\circ} A$$

$$\bar{I}_C = 8.29 | 90^\circ \text{ mA}$$

$$I_C = 0 + j(8.29) \text{ mA}$$

From KCL, we have

$$I_{\text{tot}} = I_R + I_L + I_C$$

$$\therefore I_{\text{tot}} = 50 + j(3.07) \text{ mA}$$


$$I_{\text{tot}} = 50.149 | 4.426^\circ \text{ mA}$$

1 Problem from Section 17-6

23. Find Z at resonance and f_r for the tank circuit in figure

2 Problems from Section 17-7

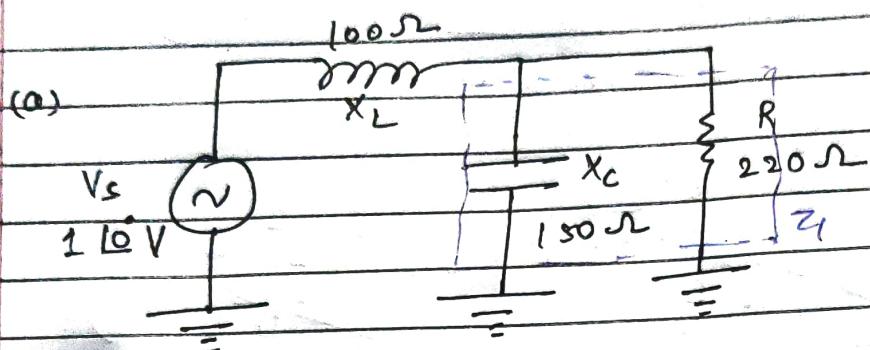20. Find the total impedance for each circuit.



$$Z_1 = Z_R \parallel Z_{X_C}$$

$$\bar{Z}_1 = \frac{220 [0^\circ] \times 150 [-90^\circ]}{220 - j 950}$$

$$\bar{Z}_1 = \frac{33000 [-90^\circ]}{266.27 [-34.294]}$$

$$\bar{Z}_1 = 123.934 [-55.706^\circ] \Omega$$

$$Z_1 = 69.829 - j (102.389) \Omega$$

and $Z_{X_L} = 0 + j (100) \Omega$

$$Z = Z_1 + Z_{X_L}$$


$$Z = 69.829 - j (2.389) \Omega$$

$$Z = 69.869 [-1.959^\circ] \Omega$$

Name: Archit Agrawal
Student ID: 202052307



(b)

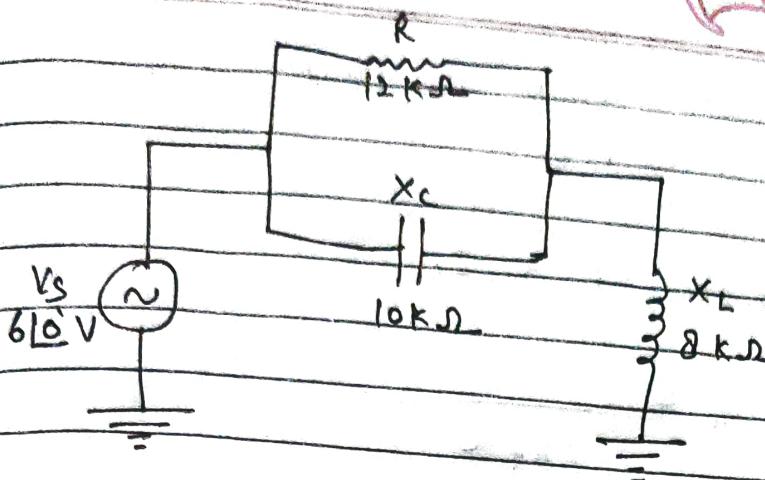

$$Z_1 = Z_R \parallel Z_{X_C}$$

$$\bar{Z}_1 = 12K [0^\circ] \times 10K [-90^\circ] \\ 12K - j10K$$

$$\bar{Z}_1 = \frac{120 \times 10^6}{15.62K} [-90^\circ] \\ 7.682 [-39.8^\circ]$$


$$\bar{Z}_1 = 7.682 [-50.2^\circ] \text{ k}\Omega$$

$$Z_1 = 4.917 - j5.902 \text{ k}\Omega$$

$$\text{and } Z_{X_L} = 0 + j8K \text{ k}\Omega$$

$$\therefore Z = 4.917 + j2.098 \text{ k}\Omega \\ \bar{Z} = 5.346 [23.107^\circ] \text{ k}\Omega$$

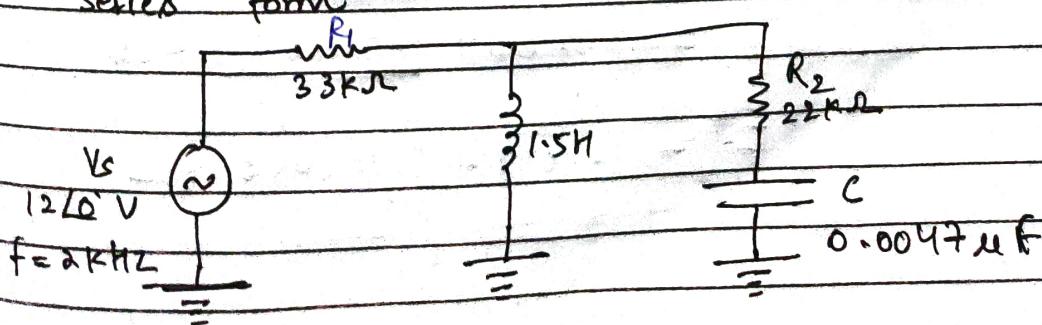29. Convert the circuit to an equivalent series form



Let us first find the impedance of the circuit.

$$\text{Let } z_1 = z_R + z_C$$

$$\text{Now, } z_C = \frac{1}{2\pi f C}$$

$$z_C = 16.94 \text{ k}\Omega$$

$$\therefore z_1 = 22 + j(-16.94) \text{ k}\Omega$$

$$\bar{z}_1 = 27.766 \angle -37.596^\circ \text{ k}\Omega$$

$$\text{Now, } z_L = 2\pi f L \\ = 8.28 \times 2000 \times 1.5$$

$$z_L = 18.84 \text{ k}\Omega$$

$$\text{Let say } z_2 = z_1 \parallel z_L$$

$$\therefore \bar{z}_2 = \frac{27.766 \angle -37.596^\circ \times 18.84 \angle 90^\circ}{(22 + j(-16.94)) + j(18.84)} \times 10^6$$

$$\bar{z}_2 = \frac{523.11 \angle 52.404^\circ}{22.082 \angle 4.936^\circ} \times 10^3$$

$$\bar{z}_2 = 23.689 \angle 47.46^\circ \text{ k}\Omega$$

$$z_2 = 16.014 + j 17.456 \text{ k}\Omega$$

Name: Archit Agrawal
Student ID: 202052307



Now, $Z = Z_R + Z_L$

$$Z = (33 + j(0) + 16.014 + j(17.456)) \text{ k}\Omega$$

$$Z = 49.014 + j(17.456) \text{ k}\Omega$$

The impedance of the circuit is Z ,

$$Z = 49.014 + j(17.456) \text{ k}\Omega$$

As the reactance X is equal to $17.456 \text{ k}\Omega$,
the reactance is inductive.


Therefore, the value of inductance at
which $X_{\text{eq}} = 17.456 \text{ k}\Omega$ is L_{eq} ,

$$X_{\text{eq}} = 2\pi f L_{\text{eq}}$$


$$L_{\text{eq}} = \frac{17.456 \text{ k}}{2 \times 3.14 \times 2000}$$

$$L_{\text{eq}} = 1.3898 \text{ H}$$

Hence, the equivalent series circuit is

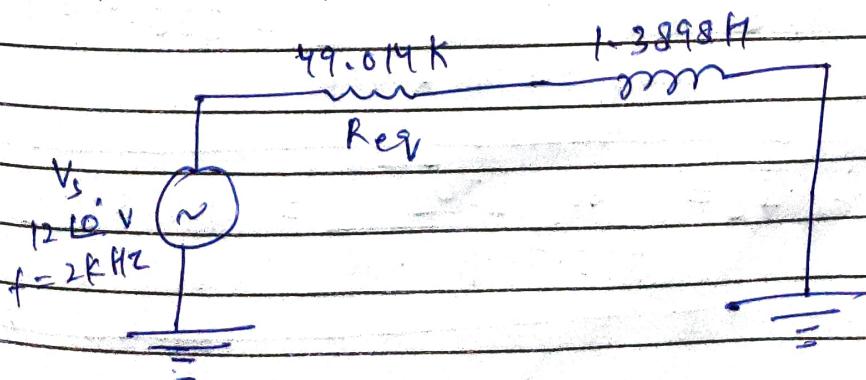

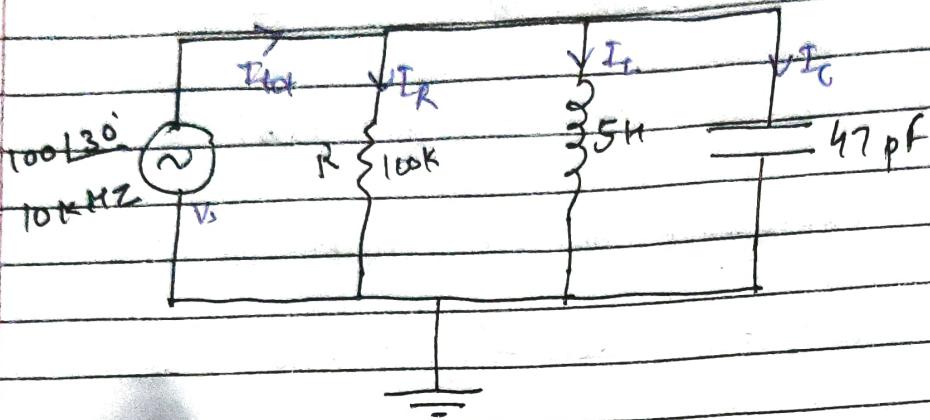Q. Find all currents and voltages and plot the phasor diagram



Since, R, L and C are in parallel

$$\bar{V}_R = \bar{V}_L = \bar{V}_C = \bar{V}_S = 100 \angle 30^\circ V$$

$$I_R = \frac{\bar{V}_S}{\bar{Z}_R} = \frac{100 \angle 30^\circ}{100k} = 1 \angle 30^\circ \text{ mA}$$

$$X_L = 2 \times 3.14 \times 10k \times 5 \\ = 314 \text{ k}\Omega$$

$$\therefore I_L = \frac{100 \angle 30^\circ}{314k \angle 90^\circ} = 0.318 \text{ mA } \angle -60^\circ$$

$$X_C = \frac{1}{2 \times 3.14 \times 10k \times 47 \mu F} = 338.799 \text{ k}\Omega$$

$$\therefore I_C = \frac{100 \angle 30^\circ}{338.799k \angle -90^\circ} = 0.295 \angle 120^\circ \text{ mA}$$

Name: Archit Agrawal
Student ID: 202052307




From KCL,

$$\bar{I}_{\text{tot}} = \bar{I}_R + \bar{I}_L + \bar{I}_C$$

$$\begin{aligned} \bar{I}_{\text{tot}} &= (0.866 + j(0.5)) + (0.159 - j(6.275)) \\ &\quad + (-0.1475 + j0.255) \text{ mA} \end{aligned}$$


$$\bar{I}_{\text{tot}} = 0.8775 + j(0.48) \text{ mA}$$
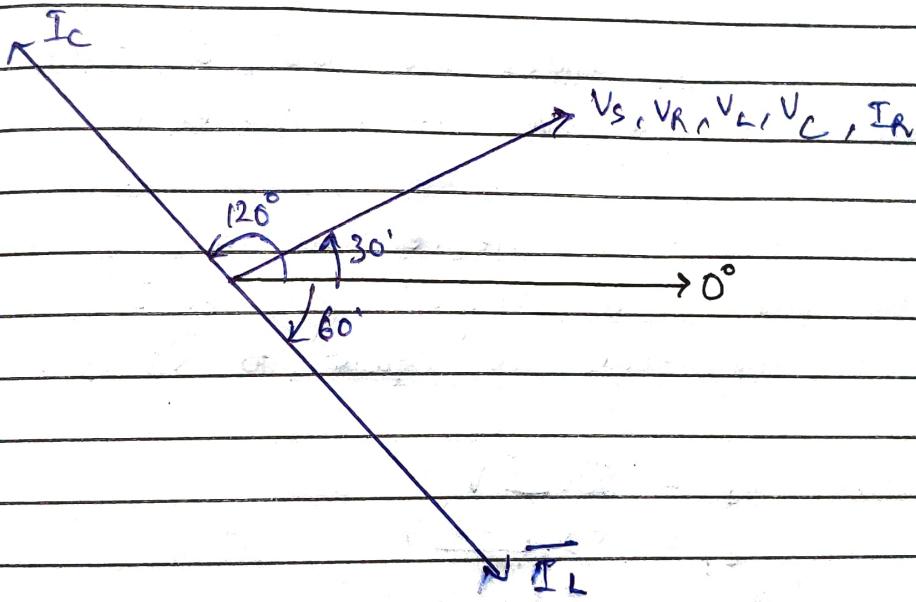
$$\boxed{\bar{I}_{\text{tot}} = 1.002 \angle 28.679^\circ \text{ mA}}$$



3 Questions from Section 21-3

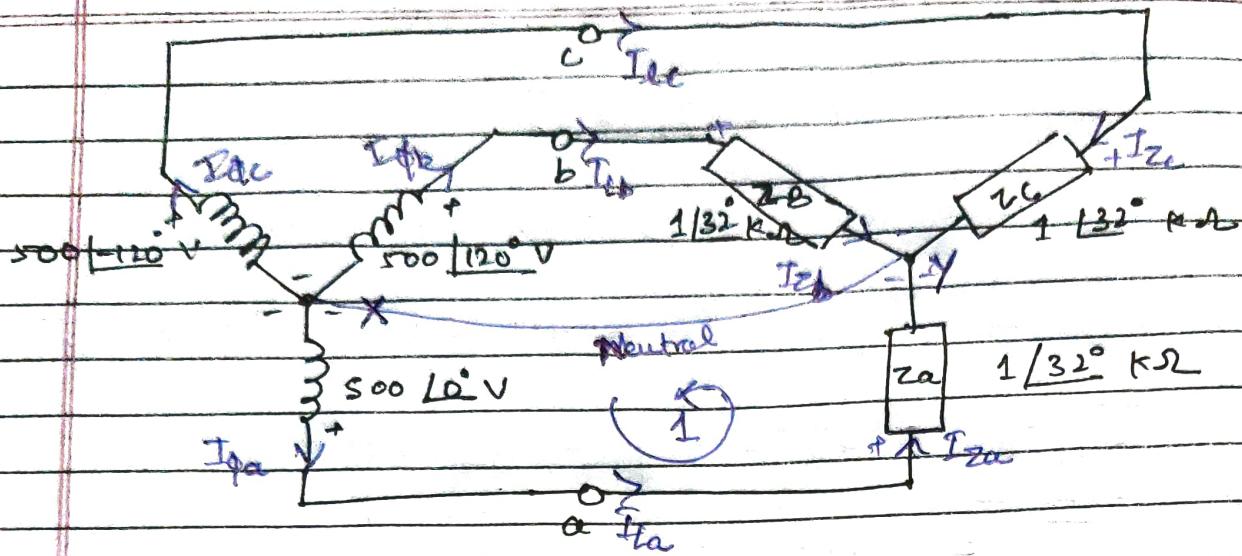7. Determine the following quantities for the Y-Y system in figure
- (a) Line voltages (b) Phase currents
 - (c) Line currents (d) Load currents
 - (e) Load voltages



As all the loads and all the sources are equal, hence the system is balanced.

As the phase angles are 120° , 0° , -120° , this is a negative phase sequence.

In negative-phase sequence (balanced system) the line-to-line voltages lag by 30° and their magnitude is equal to $\sqrt{3} V_p$.

$$\text{Given } V_{pA} = 500 \angle 0^\circ V$$

$$V_{pB} = 500 \angle 120^\circ V$$

$$V_{pC} = 500 \angle -120^\circ V$$

(a) Therefore line-to-line voltages

$$V_{L(AB)} = \sqrt{3} \times 500 \angle -30^\circ V$$

$$= 866 \angle -30^\circ V$$

$$V_{L(BC)} = 866 \angle 90^\circ V$$

$$V_{L(CA)} = 866 \angle -150^\circ V$$

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 13

(b) As the system is balanced, the current through neutral wire is zero.

Applying Kirchoff's Voltage Law,

$$\cancel{\text{---} =}$$

$$\bar{V}_{\phi_a} - \bar{I}_{Z_a} \cdot Z_a = 0$$

$$\bar{I}_{Z_a} = \frac{\bar{V}_{\phi_a}}{Z_a}$$

$$\bar{I}_{\phi_a} = \frac{500 \angle 0^\circ}{1 \angle 38^\circ \text{ k}\Omega}$$

$$(\text{as } \bar{I}_{\phi_a} = \bar{I}_{Z_a})$$

$$\bar{I}_{\phi_a} = 500 \angle -32^\circ \text{ mA}$$

$$\text{Similarly, } \bar{I}_{\phi_b} = 500 \angle 88^\circ \text{ mA}$$

$$\text{and, } \bar{I}_{\phi_c} = 500 \angle -152^\circ \text{ mA}$$

(c)(d) From the circuit it is clear that,

$$\bar{I}_{L_a} = \bar{I}_{Z_a} = \bar{I}_{\phi_a} = 500 \angle -32^\circ \text{ mA}$$

$$\bar{I}_{L_b} = \bar{I}_{Z_b} = \bar{I}_{\phi_b} = 500 \angle 88^\circ \text{ mA}$$

$$\bar{I}_{L_c} = \bar{I}_{Z_c} = \bar{I}_{\phi_c} = 500 \angle -152^\circ \text{ mA}$$

e) Using KVL in loop 1,

$$\bar{V}_{pa} - \bar{V}_{za} = 0$$

$$\therefore V_{za} = V_{pa}$$


$$V_{za} = 500[0^\circ] V$$

$$\text{Similarly, } \bar{V}_{zb} = 500[120^\circ] V$$

$$\text{and, } V_{zc} = 500[-120^\circ] V$$

9. Determine the following quantities for given circuit

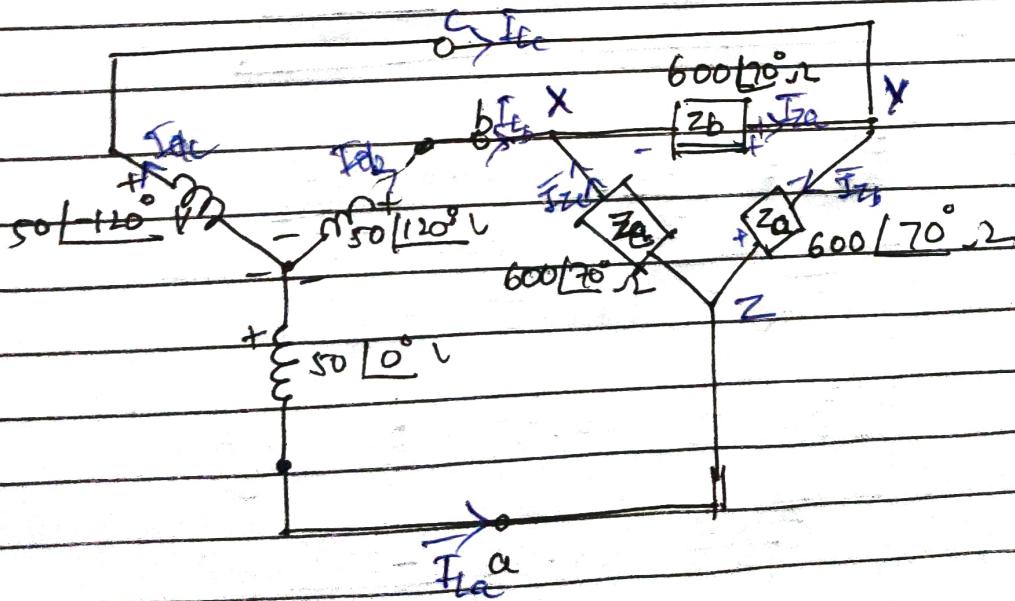- (a) Line Voltages
- (b) Load ~~voltages~~ voltages
- (c) Load ~~max~~ currents
- (d) Line currents
- (e) Phase Currents



$$(a) \bar{V}_{(ab)} = \bar{V}_{ba} - \bar{V}_{ab}$$

$$= 50 [0^\circ] - 50 [120^\circ]$$

$$\bar{V}_{(ab)} = 86.6 [-30^\circ] V$$

$$\bar{V}_{L(bc)} = 86.6 [90^\circ] V$$

$$\bar{V}_{L(a)} = 86.6 [-150^\circ] V$$

(b) from the circuit it is clear that,

$$V_{zc} = \bar{V}_{ba} - \bar{V}_{lb} = \bar{V}_{(fab)}$$

$$\therefore V_{zc} = 86.6 [-30^\circ] V$$

$$\text{and, } \bar{V}_{zb} = 86.6 [90^\circ] V$$

$$\text{and, } \bar{V}_{za} = 86.6 [-150^\circ] V$$

$$(c) \bar{I}_{zc} = \frac{\bar{V}_{zc}}{Z_c} = \frac{86.6}{600} [-30^\circ]$$

$$\bar{I}_{zc} = 144.33 [-100^\circ] mA$$

$$\bar{I}_{zb} = 144.33 [20^\circ] mA$$

$$\bar{I}_{za} = 144.33 [-220^\circ] mA$$

(d) Applying KVL at node Z.

$$\bar{I}_{Lb} = \bar{I}_{Tb} = \bar{I}_{Za}$$

$$\bar{I}_{Lb} = 144.33 \angle -100^\circ - 144.33 \angle -220^\circ$$

$$\bar{I}_{Lb} = -25.06 - j 192.13 - (-110.56 + j 92.90)$$

$$\bar{I}_{Lb} = 85.5 - j 235.03$$

$$\bar{I}_{Lb} = 250 \angle -70.009^\circ \text{ mA}$$

similarly $\bar{I}_{Lb} = 250 \angle 50^\circ \text{ mA}$


and, $\bar{I}_{Lc} = 250 \angle 170^\circ \text{ mA}$

(e) $\bar{I}_{Pa} = \bar{I}_{La} = 250 \angle -70.009^\circ \text{ mA}$

$$\bar{I}_{Pb} = \bar{I}_{Lb} = 250 \angle 50^\circ \text{ mA}$$

$$\bar{I}_{Pc} = \bar{I}_{Lc} = 250 \angle 170^\circ \text{ mA}$$

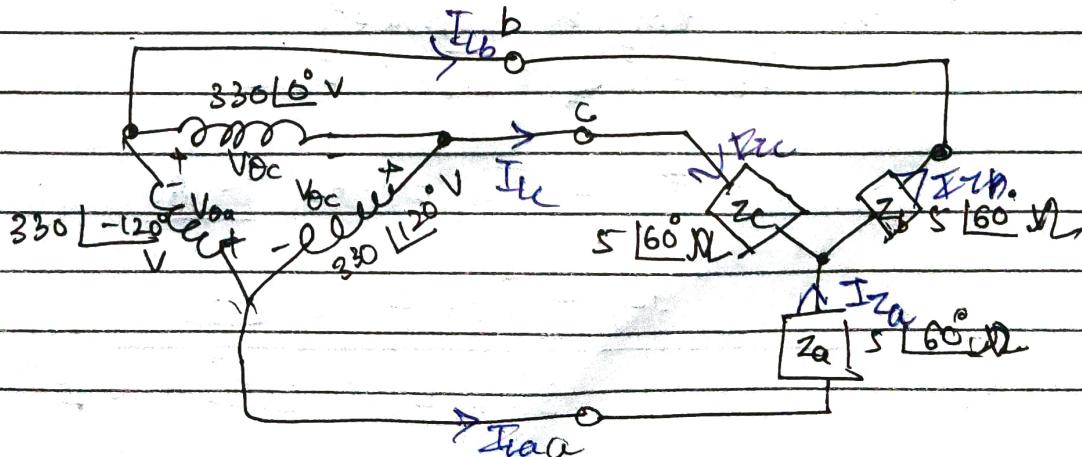Q.11 Determine the line voltages and load currents for the system.



Line to line voltages

| |
|---------------------------------------|
| $V_{L(ab)} = 330 \angle -120^\circ V$ |
| $V_{L(bc)} = 330 \angle 0^\circ V$ |
| $V_{L(ca)} = 330 \angle 120^\circ V$ |

Now,

$$V_{L(ab)} = (\bar{I}_{Zc} - \bar{I}_{Za}) Z_a \rightarrow \text{I}$$

$$V_{L(bc)} = (\bar{I}_{Zb} - \bar{I}_{Zc}) Z_b \rightarrow \text{II}$$

$$V_{L(ca)} = (\bar{I}_{Za} - \bar{I}_{Zb}) Z_c \rightarrow \text{III}$$

$$\frac{330 \angle 120^\circ}{66 \angle 60^\circ} = \bar{I}_{Zc} - \bar{I}_{Za}$$

$$66 \angle 60^\circ = \bar{I}_{Zc} - \bar{I}_{Za} \rightarrow \text{IV}$$

$$66 \angle -60^\circ = \bar{I}_{Zb} - \bar{I}_{Zc} \rightarrow \text{V}$$

$$66 \angle -180^\circ = \bar{I}_{Za} = I_{Zb} \rightarrow \text{VI}$$

\therefore the system is balanced,

$$\bar{I}_{Za} + \bar{I}_{Zb} + \bar{I}_{Zc} = 0$$

$$\therefore 2\bar{I}_{Za} + \bar{I}_{Zc} = 66 \angle -180^\circ \quad (\text{from VI})$$

$$\bar{I}_{Zc} - \bar{I}_{Za} = 66 \angle 60^\circ$$

$$3\bar{I}_{Za} = 66 \angle -180^\circ - 66 \angle 60^\circ$$

Name: Archit Agrawal
Student ID: 202052507



$$\bar{I}_{Z_a} = 22 \angle -180^\circ - 22 \angle 60^\circ$$

$$\bar{I}_{Z_a} = -33 - j 11\sqrt{3}$$

$$\bar{I}_{Z_a} = 38.2 \angle 30^\circ A$$

similarly $\bar{I}_{Z_b} = 38.2 \angle 150^\circ A$

$$\bar{I}_{Z_c} = 38.2 \angle -90^\circ A$$

3 Problems from section 29-4

- Q. In a certain Δ -connected balanced load, the line voltages are $250V$ and the impedances are $50 \angle 30^\circ \Omega$. Determine the load power.

For Δ -connected system

$$V_L = V_Z \text{ and } I_L = \sqrt{3} \bar{I}_Z$$

$$I_Z = \frac{V_Z}{Z} = \frac{250V}{50} = 5A$$

$$I_L = \sqrt{3} I_Z = 8.66 A$$

∴ Power factor, $\cos \theta = \cos 30^\circ = \frac{\sqrt{3}}{2} = 0.866$.

$$\therefore P_{L(\text{tot})} = \sqrt{3} V_L I_L \cos \theta$$


$$= \sqrt{3} (250) (8.66 A) \times 0.866$$

$$P_{L(\text{tot})} = 3.249 \text{ kW}$$

Name: Archit Agrawal
Student ID: 2020512307

Date: _____
Page: 19

Q.18. Find total load power in circuit

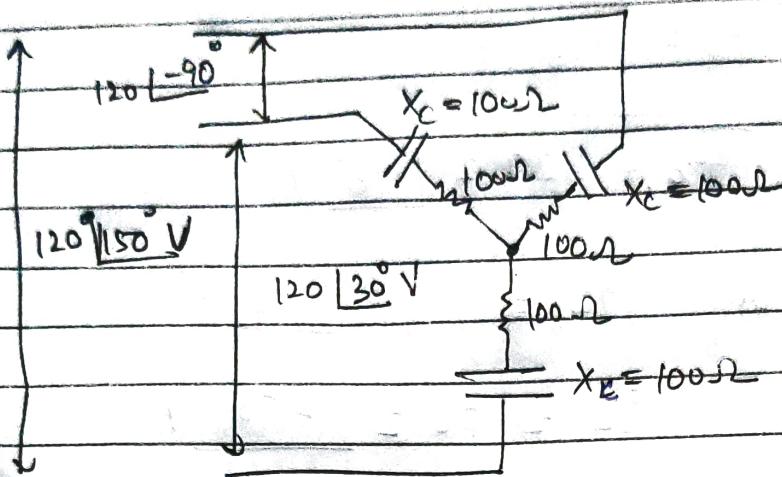

$$Z = 100 - j(100)\Omega$$

$$V_L = 120$$

$$V_\phi = \frac{V_L}{\sqrt{3}} = \frac{120}{\sqrt{3}} = 40\sqrt{3} V$$

$$\bar{Z}_\phi = 100\sqrt{2} \quad -45^\circ \Omega$$

$$\bar{I}_\phi = \frac{\bar{V}_\phi}{\bar{Z}_\phi} = \frac{69.28}{100\sqrt{2}} \text{ VA}$$

$$\underline{I}_\phi = 0.4898 A$$


$$I_L = I_\phi = 0.4898 A$$

$$\cos \phi = \cos 45^\circ = \sqrt{2}$$

$$P_L(\text{tot}) = \sqrt{3} V_L I_L \cos \phi \\ = \sqrt{3} \times 120 \times 0.4898 \times \sqrt{2}$$

$$\boxed{P_L(\text{tot}) = 71.97 W}$$

Any 5 Questions from homework

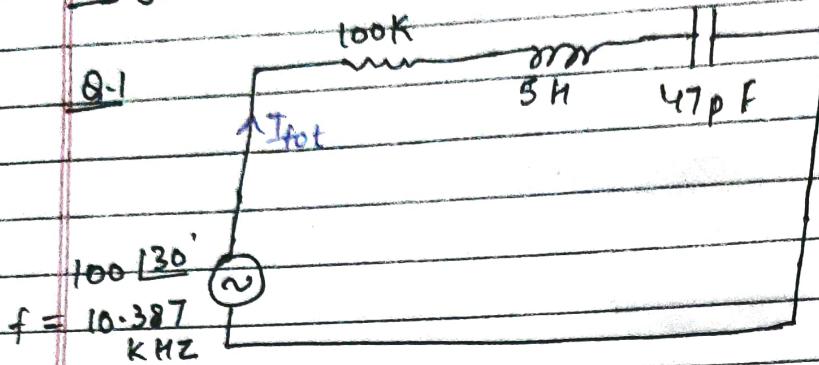

Find all currents and voltages. Draw the phasor diagram. Find true power P, reactive power Q, apparent power S.

$$X_C = \frac{1}{2 \times 3.14 \times 10.387 \text{ kHz} \times 47 \text{ p}}$$

$$X_C = 326.176 \text{ kΩ}$$

$$\text{and } X_L = 2 \times 3.14 \times 10.387 \text{ kHz} \times 5$$

$$X_L = 326.1518 \text{ kΩ}$$

as $X_C \approx X_L$,

$$\bar{Z} = \bar{Z}_R = 100\angle 0^\circ \text{ kΩ}$$

$$\therefore \bar{I}_{\text{tot}} = \frac{100\angle 30^\circ}{100\angle 0^\circ} \text{ V}$$

$\bar{I}_{\text{tot}} = 1\angle 30^\circ \text{ mA}$

As all components are in series,

$$\bar{I}_R = \bar{I}_L = \bar{I}_C = \bar{I}_{\text{tot}} = 1 \angle 30^\circ \text{ mA}$$

$$\text{Now, } \bar{V}_R = \bar{I}_{\text{tot}} \times \bar{Z}_R \\ = 1 \angle 30^\circ \times 100 \angle 0^\circ$$


$$\bar{V}_R = 100 \angle 30^\circ \text{ V}$$

$$\text{and } \bar{V}_L = 1 \angle 30^\circ \times 326.152 \angle 90^\circ$$

$$\bar{V}_L = 326.152 \angle 120^\circ \text{ V}$$

$$\text{and } \bar{V}_C = 1 \angle 30^\circ \times 326.176 \angle -90^\circ$$
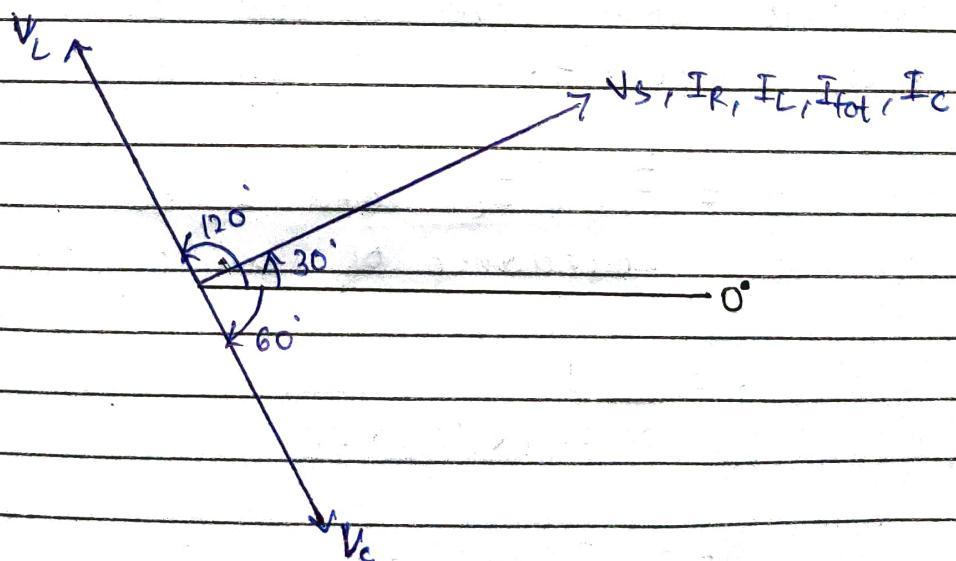
$$\bar{V}_C = 326.176 \angle -60^\circ \text{ V}$$



Name: Archit Agrawal
Student ID: 202052307


Date: _____
Page: 22

true power, $P = I^2 R$
 $P = (1 \text{ mA})^2 \times 100 \text{ k}$
 $P = 100 \text{ mW}$

reactive power, $Q = I^2 X$
 $Q = 0 \text{ VAR}$ (as $X = 0$)

Apparent power, $S = \sqrt{P^2 + Q^2}$

$S = P = 100 \text{ mVA}$

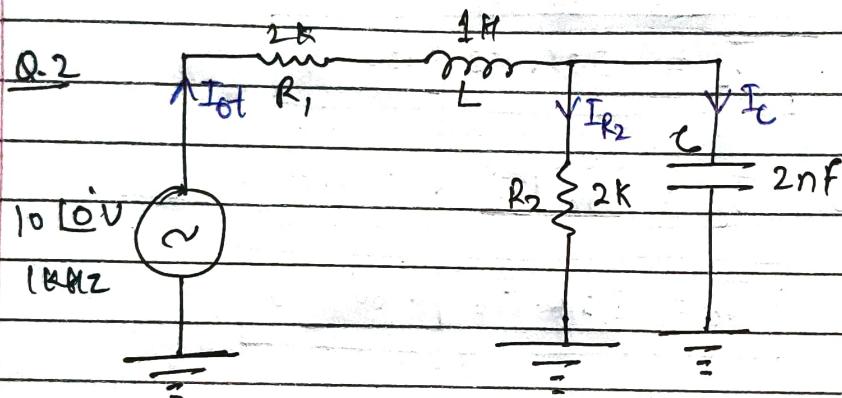


Calculate voltage and current across each component.

Let $Z_1 = Z_{R_2} \parallel Z_C$ and Z be the net impedance of the circuit.

$$Z_1 = \frac{1}{2 \times 3.14 \times 1000 \times 2n}$$

$$Z_1 = 79.618 \text{ k}\Omega$$

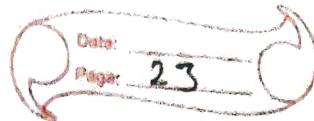Name: Archit Agrawal
Student ID: 202052307



and $X_L = 2 \times 3.14 \times 1000 \times 1$
 $X_L = 6.28 \text{ k}$

Now, $Z_T = Z_{R2} \parallel Z_C$

$$= 2 \text{ k} [0^\circ] \times 79.618 \text{ k} [-90^\circ]$$
$$2 \text{ k} - j(79.618 \text{ k})$$

$$Z_T = 2 \text{ k} [0^\circ] \times 79.618 \text{ k} [-90^\circ]$$
$$79.643 \text{ k} [-88.56^\circ]$$

$$Z_T = 1.999 [-1.44^\circ] \text{ k}\Omega$$
$$Z_T \approx 2 [-1.44^\circ] \text{ k}\Omega$$

$$Z_T = 1.9994 \text{ k} - j(0.050 \text{ k}) \Omega$$

Now, $Z = Z_T + Z_{R1} + Z_L$

$$Z = 1.9994 \text{ k} - j(0.050 \text{ k}) + 2 \text{ k} + j(6.28 \text{ k})$$

$$Z = 3.9994 \text{ k} + j(6.23 \text{ k}) \Omega$$

$$\boxed{Z = 7.403 \text{ k} [57.3^\circ] \Omega}$$

$$\therefore \bar{I}_{\text{tot}} = \frac{\bar{V}_S}{Z}$$

$$\bar{I}_{\text{tot}} = \frac{10 [0^\circ]}{7.403 \text{ k} [57.3^\circ]} \text{ A}$$

$$\boxed{\bar{I}_{\text{tot}} = 1.351 [-57.3^\circ] \text{ mA}}$$

$$\bar{I}_A = \bar{I}_L = \bar{I}_{tot} = 1.351 \angle -57.3^\circ \text{ mA}$$

Using current division,

$$\bar{I}_{R_2} = \frac{Z_C}{Z_{R_2} + Z_C} \bar{I}_{tot}$$

$$\bar{I}_{R_2} = \frac{79.618K \angle -90^\circ}{2K - j79.618K} \times 1.351 \angle -57.3^\circ \text{ mA}$$

$$\bar{I}_{R_2} = \frac{107.564K \angle -147.3^\circ \text{ mA}}{79.643K \angle -88.56^\circ}$$

$$\boxed{\bar{I}_{R_2} = 1.35 \angle -58.74^\circ \text{ mA}}$$

and $\bar{I}_C = \frac{Z_{R_2}}{Z_{R_2} + Z_C} \bar{I}_{tot}$

$$\bar{I}_C = \frac{2K \angle 0^\circ \times 1.351 \angle -57.3^\circ \text{ mA}}{79.643K \angle -88.56^\circ}$$

$$\boxed{\bar{I}_C = 33.9 \angle 31.26^\circ \mu\text{A}}$$

Now, $\bar{V}_{R_1} = \bar{I}_{tot} \times \bar{Z}_{R_1}$

$$\bar{V}_{R_1} = 1.351 \angle -57.3^\circ \times 2K \angle 0^\circ \text{ mV}$$

$$\boxed{\bar{V}_{R_1} = 2.702 \angle -57.3^\circ \text{ V}}$$

and $\bar{V}_L = \bar{I}_{tot} \times \bar{Z}_L$

$$\bar{V}_L = 1.351 \angle -57.3^\circ \times 6.28K \angle 90^\circ \text{ mV}$$


$$\boxed{\bar{V}_L = 8.494 \angle 32.7^\circ \text{ V}}$$

and, $\bar{V}_{R_2} = \bar{I}_{R_2} \times \bar{Z}_{R_2}$

$$\bar{V}_{R_2} = 1.35 \angle -58.74^\circ \times 2K \angle 0^\circ \text{ mV}$$

$$\boxed{\bar{V}_{R_2} = 2.7 \angle -58.74^\circ \text{ V}}$$

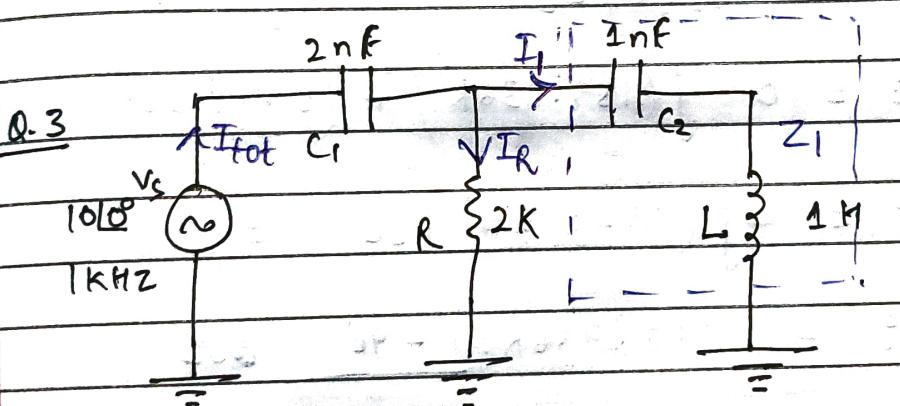and, $\bar{V}_C = \bar{V}_{R_2} = 2.7 \angle -58.74^\circ \text{ V}$



Find ~~the~~ current and voltage across each component.

Let us assume,

$$Z_1 = Z_{C_1} + Z_L$$

$$Z_2 = Z_R \parallel Z_1$$

∴ net impedance $Z = Z_{C_1} + Z_2$

Name: Archit Agrawal
Student ID: 202052307

Date: 26
Page:

$$X_L = 2 \times 3.14 \times 1000 \times 1$$

$$X_L = 6.28 \text{ k}\Omega$$

$$X_{C_1} = \frac{1}{2 \times 3.14 \times 1000 \times 2n}$$

$$X_{C_1} = 79.618 \text{ k}\Omega$$

$$\text{and } X_{C_2} = \frac{1}{2 \times 3.14 \times 1000 \times 1n}$$

$$X_{C_2} = 159.236 \text{ k}\Omega$$

Now,

$$Z_1 = Z_{C_2} + Z_L$$

$$Z_1 = (0 - j(159.236 \text{ k})) + (0 + j(6.28 \text{ k}))$$

$$Z_1 = -j(152.956) \text{ k}\Omega$$

$$\bar{Z}_1 = 152.956 \text{ k} \angle -90^\circ \text{ }\Omega$$

$$\therefore \bar{Z}_2 = \frac{\bar{Z}_R \times \bar{Z}_1}{\bar{Z}_R + \bar{Z}_1}$$

$$\bar{Z}_2 = \frac{2 \text{ k} \angle 0^\circ \times 152.956 \text{ k} \angle -90^\circ}{(2 \text{ k} + j0) + (0 - j(152.956 \text{ k}))}$$

$$\bar{Z}_2 = \frac{305.912 \times 10^6 \angle -90^\circ}{152.956 \text{ k} \angle -89.25^\circ}$$

$$\bar{Z}_2 = 1.9998 \text{ k} \angle -0.75^\circ \text{ }\Omega$$

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 27

$$\bar{Z}_2 \approx 2k \left[-0.25^\circ \right] \Omega$$

$$Z_2 = 1.9998k - j(0.026k) \Omega$$

$$\therefore Z = Z_{C_1} + Z_2$$

$$Z = (0 - j(79.618k)) + (1.998k - j(0.026k))$$

$$Z = (1.998k - j(79.644k)) \Omega$$

$$Z = 79.67k \left[-88.563^\circ \right] \Omega$$

Now,

$$\bar{I}_{tot} = \frac{\bar{V}_S}{\bar{Z}}$$

$$\bar{I}_{tot} = \frac{10 \left[0^\circ \right]}{79.67k \left[-88.563^\circ \right]}$$

$$\bar{I}_{tot} = 125.52 \left[88.563^\circ \right] \mu A$$

$$I_{C_1} = I_{tot} = 125.52 \left[88.563^\circ \right] \mu A$$

From current division, we have,

$$\bar{I}_R = \frac{Z_1}{Z_R + Z_1} \times \bar{I}_{tot}$$

$$I_R = \frac{152.956k \left[-90^\circ \right]}{152.969k \left[-89.25^\circ \right]} \times 125.52 \left[88.563^\circ \right] \mu A$$

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 28

$$\bar{I}_R = 125.51 | 87.813^\circ \mu A$$

Now, $I_1 = \frac{Z_R}{Z_L + Z_1} \times I_{\text{tot}}$

$$I_1 = \frac{2k | 0^\circ}{152.969k | -89.25^\circ} \times 125.52 | 88.563^\circ \mu A$$

$$\bar{I}_1 = 1.64 | 177.813^\circ \mu A$$

Since, L and C_2 are in series.

$$\therefore \bar{I}_L = \bar{I}_{C_2} = \bar{I}_1 = 1.64 | 177.813^\circ \mu A$$

Now,

$$\bar{V}_{C_1} = \bar{I}_{C_1} \times \bar{Z}_{C_1}$$

$$\bar{V}_{C_1} = 125.52 | 88.563^\circ \times 79.618k | -90^\circ \mu V$$

$$\bar{V}_{C_1} = 9.993 | -1.437^\circ V$$

and, $\bar{V}_R = \bar{I}_R \times \bar{Z}_R$
 $= 125.51 | 87.813^\circ \times 2k | 0^\circ \mu V$

$$\bar{V}_R = 0.251 | 87.813^\circ V$$


and, $\bar{V}_{C_2} = 1.64 | 177.813^\circ \times 159.236k | -90^\circ \mu V$

$$\bar{V}_{C_2} = 0.261 | 87.813^\circ V$$

and $\bar{V}_L = 1.64 [177.813^\circ] \times 6.28 k [90^\circ] \text{ mV}$

$\bar{V}_L = 10.3 [267.813^\circ] \text{ mV}$

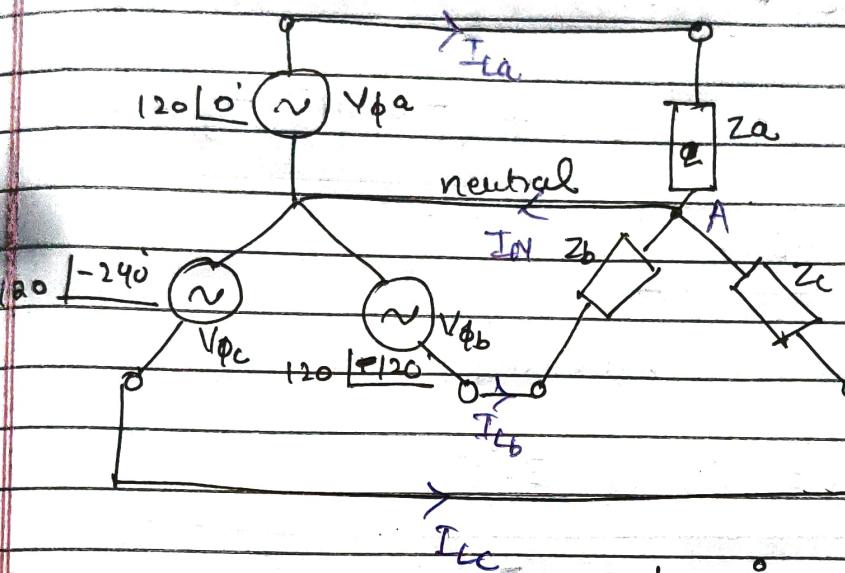4. Calculate all parameters for the circuit.



$Z_a = Z_b = Z_c = 22.4 [26.6^\circ]$

$$\bar{I}_{\phi a} = \frac{\bar{V}_{\phi a}}{Z_a} = \frac{120 L 0^\circ}{22.4 [26.6^\circ]}$$

$\bar{I}_{\phi a} = \bar{I}_{\phi b} = \bar{I}_{\phi c} = 5.35 [-26.6^\circ] \text{ A}$

$\bar{I}_{\phi b} = \bar{I}_{\phi c} = \bar{I}_{\phi a} = 5.35 [-146.6^\circ] \text{ A}$

$\bar{I}_{\phi c} = \bar{I}_{\phi a} = \bar{I}_{\phi b} = 5.35 [-266.6^\circ] \text{ A}$

Name: Archit Agrawal
Student ID: 202052307

Date: _____
Page: 30

using KCL at node A,

$$\bar{I}_N = \bar{I}_{ZA} + \bar{I}_{ZB} + \bar{I}_{ZC}$$

$$\bar{I}_N = 5.35 \angle -26.6^\circ + 5.35 \angle -146.6^\circ + 5.35 \angle -266.6^\circ A$$

$$I_N = (4.784 - j(2.395)) + (-4.466 - j 2.945)$$

$$+ (-0.317 + j 5.34) A$$

$$I_N = 0 A$$

As the system is balanced,

$$\bar{V}_L(a,b) = \sqrt{3} V_\phi \angle 30^\circ$$

$$\bar{V}_{L(b,c)} = 207.84 \angle 30^\circ V$$

$$\text{and, } \bar{V}_{L(c,a)} = 207.84 \angle -90^\circ V$$

$$\text{and, } \bar{V}_{L(a,b)} = 207.84 \angle -210^\circ V$$

and, load voltages


$$\bar{V}_{za} = \bar{V}_{\phi a} = 120 \angle 0^\circ V$$

$$\bar{V}_{zb} = \bar{V}_{\phi b} = 120 \angle -120^\circ V$$

$$\bar{V}_{zc} = \bar{V}_{\phi c} = 120 \angle -240^\circ V$$

Name : Archit Agrawal
 Student ID: 202052307

Date: _____
 Page: 31

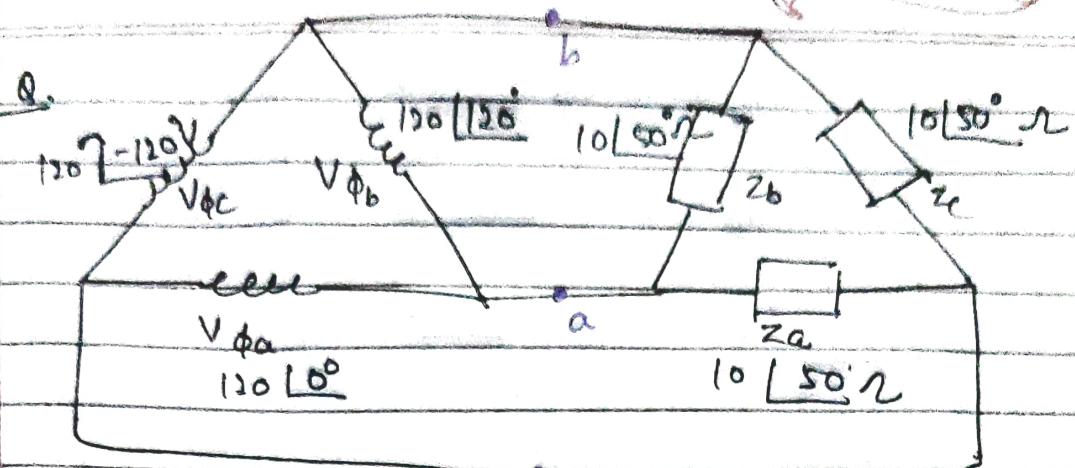

Find all the parameters for the circuit.

The system is balanced.

$$V_{\phi_b} = V_{L(b)} = \bar{V}_{Z_b} = 120 [120^\circ] V$$

$$V_{\phi_a} = V_{L(a)} = \bar{V}_{Z_a} = 120 [0^\circ] V$$

$$V_{\phi_c} = V_{L(c)} = \bar{V}_{Z_c} = 120 [-120^\circ] V$$

$$\text{and, } I_Z = I_{Z_a} = I_{Z_b} = I_{Z_c} = \frac{\bar{V}_{Z_a}}{Z_a}$$

$$I_Z = \frac{120}{10} = 12 A$$

$$I_{Z_a} = 12 [0^\circ] A$$


$$I_{Z_b} = 12 [70^\circ] A$$

$$I_{Z_c} = 12 [-170^\circ] A$$

for $\Delta-\Delta$ connection

$$I_L = \sqrt{3} I_Z$$

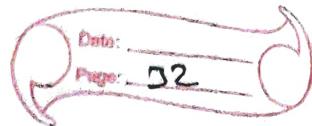Name: Archit Agrawal
Student ID: 202052307



$$\therefore I_{L_a} = 12\sqrt{3} \angle -50^\circ A$$

$$I_{L_b} = 12\sqrt{3} \angle 70^\circ A$$

$$I_{L_c} = 12\sqrt{3} \angle -170^\circ A$$